
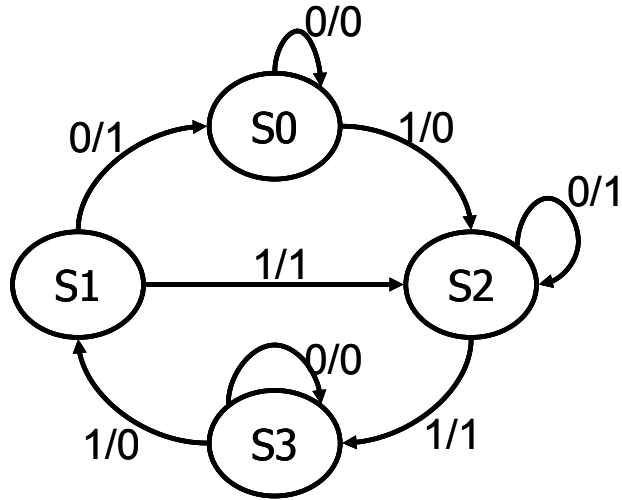


Using D flip-flop

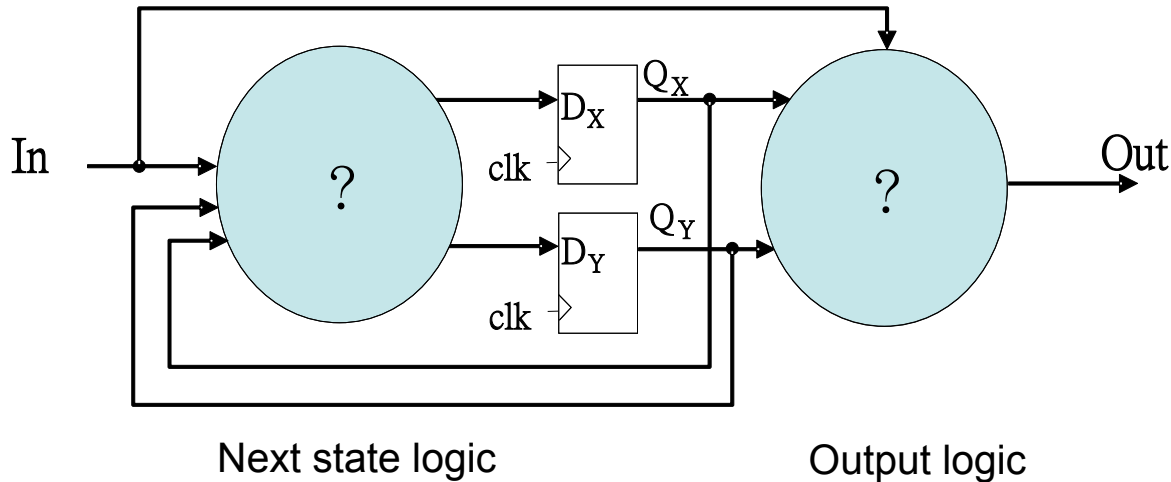

Input			Output		
	Current state		Next state		Output
In	$Q_X(t)$	$Q_Y(t)$	$Q_X(t+1)$	$Q_Y(t+1)$	Out
0	0	0	0	0	0
0	0	1	0	0	1
0	1	0	1	0	1
0	1	1	1	1	0
1	0	0	1	0	0
1	0	1	1	0	1
1	1	0	1	1	1
1	1	1	0	1	0



Input			Output		
	Current state		Next state		Output
In	$Q_X(t)$	$Q_Y(t)$	$Q_X(t+1)$	$Q_Y(t+1)$	Out
0	0	0	0	0	0
0	0	1	0	0	1
0	1	0	1	0	1
0	1	1	1	1	0
1	0	0	1	0	0
1	0	1	1	0	1
1	1	0	1	1	1
1	1	1	0	1	0

		$Q_X(t) Q_Y(t)$			
		00	01	11	10
D_X ($Q_X(t+1)$)	0	0	0	1	1
	1	1	1	0	1

		$Q_X(t) Q_Y(t)$			
		00	01	11	10
D_Y ($Q_Y(t+1)$)	0	0	0	1	0
	1	0	0	1	1

		$Q_X(t) Q_Y(t)$			
		00	01	11	10
Out	0	0	1	0	1
	1	0	1	0	1

$$D_X = \text{In}Q_X'(t) + \text{In}'Q_X(t) + Q_X(t)Q_Y'(t)$$


$$D_Y = Q_X(t)Q_Y(t) + \text{In}Q_X(t)$$

$$\text{Out} = Q_X(t)Q_Y'(t) + Q_X'(t)Q_Y(t)$$



$$D_X = \text{In}Q_X'(t) + \text{In}'Q_X(t) + Q_X(t)Q_Y'(t)$$

$$D_Y = Q_X(t)Q_Y(t) + \text{In}Q_X(t)$$
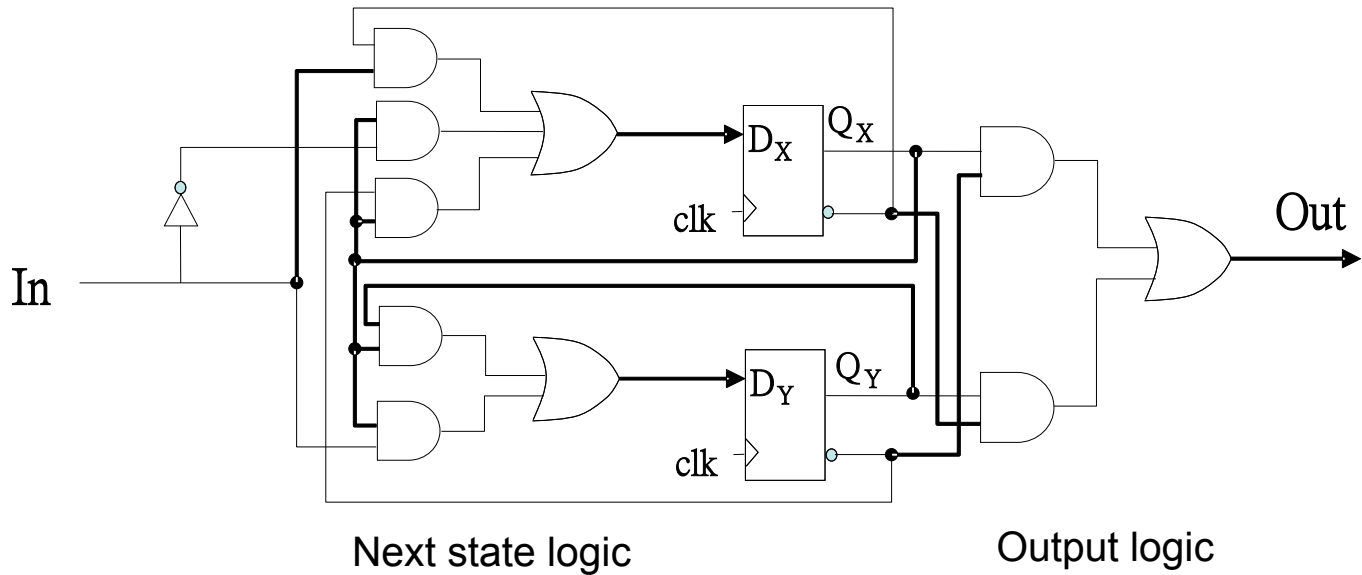
$$\text{Out} = Q_X(t)Q_Y'(t) + Q_X'(t)Q_Y(t)$$



Using JK flip-flop

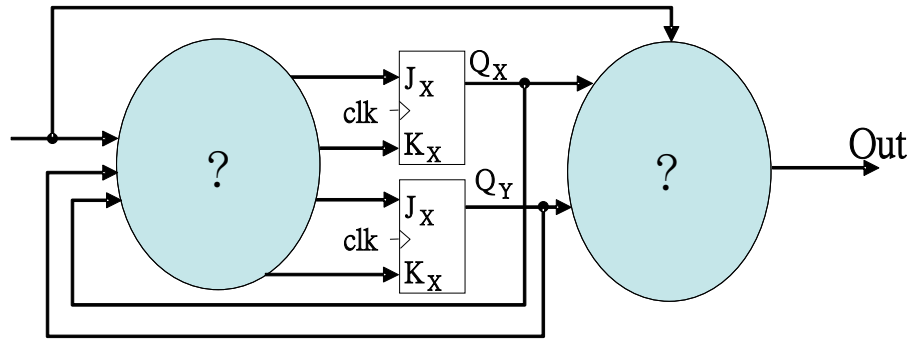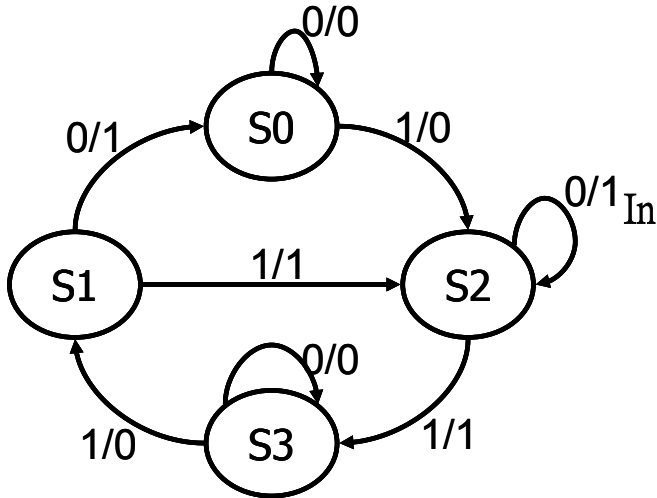

Next state logic

Output logic

Input			Output						
	current state		next state		X		Y		Out
In	Q _x (t)	Q _y (t)	Q _x (t+1)	Q _y (t+1)	J _x	K _x	J _y	K _y	Out
0	0	0	0	0	0	X	0	X	0
0	0	1	0	0	0	X	X	1	1
0	1	0	1	0	X	0	0	X	1
0	1	1	1	1	X	0	X	0	0
1	0	0	1	0	1	X	0	X	0
1	0	1	1	0	1	X	X	1	1
1	1	0	1	1	X	0	1	X	1
1	1	1	0	1	X	1	X	0	0

Synthesis using JK flip-flops

- A state diagram \Rightarrow flip-flop input functions
 - straightforward for D flip-flops
 - we need excitation tables for JK and T flip-flops

J	K	D	Q(t+1)	Function
0	0	Q(t)	Q(t)	no change
0	1	0	0	reset FF to 0
1	0	1	1	set FF to 1
1	1	Q'(t)	Q'(t)	complement output

T	D	Q(t+1)	
0	Q	Q(t)	no change
1	Q'	Q'(t)	complement

Table 5.12
Flip-Flop Excitation Tables

Q(t)	Q(t = 1)	J	K	Q(t)	Q(t = 1)	T
0	0	0	X	0	0	0
0	1	1	X	0	1	1
1	0	X	1	1	0	1
1	1	X	0	1	1	0

(a) JK

(b) T

Input			Output						
	current state		next state		X		Y		Out
In	$Q_X(t)$	$Q_Y(t)$	$Q_X(t+1)$	$Q_Y(t+1)$	J_X	K_X	J_Y	K_Y	Out
0	0	0	0	0	0	X	0	X	0
0	0	1	0	0	0	X	X	1	1
0	1	0	1	0	X	0	0	X	1
0	1	1	1	1	X	0	X	0	0
1	0	0	1	0	1	X	0	X	0
1	0	1	1	0	1	X	X	1	1
1	1	0	1	1	X	0	1	X	1
1	1	1	0	1	X	1	X	0	0

$Q(t)$	$Q(t+1)$	J	K
0	0	0	X
0	1	1	X
1	0	X	1
1	1	X	0

$Q_X(t) Q_Y(t)$

In	00	01	11	10
J_X				
0	0	0	X	X
1	1	1	X	X

$Q_X(t) Q_Y(t)$

In	00	01	11	10
K_X				
0	X	X	0	0
1	X	X	1	0

$Q_X(t) Q_Y(t)$

In	00	01	11	10
J_Y				
0	0	X	X	0
1	0	X	X	1

$Q_X(t) Q_Y(t)$

In	00	01	11	10
K_Y				
0	X	1	0	X
1	X	1	0	X

$Q_X(t) Q_Y(t)$

In	00	01	11	10
Out				
0	0	1	0	1
1	0	1	0	1

$$J_X = \text{In} \quad K_X = \text{In}Q_Y(t)$$


$$J_Y = \text{In}Q_X(t) \quad K_Y = Q_X'(t)$$

$$\text{Out} = Q_X(t)Q_Y'(t) + Q_X'(t)Q_Y(t)$$

$$J_X = \text{In} \quad K_X = \text{In}Q_Y(t)$$

$$J_Y = \text{In}Q_X(t) \quad K_Y = Q_X'(t)$$
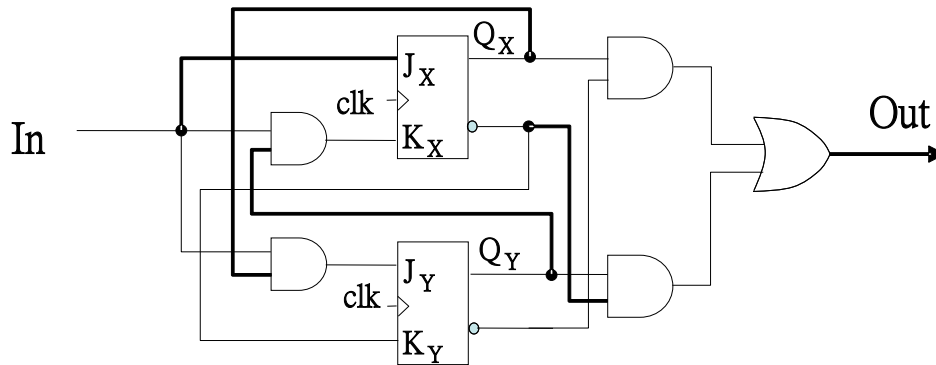
$$\text{Out} = Q_X(t)Q_Y'(t) + Q_X'(t)Q_Y(t)$$




Next state logic

Output logic



Difference?


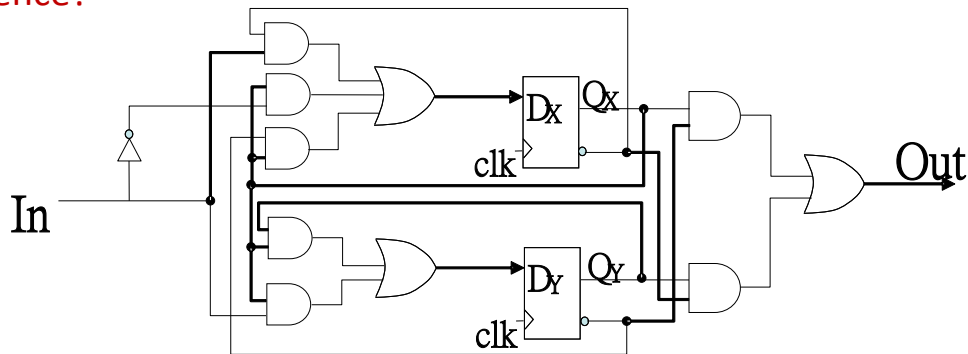


Next state logic

Output logic

Synchronous Counter

00、01、10、11

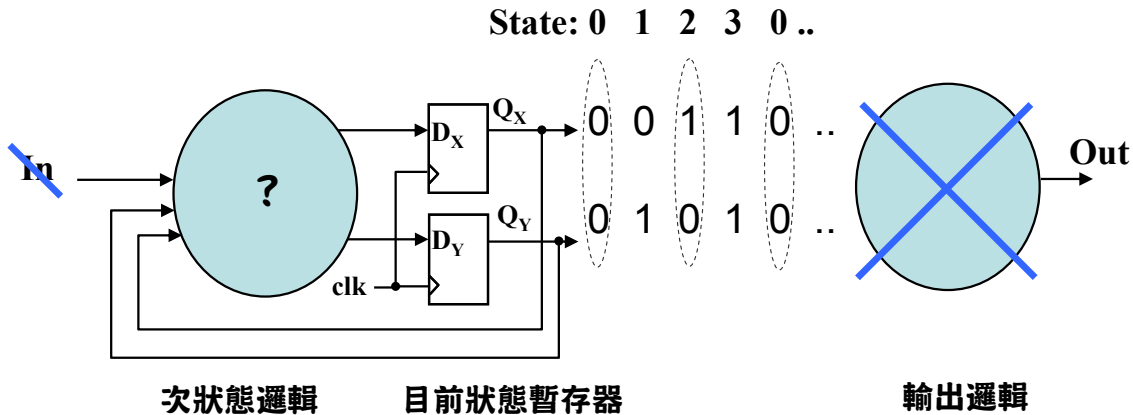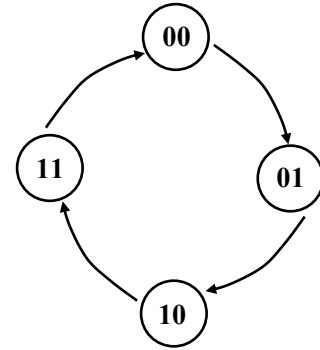

Using JK flip-flop

00、01、10、11

Input		Output					
current state		Next state		X		Y	
$Q_X(t)$	$Q_Y(t)$	$Q_X(t+1)$	$Q_Y(t+1)$	J_X	K_X	J_Y	K_Y
0	0	0	1	0	X	1	X
0	1	1	0	1	X	X	1
1	0	1	1	X	0	1	X
1	1	0	0	X	1	X	1

		$Q_Y(t)$	
		0	1
$Q_X(t)$	0		1
	1	X	X

		$Q_Y(t)$	
		0	1
$Q_X(t)$	0	X	X
	1		1

$$J_X = Q_Y(t) \quad K_X = Q_Y(t)$$


$$J_Y = 1 \quad K_Y = 1$$

		$Q_Y(t)$	
		0	1
$Q_X(t)$	0	1	X
	1	1	X

		$Q_Y(t)$	
		0	1
$Q_X(t)$	0	X	1
	1	X	1


$$J_X = Q_Y(t) \quad K_X = Q_Y(t)$$

$$J_Y = 1 \quad K_Y = 1$$

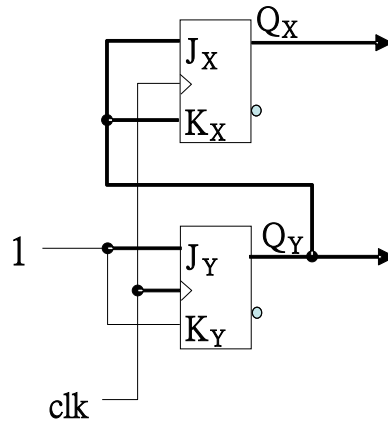

Next state logic

Using D flip-flop

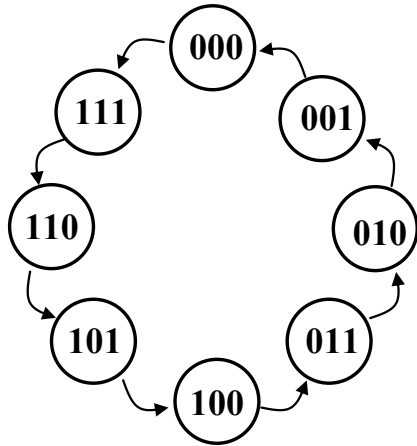

Current state			Next state		
$Q_X(t)$	$Q_Y(t)$	$Q_Z(t)$	$Q_X(t+1)$	$Q_Y(t+1)$	$Q_Z(t+1)$
0	0	0	1	1	1
0	0	1	0	0	0
0	1	0	0	0	1
0	1	1	0	1	0
1	0	0	0	1	1
1	0	1	1	0	0
1	1	0	1	0	1
1	1	1	1	1	0

		$Q_Y(t)Q_Z(t)$			
		00	01	11	10
$Q_X(t)$	0	1			
	1		1	1	1

D_X
 $Q_X(t+1)$

		$Q_Y(t)Q_Z(t)$			
		00	01	11	10
$Q_X(t)$	0	1		1	
	1	1		1	

D_Y
 $Q_Y(t+1)$

		$Q_Y(t)Q_Z(t)$			
		00	01	11	10
$Q_X(t)$	0	1			1
	1	1			1

D_Z
 $Q_Z(t+1)$

$$Q_X(t+1) = D_X = Q_X(t)Q_Z(t) + Q_X(t)Q_Y(t) + Q_X'(t)Q_Y'(t)Q_Z'(t) \circ$$


$$Q_Y(t+1) = D_Y = Q_Y'(t)Q_Z'(t) + Q_Y(t)Q_Z(t) \circ$$

$$Q_Z(t+1) = D_Z = Q_Z'(t) \circ$$

$$Q_X(t+1) = D_X = Q_X(t)Q_Z(t) + Q_X(t)Q_Y(t) + Q_X'(t)Q_Y'(t)Q_Z'(t) \circ$$

$$Q_Y(t+1) = D_Y = Q_Y'(t)Q_Z'(t) + Q_Y(t)Q_Z(t) \circ$$

$$Q_Z(t+1) = D_Z = Q_Z'(t) \circ$$

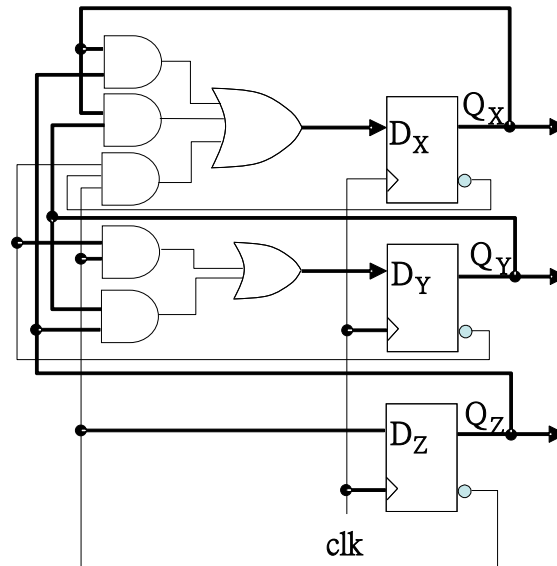

Next state logic