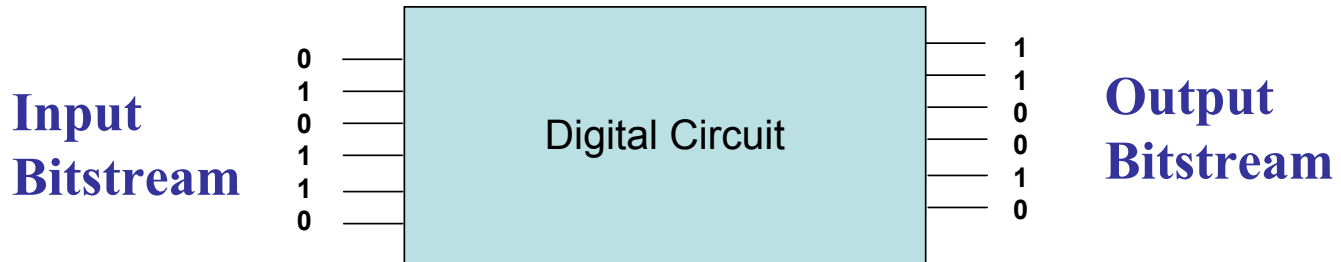


A Digital Circuit/System

Processing/Computing



數位電路都是由一連串的0或1的位元(bit)來表示輸入/輸出訊號, 所以電路內的運算處理過程也應以二進制0或1的方式進行。電路設計者需要決定那些0或1代表什麼資訊、如何解釋。

- (1)如何透過輸入裝置將輸入訊號輸入系統中
- (2)電路如何執行所需0與1的計算
- (3)如何將結果展示於輸出裝置上

例如：按鍵被按住表示輸入1，按鍵被放開表示輸入0

輸出0101時，螢幕秀出數字5；

輸出1001時，螢幕秀出數字9。

或是輸出0表示某個LED燈要點亮，輸出1表示某個LED燈要熄滅。



Basic Elements of a Digital Circuit

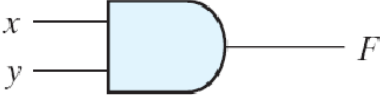
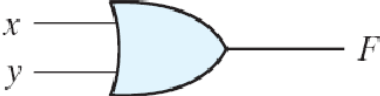
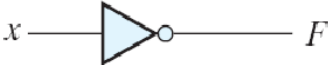

Name	Graphic symbol	Algebraic function	Truth table 真值表
			input output
AND		$F = xy$	$x \quad y \quad \quad F$
			0 0 0
			0 1 0
			1 0 0
			1 1 1
OR		$F = x + y$	$x \quad y \quad \quad F$
			0 0 0
			0 1 1
			1 0 1
			1 1 1
Inverter		$F = x'$	$x \quad \quad F$
			0 1
			1 0
Buffer		$F = x$	$x \quad \quad F$
			0 0
			1 1

Figure 2.5 Digital logic gates (continued)

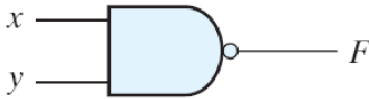
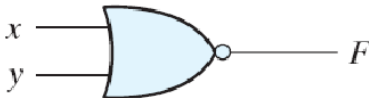
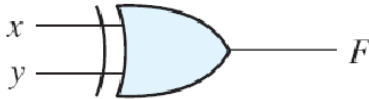
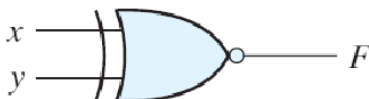
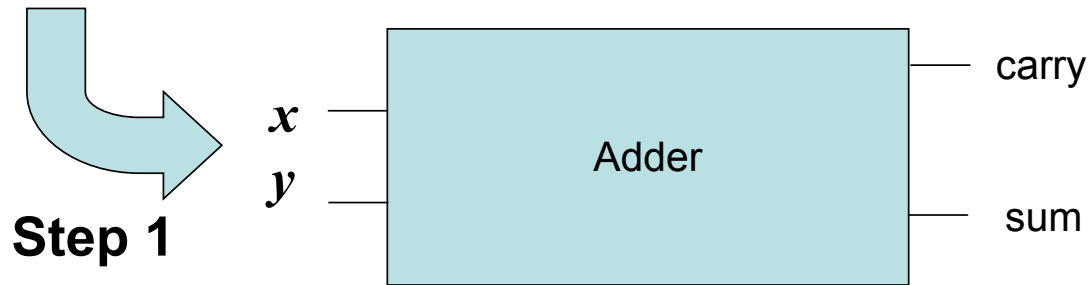
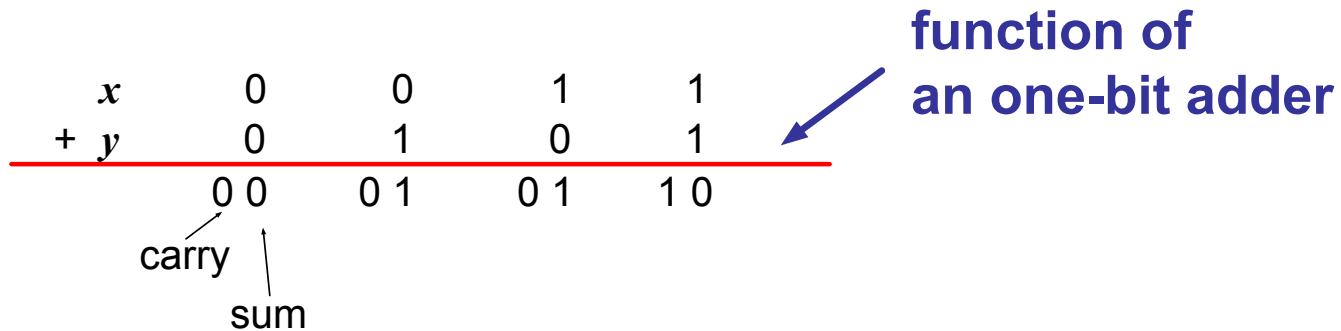
NAND	 $F = (xy)'$	<table> <tr> <th>x</th><th>y</th><th>F</th></tr> <tr><td>0</td><td>0</td><td>1</td></tr> <tr><td>0</td><td>1</td><td>1</td></tr> <tr><td>1</td><td>0</td><td>1</td></tr> <tr><td>1</td><td>1</td><td>0</td></tr> </table>	x	y	F	0	0	1	0	1	1	1	0	1	1	1	0
x	y	F															
0	0	1															
0	1	1															
1	0	1															
1	1	0															
NOR	 $F = (x + y)'$	<table> <tr> <th>x</th><th>y</th><th>F</th></tr> <tr><td>0</td><td>0</td><td>1</td></tr> <tr><td>0</td><td>1</td><td>0</td></tr> <tr><td>1</td><td>0</td><td>0</td></tr> <tr><td>1</td><td>1</td><td>0</td></tr> </table>	x	y	F	0	0	1	0	1	0	1	0	0	1	1	0
x	y	F															
0	0	1															
0	1	0															
1	0	0															
1	1	0															
Exclusive-OR (XOR)	 $F = xy' + x'y$ $= x \oplus y$	<table> <tr> <th>x</th><th>y</th><th>F</th></tr> <tr><td>0</td><td>0</td><td>0</td></tr> <tr><td>0</td><td>1</td><td>1</td></tr> <tr><td>1</td><td>0</td><td>1</td></tr> <tr><td>1</td><td>1</td><td>0</td></tr> </table>	x	y	F	0	0	0	0	1	1	1	0	1	1	1	0
x	y	F															
0	0	0															
0	1	1															
1	0	1															
1	1	0															
Exclusive-NOR or equivalence	 $F = xy + x'y'$ $= (x \oplus y)'$	<table> <tr> <th>x</th><th>y</th><th>F</th></tr> <tr><td>0</td><td>0</td><td>1</td></tr> <tr><td>0</td><td>1</td><td>0</td></tr> <tr><td>1</td><td>0</td><td>0</td></tr> <tr><td>1</td><td>1</td><td>1</td></tr> </table>	x	y	F	0	0	1	0	1	0	1	0	0	1	1	1
x	y	F															
0	0	1															
0	1	0															
1	0	0															
1	1	1															

Figure 2.5 Digital logic gates

A Simple Digital Circuit --- Adder (1/3)



Step 2

Truth Table

x	y	carry	sum
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0


A Simple Digital Circuit --- Adder (2/3)

x	y	C	
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

Truth Table

The same

Step 3

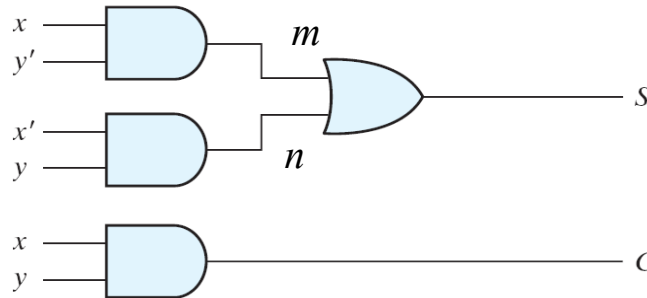


(a) $S = xy' + x'y$
 $C = xy$

Why?


x	y	x'	y'	m	n	C	S
0	0	1	1	0	0	0	
0	1	1	0	0	1	0	
1							

A Simple Digital Circuit --- Adder (3/3)

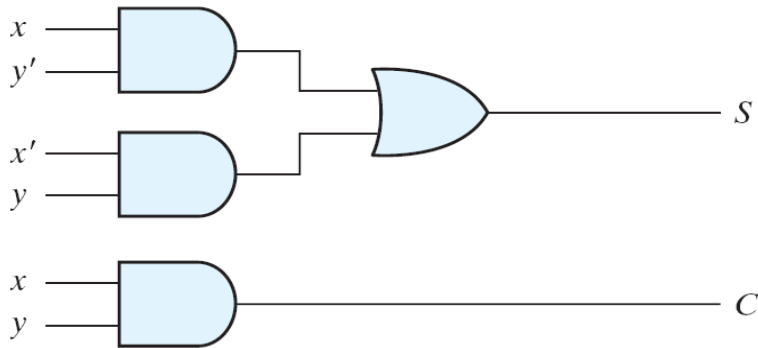


(a) $S = xy' + x'y$
 $C = xy$

One-bit Adder

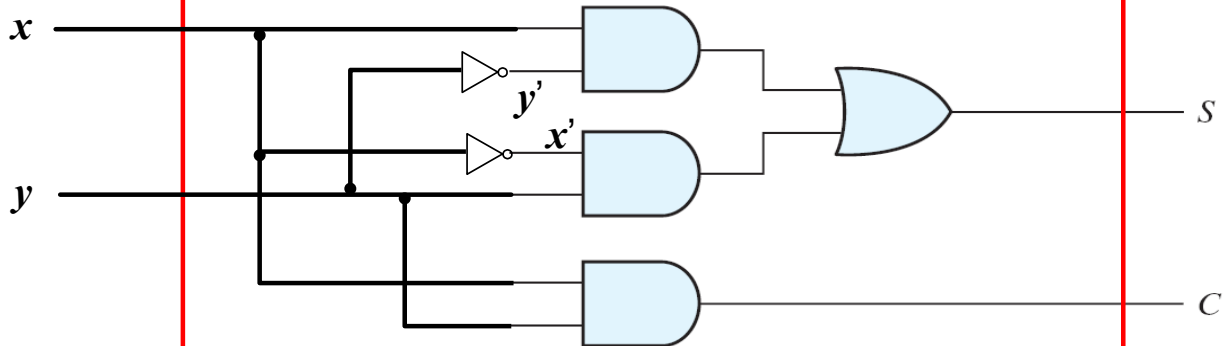

(a) $S = xy' + x'y$
 $C = xy$


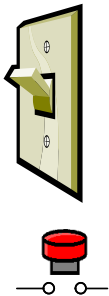


Constructing Gates

How to implement the digital circuit?


How to realize those different gates?

→ Semiconductor Technology

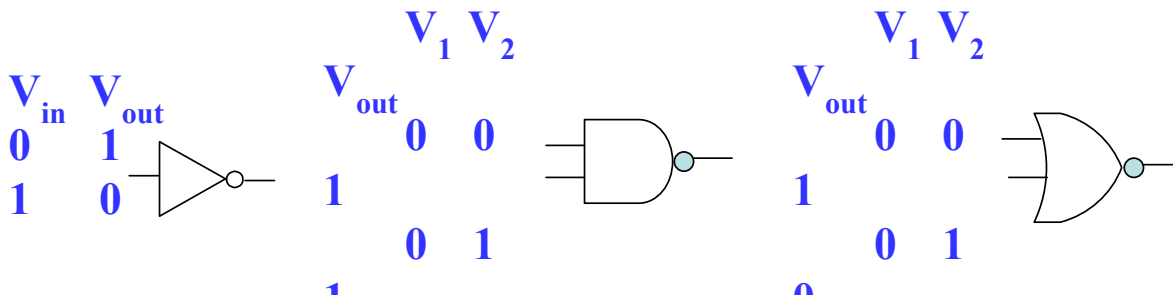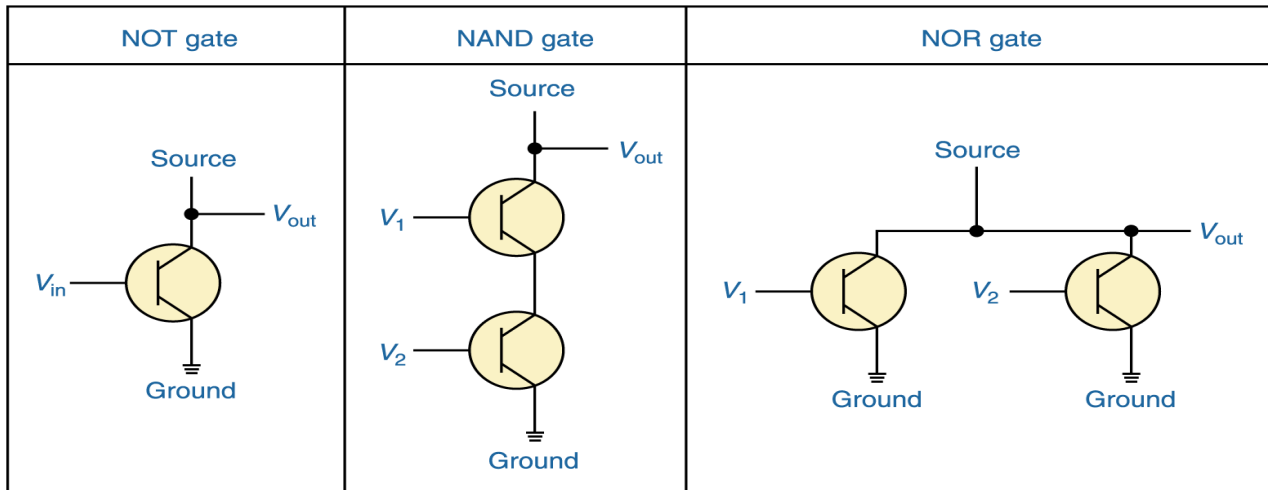


MOS電晶體示意圖 (semiconductor)

Transisto
r

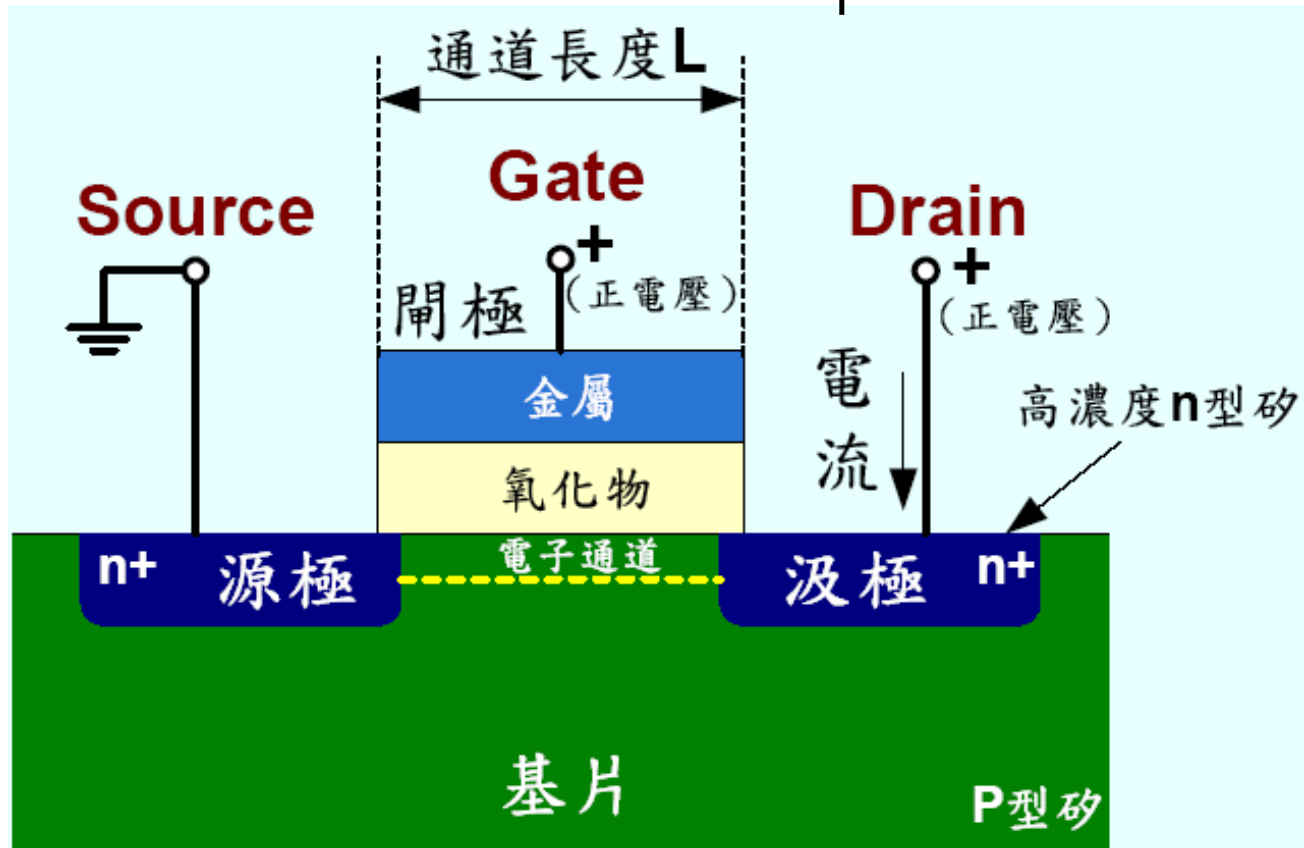

Transistor (電晶體)

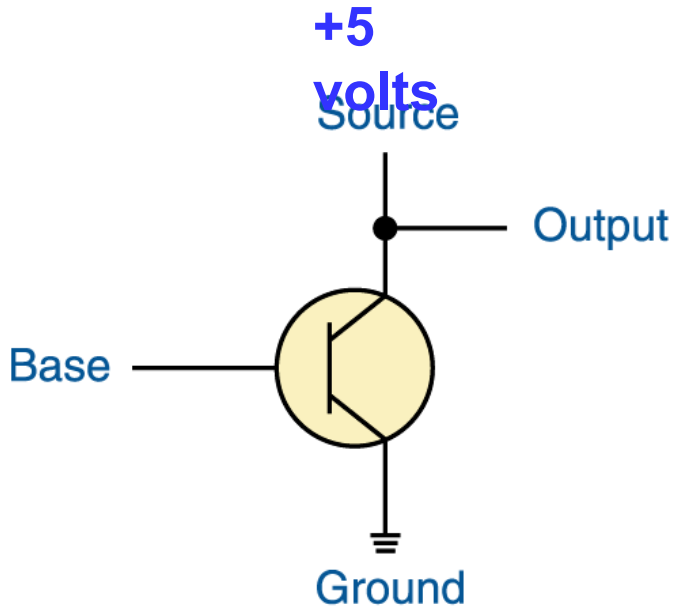

- A transistor has three terminals
 - A source (feed with 5 volts)
 - A base
 - An emitter, typically connected to a ground wire
- If the base signal is high (close to +5 volts), the source signal is grounded and the output signal is low (0). If the base signal is low (close to 0 volts), the source signal stays high and the output signal is high (1)

Circuits

- **Gate (1 gate \approx 2~14 transistors)**

A combination of interacting transistors

- **Circuit**

A combination of interacting gates designed to accomplish a specific logical function → **Integrated Circuit (IC)**

- **System**


A combination of some circuits ? ? ?

→ **PCB (printed circuit board)**



IC Design (with CMOS semiconductor technology)

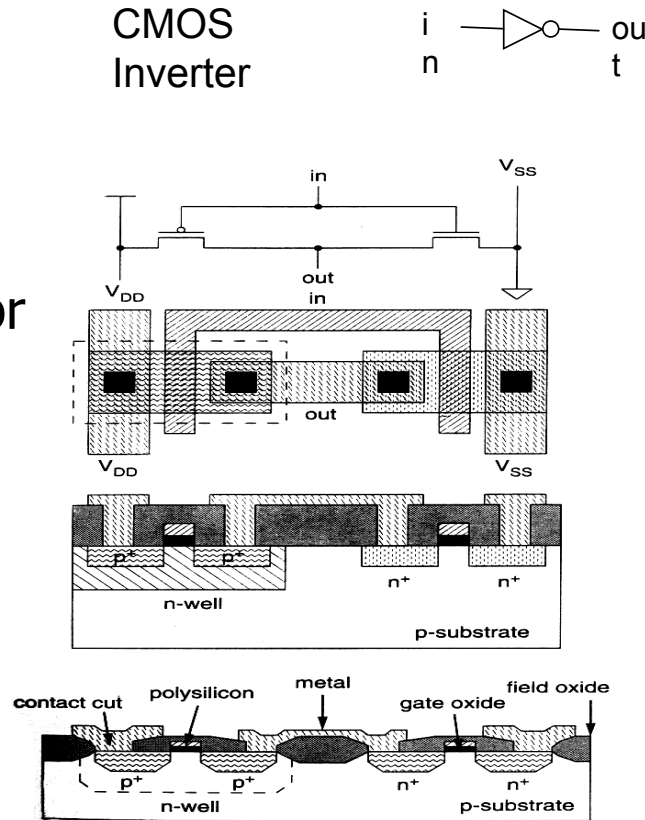One npn transistor
and one pnp transistor
are used to construct
one inverter.





done by
chip
designer


maskin
g



done by
TSMC,
UMC

Packing,
Testing




Chip/Circuit Everywhere!

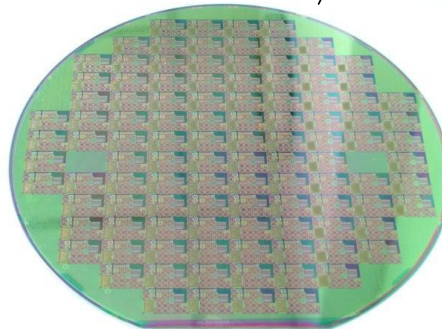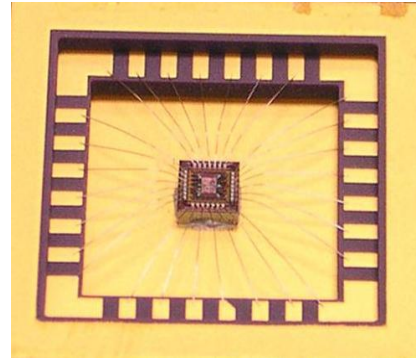




in \rightarrow  out

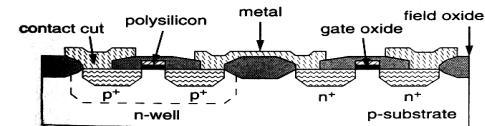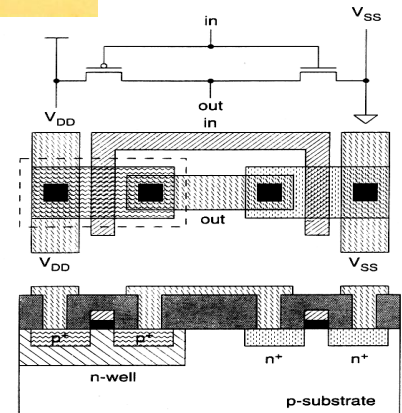

Integrated Circuits

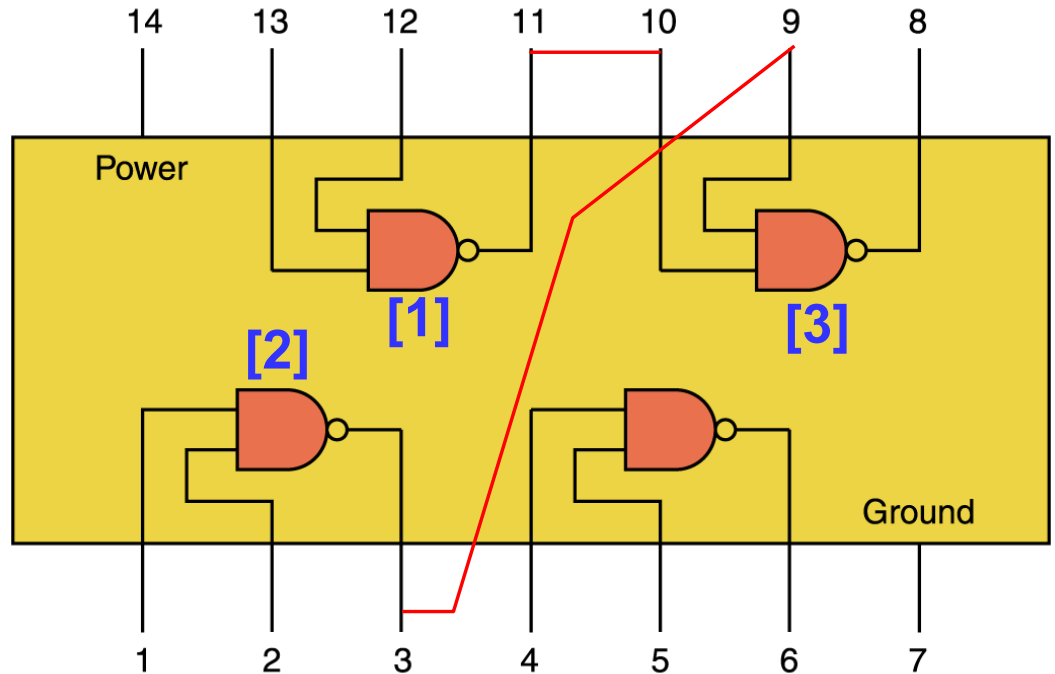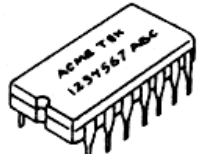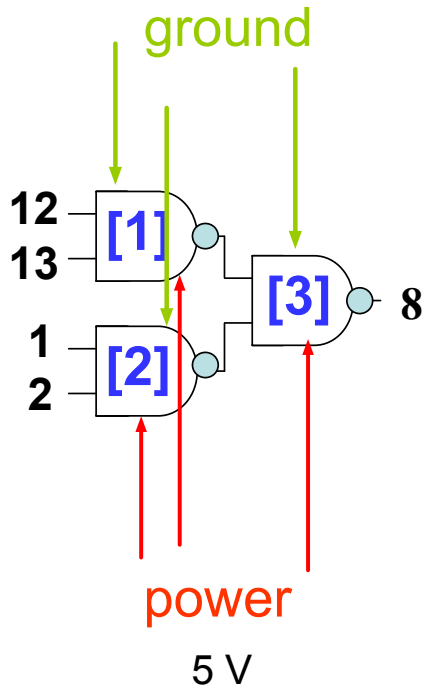

Integrated Circuits



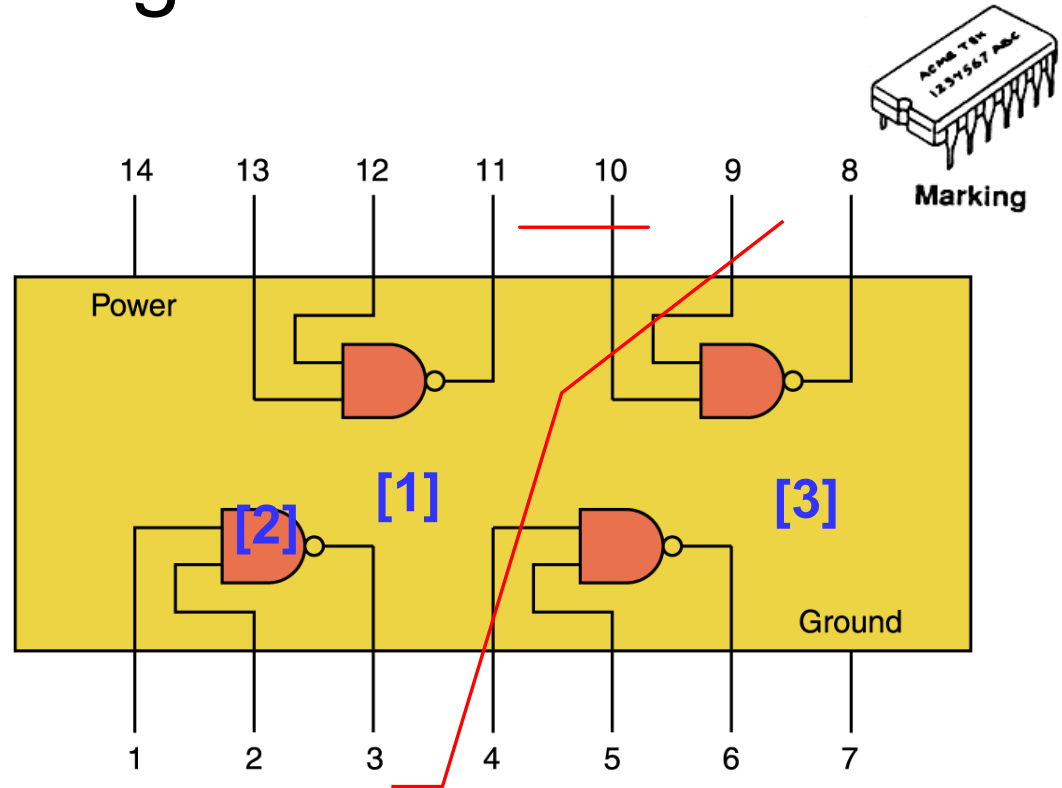
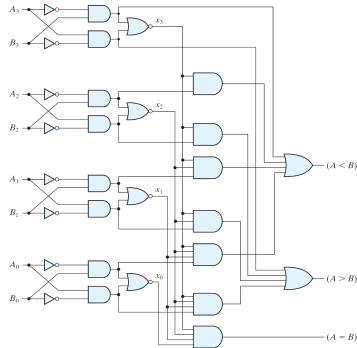
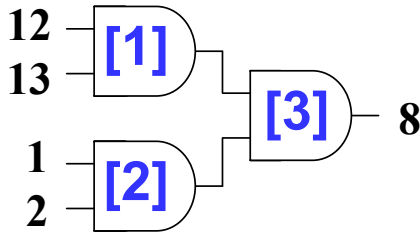


• Multiple chips (gates) combined to a circuit to solve a specific problem(解決特定問題)




2. A dedicated chip (ASIC, application specific integrated circuit)



5 V

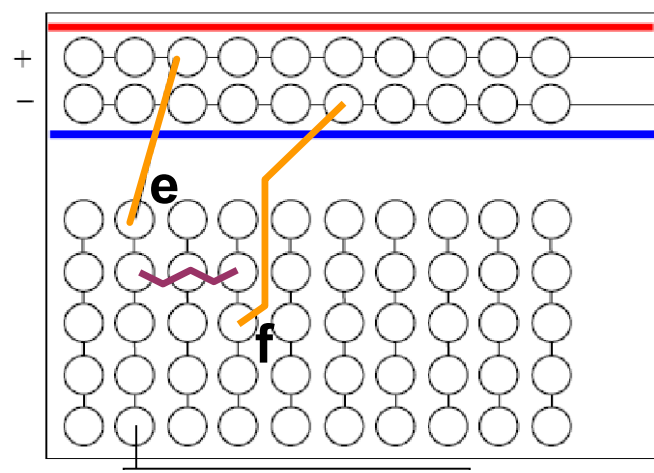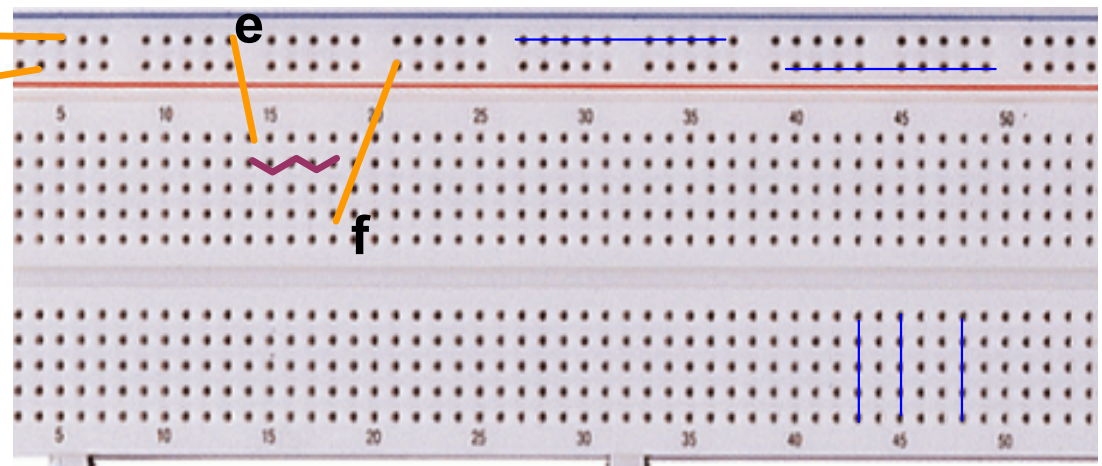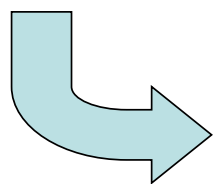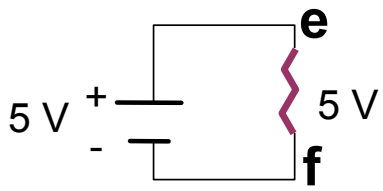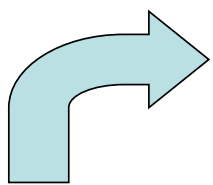

Two ways

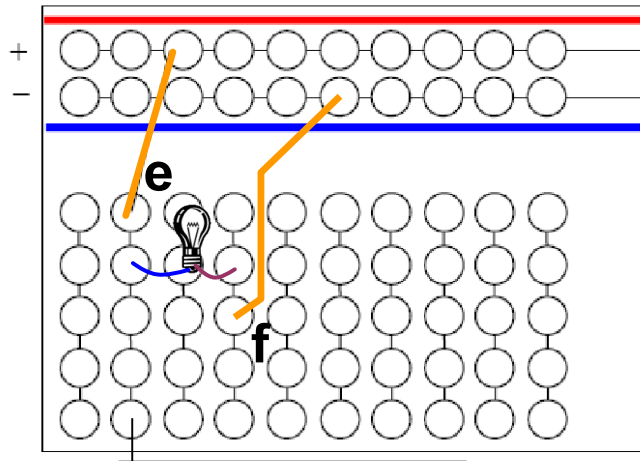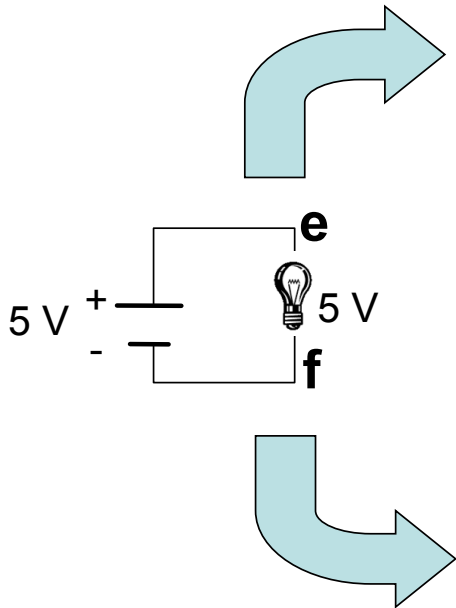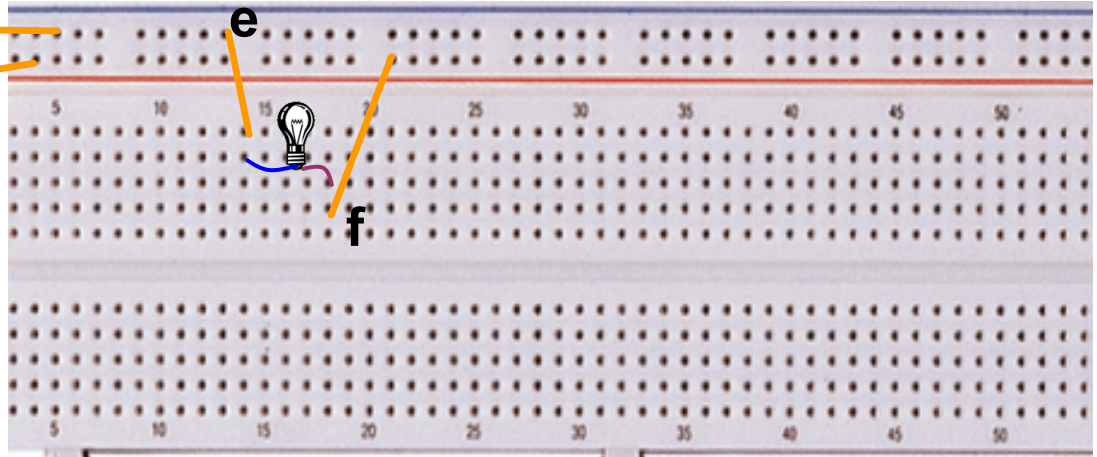

VCC


GND

Two ways

Solderless Breadboard




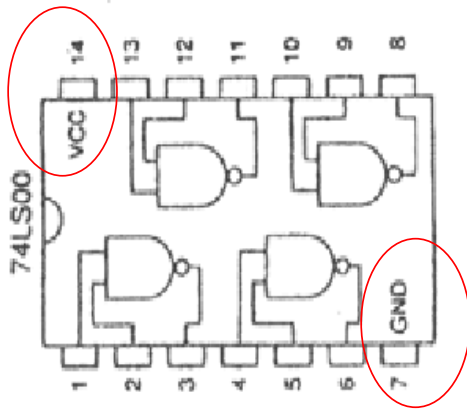- **Example**
 - **VCC & GND must be connected**



Check the data sheet !!!!!

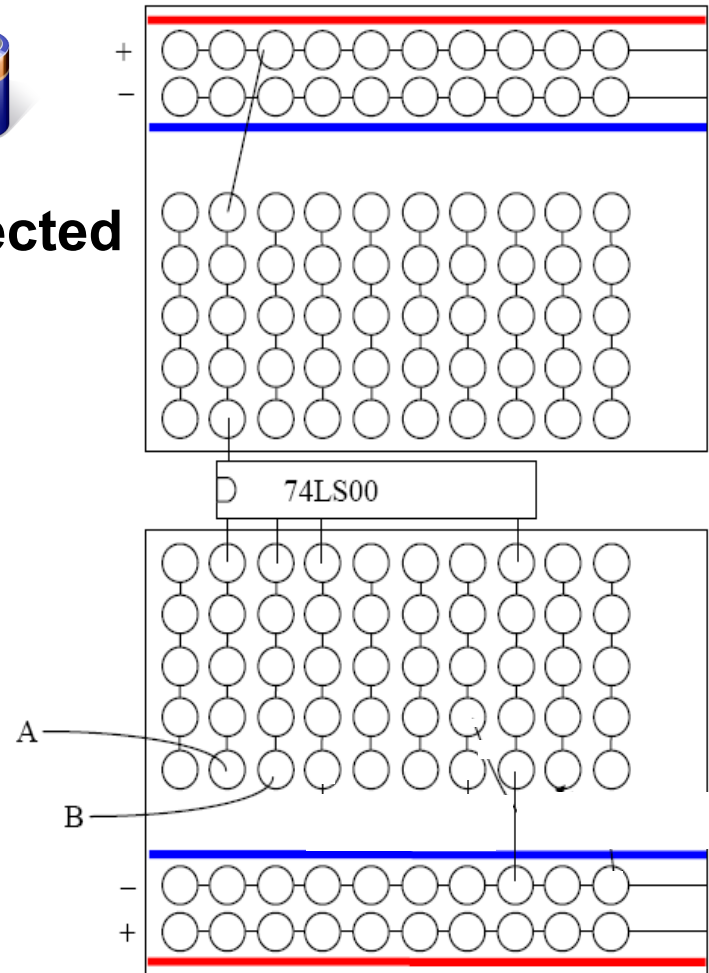Different ICs might require different voltages (5V, 3.3V, 1.8V,)



Specification (datasheet) of ICs

TTL Combinational SSI Devices

