




成功大學

National Cheng Kung University

# Chapter 3


Arithmetic for Computers

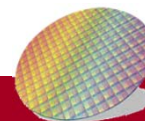

# Basic Arithmetic Logic Unit


From B.5 (Constructing a Basic Arithmetic Logic Unit)

- Basic ALU

 


One-bit ALU that performs **AND** and **OR**

Operation(Op.)	Funct.
0	a AND b
1	a OR b


 


Operation(Op.)	Funct.
0	a AND b
1	a OR b
2	a + b

 

 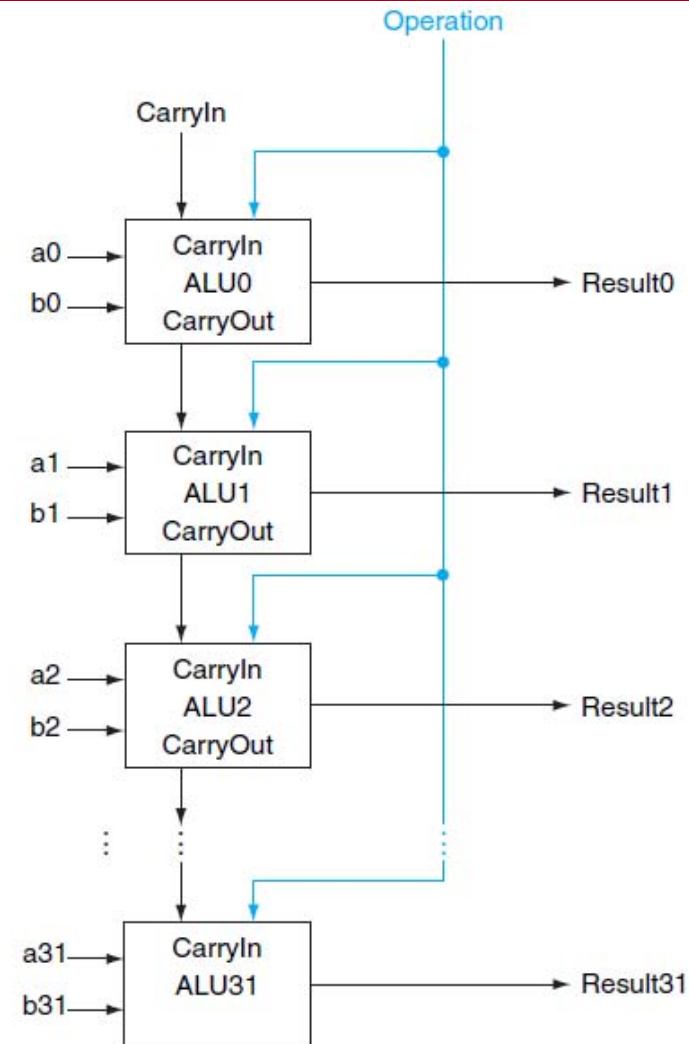
# 32-bit ALU

- Cascading 1-bit ALU to 32-bit ALU
- **carry-out** is the **carry-in** of the next bit



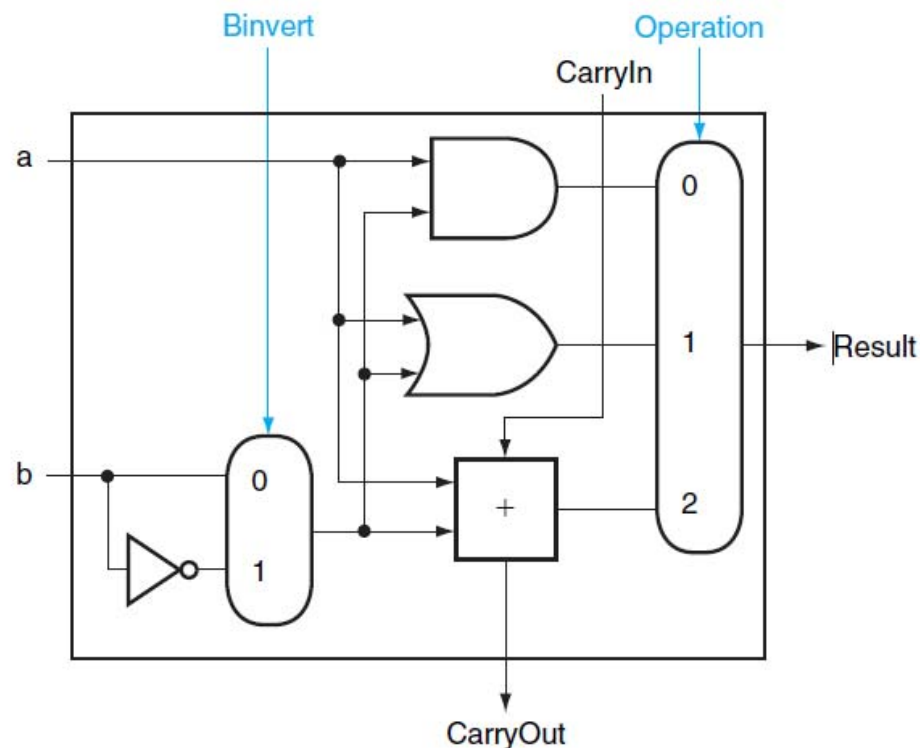
# Enhanced Arithmetic Logic Unit

- ALU that performs (a **AND** b), (a **OR** b) and (a + b ) and (a- b= $a + \bar{b} + 1$  )
- To perform a-b => Binvert=**1** and carryIn=**1**




$$a - b = a + \bar{b} + 1$$

Binvert	CarryIn	Op.	Function
0	X	0	a and b
0	X	1	a or b
0	0	2	a + b
1	1	2	a-b

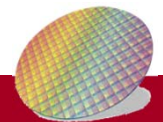

# Enhanced Arithmetic Logic Unit


- Enhanced with **NOR** and **NAND**

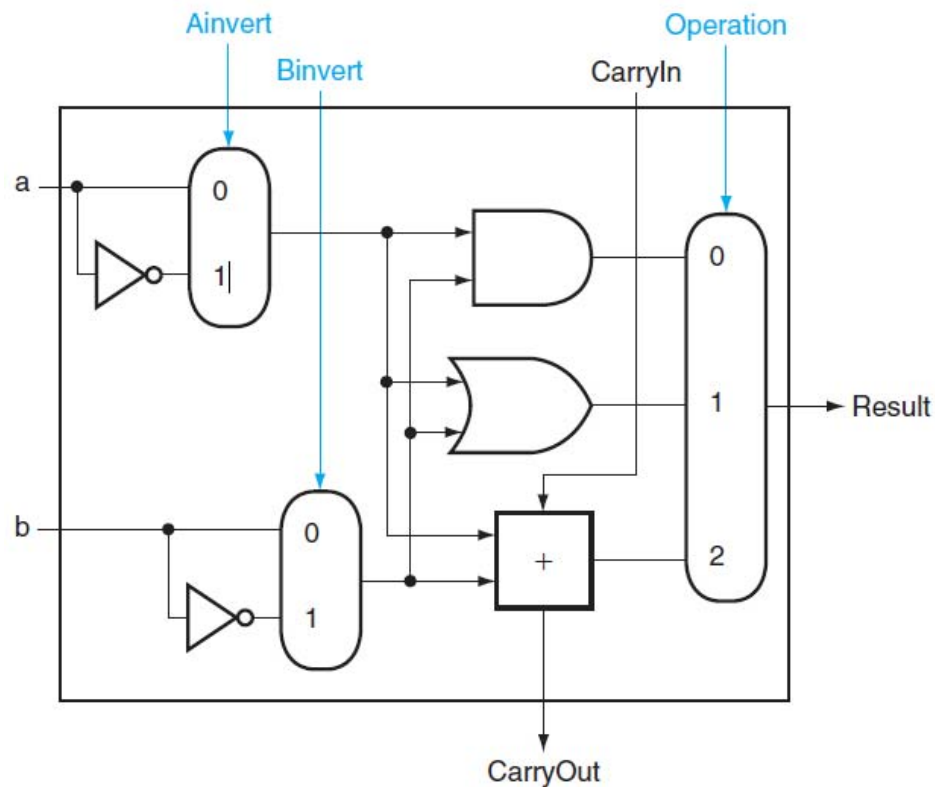

$$\overline{a} \overline{b} = \overline{a} \vee \overline{b}$$

$$\overline{a \vee b} = \overline{a} \overline{b}$$

Ainvert	Binvert	CarryIn	Op.	Func.
0	0	X	0	a and b
0	0	X	1	a or b
0	0	0	2	a + b
0	1	1	2	a-b
1	1	X	0	$\overline{a + b}$
1	1	X	1	$\overline{a} \overline{b}$


 


# ALUs with Set Less Than

Review: Set less than

`slt $t0 $t1 $t2`  $\Rightarrow$  When  $\$t1 < \$t2$ ,  $\$t0 = 1$ , otherwise  $\$t0 = 0$

 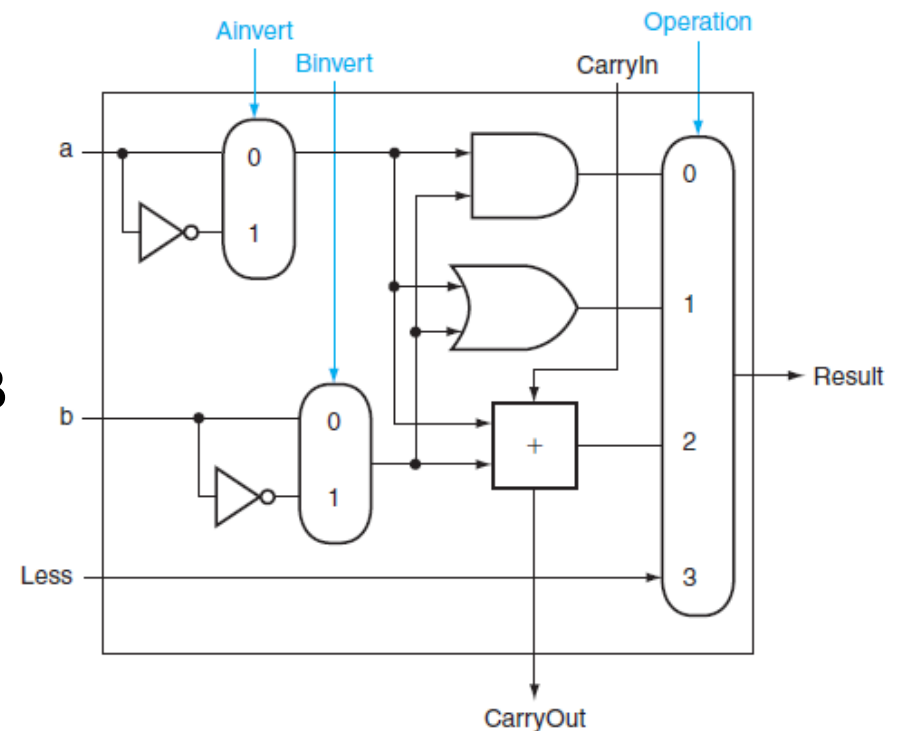- Use  $a-b$  to implement slt
  - When  $a-b < 0$ , signed bit = 1
  - When  $a-b \geq 0$ , signed bit = 0
- Less signal is the **LSB** that
  - Connect to the **signed** bit of MSB (See next slide)
  - Other signals are assigned to 0







# 32-bit ALU with Set Less than

- Less signal= $\Rightarrow$ 
  - Connect LSB to the signed bit of MSB
  - Other signals are assigned to 0


When  $a_{31}...a_0 < b_{31}...b_0$ , result is  $0.....1$ , otherwise  $0.....0$

 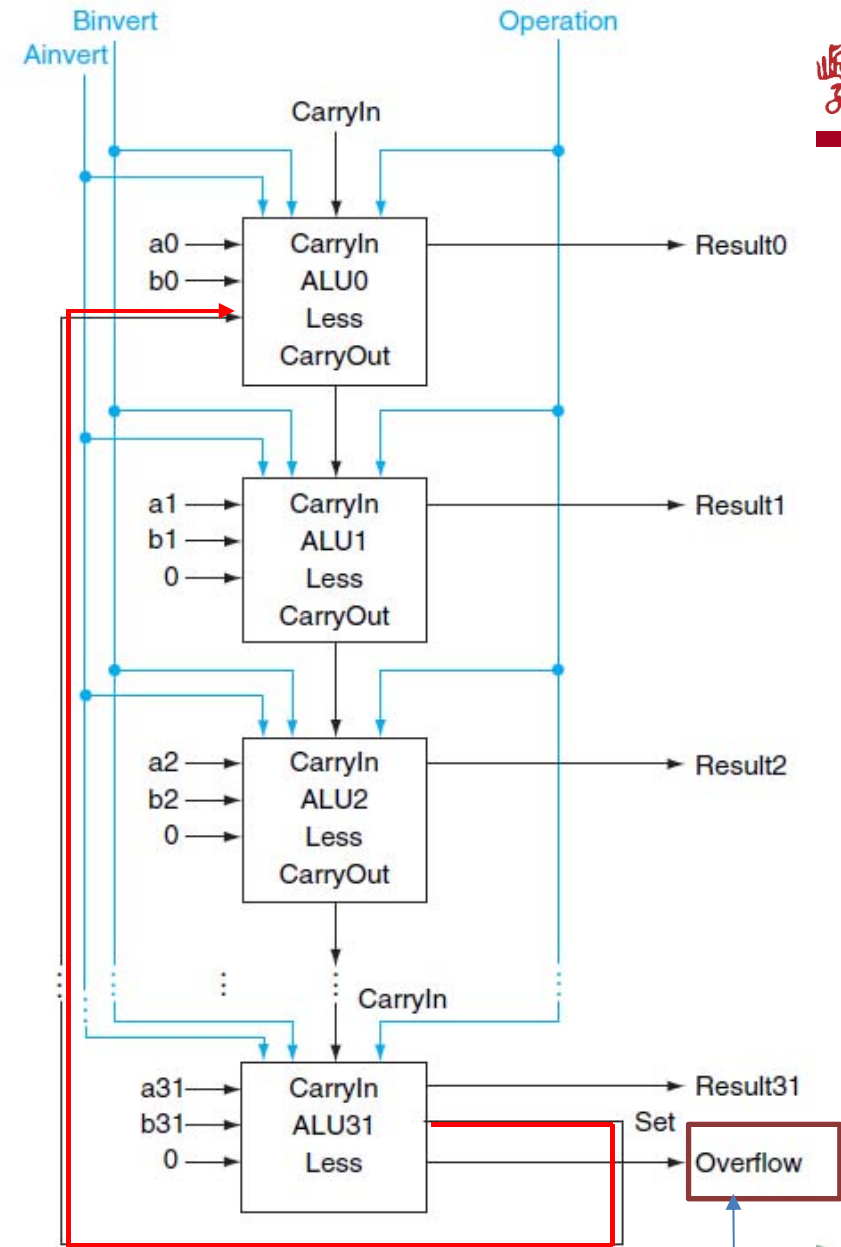Note that **MSB** is different than other bits= $\Rightarrow$  it has one additional signal (Overflow) which will be discussed later



# Integer Addition and Subtraction


- Addition Example:  $7 + 6$

 

- Subtraction Example:  $7 - 6 = 7 + (-6)$

$$\begin{array}{r}
 00000111 \\
 - 00000110 \\
 \hline
 00000001
 \end{array}$$
 
$$\begin{array}{r}
 +7: 0000\ 0000\ \dots\ 0000\ 0111 \\
 +(-6): 1111\ 1111\ \dots\ 1111\ 1010 \\
 \hline
 +1: 0000\ 0000\ \dots\ 0000\ 0001
 \end{array}$$








# Overflow

- Overflow : Sum/difference of two 32-bit numbers is too large to be represented in 32 bits.

$$\begin{array}{rcl} \text{Bit } 31 & 30 & \\ 0111 & 1111 \dots 1111 & = 2,147,483,647 \\ +) & 0000 & 0000 \dots 0010 = 2 \\ \hline 10 & \dots & 0001 = -2,147,483,647 \end{array}$$

check sign bit

 


## Overflow condition

- Exception: An unscheduled event that disrupts program execution; used to detect **overflow**.
- Situation that overflow occurs for signed integers
- Instruction that **causes** exception when overflow: **add, addi, sub**
- Instruction that **does not cause exception** when overflow: **addu, addiu, subu**

Operation	A	B	Result when Overflow
A+B	A>=0	B>=0	<0
A+B	<0	<0	>=0
A-B	A>=0	B<0	<0
A-B	A<0	B>=0	>=0



$$\begin{array}{r} 0111 \\ +0001 \\ \hline 1000 \end{array} \quad 7+1 \neq -8$$
 
$$\begin{array}{r} 1111 \\ +1000 \\ \hline 0111 \end{array} \quad -1+(-8) \neq 7$$




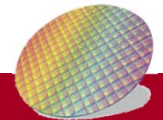 
## How to handle overflow in HW?

- MIPS detects overflow and causes **exception** (which is essentially an unplanned procedure call).
- Steps: (HW interrupt)
  - The address of the instruction that caused overflow is saved in a **EPC (exception program counter) register (\$R14 in Coprocessor 0)**
  - Jump to the **service routine** for that exception
  - Return to the program
- MIPS uses
  - Instruction “**move from CoProc 0 (MFC0)**” to copy **EPC** into a register so that MIPS software can return to the **offending** instruction via “**jr \$reg**” instruction.



# Exception flow

 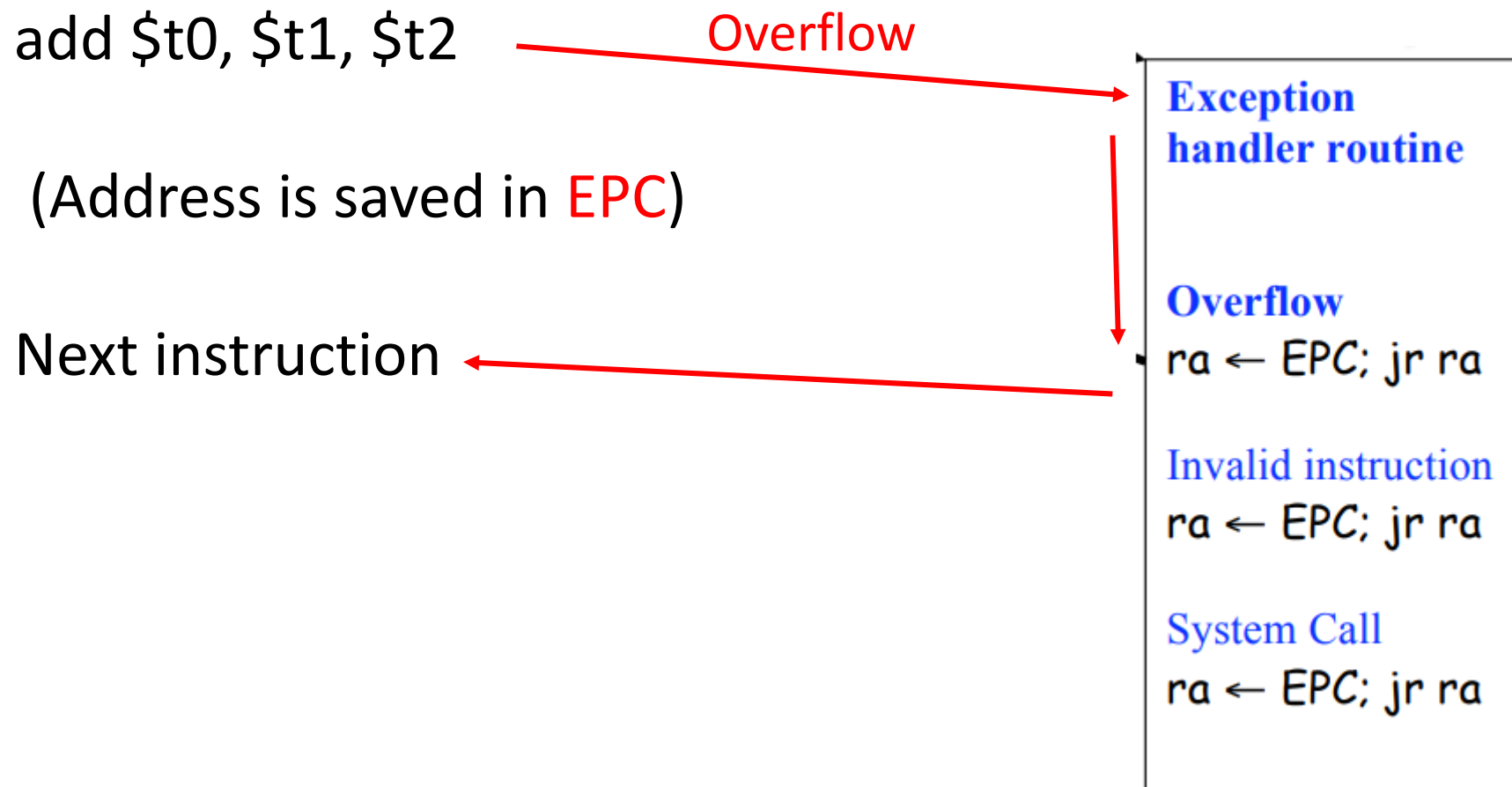


# Final 32-bit ALU

- Binvert is compatible to CarryIn => Connect **Binvert** to CarryIn  
=> is renamed to Bnegate
- Add **Zero detection circuit** => If all bit is 0 => Zero=1

Ainvert	Binvert	CarryIn	Op.	Func.
0	0	X	0	a and b
0	0	X	1	a or b
0	0	0	2	a + b
0	1	1	2	a - b
0	1	1	3	slt

Bnegate	Op[1:0]	Func.
0	00	a and b
0	01	a or b
0	10	a + b
1	10	a - b
1	11	slt

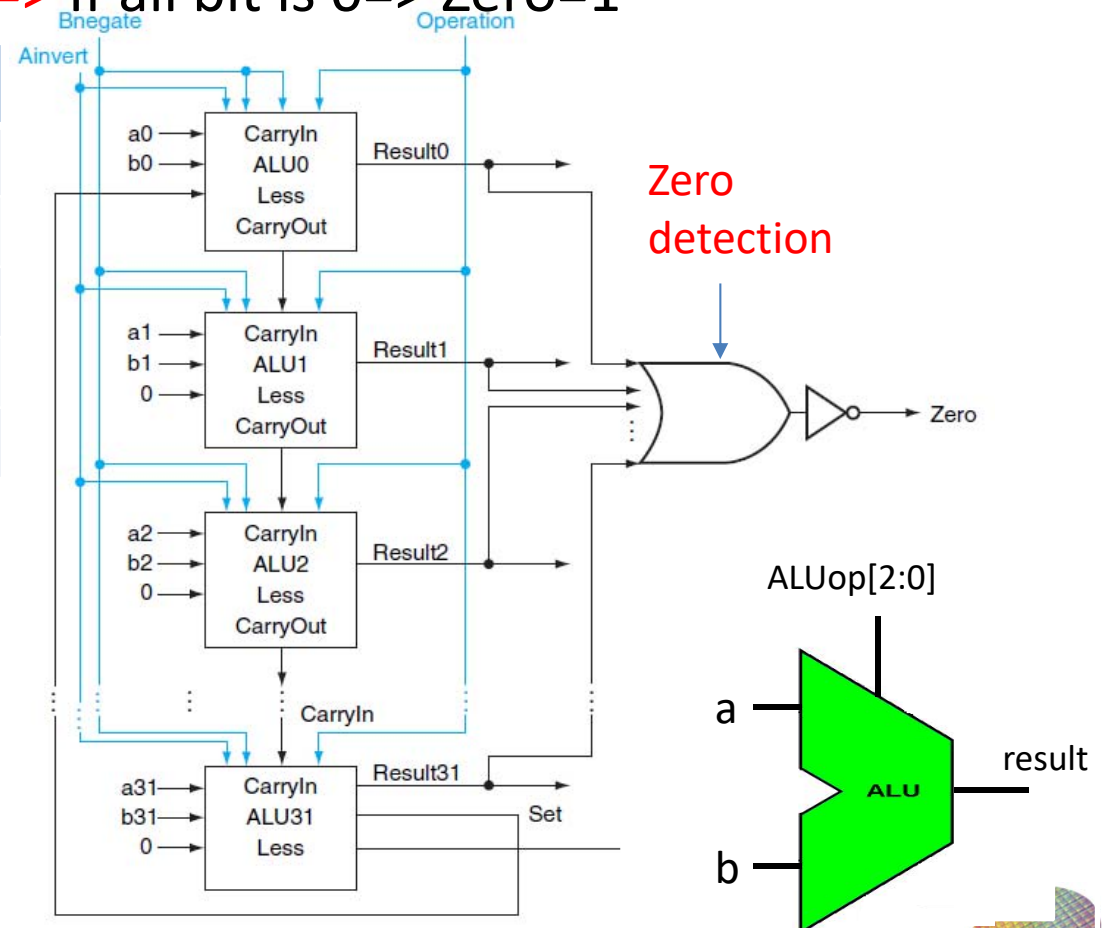

# Recap: Faster adder-Carry Lookahead

- Taught in **digital system design** course

$$g_i = a_i b_i$$



$$p_i = a_i + b_i$$

$$c1 = g0 + (p0 \cdot c0)$$

$$c2 = g1 + (p1 \cdot g0) + (p1 \cdot p0 \cdot c0)$$



$$c3 = g2 + (p2 \cdot g1) + (p2 \cdot p1 \cdot g0) + (p2 \cdot p1 \cdot p0 \cdot c0)$$
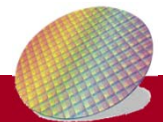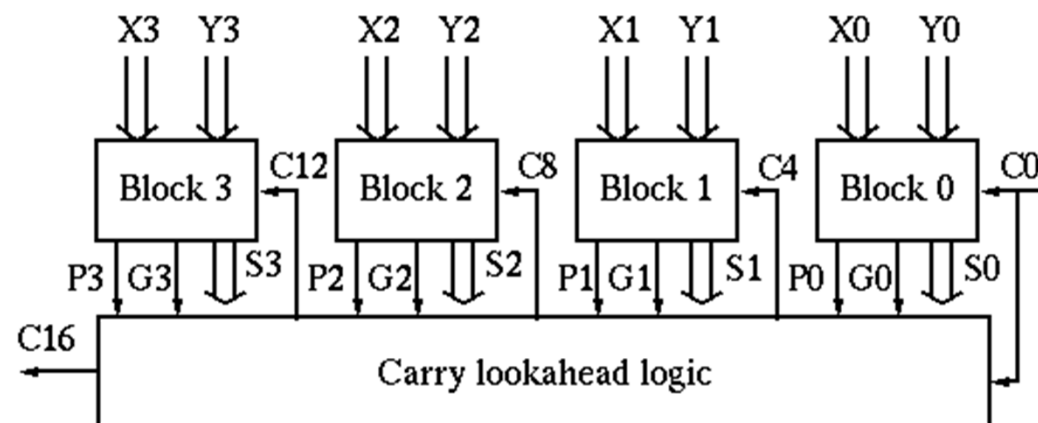
$$c4 = g3 + (p3 \cdot g2) + (p3 \cdot p2 \cdot g1) + (p3 \cdot p2 \cdot p1 \cdot g0) + (p3 \cdot p2 \cdot p1 \cdot p0 \cdot c0)$$



  
# Multiplication

- Binary multiplication is just a *bunch* of right shifts and adds




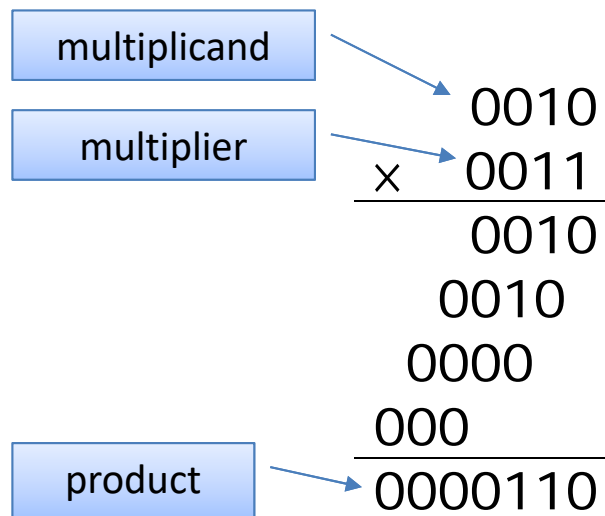
# Multiplication

- Start with long-multiplication approach



 
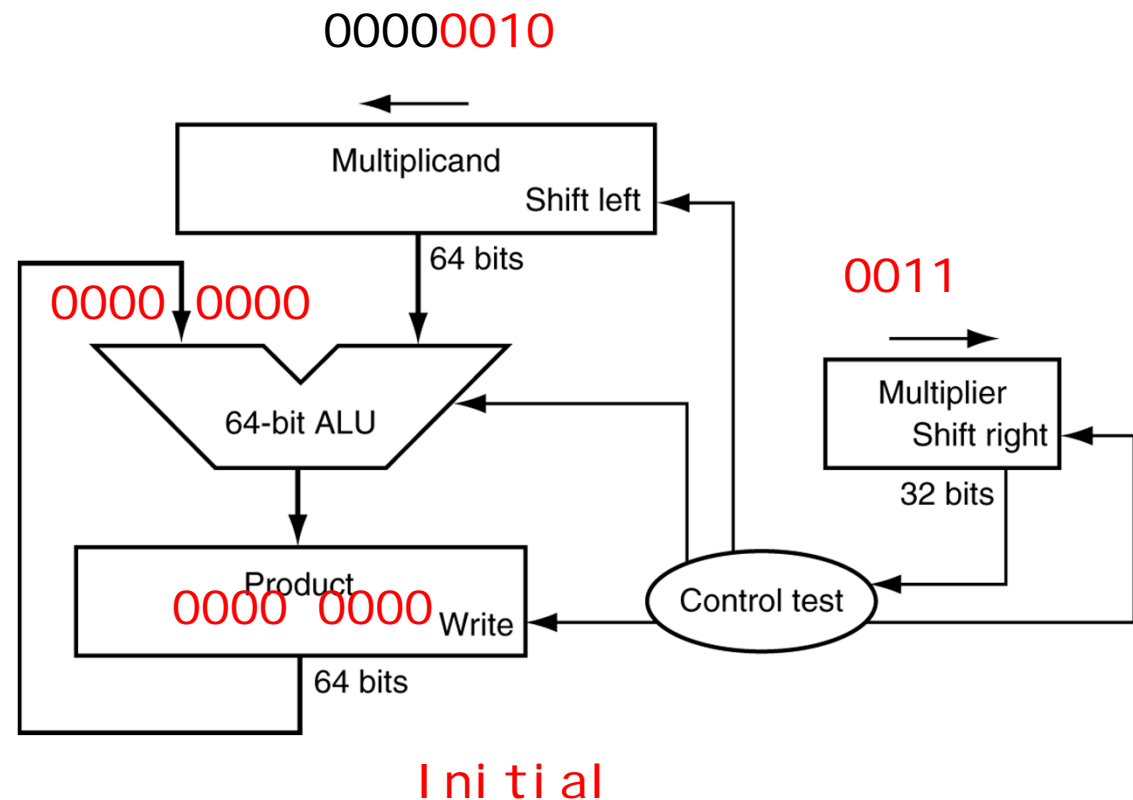
Length of product is the sum of operand lengths





 
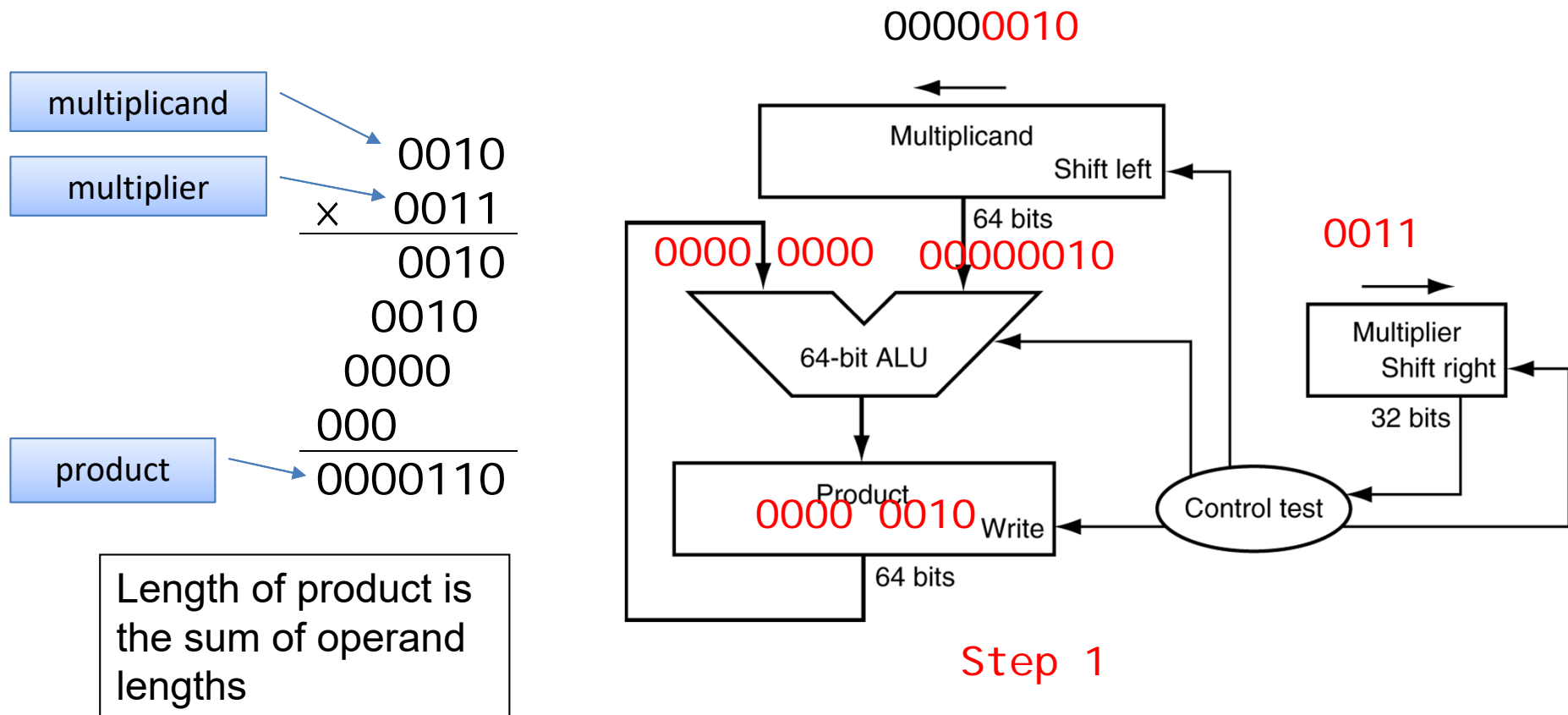
# Multiplication

- Start with long-multiplication approach



 
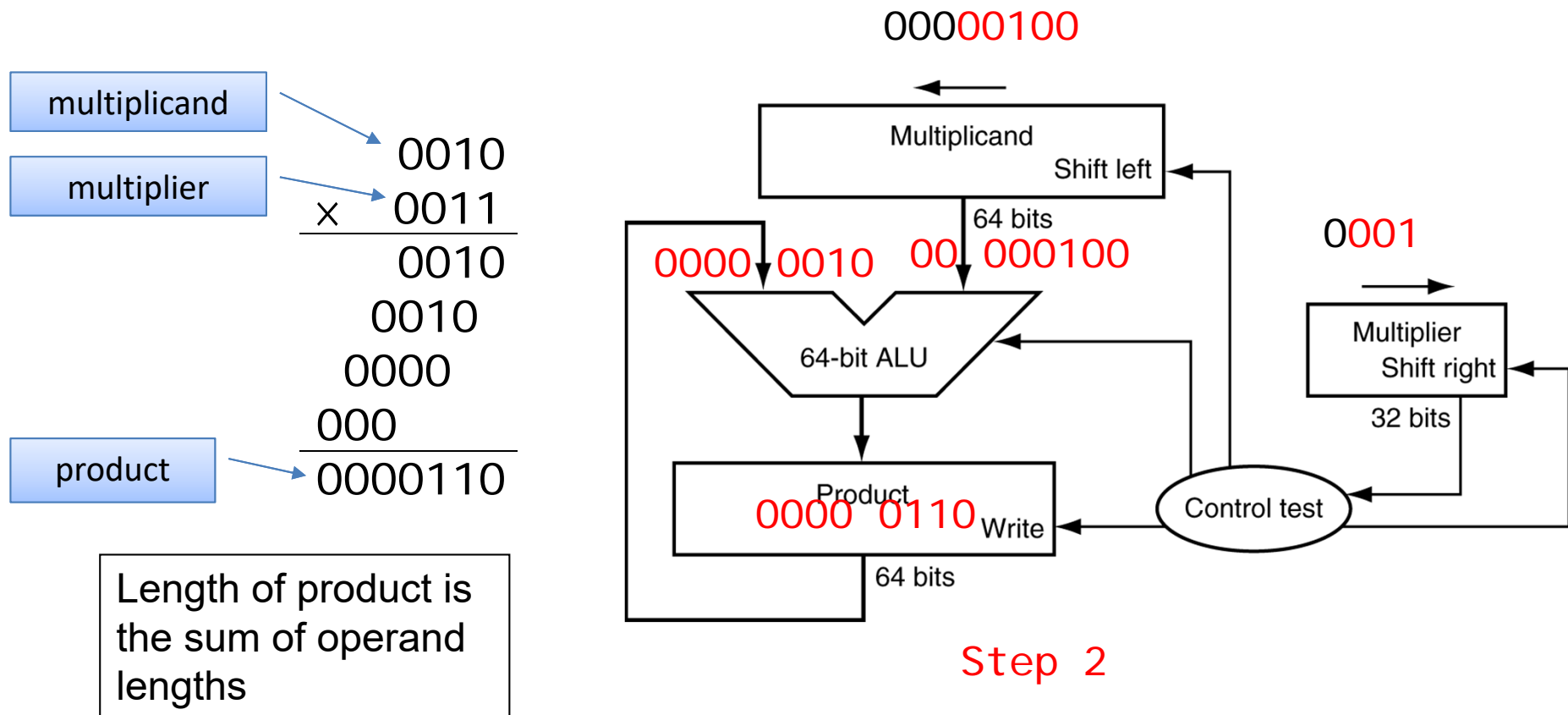
# Multiplication

- Start with long-multiplication approach



 
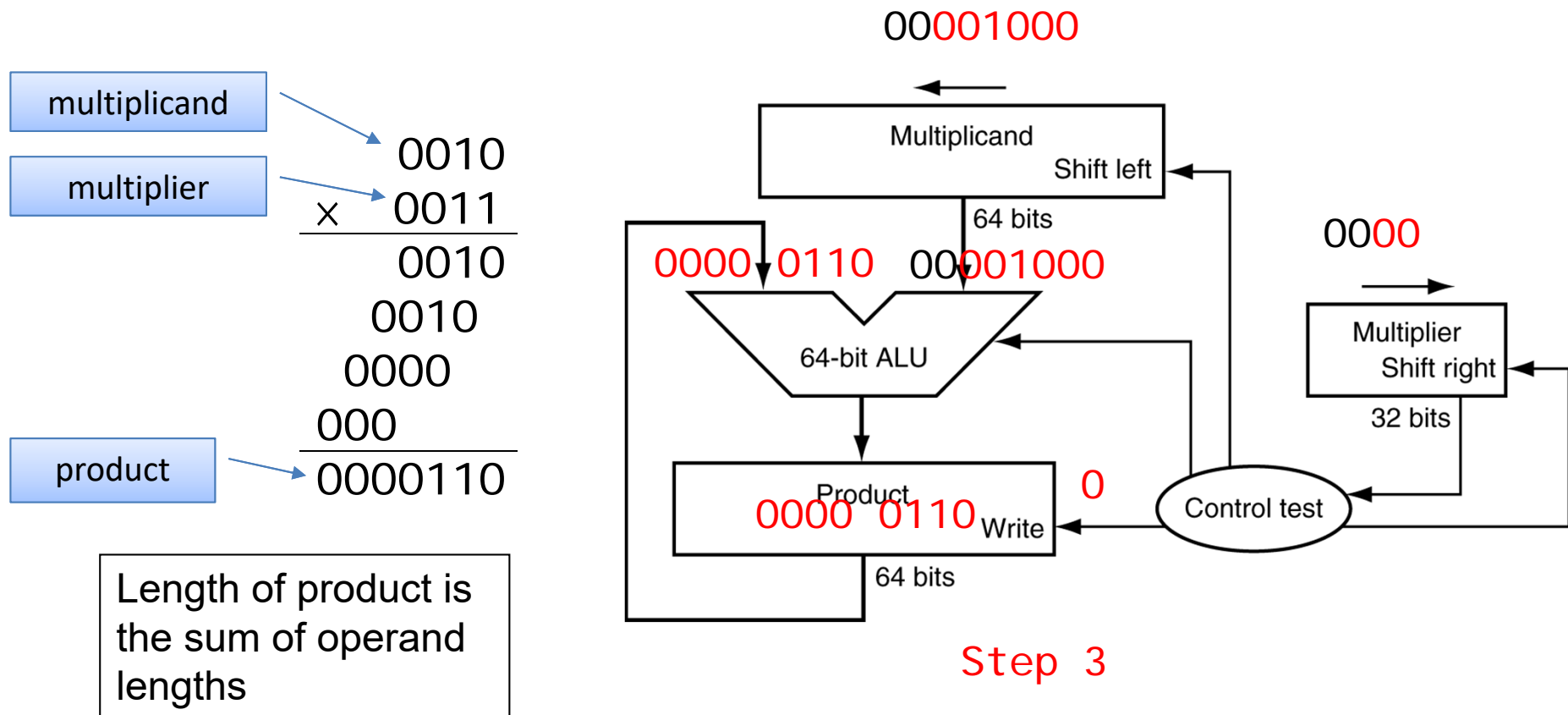
# Multiplication

- Start with long-multiplication approach


 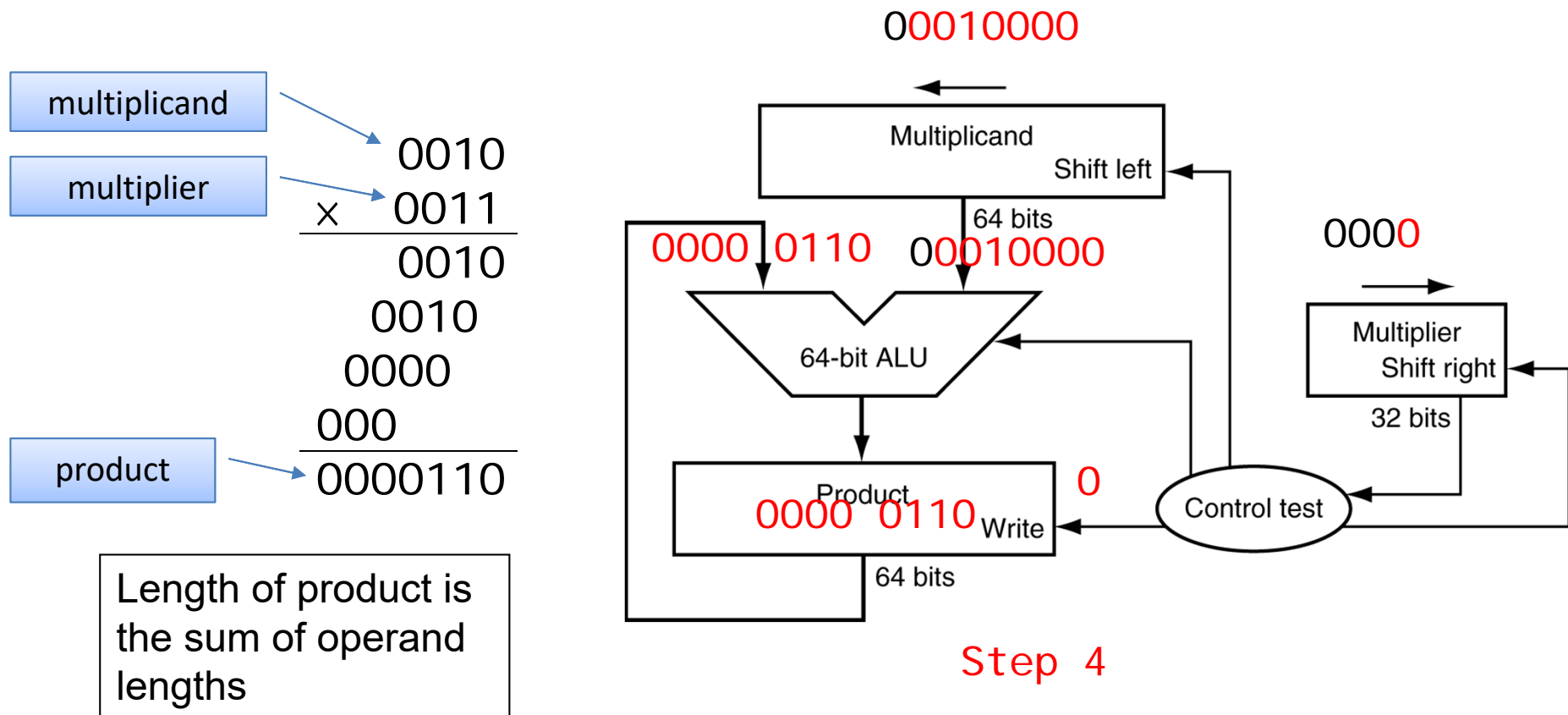
# Multiplication



- Start with long-multiplication approach




# Multiplication Hardware



成功大學

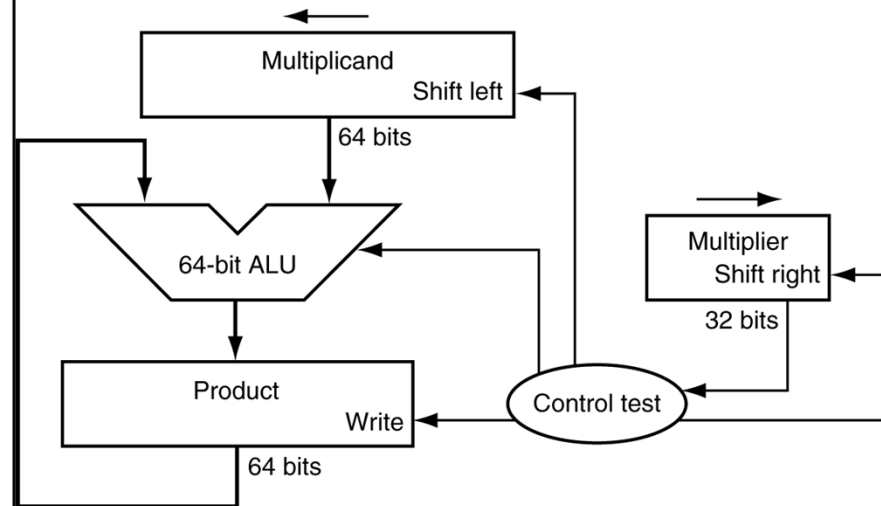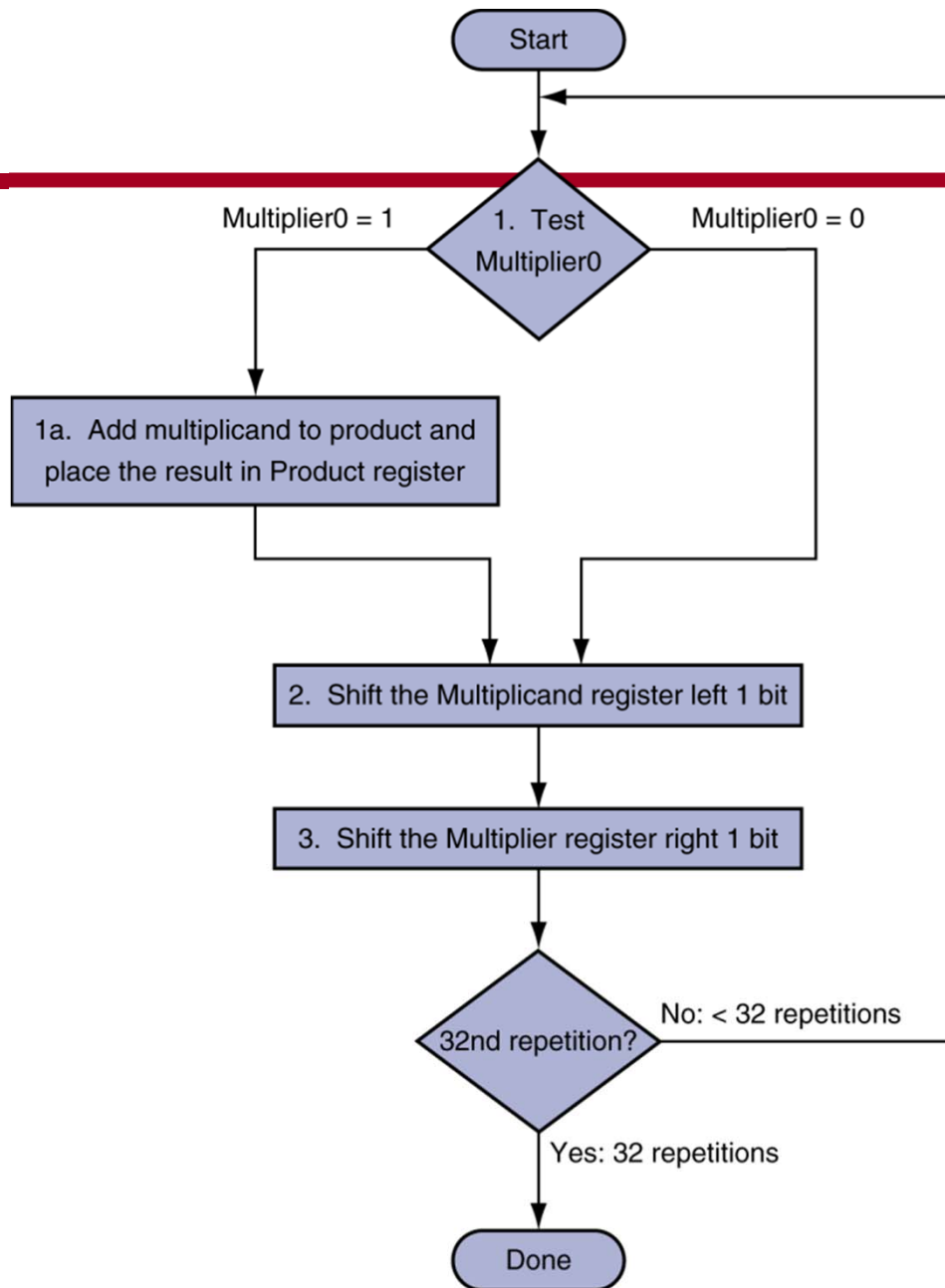

 Multiplicand: 64 bits  
Product: 64 bits  
Multiplier: 32 bits



# Optimized Multiplier

- Observations: Two ways of multiplication
  - Shift **multiplicand left** or shift **product right**


$\begin{array}{r} 1000 \\ \times 1011 \\ \hline 1000 \end{array}$	$\begin{array}{r} 1000 \\ \times 1011 \\ \hline 1000 \\ 1000 \\ \hline 11000 \end{array}$	$\begin{array}{r} 1000 \\ \times 1011 \\ \hline 11000 \\ 0000 \\ \hline 11000 \end{array}$	$\begin{array}{r} 1000 \\ \times 1011 \\ \hline 011000 \\ 1000 \\ \hline 1011000 \end{array}$
---	---	--	---

Shift multiplicand  
left 1 bit and add

Shift multiplicand  
left 2 bit but **no** add

$\begin{array}{r} 1000 \\ \times 1011 \\ \hline 1000 \end{array}$	$\begin{array}{r} 1000 \\ \times 1011 \\ \hline 1000 \\ 1000 \\ \hline 11000 \end{array}$	$\begin{array}{r} 1000 \\ \times 1011 \\ \hline 11000 \\ 0000 \\ \hline 011000 \end{array}$	$\begin{array}{r} 1000 \\ \times 1011 \\ \hline 011000 \\ 1000 \\ \hline 1011000 \end{array}$
---	---	---	---

**product shift right and add**

 




成都大學
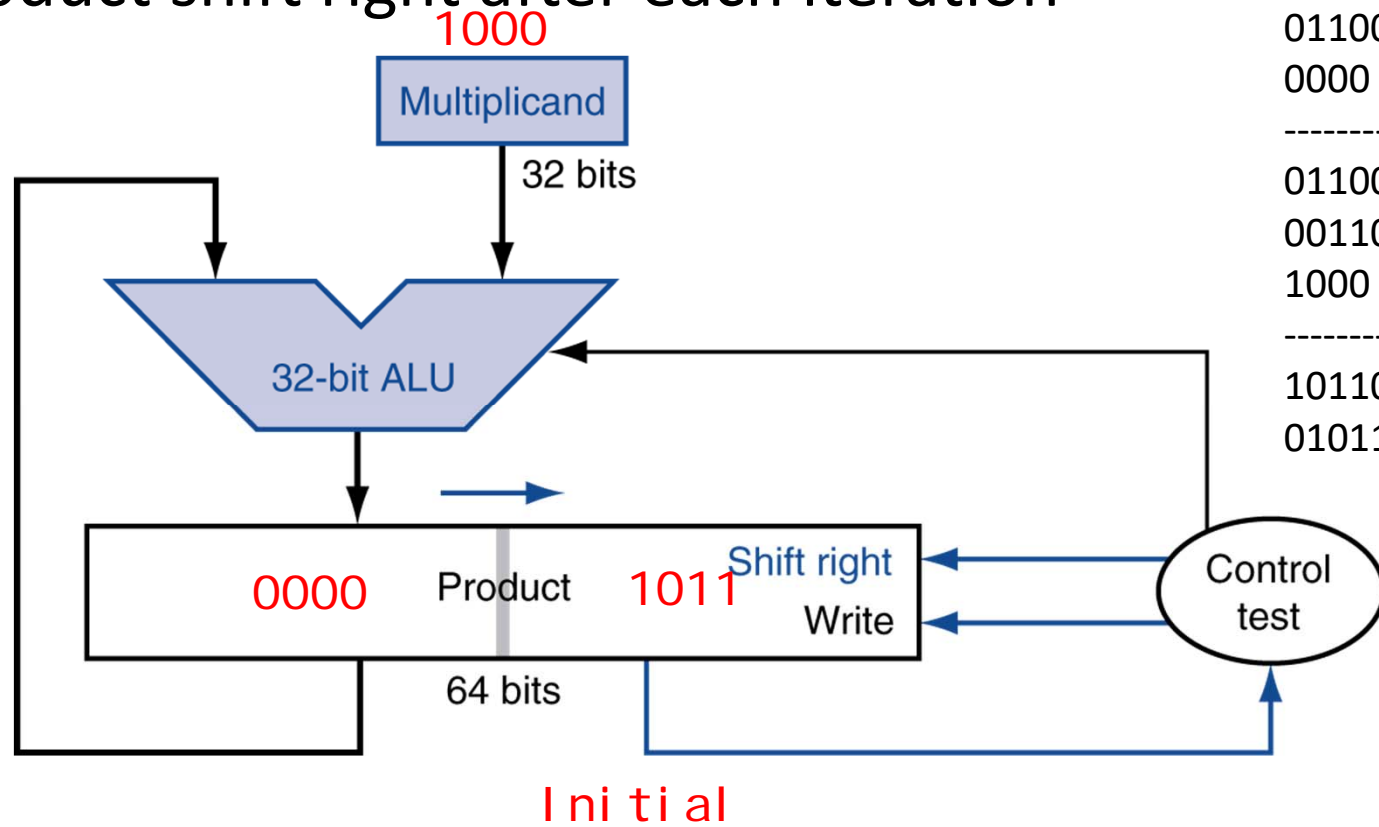
# Optimized Multiplier

- Initial: 32 bit multiplicand, multiplier is stored in right side of product
- Product shift right after each iteration



1000  
1011


add

10001011 shift  
01000 101  
1000 add

11000 101 shift  
011000 10  
0000 add

011000 10 shift  
0011000 1  
1000 add

1011000 1 shift  
01011000


 




成功大學

# Optimized Multiplier

- Step 1

 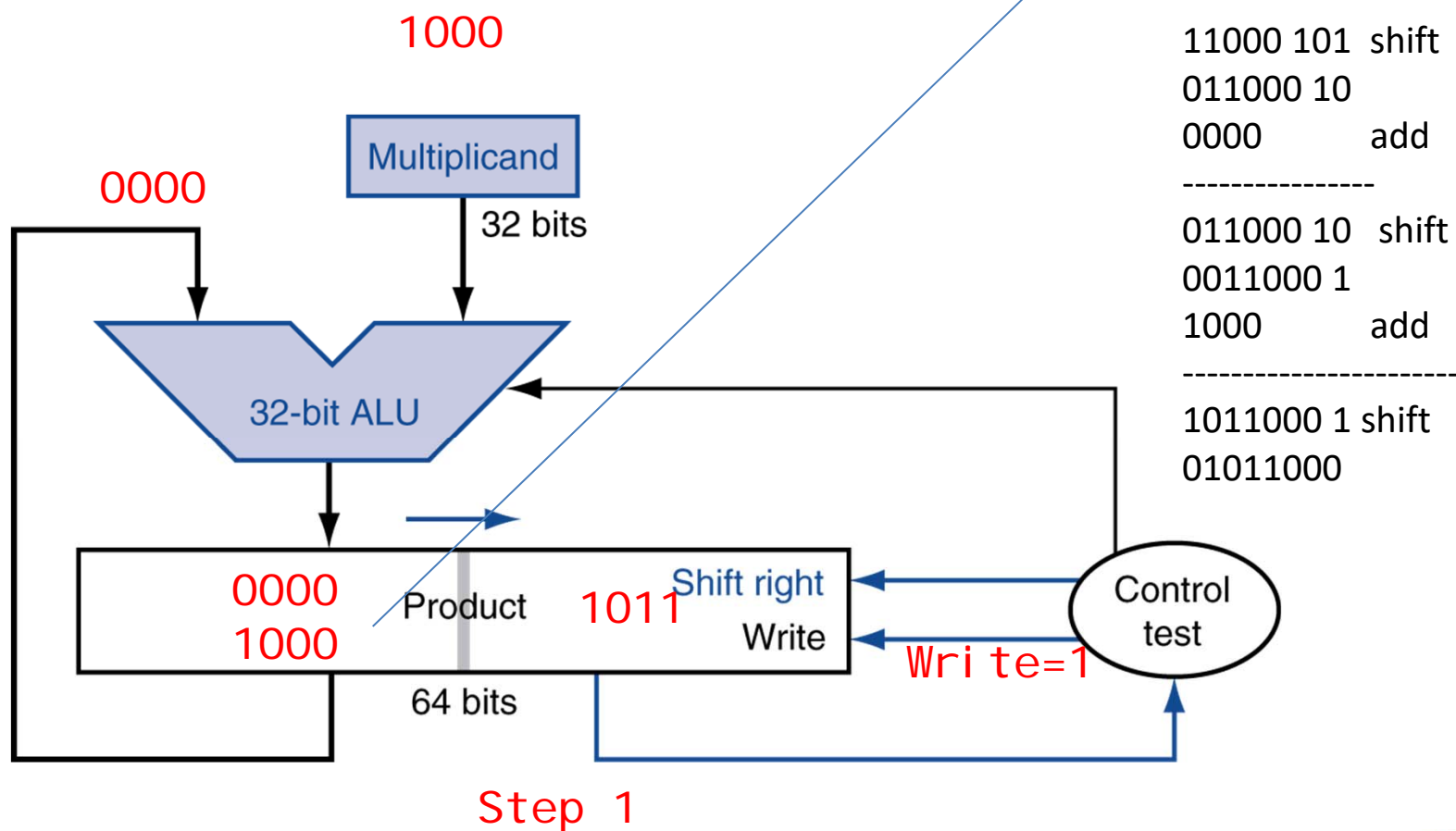







成功大學

# Optimized Multiplier

- Step 2

 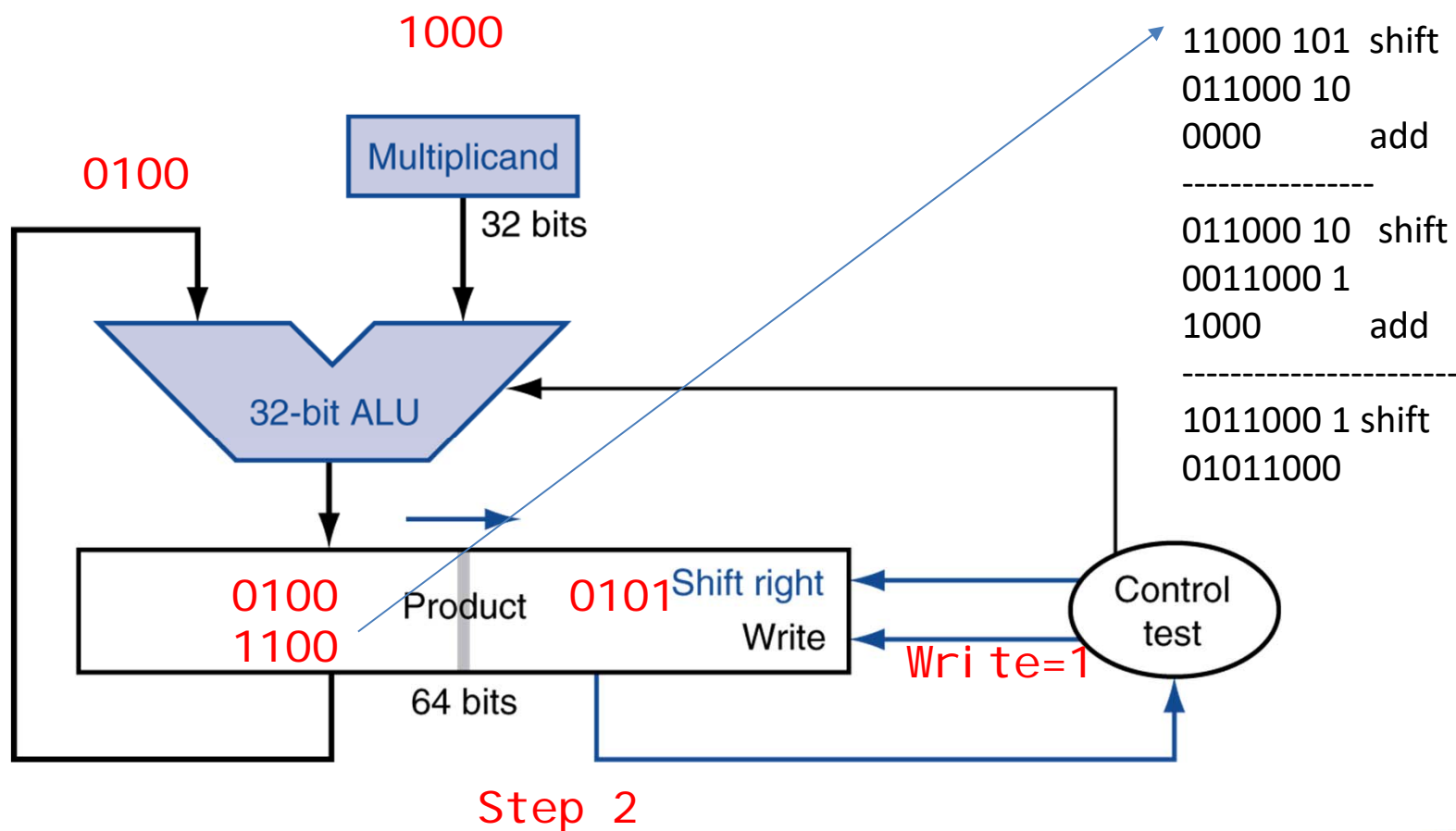




成功大學

# Optimized Multiplier

- Step 3

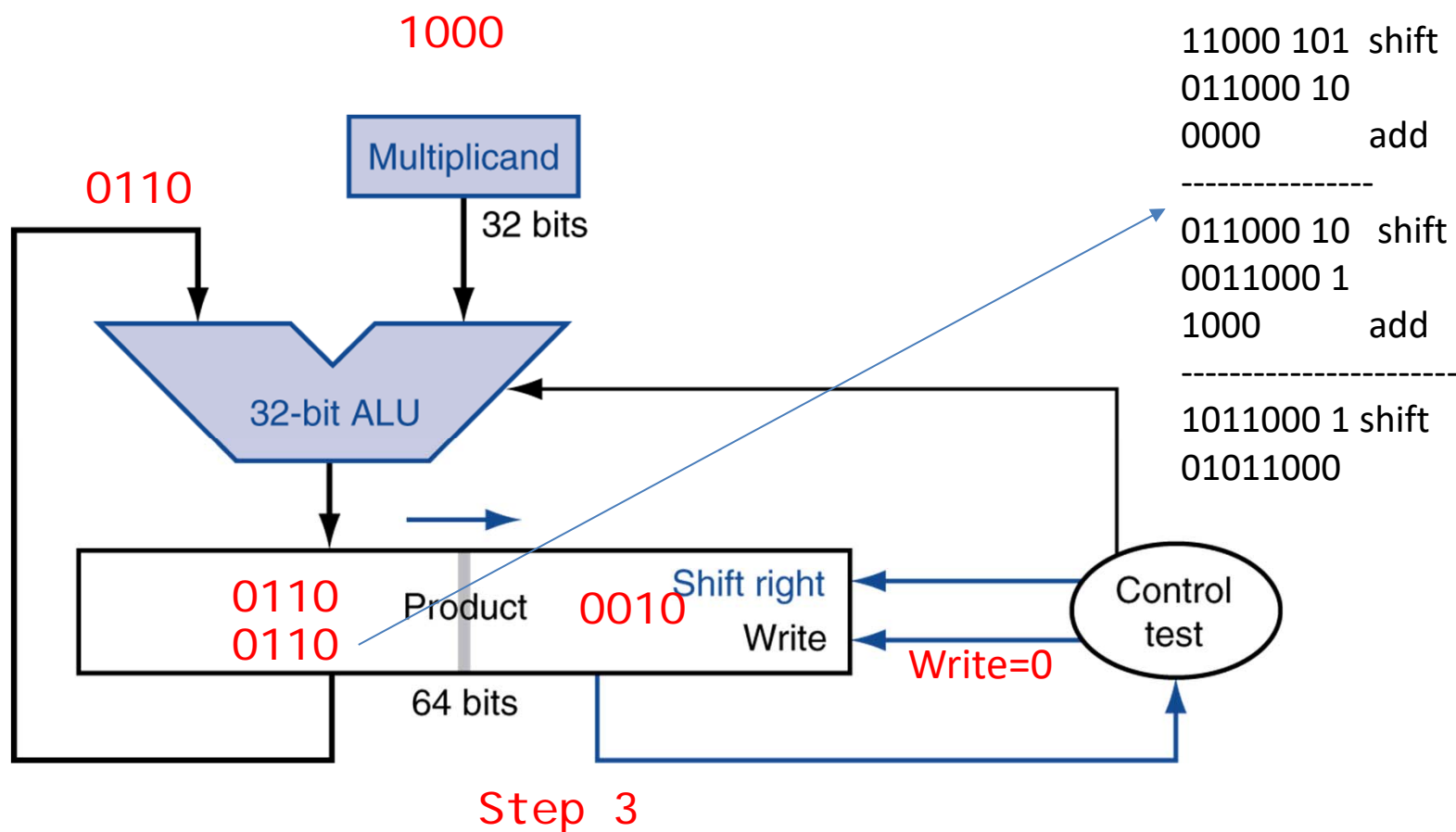


1000  
1011

10001011 shift  
01000 101  
1000 add

11000 101 shift  
011000 10  
0000 add

011000 10 shift  
0011000 1  
1000 add

1011000 1 shift  
01011000

 




成功大學  
Tsinghua University

# Optimized Multiplier

- Step 4:

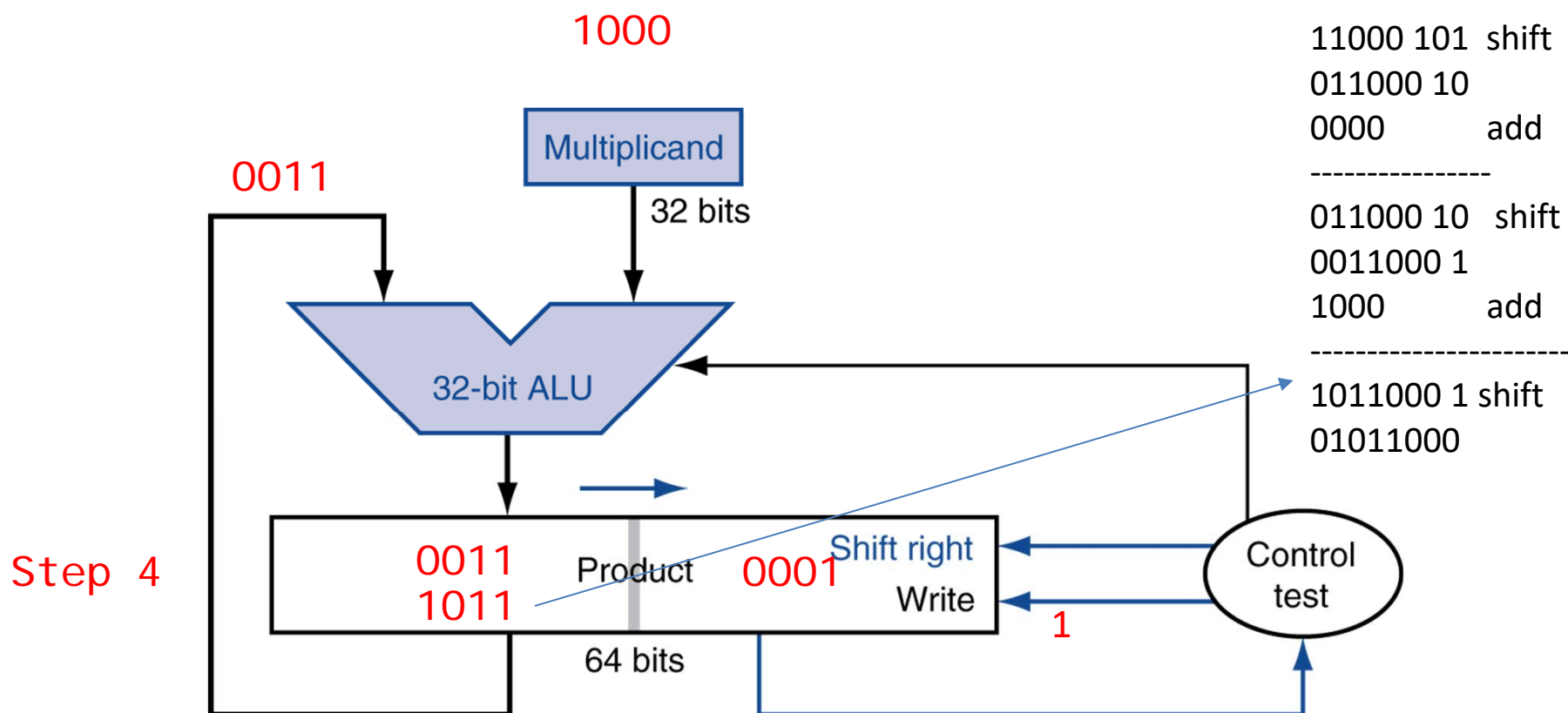


1000  
1011

10001011 shift  
01000 101  
1000 add

11000 101 shift  
011000 10  
0000 add

011000 10 shift  
0011000 1  
1000 add


1011000 1 shift  
01011000

 



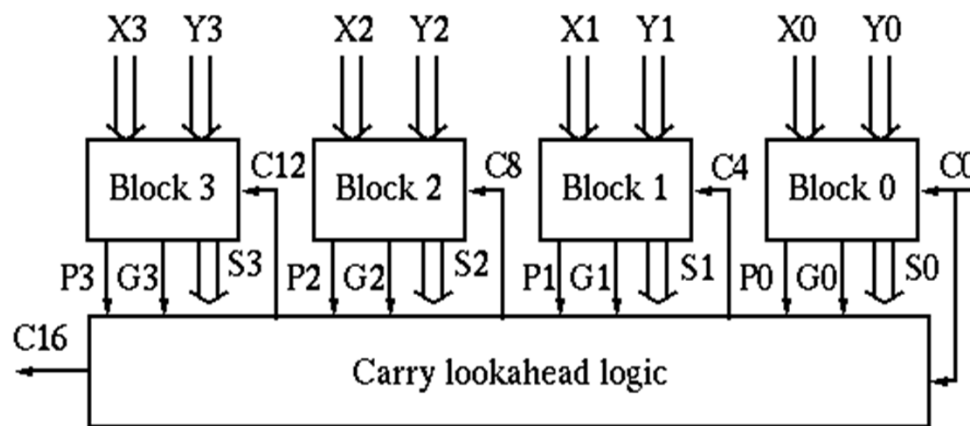
# Faster Multiplier


- Uses faster adder
  - Addition is repetitively performed
  - Faster adder can improve multiplication speed
  - E.g. carry lookahead adder, carry save adder, etc.
  - See appendix C



Carry lookahead adder

 

Carry save adder

 





# Faster Multiplier

- Perform **addition** in **parallel**
  - Uses multiple adders
  - Can be pipelined to reduce critical paths

$$\begin{array}{r} 0010 \\ \times 0011 \\ \hline 0010 \\ 0010 \\ \hline 0000 \\ 0000 \\ \hline 0000110 \end{array}$$

Perform addition in parallel

  

# MIPS Multiplication-mul

- mul

mul \$rd \$rs \$rt

$\$rd = \$rs * \$rt$

Only **low-order 32 bits** of  
the product is preserved  
in \$rd

Without Overflow

.text

addi \$s0, \$zero, 10


addi \$s1, \$zero, 4

mul \$t0, \$s0, \$s1

li \$v0, 1


add \$a0, \$zero, \$t0

syscall

 

# MIPS Multiplication-mult

- If the product may be larger than 32 bit => use mult
- **Two** special 32-bit registers for **product**
  - HI: most-significant 32 bits
  - LO: least-significant 32-bits
- Instructions
  - mult rs, rt      #  $HI|LO = \$rs * \$rt$  , result is stored in 64 bit HI|LO
  - mf**hi** rd / mf**lo** rd
    - Move from HI/LO to rd
    - Can test **HI** value to see if product overflows 32 bits

 


## Example

- Write a program that evaluates the formula  $5 * 12 - 74$ .
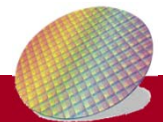
## Program to calculate  $5 * 12 - 74$


.text

```
addi    $t0, $0, 12      # put 12 into $t0
addi    $t1, $0, 5       # put 5 into $t1
mult    $t0, $t1          # lo = 5x12
mflo    $t1               # $t1 = 5x12
addi    $t1, $t1, -74     # $t1 = 5x12 - 74
```






# Division


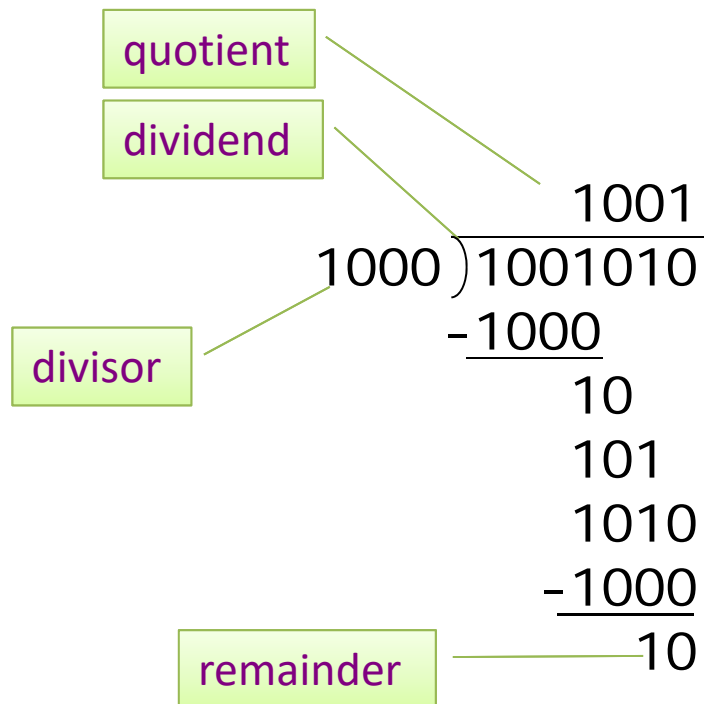


$n$ -bit operands yield  $n$ -bit quotient and remainder

 
- Check if divisor = 0
- Long division approach
  - If divisor  $\leq$  dividend bits
    - 1 bit in quotient, subtract
  - Otherwise
    - 0 bit in quotient, bring down next dividend bit
- Division is just a bunch of **quotient digit guesses** and **left shifts** and **subtracts**



# First version of Division hardware

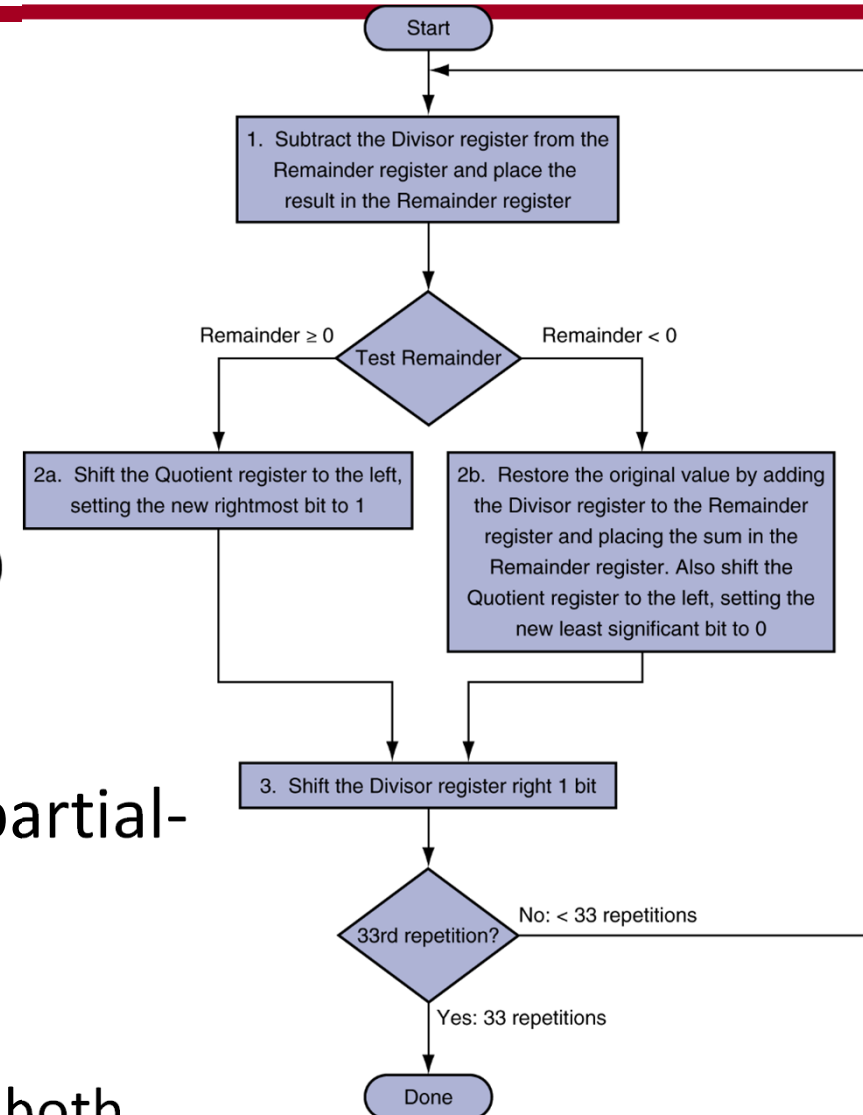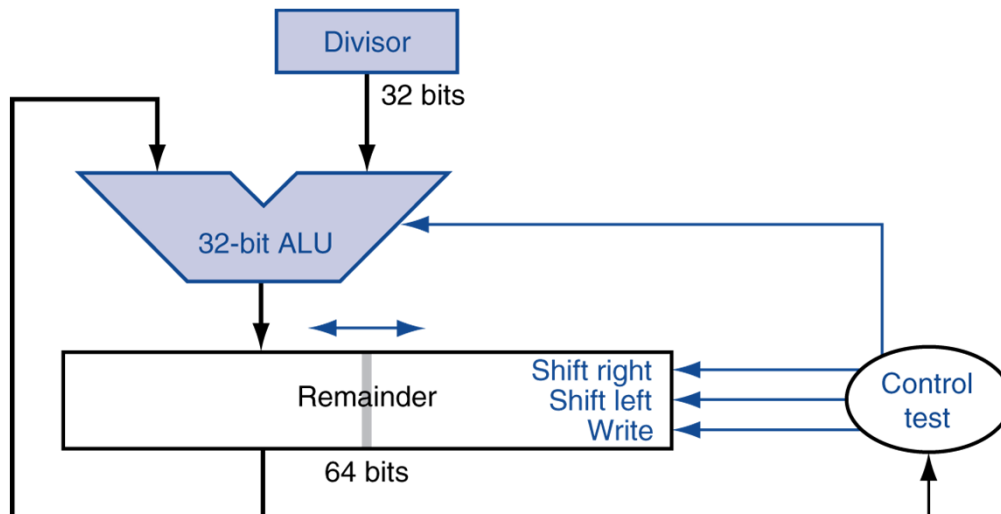

 
- One cycle is needed for each partial-remainder subtraction
- Looks a lot like a multiplier!
  - Same hardware can be used for both






# Restoring Division Example

Iteration	Step	Quotient	Divisor	Remainder
0	Initial values	0000	0010 0000	0000 0111
1	1: Rem = Rem - Div	0000	0010 0000	①110 0111
	2b: Rem < 0 $\Rightarrow$ +Div, sll Q, Q0 = 0	0000	0010 0000	0000 0111
	3: Shift Div right	0000	0001 0000	0000 0111
2	1: Rem = Rem - Div	0000	0001 0000	①111 0111
	2b: Rem < 0 $\Rightarrow$ +Div, sll Q, Q0 = 0	0000	0001 0000	0000 0111
	3: Shift Div right	0000	0000 1000	0000 0111
3	1: Rem = Rem - Div	0000	0000 1000	①111 1111
	2b: Rem < 0 $\Rightarrow$ +Div, sll Q, Q0 = 0	0000	0000 1000	0000 0111
	3: Shift Div right	0000	0000 0100	0000 0111
4	1: Rem = Rem - Div	0000	0000 0100	①000 0011
	2a: Rem $\geq$ 0 $\Rightarrow$ sll Q, Q0 = 1	0001	0000 0100	0000 0011
	3: Shift Div right	0001	0000 0010	0000 0011
5	1: Rem = Rem - Div	0001	0000 0010	①000 0001
	2a: Rem $\geq$ 0 $\Rightarrow$ sll Q, Q0 = 1	0011	0000 0010	0000 0001
	3: Shift Div right	0011	0000 0001	0000 0001

 

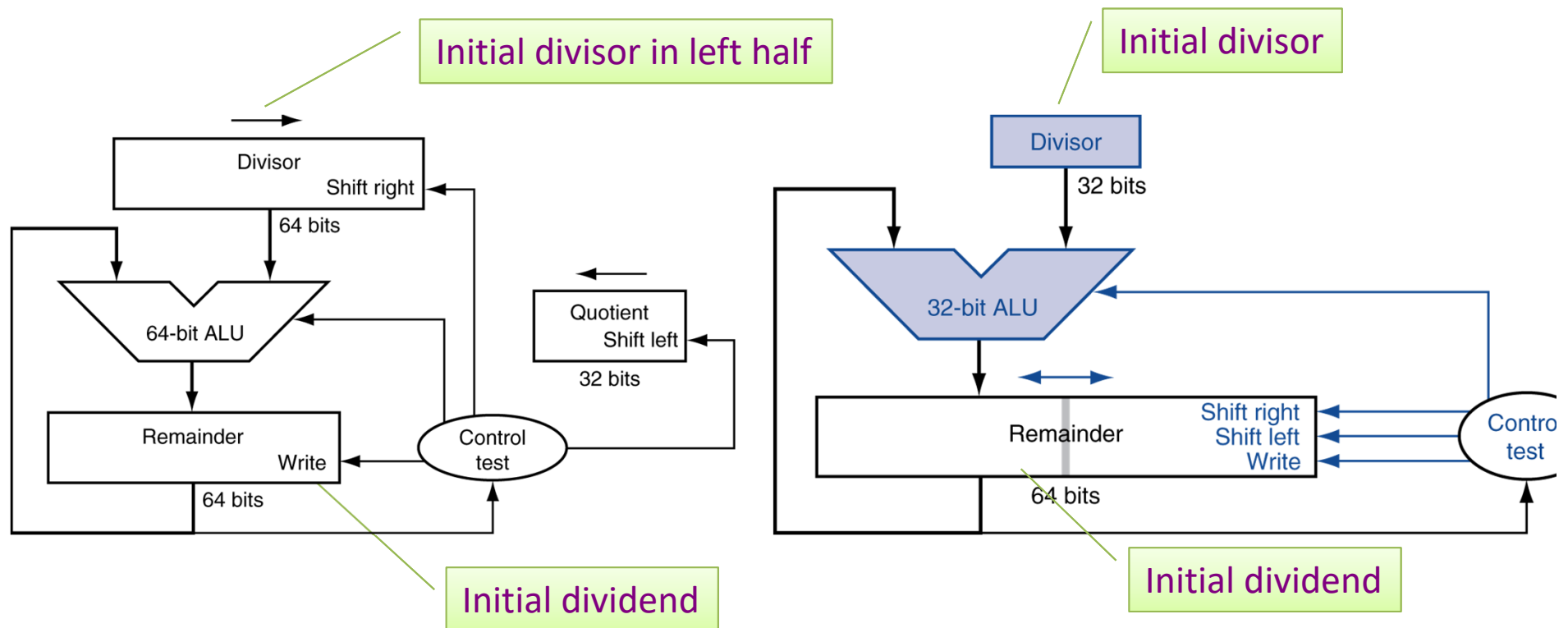
# Optimized division hardware

- Division is similar to multiplication, so is hardware




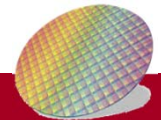Improved hardware  
 32-bit Divisor  
 No extra bit for Quotient



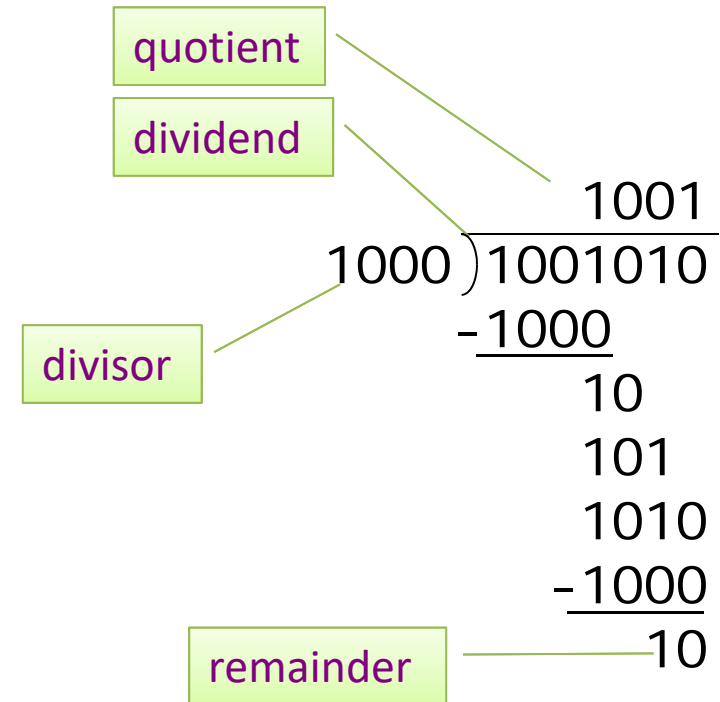
# Why Division is slower?

- Division is slower than multiplication because
  - Need **remainder** to decide next quotient bit
  - Division is done **sequentially**
  - Can't be done in parallel
- Different Division (skipped)
  - Restoring
  - Nonrestoring
  - SRT



 $n$ -bit operands yield  $n$ -bit quotient and remainder




# MIPS Division

- Use HI/LO registers for result
  - HI: 32-bit remainder
  - LO: 32-bit quotient
- Instructions (only two operands)

- `div rs, rt`
- `divu rs, rt`

```
div    $s0, $s1    # lo = $s0 / $s1
                        # hi = $s0 mod $s1
mfhi    $t0        #move remainder to $t0
mflo    $t1        #move quotient to $t1
```

 - Use **mfhi rd** and **mflo rd** are provided to move the quotient and remainder to user accessible registers
- No overflow or divide-by-0 checking
  - Software must perform checks if required



## Division Example

- Calculate  $13/5$ , put the quotient in **\$t1**, and reminder in **\$t0**

.text

.globl main

main:


ori \$t5, \$zero, 13 # put 13 into \$5

ori \$t6, \$zero, 5 # put 5 into \$6

div \$t5, \$t6 # **Lo** = \$t5 / \$t6 (integer quotient)  
# **Hi** = \$t5 mod \$t6 (remainder)

mfhi \$t0 # move reminder from **Hi to \$t0: \$t0 = Hi**

 mflo \$t1 # move quotient from **Lo to \$t1: \$t1 = Lo**  
# used to get at result of product or quotient





成功大學

National Cheng Kung University

# Backup slides

