

# Chapter 4

## The Processor

# Introduction

- CPU performance factors

$$\text{CPU Time} = \text{Instruction Count} \times \text{CPI} \times \text{Clock Cycle Time}$$

- Instruction count

- Determined by ISA and compiler

- CPI and Cycle time

- Determined by CPU hardware

- We will examine two MIPS implementations

- A simplified version (Single-cycle implementation)

- A more realistic pipelined version

- Multi-cycle version is removed in this version)

- Implement simple subset, but shows most aspects

- Memory reference: lw, sw

- Arithmetic/logical: add, sub, and, or, slt

- Control transfer: beq, j




# Review: MIPS Instruction Set Architecture (ISA)

- Instruction Categories

- Arithmetic
- Load/Store
- Jump and Branch
- Floating Point
  - coprocessor
- Memory Management
- Special

## Registers

 

## 3 Instruction Formats: all 32 bits wide




## Review: MIPS Register Convention

Name	Register Number	Usage	Preserve on call?
\$zero	0	constant 0 ( <b>hardware</b> )	n.a.
\$at	1	<b>reserved</b> for assembler	n.a.
\$v0 - \$v1	2-3	returned values	no
\$a0 - \$a3	4-7	arguments	<b>yes</b>
\$t0 - \$t7	8-15	temporaries	no
\$s0 - \$s7	16-23	saved values	<b>yes</b>
\$t8 - \$t9	24-25	temporaries	no
\$gp	28	global pointer	<b>yes</b>
\$sp	29	stack pointer	<b>yes</b>
\$fp	30	frame pointer	<b>yes</b>
\$ra	31	return addr ( <b>hardware</b> )	<b>yes</b>


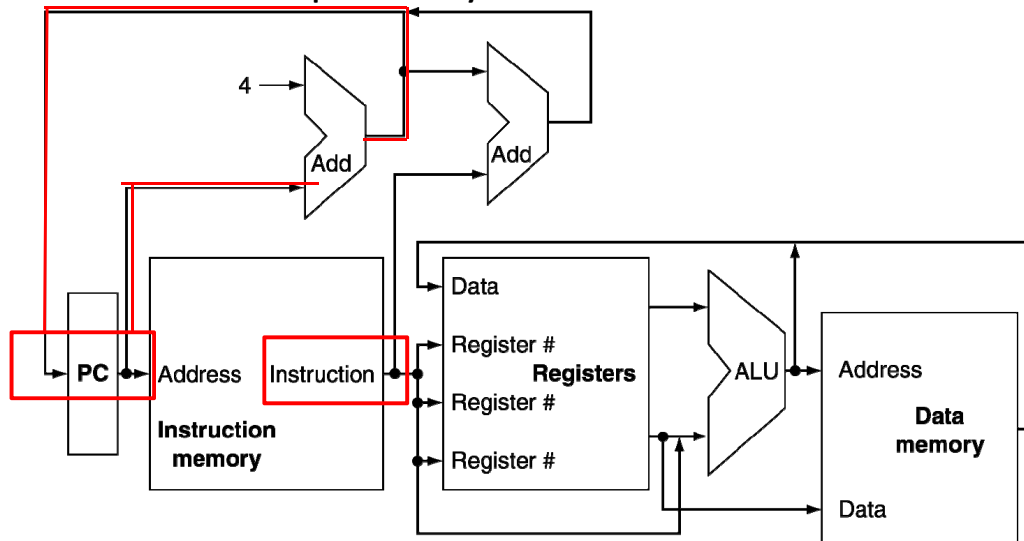
# Instruction Execution

- PC (Program counter) is used to fetch instruction in the **instruction** memory
- After **instruction** is obtained, **register numbers** in instructions is used to register file, read registers
- $PC \leftarrow PC + 4$  for sequentially execution 每個instruction 4 bit



- Depending on instruction class, different actions are performed

– Use **ALU** to calculate

- Arithmetic result

`add $t0, $s1, $s2`

- Memory address for load/store

`lw $s1, 20($s2)`

- Branch target address


`bne $t0, $s5, Exit (compare $t0, $s5)`

– Access data memory for load/store

`lw $s1, 20($s2)`


–  $PC \leftarrow$  target address

`j Loop`

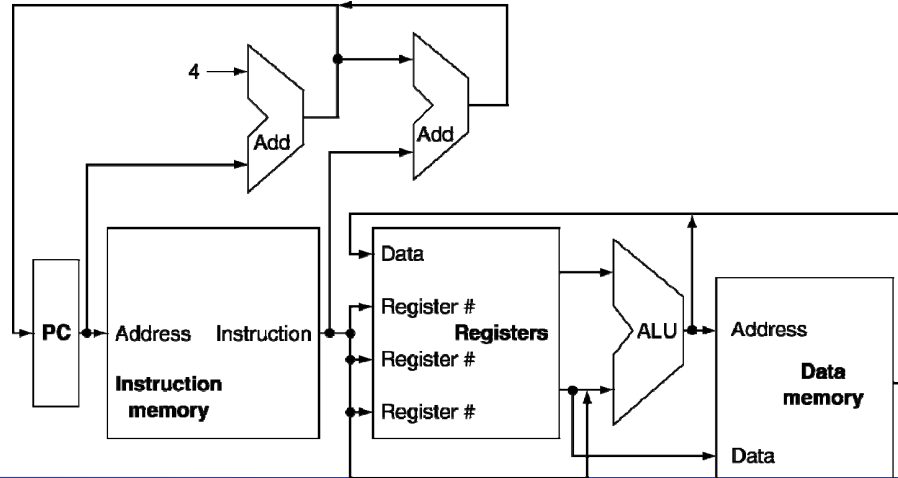


# Multiplexers

會衝突

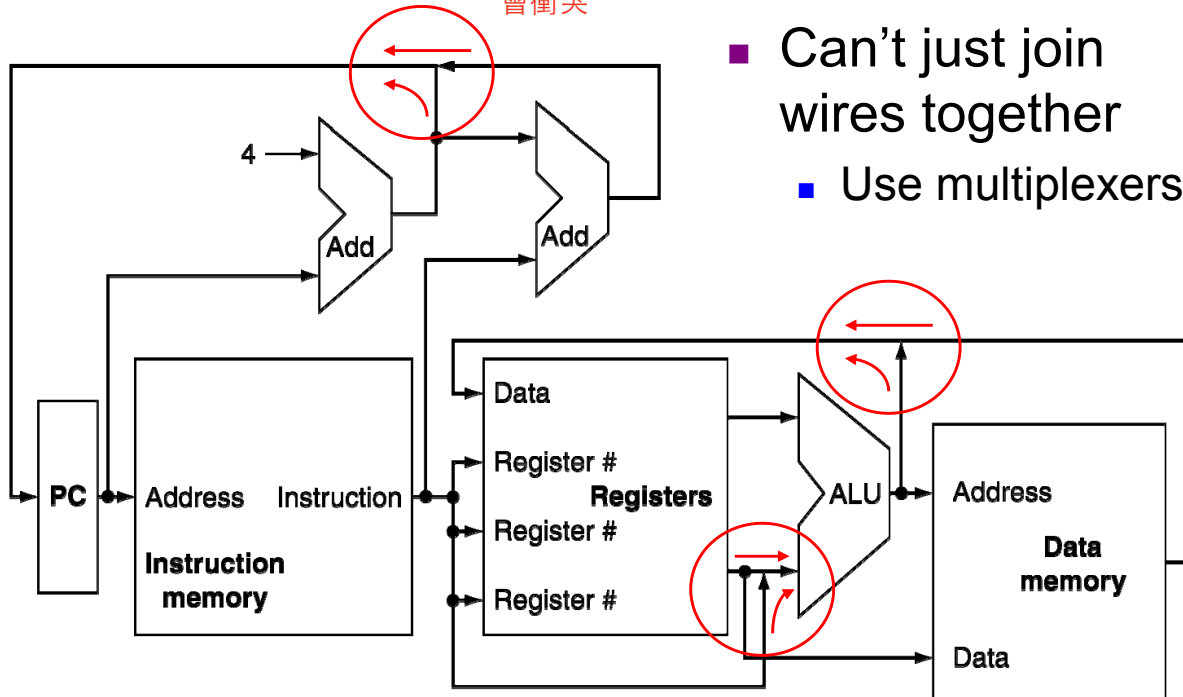

- Can't just join wires together
  - Use multiplexers

# CPU Overview

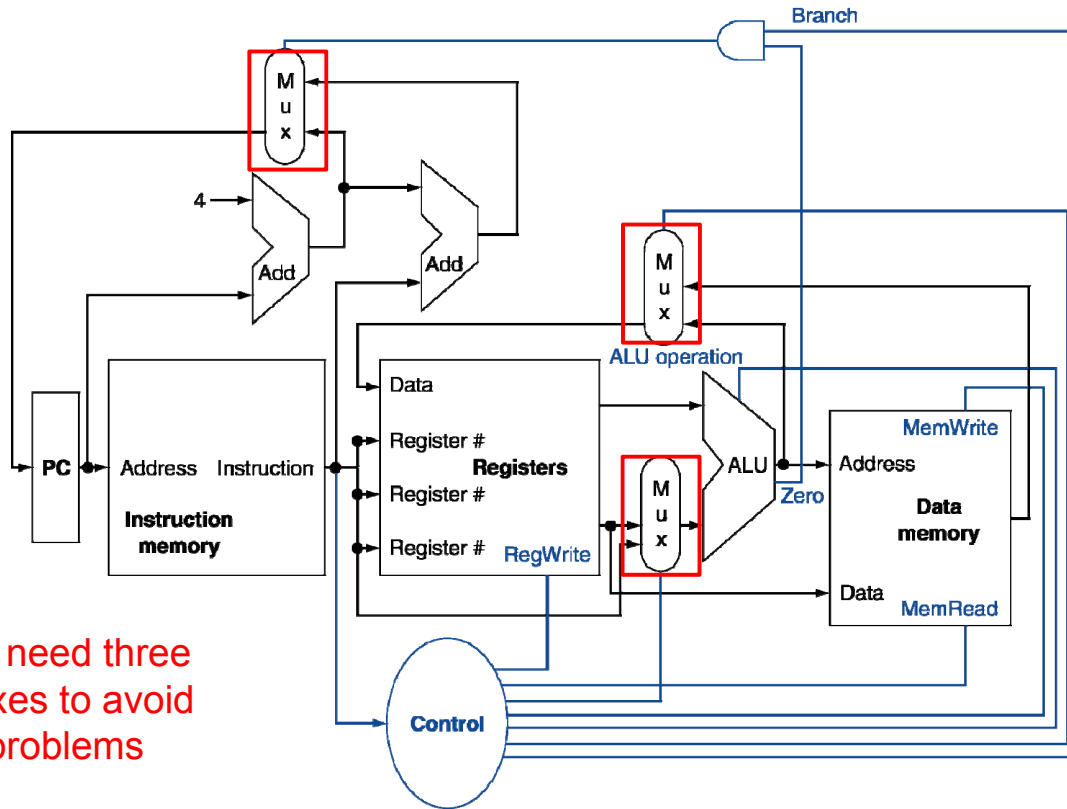

We need three  
Muxes to avoid  
problems

Details of each Mux and Control will be introduced later





 
# Logic Design Basics

- Information encoded in binary

- Low voltage = 0, High voltage = 1
- One wire per bit
- Multi-bit data encoded on multi-wire buses



- Combinational element (See next slide)

- Operate on data
- Output is a function of input

- State (sequential) elements


- Output is a function of input and current states
- Store information

32-bit bus




## Review: Combinational Elements


- AND-gate
  - $Y = A \& B$

 


- Multiplexer
  - $Y = S ? I1 : I0$

 

- Adder
  - $Y = A + B$


 


 - Arithmetic/Logic Unit
  - $Y = F(A, B)$



 
 
# Review: Sequential Elements

- Register: stores data in a circuit
  - Uses a **clock** signal to determine when to update the stored value
  - **Edge-triggered**: update when **Clk** changes (0-> 1 or 1-> 0)
  - The following figure is **positive edge-triggered**: update when Clk changes from **0 to 1**


  
## Review: Sequential Elements (with write enable)


- Register with write control
  - Only updates on clock edge when **write control** input is 1
  - Used when stored value is required later



Q is not changed when **Write=0**

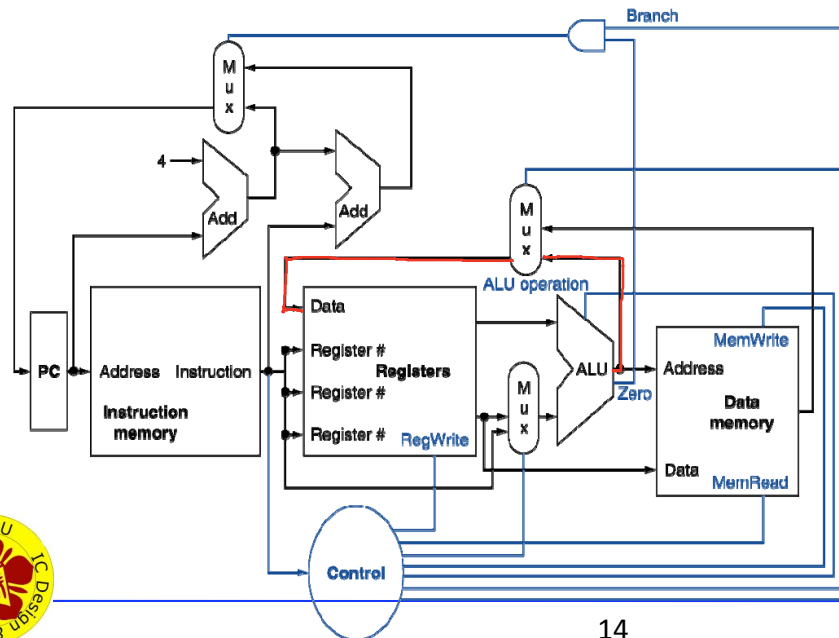
## Building a Datapath

- Datapath : Elements that process data and addresses in the CPU
  - Registers, ALUs, mux's, memories, ...



We will show how to build MIPS datapath



# Instruction Fetch

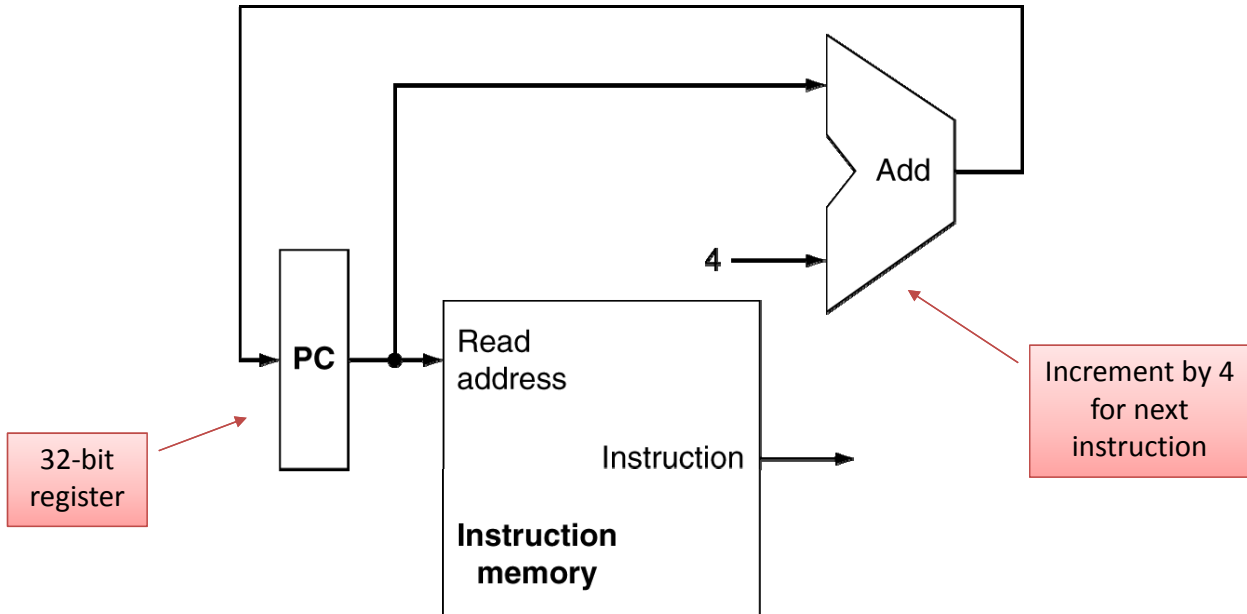

# R-Format Instructions



- Read two register operands
- Perform arithmetic/logical operation
- Write results into destination registers

add \$t0, \$s1, \$s2

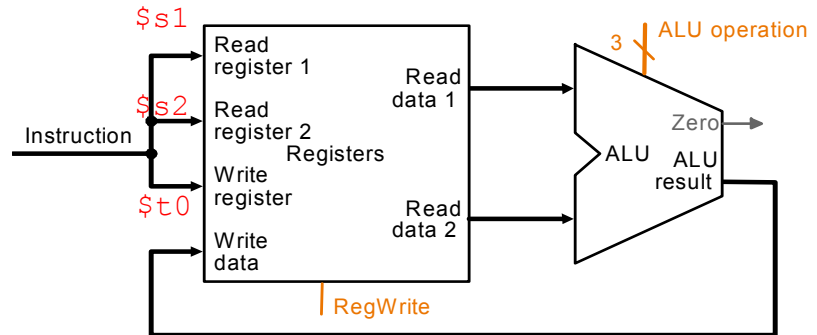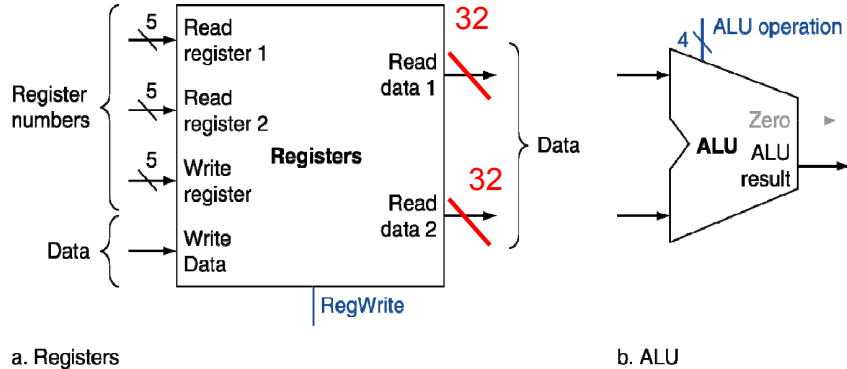
  
# Load/Store Instructions (need 4 components)

- Read register operands => register files
- Calculate address using 16-bit offset
  - Use ALU, but sign-extend offset  
16 bit → 32 bit
- Load/store: read memory and update register, and write register value to memory
  - Need data memory




16 bit  
lw \$t0, 4(\$s3) #load word from memory  
sw \$t0, 8(\$s3) #store word to memory





# Datapath: Load/Store Instruction

- Load/store

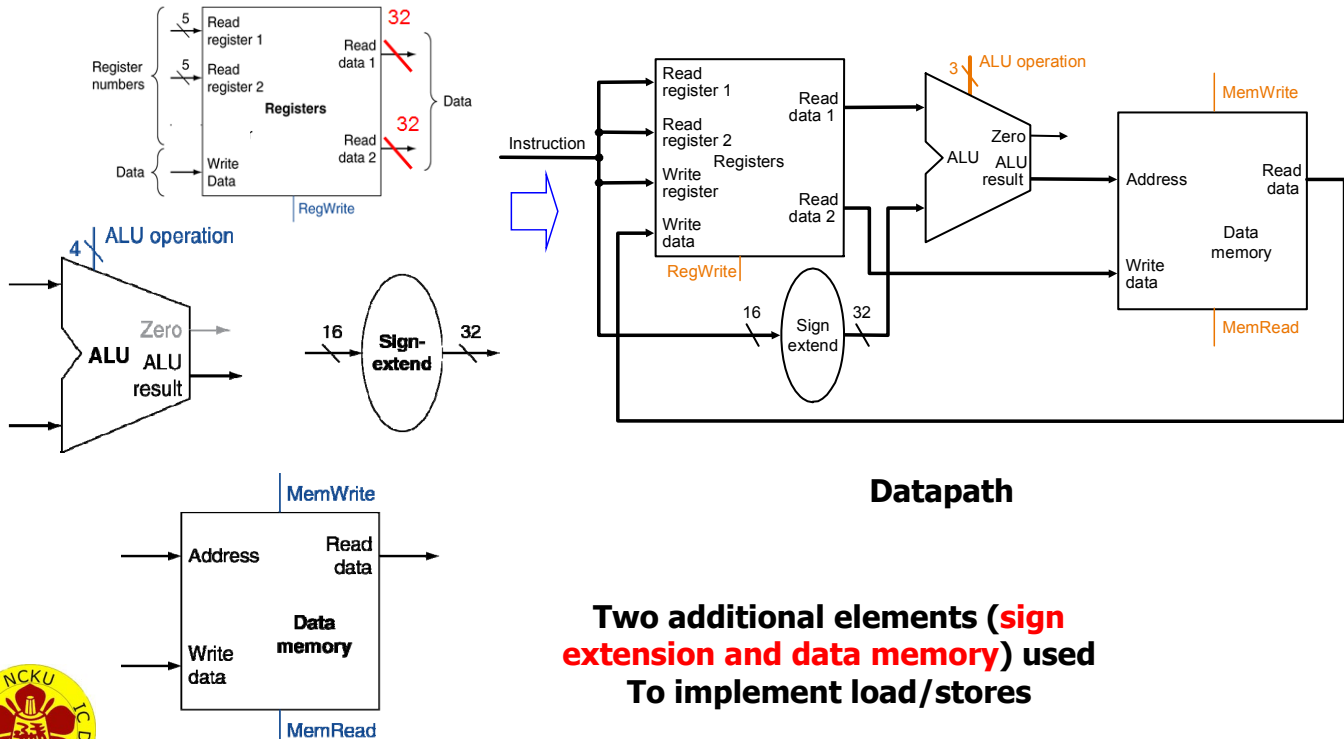

Datapath

Two additional elements (**sign extension** and **data memory**) used To implement load/stores



# Animating the Datapath- load

- Load

RN1: register number 1


RN2: register number 2

WN: write number

WD: write data


**lw rt, offset(rs)**

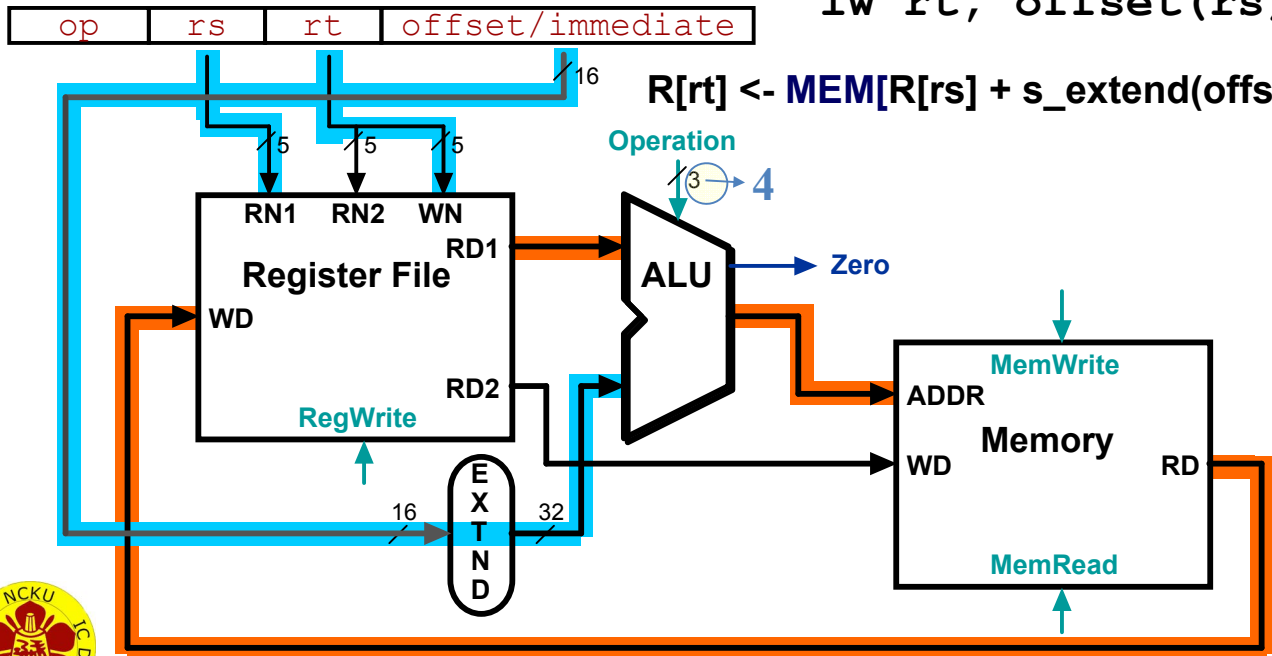**$R[rt] \leftarrow MEM[R[rs] + s\_extend(offset)];$**



# Animating the Datapath- store

- store

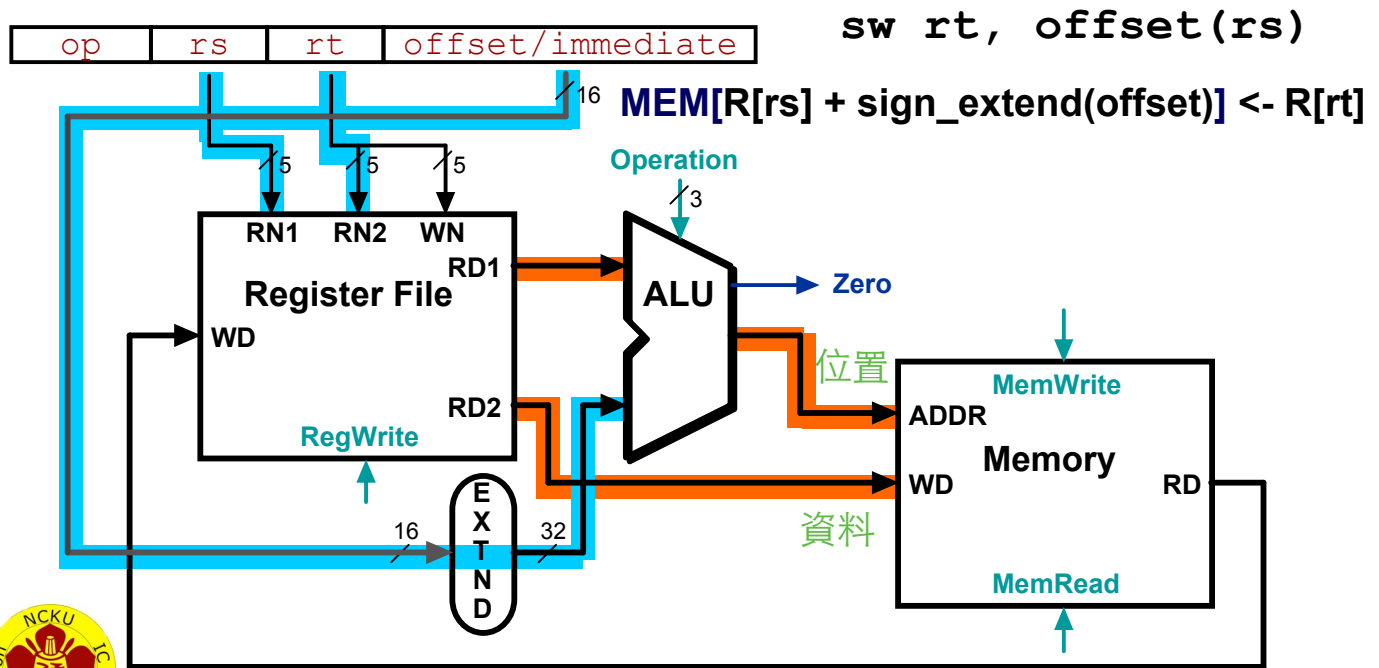

# Specifying Branch Destinations


- MIPS conditional branch instructions:

op	rs	rt	offset
6 bits	5 bits	5 bits	16 bits

- PC-relative addressing


beq \$s0 \$t1 L1

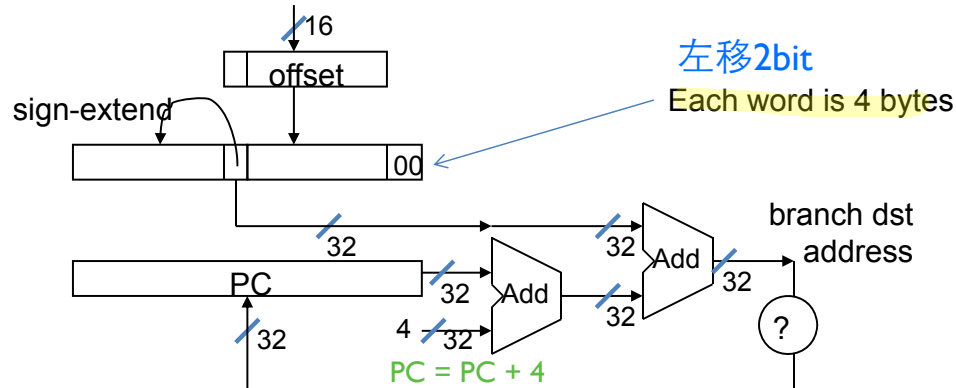- Target address =  $PC + \text{offset} \times 4$  將捨去的兩個bit補回 (左移2)
- PC already incremented by 4 by this time  
from the low order 16 bits of the branch instruction


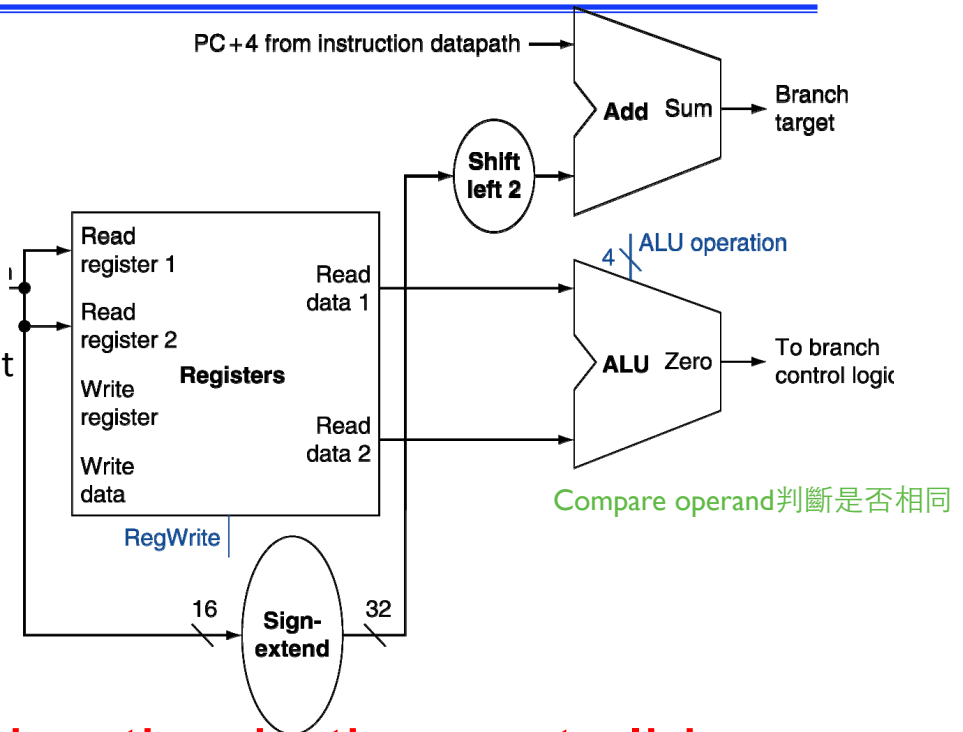
# Branch Instructions

- Read register operands
- Compare operands
  - Use **ALU**, subtract and check Zero output
- Calculate target address
  - Sign-extend displacement
  - Shift left 2 places (word displacement)
  - Add to PC + 4 (already calculated by instruction fetch)




See animation in the next slide




## Animating the Datapath (beq)

- beq

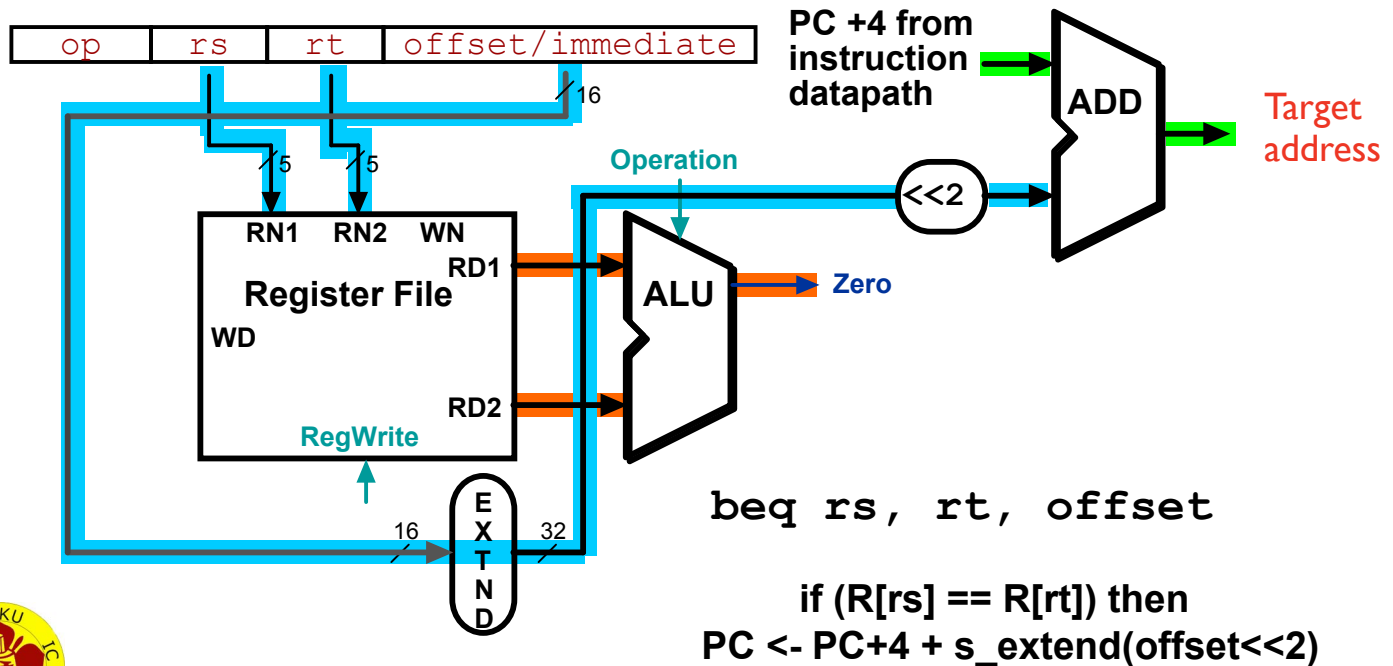
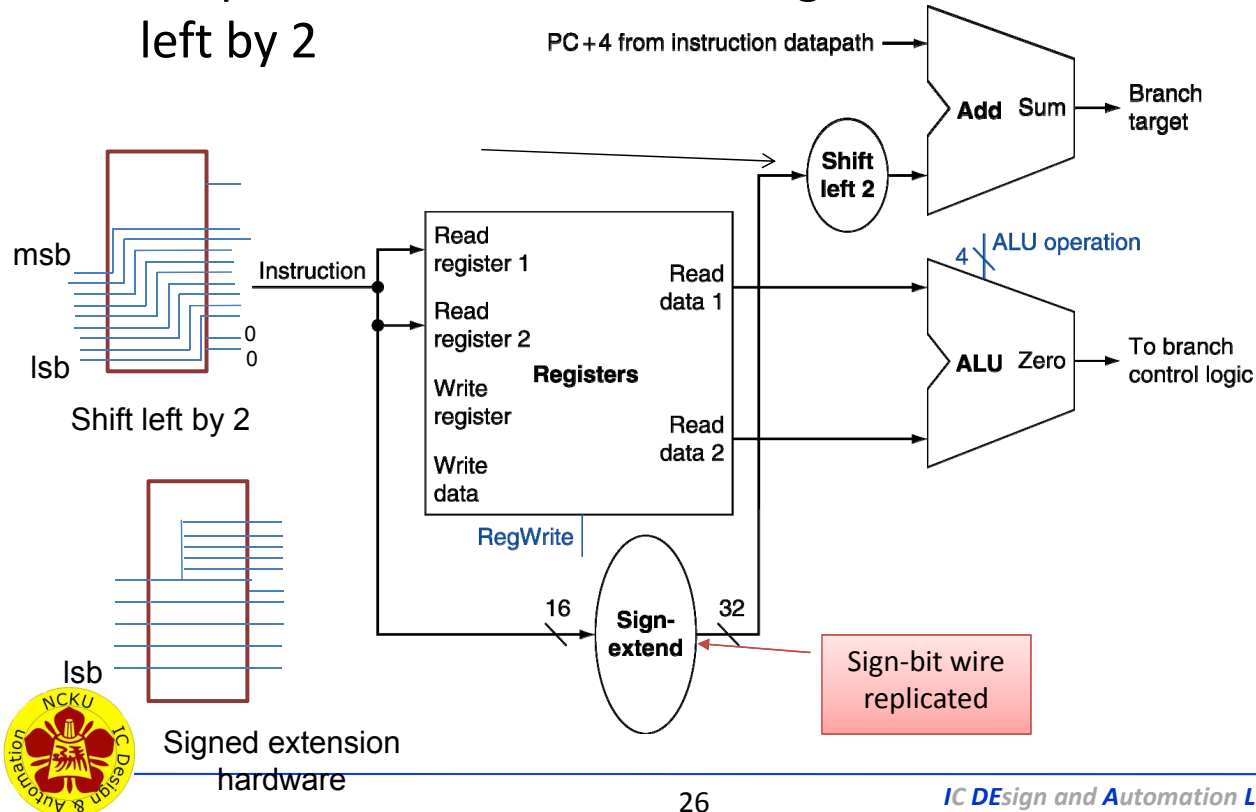
# Sign-extension and shift left by 2 hardware

- Simple hardware is used for sign extension and shift left by 2



## Composing the Elements

---


- Make Data path do an instruction in **one clock cycle**
  - Each datapath **element** can only do **one** function at a time
  - Hence, we need **separate instruction** and **data** memories
- Use **multiplexers** where alternate data sources are used for different instructions





# R-Type/Load/Store Datapath

## A Single Cycle Datapath

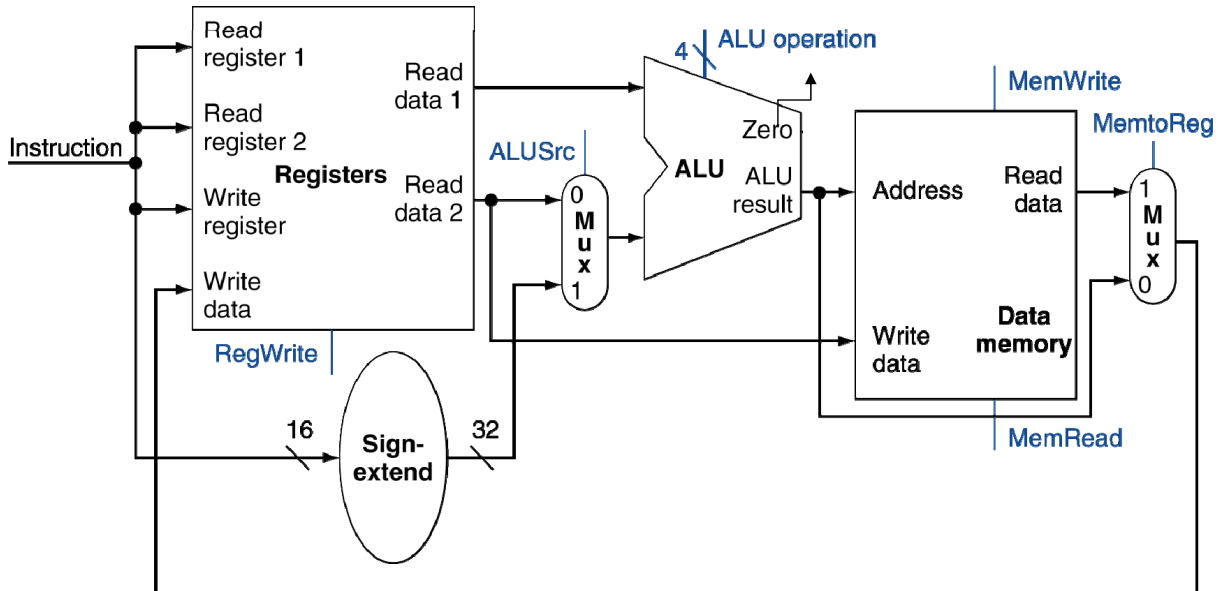


Correct Control signal (**RegWrite**, **ALUSrc**, **ALU operation**, **MemWrite**, **MemtoReg**, **MemRead**) are needed to make sure correct operation is done





# Full Datapath (Single Cycle Datapath)

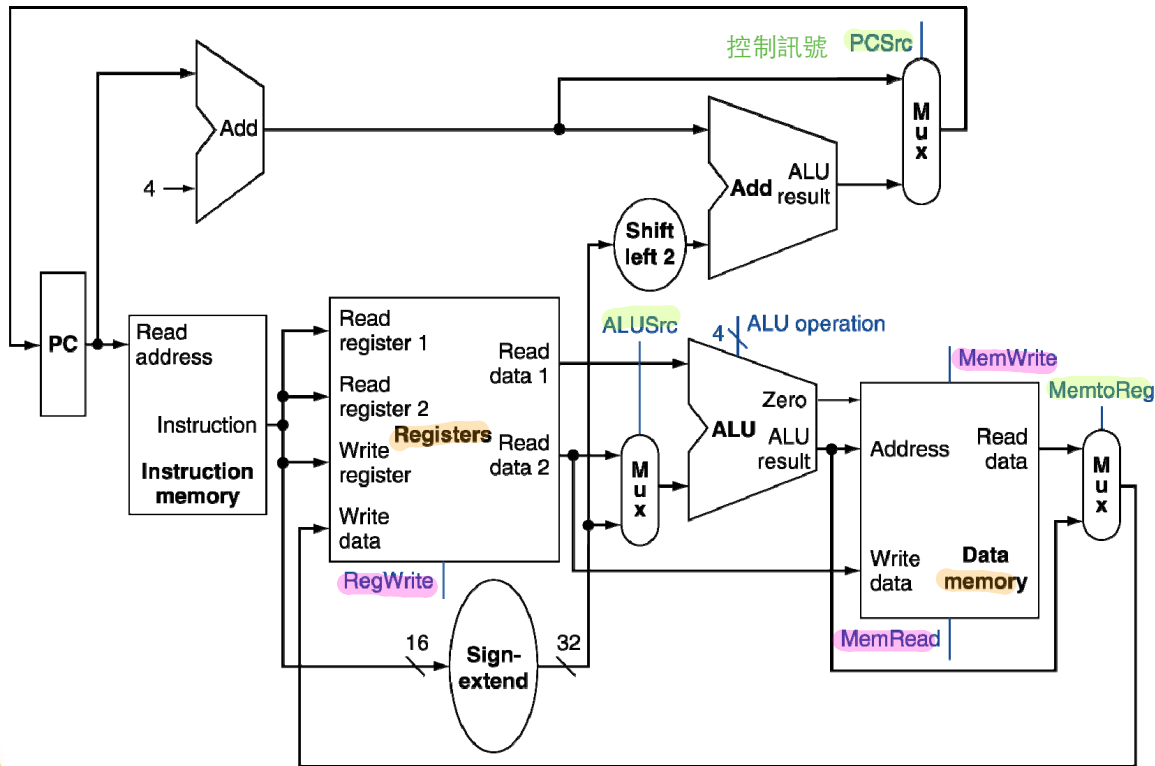


# Outline

---

- Designing a processor
- A single-cycle implementation (the datapath)
- **Control for the single-cycle CPU**
  - Control of CPU operations
  - ALU controller
  - Main controller




## Next: Building Datapath With Control

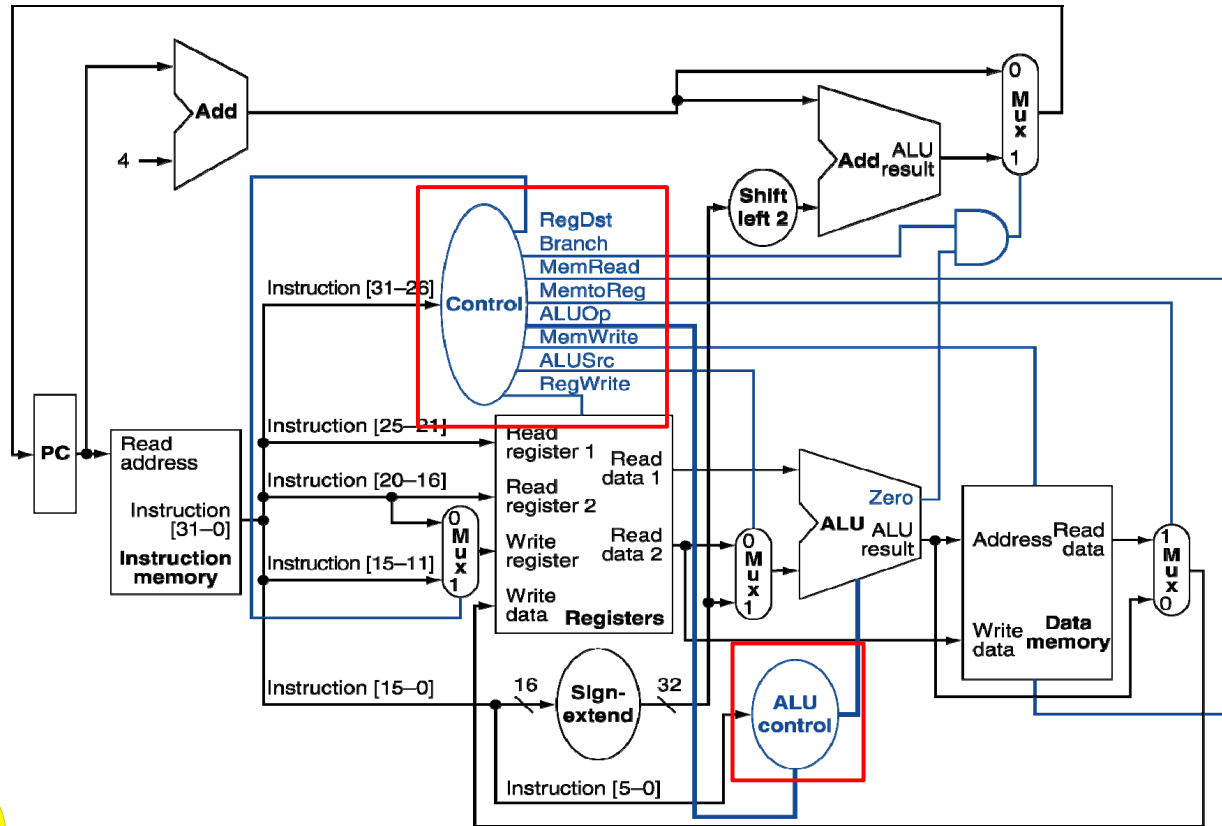
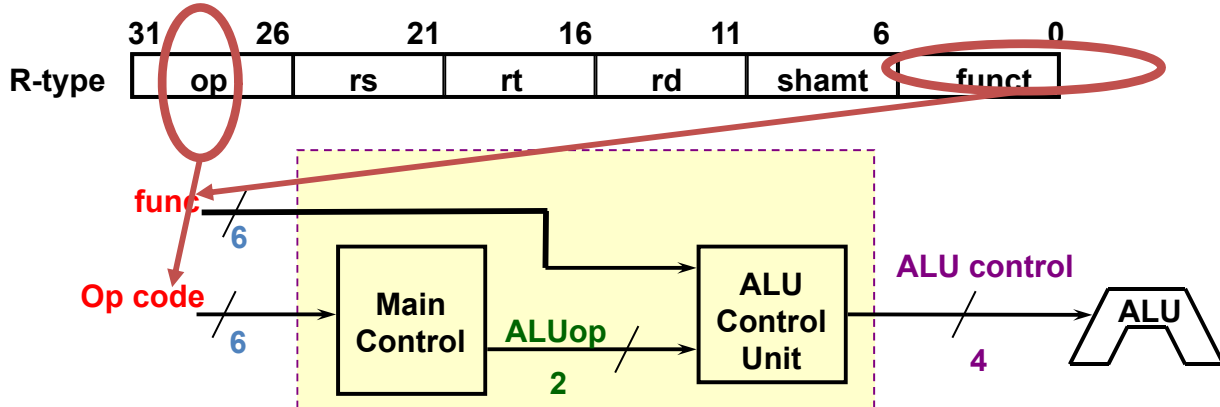
# Main Control and ALU Control

- **Main Control**: Based on opcode: generate RegDst, Branch, MemRead MemtoReg, ALUOp MemWrite, ALUSrc, RegWrite
- **ALU Control**: Based on **2-bit ALUOp** and the **6-bit func** field of instruction, the ALU control unit generates the 4-bit ALU control field



## Deciding ALU Control

- Assume 2-bit ALUOp derived from opcode
  - Combinational logic derives ALU control

opcode	ALUOp	Operation	funct	ALU function	ALU control
lw	00	load word	XXXXXX	add	?
sw	00	store word	XXXXXX	add	?
beq	01	branch equal	XXXXXX	subtract	?
R-type	10	add	100000	add	?
		subtract	100010	subtract	?
		AND	100100	AND	?
		OR	100101	OR	?
		set-on-less-than	101010	set-on-less-than	?


$lw \ \$\$1, \ 4(\$s0), \ [\$s0] + 4$   
 $sw \ \$\$1, \ 4(\$s0), \ [\$s0] + 4$



# ALU Control

- ALU Control has 4 four bits: **Ainvert**, **Binvert**, and **Operation** (2 bits)

Function	ALU control
AND	<u>0</u> 000
OR	000 <u>1</u>
add	<u>0</u> 010
subtract	011 <u>0</u>
set-on-less-than	011 <u>1</u>
NOR	<u>1</u> 100

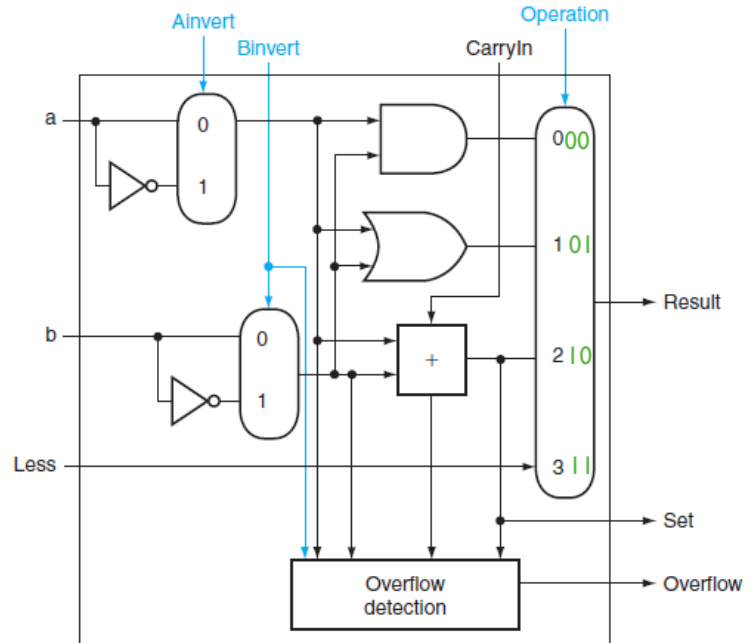

# ALU Control

- ALU used for
  - Load/Store: F = add
  - Branch: F = subtract
  - R-type: F depends on **funct** field
- Assume 2-bit ALUOp derived from opcode
  - Combinational logic derives ALU control

根據ALU function


opcode	ALUOp	Operation	funct	ALU function	ALU control
lw	00	load word	XXXXXX	add	0010
sw	00	store word	XXXXXX	add	0010
beq	01	branch equal	XXXXXX	subtract	0110
R-type	10	add	100000	add	0010
		subtract	100010	subtract	0110
		AND	100100	AND	0000
		OR	100101	OR	0001
		set-on-less-than	101010	set-on-less-than	0111






# Deciding Main Control Signals

- Control I signal

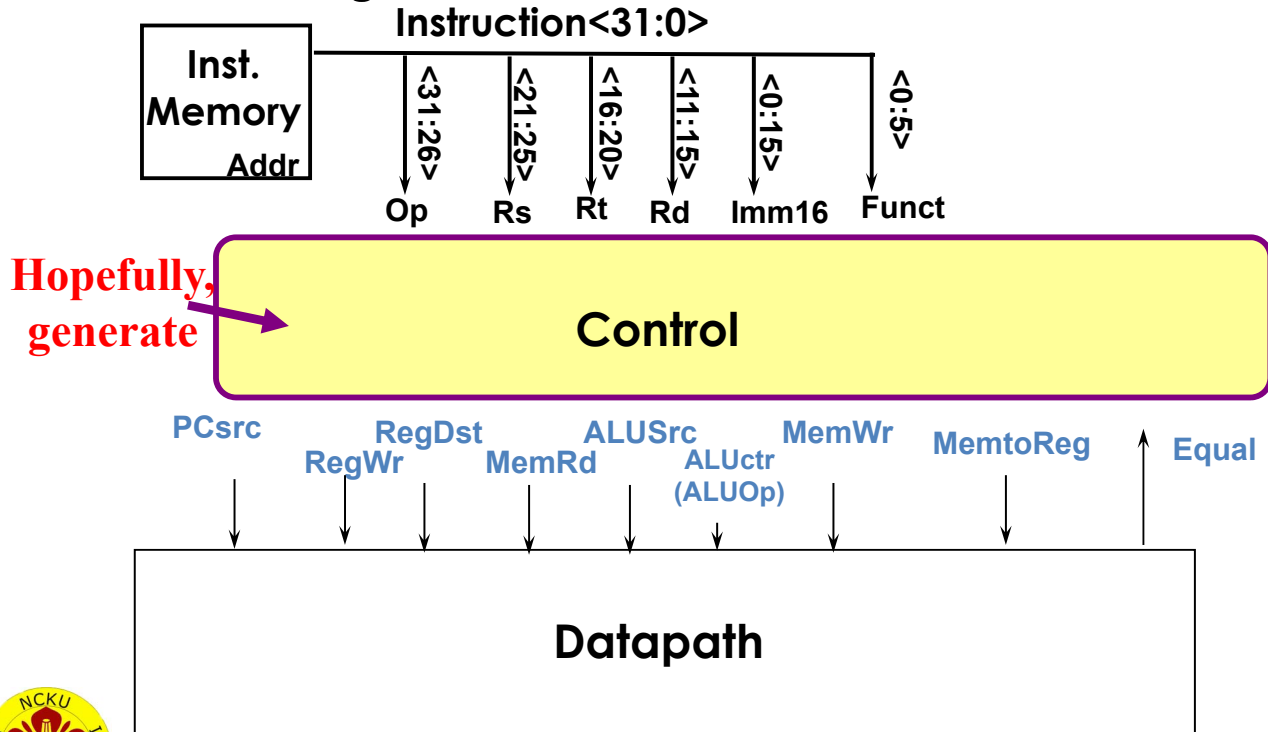

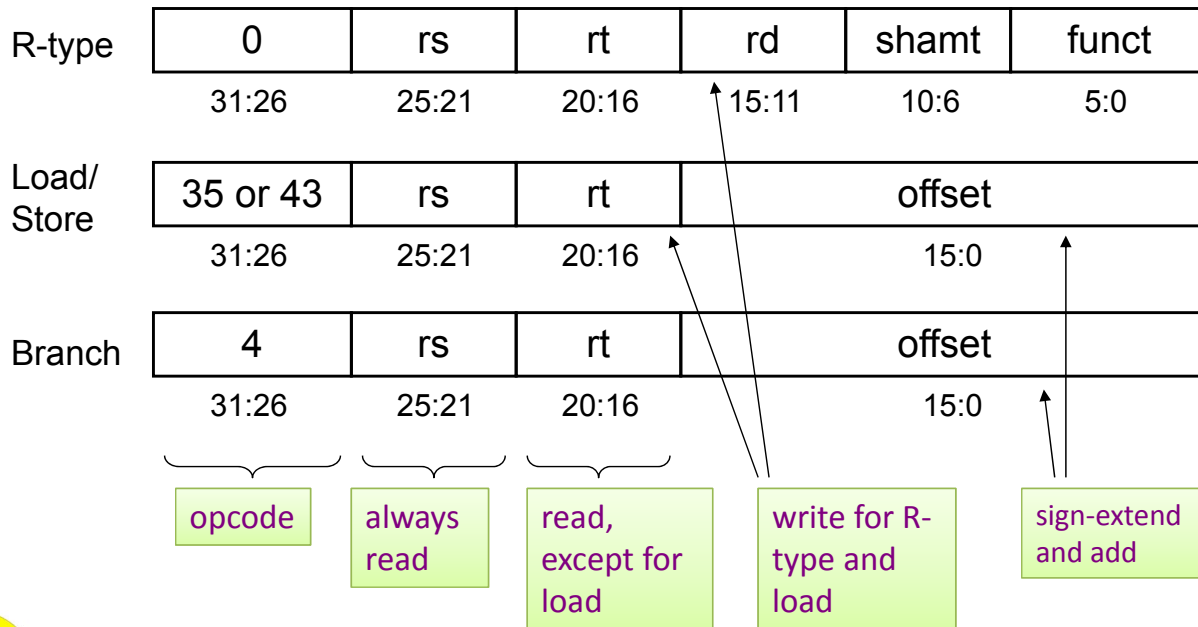
## Review: The Main Control Unit

- Control signals derived from instruction




# Control Signals for R-Type Instruction

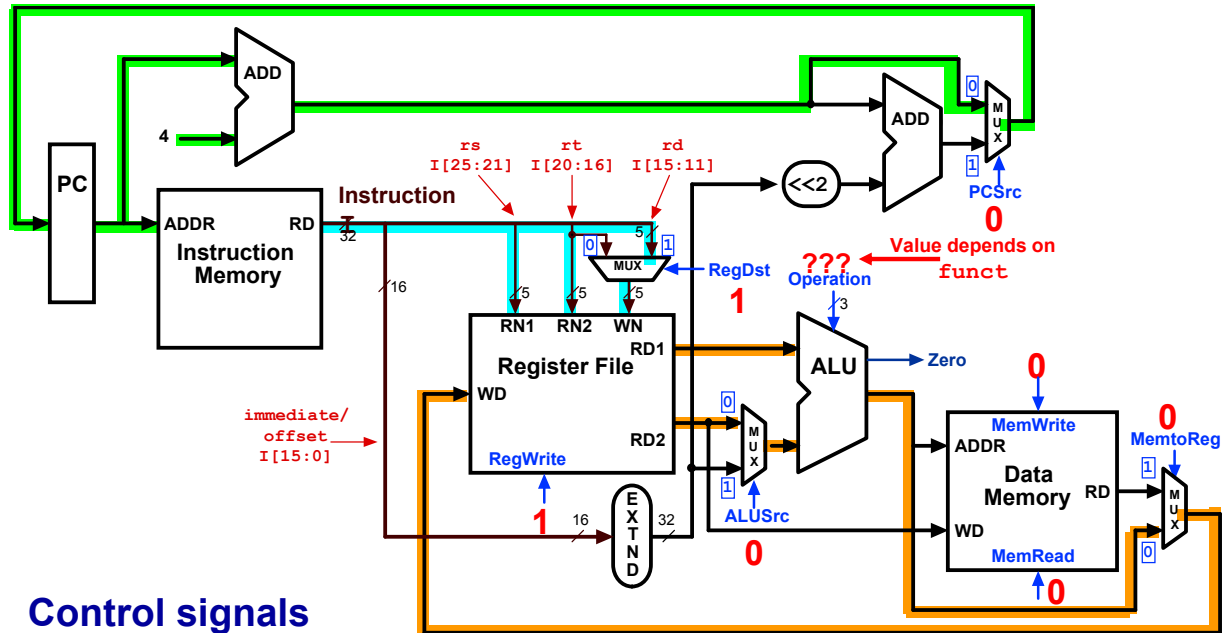


Control signals  
shown in blue




# Control Signals: $lw$ Instruction

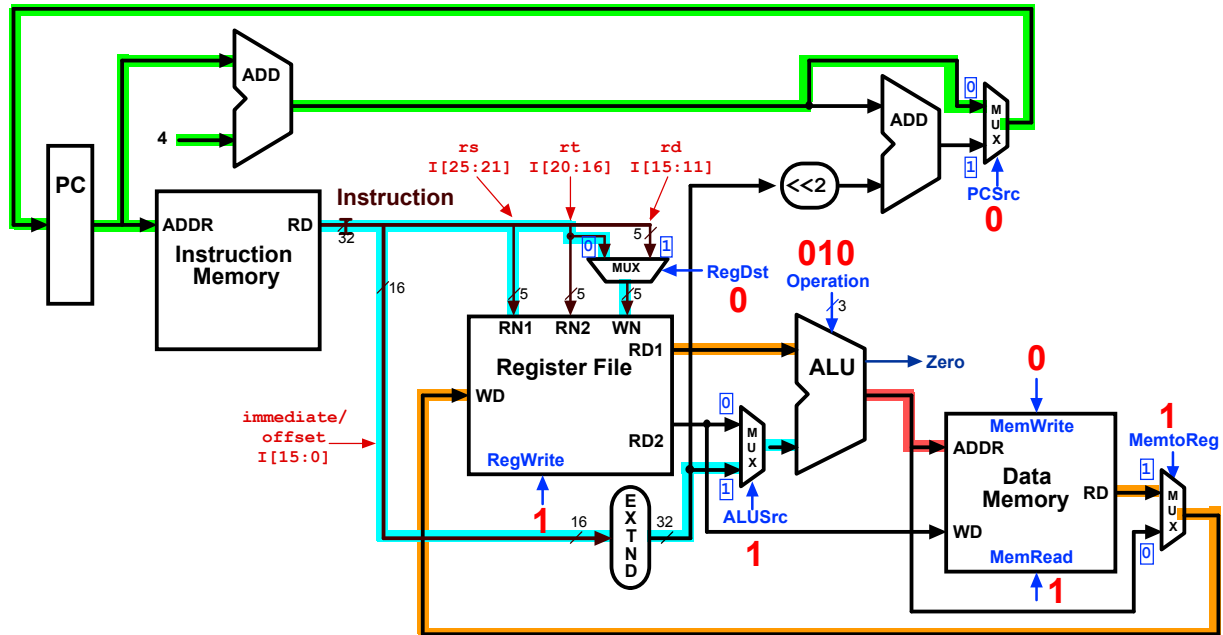


# Control Signals: $S_W$ Instruction

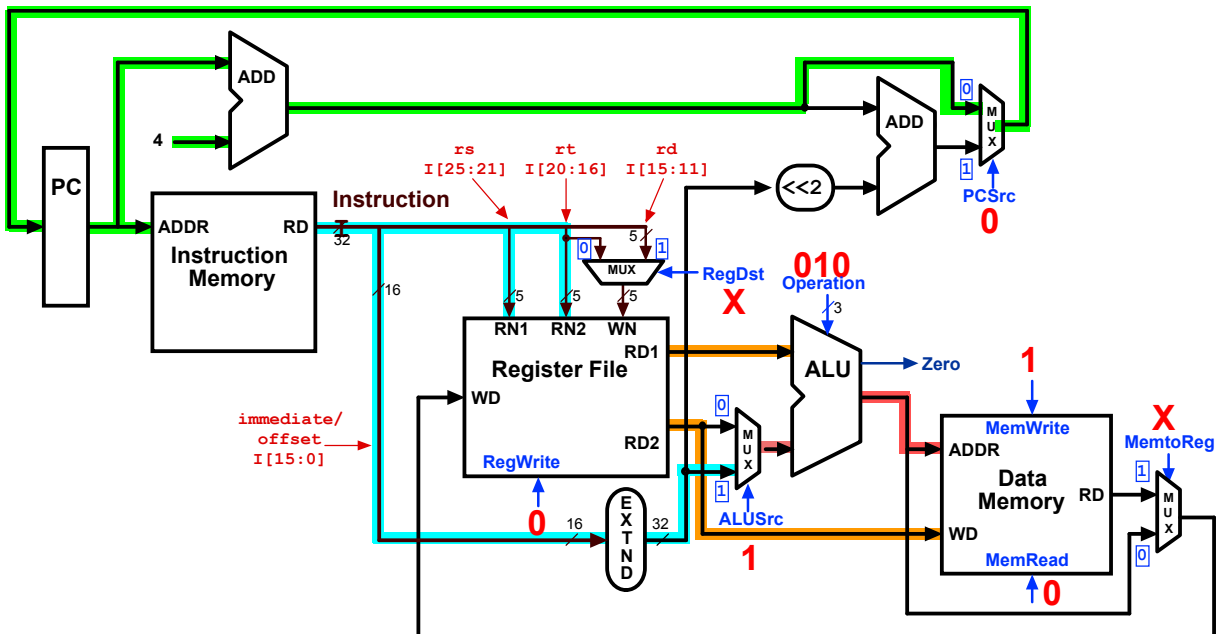


# Control Signals: beq Instruction

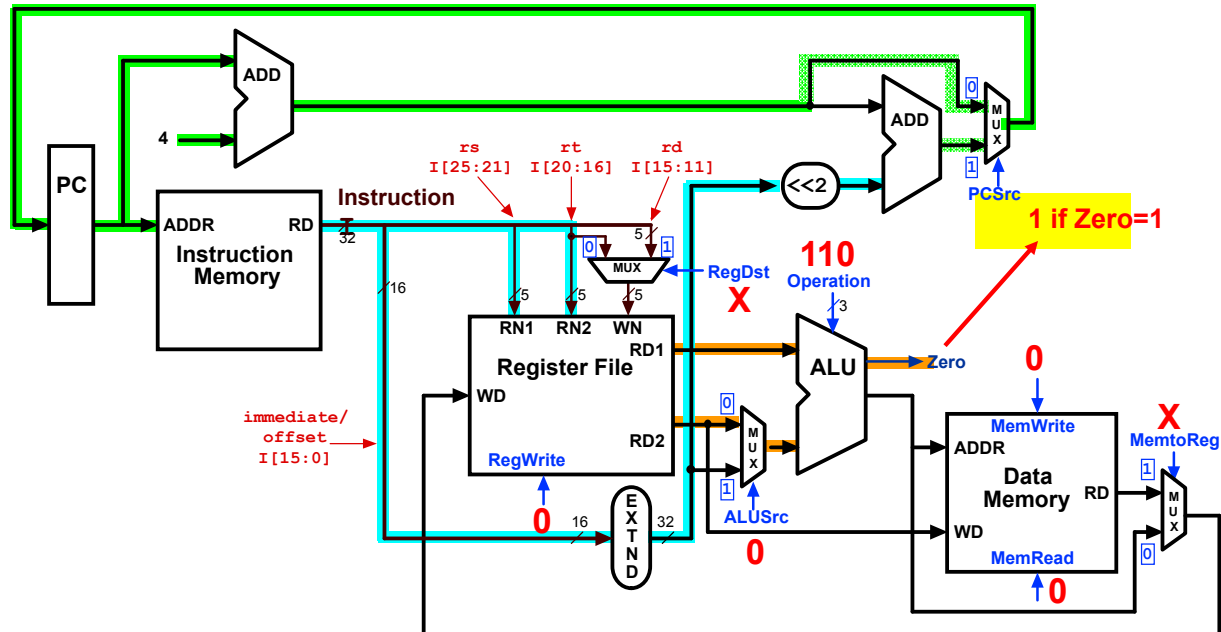

## Review: Implementing Jumps

 


 - Jump uses **word** address
- Update **PC** with concatenation of
  - Top **4** bits of **old PC**
  - **26**-bit jump address
  - **00**
- Need an extra control signal decoded from opcode



# Datapath Executing j

• j

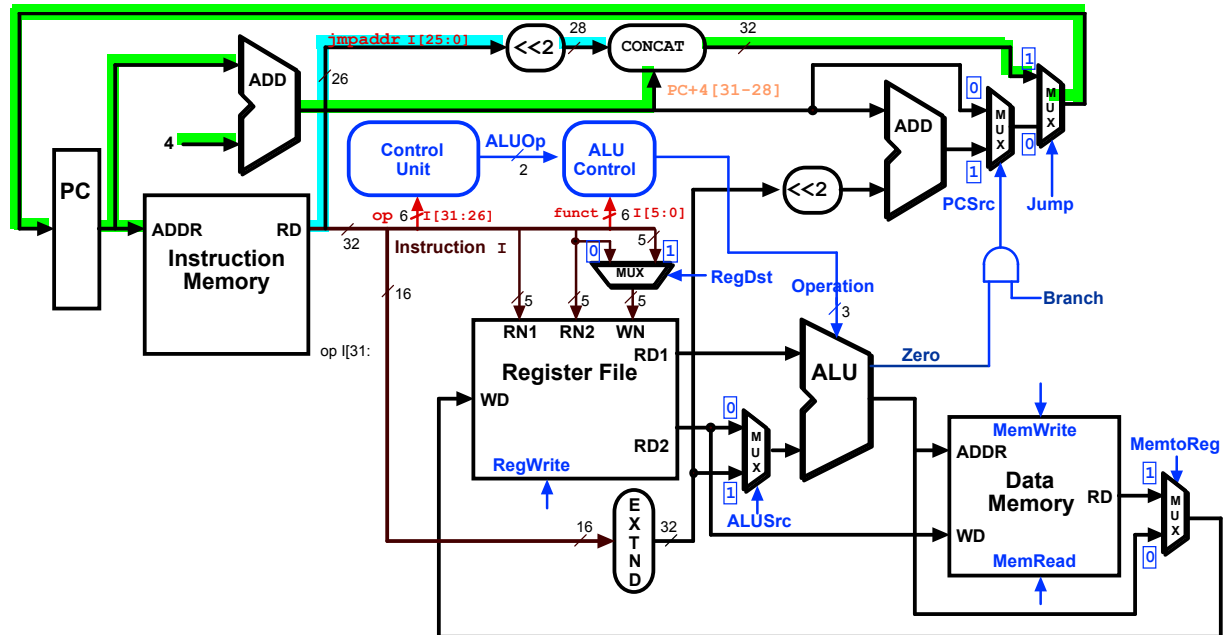



# Truth Table for Main Control Signals

- Current design of control is for
  - lw, sw, beq, and, or, add, sub, slt, nor
- I-format: lw, sw, beq
- R-format: and, or, add, sub, slt, nor
- Given 4 OP codes (each 6 bits) as “inputs”, the “outputs” are as follows  
=> a main control logic (the next slide)

See **appendix D**  
for details

inputs ← outputs →

Instruction	RegDst	ALUSrc	Memto-Reg	Reg Write	Mem Read	Mem Write	Branch	ALUOp1	ALUOp0
R-format									
000000	1	0	0	1	0	0	0	1	0
lw									
100011	0	1	1	1	1	0	0	0	0
sw									
101011	X	1	X	0	0	1	0	0	0
beq									
000100	X	0	X	0	0	0	1	0	1
addi	0	1	0	1	0	0	0	0	0




# Implementation of Main Control Block (Use PLA)

- Use PLA

	Signal	R-name	lw format	sw	beq
Inputs	Op5	0	1	1	0
	Op4	0	0	0	0
	Op3	0	0	1	0
	Op2	0	0	0	1
	Op1	0	1	1	0
	Op0	0	1	1	0
Outputs	RegDst	1	0	x	x
	ALUSrc	0	1	1	0
	MemtoReg	0	1	x	x
	RegWrite	1	1	0	0
	MemRead	0	1	0	0
	MemWrite	0	0	1	0
	Branch	0	0	0	1
	ALUOp1	1	0	0	0
	ALUOp2	0	0	0	1

**Truth table for main control signals**

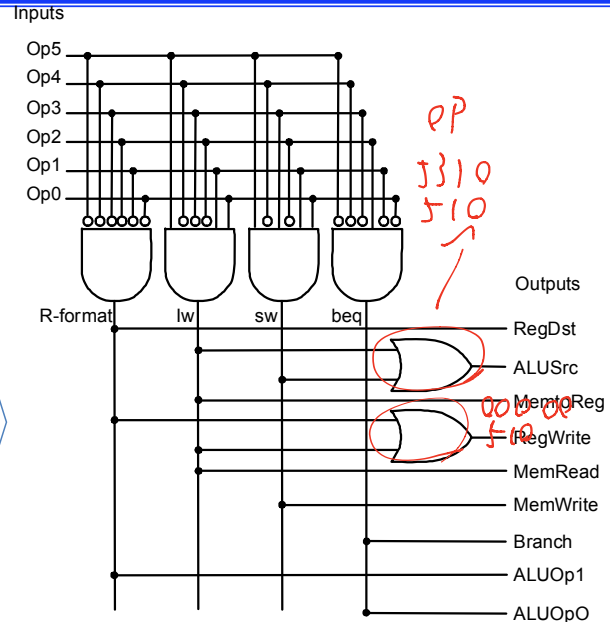

**Main control PLA (programmable logic array)**

$$RegDst = \overline{Op5} \cdot \overline{Op4} \cdot \overline{Op3} \cdot \overline{Op2} \cdot \overline{Op1} \cdot \overline{Op0}$$

ALUSrc=?



Instruction opcode	ALUOp	Instruction operation	Funct field	Desired ALU action	ALU control input
LW	00	load word	XXXXXX	add	0010
SW	00	store word	XXXXXX	add	0010
Branch equal	01	branch equal	XXXXXX	subtract	0110
R-type	10	add	100000	add	0010
R-type	10	subtract	100010	subtract	0110
R-type	10	AND	100100	AND	0000
R-type	10	OR	100101	OR	0001
R-type	10	set on less than	101010	set on less than	0111

## Truth Table for ALU control signals

	inputs								outputs	
	ALUOp		Funct field						Operation $C_3C_2C_1C_0$	
	ALUOp1	ALUOp0	F5	F4	F3	F2	F1	F0		
Merge LW & SW	0	0	X	X	X	X	X	X	0010	add
	0	1	X	X	X	X	X	X	0110	subtract
	1	X	X	X	0	0	0	0	0010	add
	1	X	X	X	0	0	1	0	0110	subtract
	1	X	X	X	0	1	0	0	0000	and
	1	X	X	X	0	1	0	1	0001	or
	1	X	X	X	1	0	1	0	0111	slt



# Implementation of ALU Control Block

- C3=0

C2


ALUOp		Function code fields					
ALUOp1	ALUOp0	F5	F4	F3	F2	F1	F0
0	1	X	X	X	X	X	X
1	X	X	X	X	X	1	X

C1

ALUOp		Function code fields					
ALUOp1	ALUOp0	F5	F4	F3	F2	F1	F0
0	X	X	X	X	X	X	X
X	X	X	X	X	0	X	X

C0

ALUOp		Function code fields					
ALUOp1	ALUOp0	F5	F4	F3	F2	F1	F0
1	X	X	X	X	X	X	1
1	X	X	X	1	X	X	X

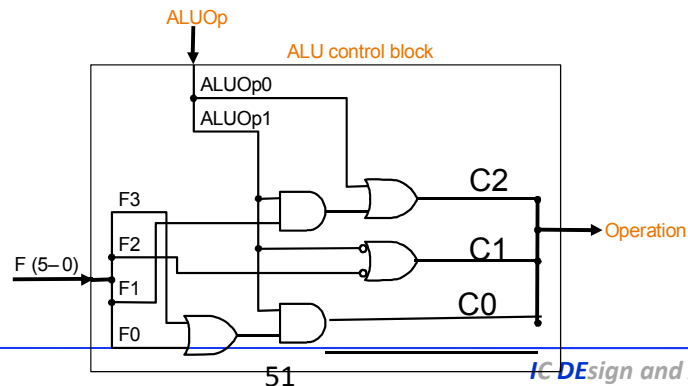

# Performance Issues

---

- Longest delay determines clock period
  - Critical path: load instruction
  - Instruction memory → register file → ALU → data memory → register file
- Not feasible to vary period for different instructions
- Violates design principle
  - Making the common case fast
- We will improve performance by pipelining



# Backup Slides