

- P12.9** (a) This NMOS transistor is operating in saturation because we have $v_{GS} \geq V_{to}$ and $v_{DS} \geq v_{GS} - V_{to}$. Thus, $I_a = K(v_{GS} - V_{to})^2 = 1.8 \text{ mA}$.
 (b) This PMOS transistor is operating in saturation because we have $v_{GS} \leq V_{to}$ and $v_{DS} = -4 \leq v_{GS} - V_{to} = -3 - (-1) = -2$. Thus, $I_b = K(v_{GS} - V_{to})^2 = 0.8 \text{ mA}$.
 (c) This PMOS transistor is operating in the triode region because we have $v_{GS} \leq V_{to}$ and $v_{DS} = -1 \geq v_{GS} - V_{to} = -5 - (-1) = -4$. Thus, $I_c = K[2(v_{GS} - V_{to})v_{DS} - v_{DS}^2] = 1.4 \text{ mA}$.
 (d) This NMOS transistor is operating in the triode region because we have $v_{GS} \geq V_{to}$ and $v_{DS} = 1 \leq v_{GS} - V_{to} = 3 - 1 = 2$. Thus, $I_d = K[2(v_{GS} - V_{to})v_{DS} - v_{DS}^2] = 0.6 \text{ mA}$.

P12.13

$$i_D = k(V_{GS} - V_{t0})^2$$

$$0.8 = 0.2(V_{GS} - 1)^2$$

$$V_{GS} = 1 \text{ V}$$

- P12.31*** We can write $V_{DD} = V_{DSQ} + R_S I_{DQ}$. Substituting values and solving, we obtain $R_S = 3 \text{ k}\Omega$. Next we have $K = \frac{1}{2} KP(W/L) = 2 \text{ mA/V}^2$. Assuming that the NMOS operates in saturation, we have

Substituting values and solving, we find $V_{GSQ} = 0 \text{ V}$ and $V_{GSQ} = 2 \text{ V}$. The correct root is $V_{GSQ} = 2 \text{ V}$. (As a check we see that the device does operate in saturation because we have $V_{GSQ} > V_{t0}$ and $V_{DSQ} > V_{GSQ} - V_{t0}$.) Then we have $V_G = V_{GSQ} + R_S I_{DQ} = 8 \text{ V}$. However we also have

Substituting values and solving, we obtain $R_2 = 2 \text{ M}\Omega$.

- P12.33** We have $V_G = V_{GSQ} = 5R_2/(R_1 + R_2) = 2.5 \text{ V}$. Then we have $I_{DQ} = K(V_{GSQ} - V_{t0})^2 = 1.28 \text{ mA}$. $V_{DSQ} = V_{DD} - R_D I_{DQ} = -0.12 \text{ V}$. For the MOSFET to operate in saturation R_D cannot exceed $2.65 \text{ k}\Omega$.

P12.53* (a) $V_G = V_{DD} \frac{R_2}{R_1 + R_2} = 20 \frac{0.3}{1.7 + 0.3} = 3 \text{ V}$

$$V_{GSQ} = V_G = 3 \text{ V}$$

$$K = \frac{1}{2} KP(W/L) = 2.5 \text{ mA/V}^2$$

$$I_{DQ} = K(V_{GSQ} - V_{to})^2 = 10 \text{ mA}$$

$$V_{DSQ} = V_{DD} - R_D I_{DQ} = 10 \text{ V}$$

$$g_m = 2\sqrt{KI_{DQ}} = 0.01 \text{ S}$$

(b) $R'_L = \frac{1}{1/R_D + 1/R_L} = 500 \Omega$

$$A_v = -g_m R'_L = -5$$

$$R_{in} = \frac{1}{1/R_1 + 1/R_2} = 255 \text{ k}\Omega$$

$$R_o = R_D = 1 \text{ k}\Omega$$

P12.62

