 


# ***Chapter 6***

## **Registers and Counters**

# Sequential Circuits

- **Clocked sequential circuits (循序, 序向, 順序)**
    - **a group of flip-flops and combinational gates**
    - **connected to form a feedback path**
- Flip-flops + (essential)**      **Combinational gates (optional)**



# Registers

Register:


- a group of flip-flops (正反器)
- gates that determine how the information is transferred into the register

Function table


$R$	$C$	$D$	$Q$	$Q'$
0	X	X	0	1
1	↑	0	0	1
1	↑	1	1	0

A  $n$ -bit register

 - $n$  flip-flops capable of storing  $n$  bits of binary information
- 4-bit register




 If  $Clear=0$   
clear (reset);  
else  
normal mode;



# 4-bit register with parallel load

Four-bit register  
with parallel load

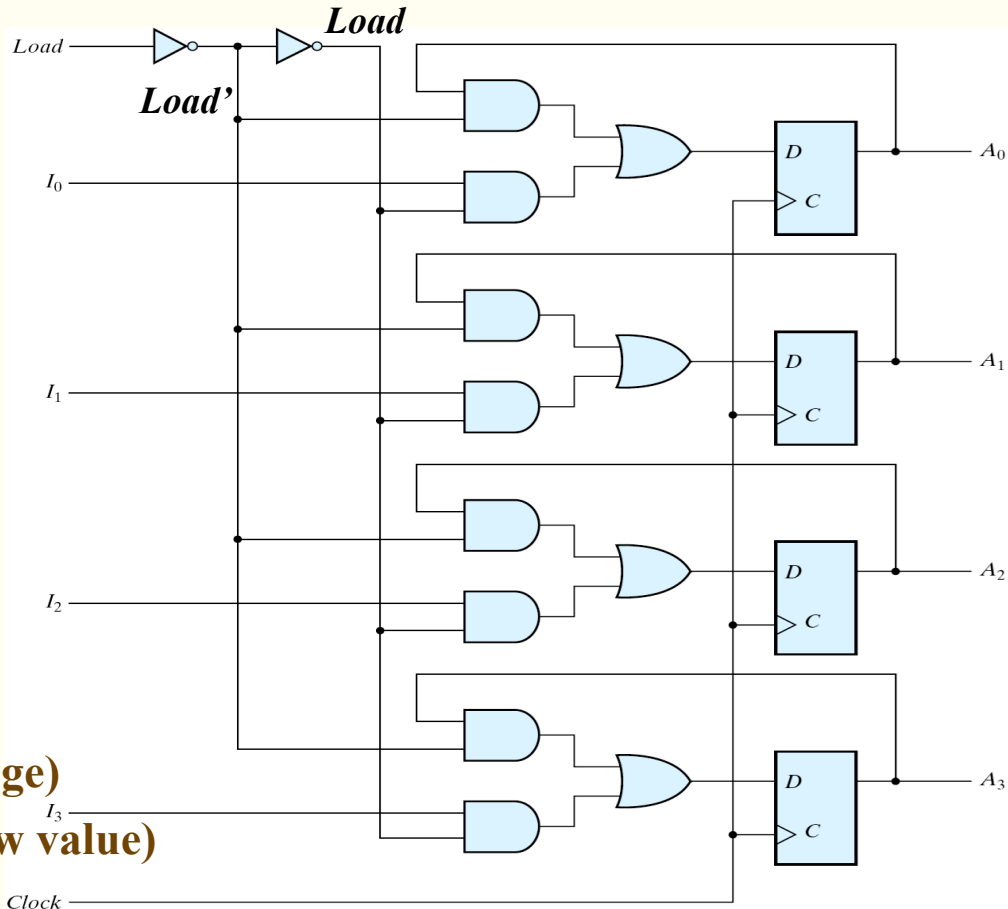

<i>Load</i>	<i>Clock</i>	$A(t+1)$
-------------	--------------	----------

0	↑	$A(t)$ (no change)
---	---	--------------------

1	↑	$I$ (load new value)
---	---	----------------------

# Shift Registers (1/2)

- **Shift register**
  - **a register capable of shifting its binary information in one or both directions**
- **Simplest shift register**


 


Fig. 6.3 Four-bit shift register

## Shift Registers (2/2)

 

Note: output value is the same if no clock comes

- A chain of FFs in cascade
- All FFs receive common clock pulses that activate the shift from one stage to the next
- Each clock pulse shifts the contents of the register one bit position to the right
- Serial input determines what goes into the leftmost FF during the shift
- Serial output is taken from the output of the rightmost FF.

# Shifter

## Serial transfer vs. Parallel transfer


- Serial transfer

- Information is transferred one bit at a time
- shifts the bits out of the source register into the destination register


- Parallel transfer:

- All the bits of the register are transferred at the same time

# Serial transfer from reg A to reg B

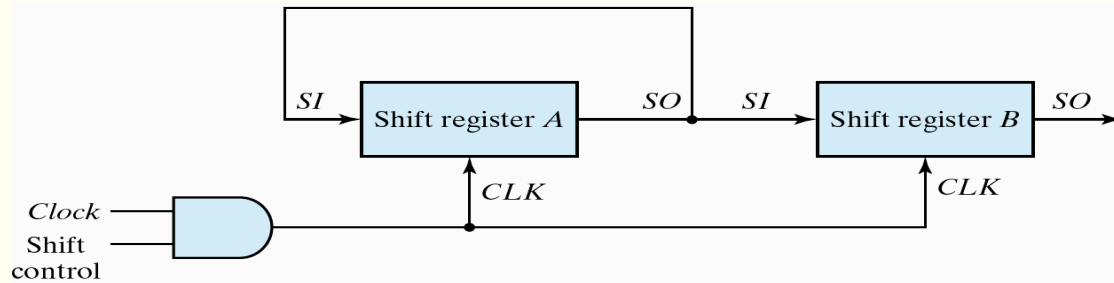

(a) Block diagram

 

(b) Timing diagram

**Table 6.1**  
*Serial-Transfer Example*

Timing Pulse	Shift Register A				Shift Register B			
Initial value	1	0	1	1	0	0	1	0
After $T_1$	1	1	0	1	1	0	0	1
After $T_2$	1	1	1	0	1	1	0	0
After $T_3$	0	1	1	1	0	1	1	0
After $T_4$	1	0	1	1	1	0	1	1




# Serial addition using D flip-flops

$$A = A + B$$

If both A and B are  
4-bit SRs, the correct  
result will come out  
after 5 cycles.  
(serial input=0)

Fig. 6.5  
Serial adder

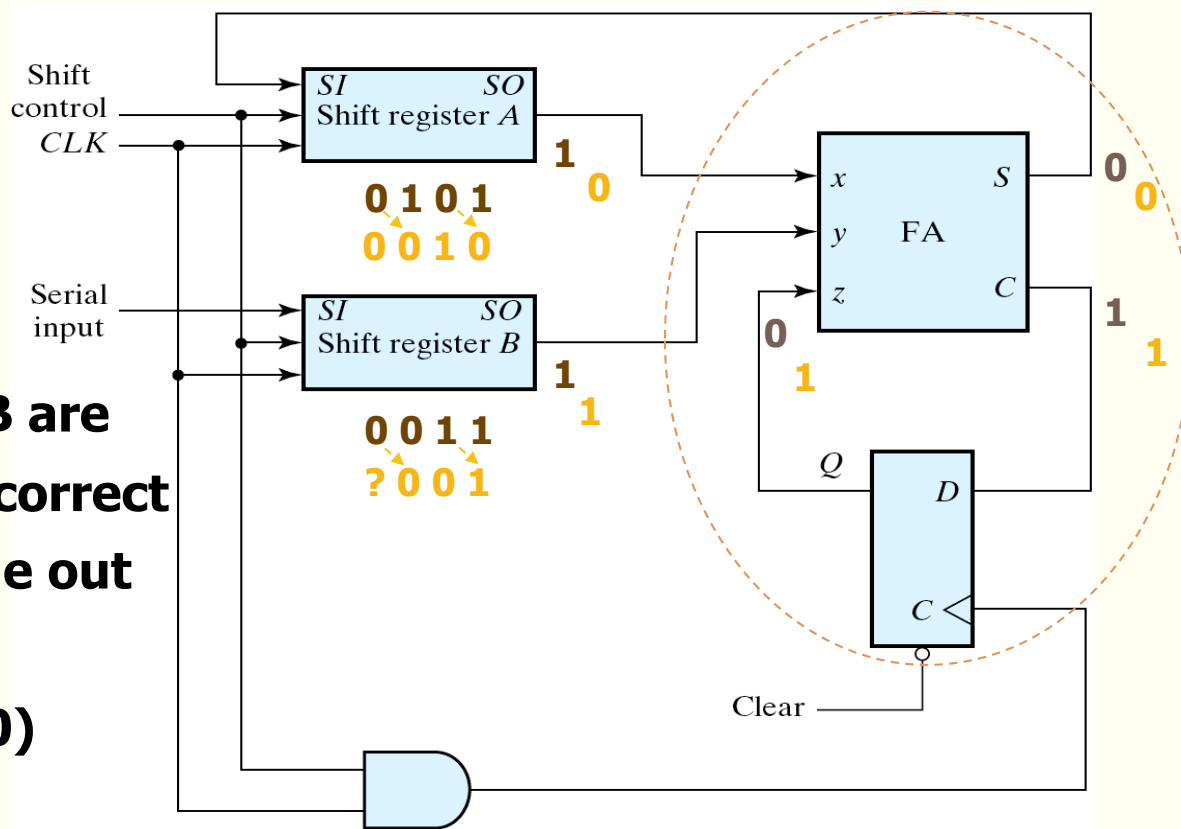

# Serial adder using JK flip-flops

carry

**Table 6.2**

*State Table for Serial Adder*

Present State $Q$	Inputs $x \quad y$		Next State $Q$	Output $S$	Flip-Flop Inputs	
					$J_Q$	$K_Q$
0	0	0	0	0	0	X
0	0	1	0	1	0	X
0	1	0	0	1	0	X
0	1	1	1	0	1	X
1	0	0	0	1	X	1
1	0	1	1	0	X	0
1	1	0	1	0	X	0
1	1	1	1	1	X	0

Excitation Table

$Q(t)$	$Q(t+1)$	J	K
0	0	0	x
0	1	1	x
1	0	x	1
1	1	x	0

		$xy$			
		00	01	11	10
$Q$	0	0	0	1	0
	1	X	X	X	X

$J = xy$

		$xy$			
		00	01	11	10
$Q$	0	1	0	0	0
	1	X	X	X	X

$K = (x+y)'$




		$xy$			
		00	01	11	10
$Q$	0	0	1	0	1
	1	1	0	1	0

$$S = x \oplus y \oplus Q$$
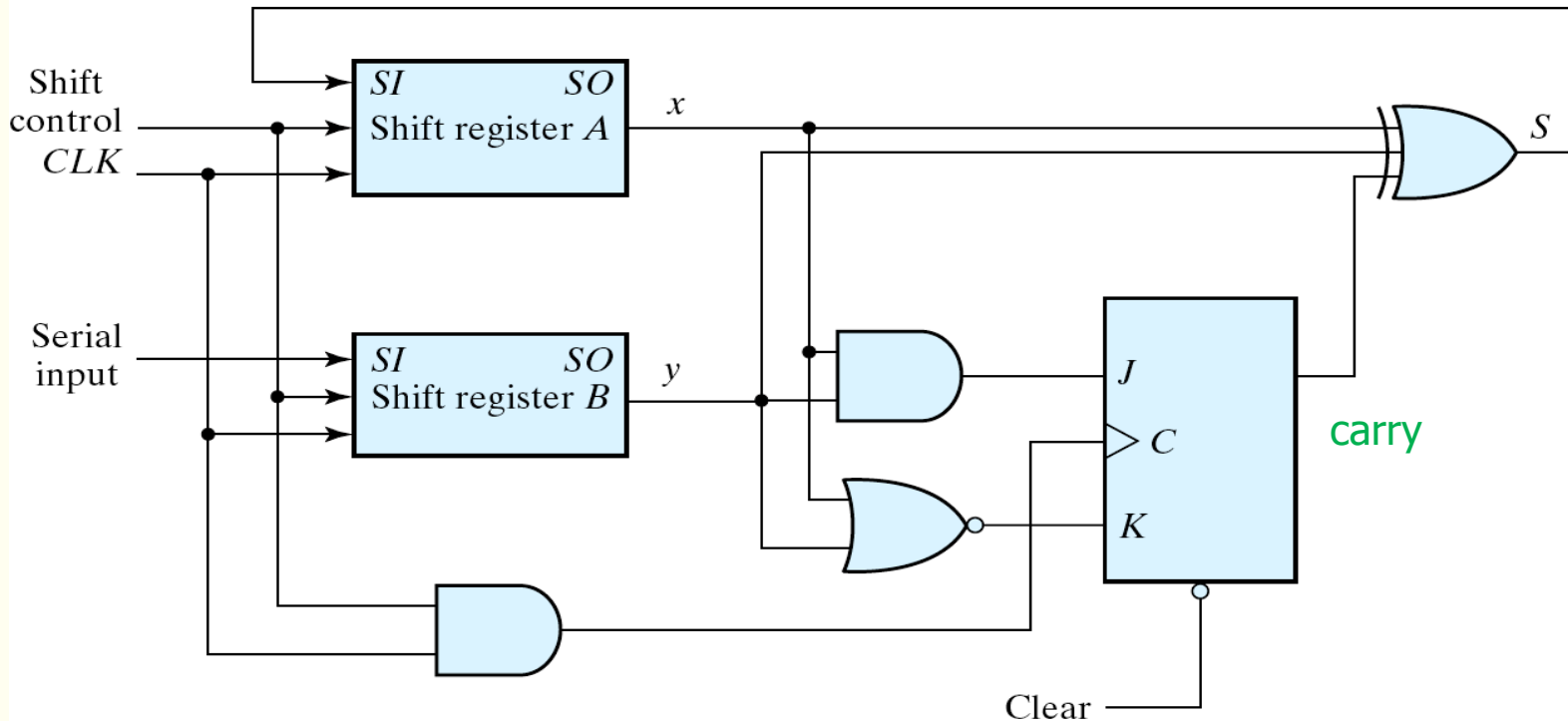
## Circuit Diagram

$$JQ = x y$$



$$KQ = x' y' = (x + y)' \quad S = x \oplus y \oplus Q$$



# Universal Shift Register

- **Universal Shift Register**
  - **Unidirectional shift register**
  - **Bidirectional shift register**
  - **Universal shift register:**
    - **has both direction shifts & parallel load/out capabilities**

# Parallel Load + Shift

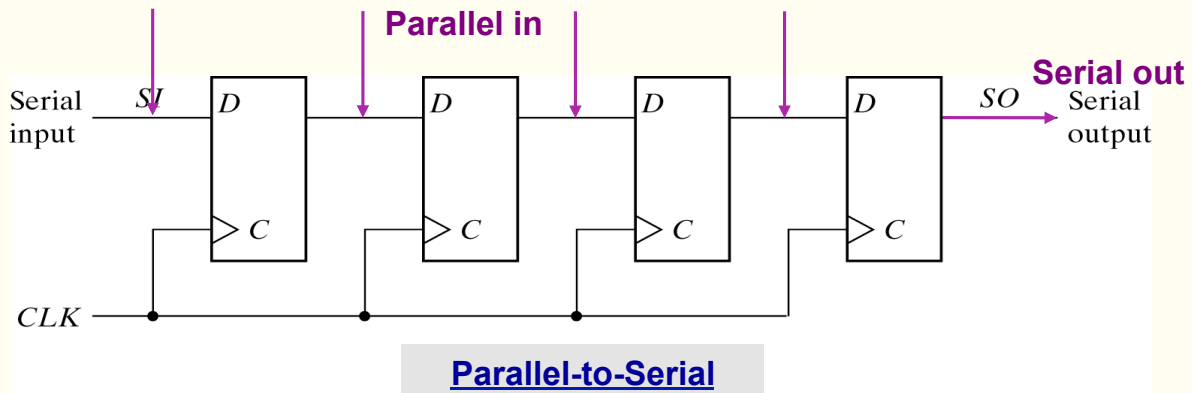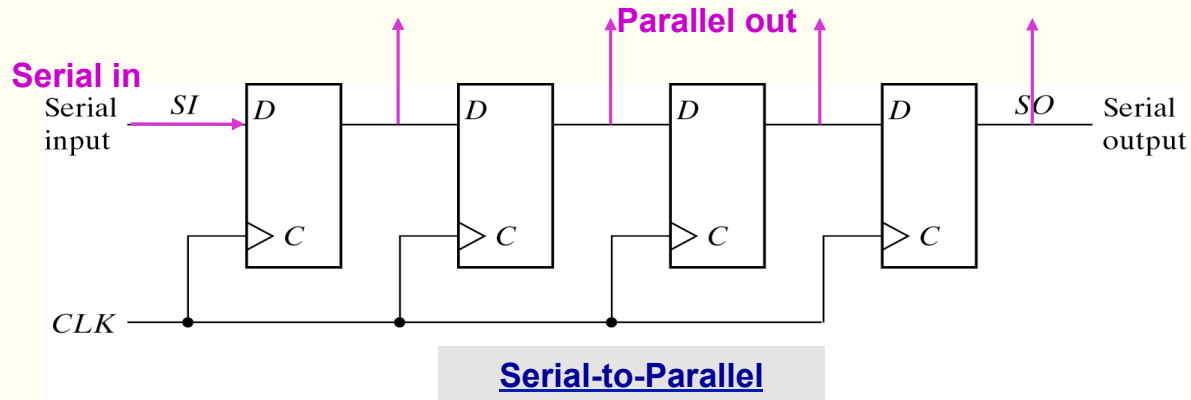

# 4-Bit Universal Shift Register (1/2)

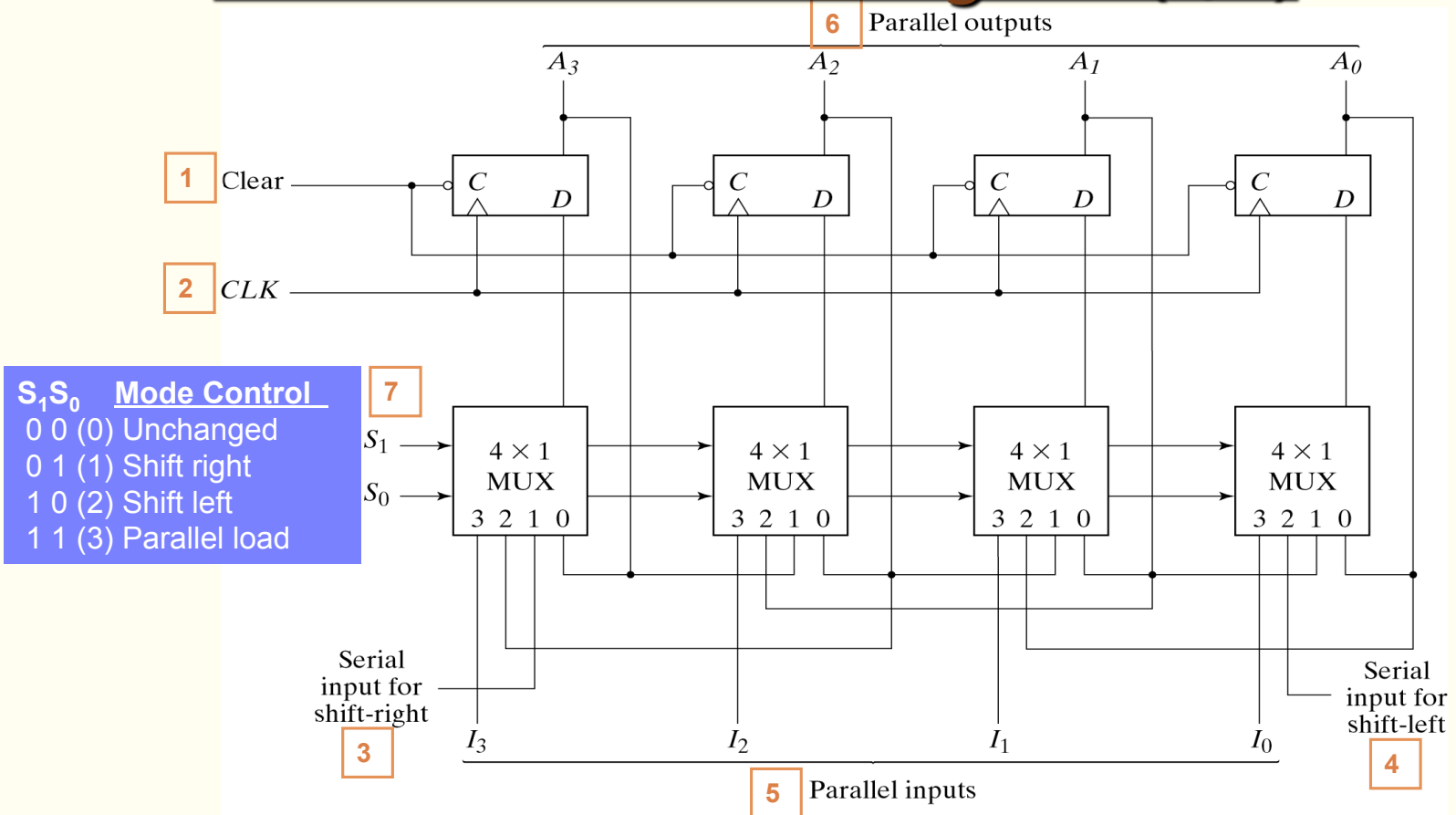


Fig. 6-7 4-Bit Universal Shift Register

# 4-Bit Universal Shift Register (2/2)

1. A *clear* control to clear the register to 0.
2. A *clock* input to synchronize the operations.
3. A *shift-right* control to enable the shift right operation and the *serial input* and *output* lines associated w/ the shift right.
4. A *shift-left* control to enable the shift left operation and the *serial input* and *output* lines associated w/ the shift left.
5. A *parallel-load* control to enable a parallel transfer and the *n parallel input* lines associated w/ the parallel transfer.
6. *n parallel output* lines.
7. A control state that leaves the information in the register

# Ripple Counters

## Counter:

- a register that goes through a prescribed sequence of states
- upon the application of input pulses
  - Input pulses: may be clock pulses or  
originate from some external source
  - The sequence of states:  
may follow the binary number sequence  
( $\Rightarrow$  Binary Counter) or any other sequence of states



# Counter

## Categories of counters

### 1. Ripple counters

The flip-flop output transition serves as a source for triggering other flip-flops

⇒ no common clock pulse (not synchronous)

### 2. Synchronous counters:

The CLK inputs of all flip-flops receive a common clock


# Synchronous/Asynchronous Counter

## Synchronous counter:

All flip-flops in a synchronous counter receive the same clock pulse and so change state simultaneously.

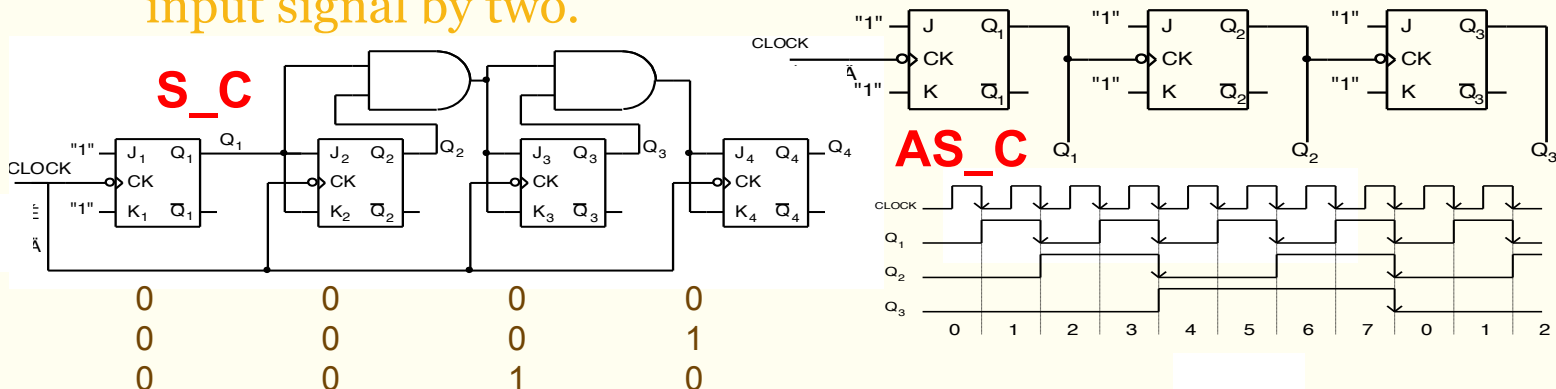
## Asynchronous (Ripple) counter:

Flip-flops transitions ripple through from one flip-flop to the next in sequence until all flip-flops reach a new stable value (state). Each single flip-flop stage divides the frequency of its input signal by two.



# Counter Implementation

## Synchronous counter

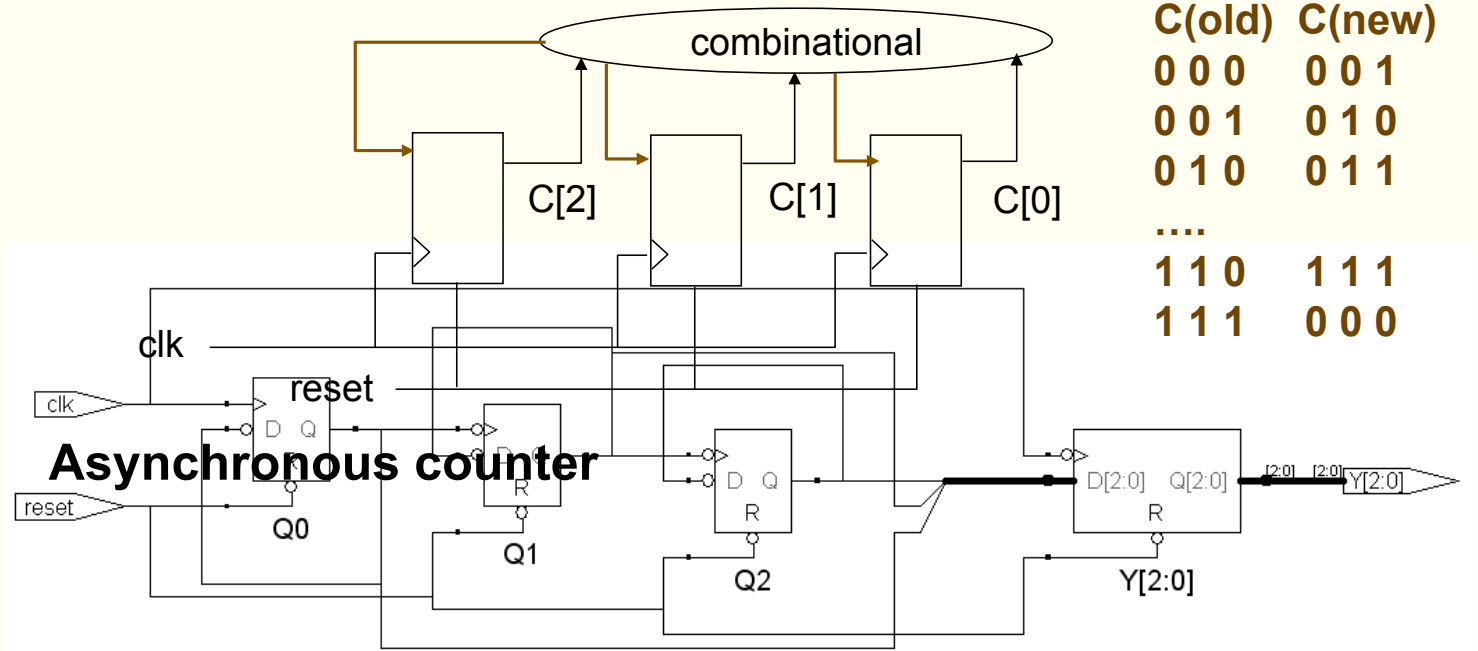

## Asynchronous counter

# Synchronous Counters

- **Synchronous Counter**
  - A common clock triggers all flip-flops simultaneously
- **Design procedure**
  - apply the same procedure of synchronous sequential circuits
  - synchronous counter is simpler than general synchronous sequential circuits

# 4-bit Binary Counter

0 0 1 1  
0 1 0 0

$A_0=1, A_1=1, A_2=0, A_3=0$

$\Rightarrow JA_0=1, KA_0=1$


$C_{en}A_0=1 \Rightarrow JA_1=1, KA_1=1$

$C_{en}A_0A_1=1 \Rightarrow JA_2=1, KA_2=1$

$C_{en}A_0A_1A_2=0 \Rightarrow JA_3=0, KA_3=0$

$\uparrow A_0=0, A_1=0, A_2=1, A_3=0$

Four-bit synchronous binary counter

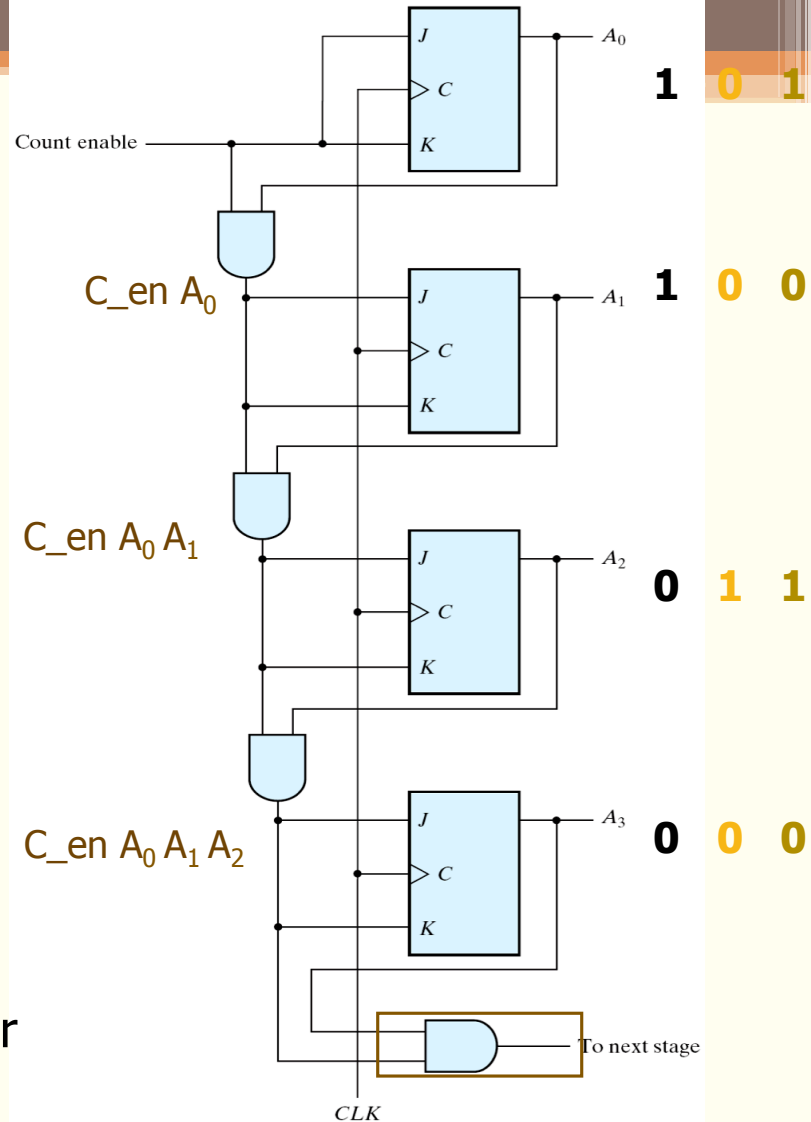

## 4-bit Up/Down Binary Counter


## Up Counter

010 → 011 → 100 → 101 → ...

## Down Counter


110 → 101 → 100 → 011 → ...

## Four-bit up-down binary counter

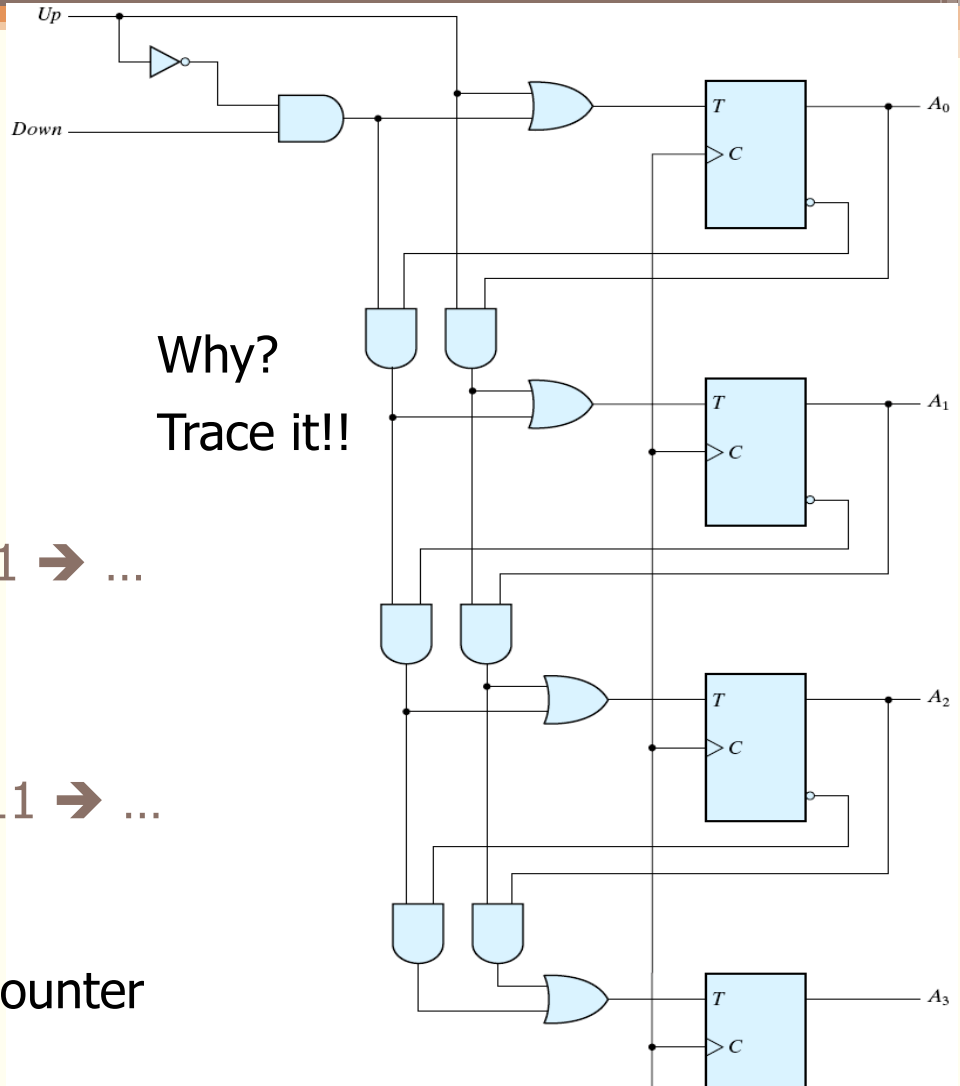

# Synchronous Counter

## Synchronous Counter

 

C(old)	C(new)
0 0 0	0 0 1
0 0 1	0 1 0
0 1 0	0 1 1
...	
1 1 0	1 1 1
1 1 1	0 0 0

Draw three K-maps

0 → 1 → 2 → 3 → 4 → 5 → 6 → 7 → 0 → 1 → ...

0 → 1 → 2 → 3 → 4 → 5 → 6 → 0 → 1 → 2 → ....

Draw three K-maps

C(old)	C(new)
0 0 0	0 0 1
0 0 1	0 1 0
0 1 0	0 1 1
...	
...	1 1 0
1 1 0	0 0 0
0 0 0	0 0 1

# Other Counters (1/2)

- **Counters:**
  - can be designed to generate any desired sequence of states
- **Divide-by- $N$  counter (modulo- $N$  counter)**
  - a counter that goes through a repeated sequence of  $N$  states
  - The sequence may follow the binary count or may be any other arbitrary sequence



## Other Counters (2/2)

- $n$  flip-flops  $\Rightarrow 2^n$  binary states
- Unused states
  - states that are not used in specifying the FSM
  - may be treated as don't-care conditions or may be assigned specific next states

**Table 6.7**  
*State Table for Counter*

0 → 1 → 2 → 4 → 5 → 6 → 0 → 1 → 2 → .....

Present State			Next State			Flip-Flop Inputs					
A	B	C	A	B	C	$J_A$	$K_A$	$J_B$	$K_B$	$J_C$	$K_C$
0	0	0	0	0	1	0	X	0	X	1	X
0	0	1	0	1	0	0	X	1	X	X	1
0	1	0	1	0	0	1	X	X	1	0	X
1	0	0	1	0	1	X	0	0	X	1	X
1	0	1	1	1	0	X	0	1	X	X	1
1	1	0	0	0	0	X	1	X	1	0	X

# An Example Two unused states: 011 & 111

**Table 6.7**  
*State Table for Counter*

Present State			Next State			Flip-Flop Inputs					
A	B	C	A	B	C	$J_A$	$K_A$	$J_B$	$K_B$	$J_C$	$K_C$
0	0	0	0	0	1	0	X	0	X	1	X
0	0	1	0	1	0	0	X	1	X	X	1
0	1	0	1	0	0	1	X	X	1	0	X
1	0	0	1	0	1	X	0	0	X	1	X
1	0	1	1	1	0	X	0	1	X	X	1
1	1	0	0	0	0	X	1	X	1	0	X
<b>0</b>	<b>1</b>	<b>1</b>				<b>X</b>	<b>X</b>	<b>X</b>	<b>X</b>	<b>X</b>	<b>X</b>
<b>1</b>	<b>1</b>	<b>1</b>				<b>X</b>	<b>X</b>	<b>X</b>	<b>X</b>	<b>X</b>	<b>X</b>

$$J_A = B \quad \dots$$

		$J_A$			
		00	01	11	10
A	0			X	1
	1	X	X	X	X

# Logic Diagram


The simplified flip-flop  
input equations:

$$J_A = B, \quad K_A = B$$


$$J_B = C, \quad K_B = 1$$

$$J_C = B', \quad K_C = 1$$

Counter with unsigned  
states

 

(a) Logic diagram

 


(b) State diagram

# Four-bit Binary Ripple Counter

**Table 6.4**  
*Binary Count Sequence*

$A_3$	$A_2$	$A_1$	$A_0$
0	0	0	0
0	0	0	1
0	0	1	0
0	0	1	1
0	1	0	0
0	1	0	1
0	1	1	0
0	1	1	1
1	0	0	0


Four-bit binary ripple counter

 

(a) With T flip-flops


(b) With D flip-flops

# BCD ripple counter

 

State diagram of a decimal BCD counter

 The diagram illustrates a 4-bit ripple-carry counter using four J-K flip-flops. The inputs are *Count* and *Logic 1*. The outputs are  $Q_1$ ,  $Q_2$ ,  $Q_4$ , and  $Q_8$ . The circuit shows the propagation of the count signal through the flip-flops, with the output of one flip-flop serving as the clock for the next.



0 0 0



0 0 0

1 0 0

**9 → 10**

# Three-decade BCD counter

trigger when  $Q_8$  changes from 1 to 0

0 0 0 0

...

0	1	0	0	1
1	0	0	0	0

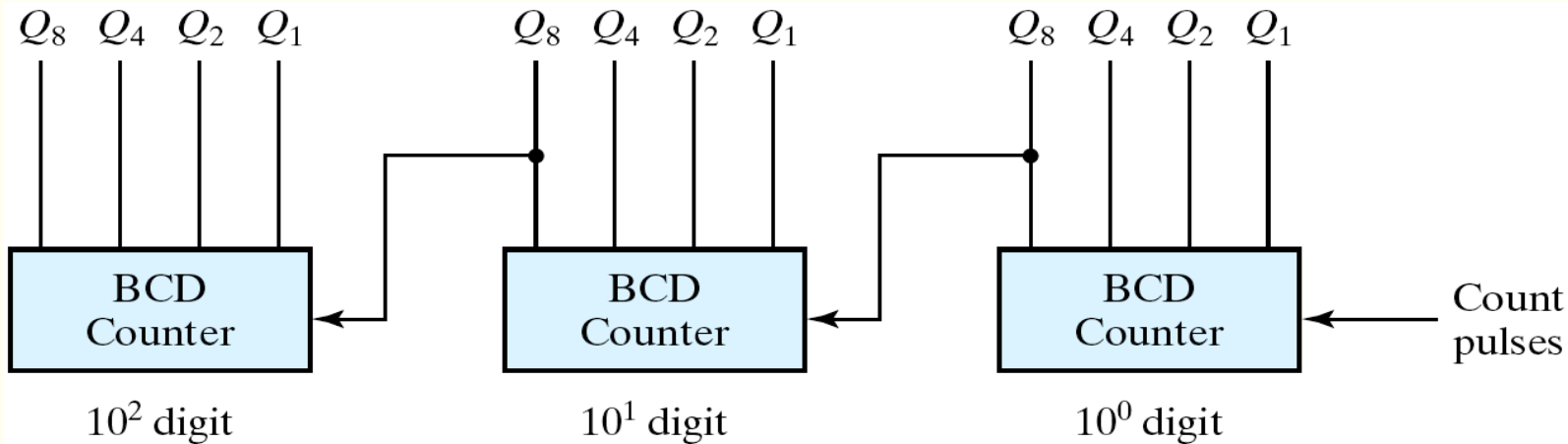



Fig. 6.11

Block diagram of a three-decade decimal BCD counter

# Ring counter (1/2)

- a circular shift register w/ only one flip-flop being set at any particular time, all others are cleared  
(initial value = 1 0 0 ... 0 )
- The single bit is shifted from one flip-flop to the next to produce the sequence of timing signals.



$A_2$	$A_2$	$A_1$	$A_0$
1	0	0	0
0	1	0	0
0	0	1	0
0	0	0	1
1	0	0	0

 

(a) Ring-counter (initial value = 1000)



# Ring counter (2/2)

  

# Johnson Counter

## Ring counter vs. Switch-tail ring counter


### ▫ Ring counter

- a  $k$ -bit ring counter circulates a single bit among the flip-flops to provide  $k$  distinguishable states.

### ▫ Switch-tail ring counter (Johnson Counter)

- is a circular shift register w/ the complement output of the last flip-flop connected to the input of the first flip-flop
- a  $k$ -bit switch-tail ring counter will go through a sequence of  $2k$  distinguishable states. (initial value = 0 0 ... 0)

# Johnson Counter

 

(a) Four-stage switch-tail ring counter

Sequence number	Flip-flop outputs				AND gate required for output
	A	B	C	E	
1	0	0	0	0	$A'E'$
2	1	0	0	0	$AB'$
3	1	1	0	0	$BC'$
4	1	1	1	0	$CE'$
5	1	1	1	1	$AE$
6	0	1	1	1	$A'B$
7	0	0	1	1	$B'C$
8	0	0	0	1	$C'E$

(b) Count sequence and required decoding

Fig. 6.18  
Construction of  
a Johnson  
counter