

# Chapter 4

## The Processor

Da-Wei Chang, OSES Lab.  
CSIE Dept., NCKU

# Introduction

---

- CPU performance factors

$$\text{CPU Time} = \text{Instruction Count} \times \text{CPI} \times \text{Clock Cycle Time}$$

- Instruction count

- Determined by ISA and compiler

- CPI and Cycle time

- Determined by CPU hardware

- We will examine two MIPS implementations

- A simplified version (single-cycle implementation)
  - A more realistic pipelined version

- Implement simple subset

- Memory reference: lw, sw
  - Arithmetic/logical: add, sub, and, or, slt
  - Control transfer: beq, j


- \*illustrates key principles in creating a datapath and designing the control

# Review: MIPS Instruction Set Architecture (ISA)

- Instruction Categories

- Arithmetic
- Load/Store
- Jump and Branch
- Floating Point
  - coprocessor
- Memory Management
- Special

Registers

 

**3 Instruction Formats: all 32 bits wide**


OP	rs	rt	rd	sa	funct	R format
OP	rs	rt	immediate			I format
OP	jump target					J format

## Review: MIPS Register Convention

Name	Register Number	Usage	Preserve on call?
\$zero	0	constant 0 ( <b>hardware</b> )	n.a.
\$at	1	<b>reserved</b> for assembler	n.a.
\$v0 - \$v1	2-3	returned values	no
\$a0 - \$a3	4-7	arguments	<b>yes</b>
\$t0 - \$t7	8-15	temporaries	no
\$s0 - \$s7	16-23	saved values	<b>yes</b>
\$t8 - \$t9	24-25	temporaries	no
\$gp	28	global pointer	<b>yes</b>
\$sp	29	stack pointer	<b>yes</b>
\$fp	30	frame pointer	<b>yes</b>
\$ra	31	return addr ( <b>hardware</b> )	<b>yes</b>
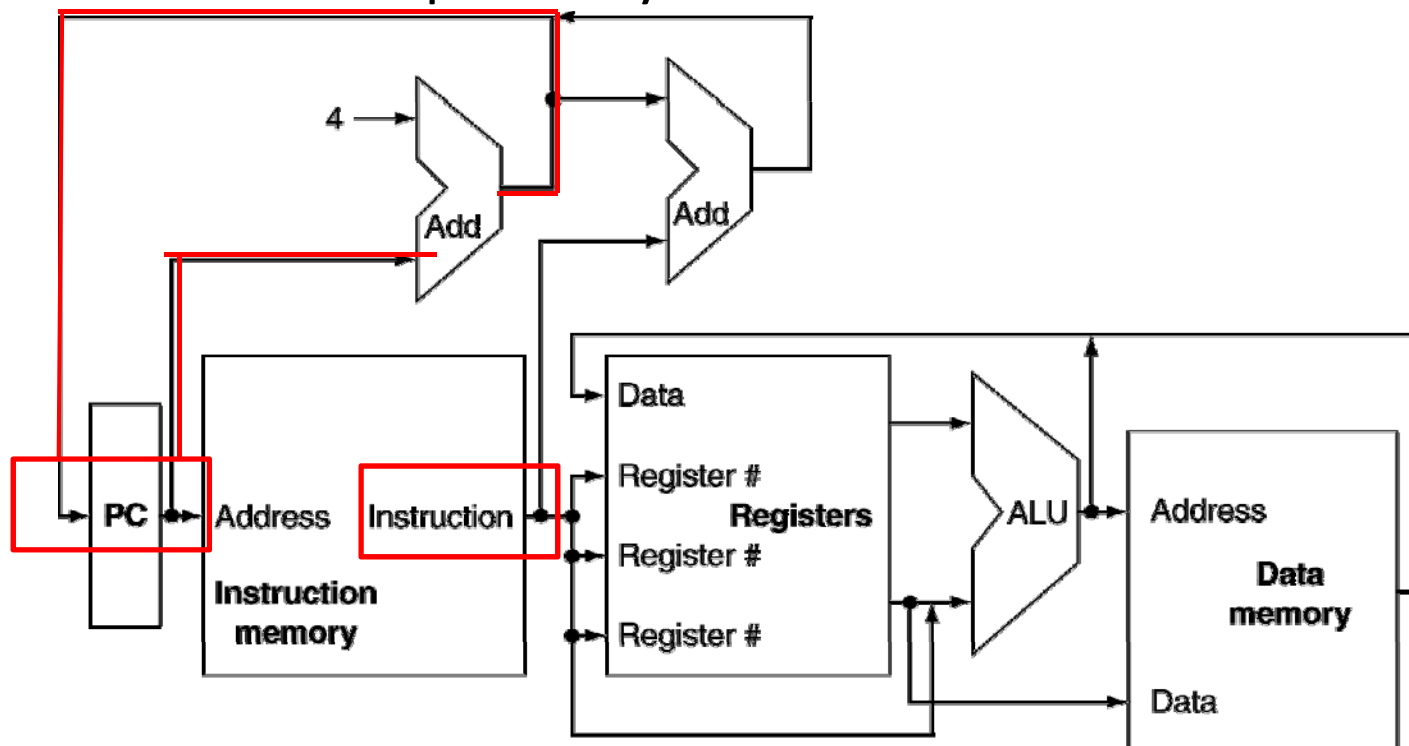
# Instruction Execution


- PC (Program counter) is used to fetch instruction in the **instruction** memory)
- After **instruction** is obtained, **register numbers** in instructions is used to read registers in register files.
- $PC \leftarrow PC + 4$  for sequentially execution



- Arithmetic result
  - Memory address for load/store
  - Branch target address
- ```
add $t0, $s1, $s2
lw $s1, 20($s2)
bne $t0, $s5, Exit
```


- I w \$s1, 20(\$s2)

- j Loop

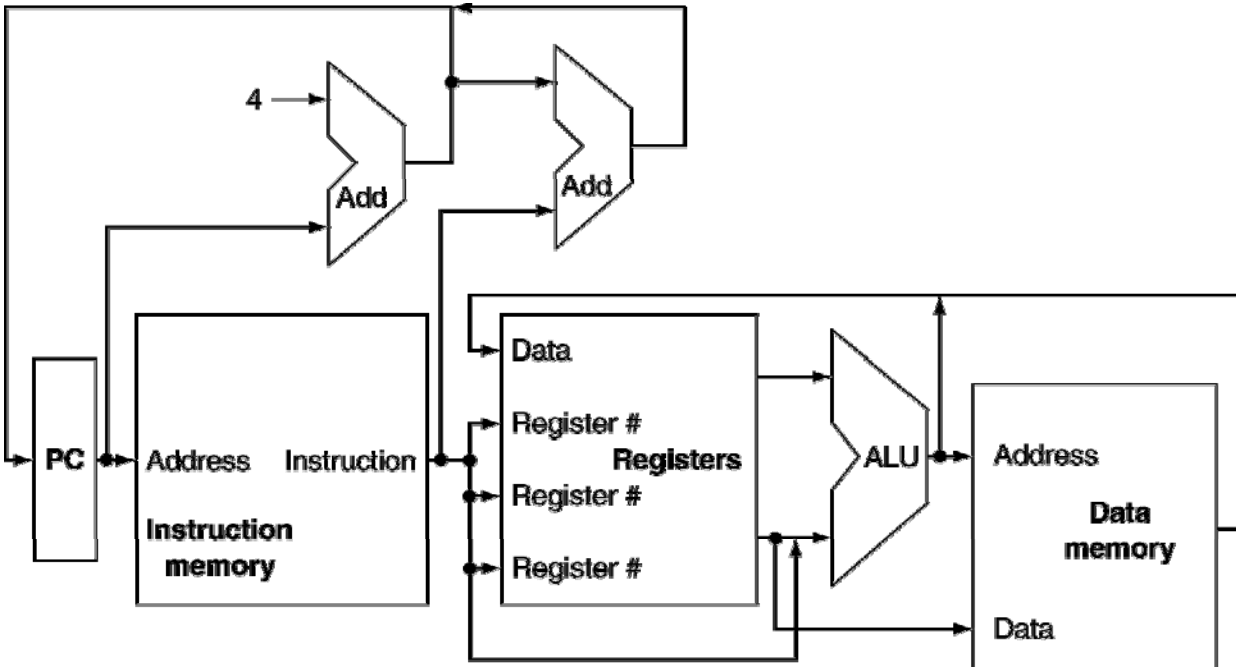

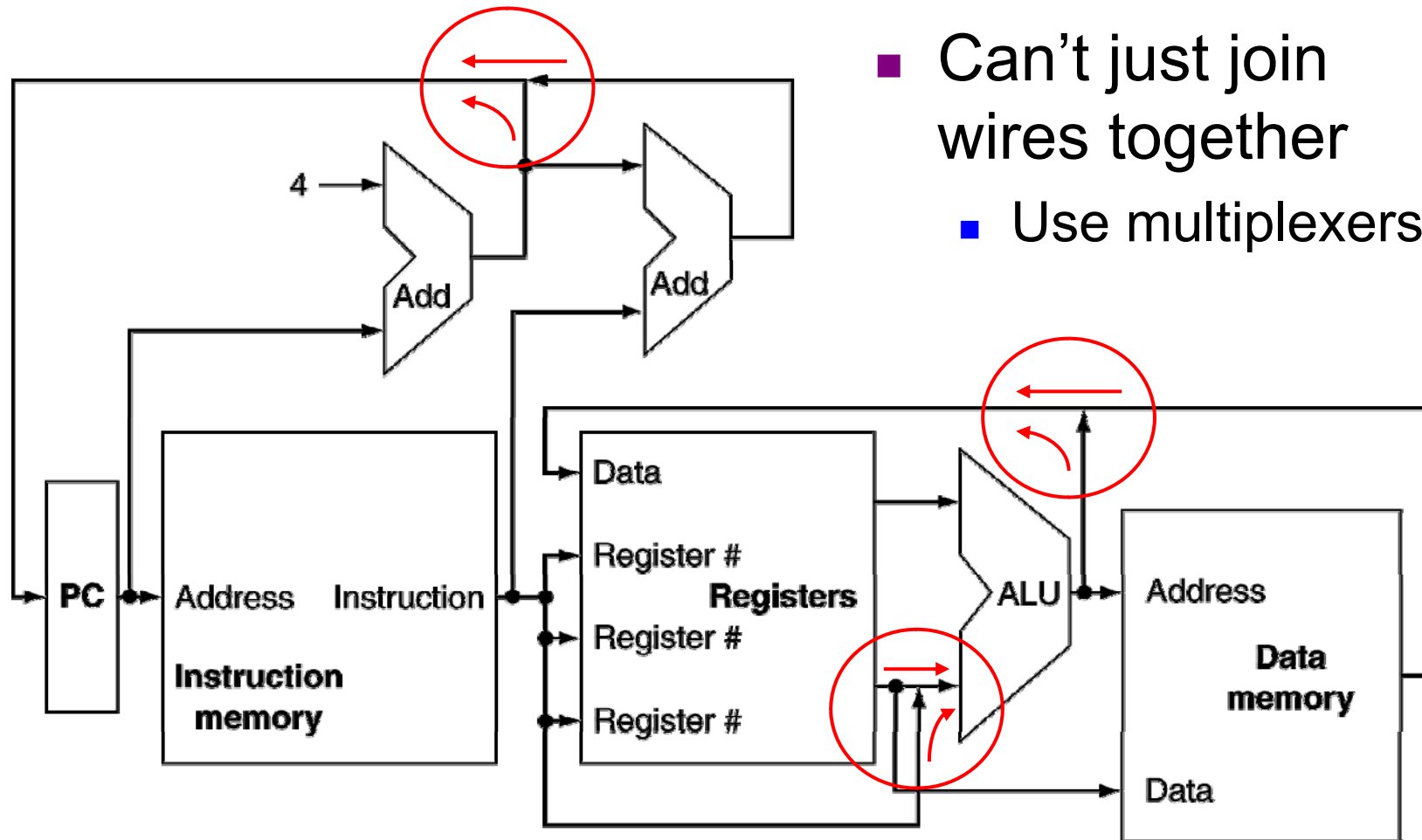
# Multiplexers

- Can't just join wires together
  - Use multiplexers



# CPU Overview

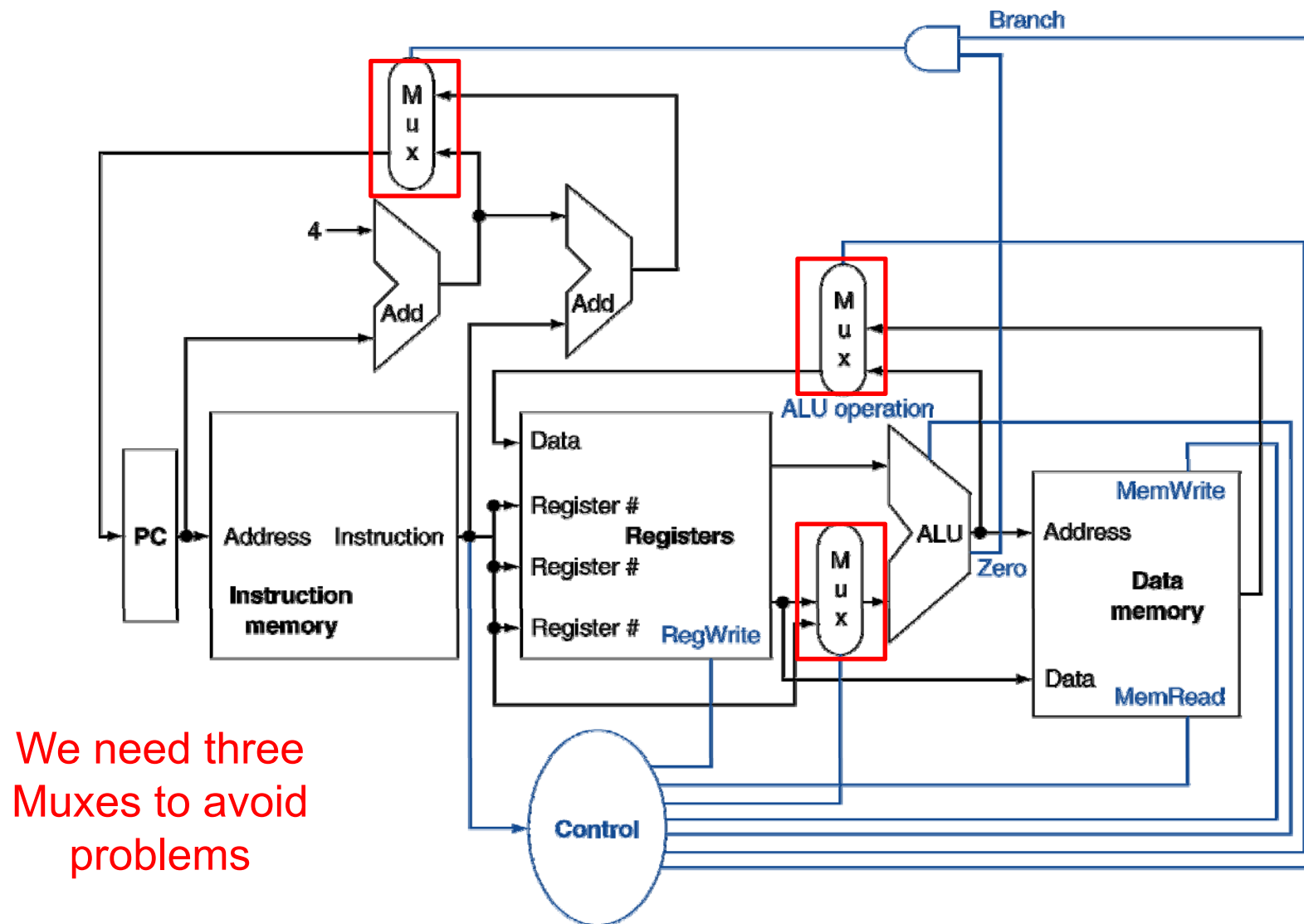

We need three  
Muxes to avoid  
problems

Details of each Mux and Control will be introduced later



# Logic Design Basics


---

- Information encoded in binary

- Low voltage = 0, High voltage = 1

- One wire per bit

 - Multi-bit data encoded on multi-wire buses



32-bit bus

- Combinational element (See next slide)

- Operate on data

- Output is a function of input

- State (sequential) elements

- Output is a function of input and current states


- Store information

# Review: Combinational Elements

---


- AND-gate

- $Y = A \& B$

 


- Multiplexer

- $Y = S ? I1 : I0$

 


- Adder

- $Y = A + B$

 


- Arithmetic/Logic Unit

- $Y = F(A, B)$

 

 
# Review: State/Sequential Elements

- Register: stores data in a circuit
  - Uses a **clock** signal to determine when to update the stored value
  - **Edge-triggered**: update when **Clk** changes (0-> 1 or 1-> 0)
  - The following figure is **positive edge-triggered**: update when Clk changes from **0 to 1**



 
## Review: State Elements (with write enable)

- Register with write control
  - Only updates on clock edge when **write control** input is 1
  - Used when stored value is required later



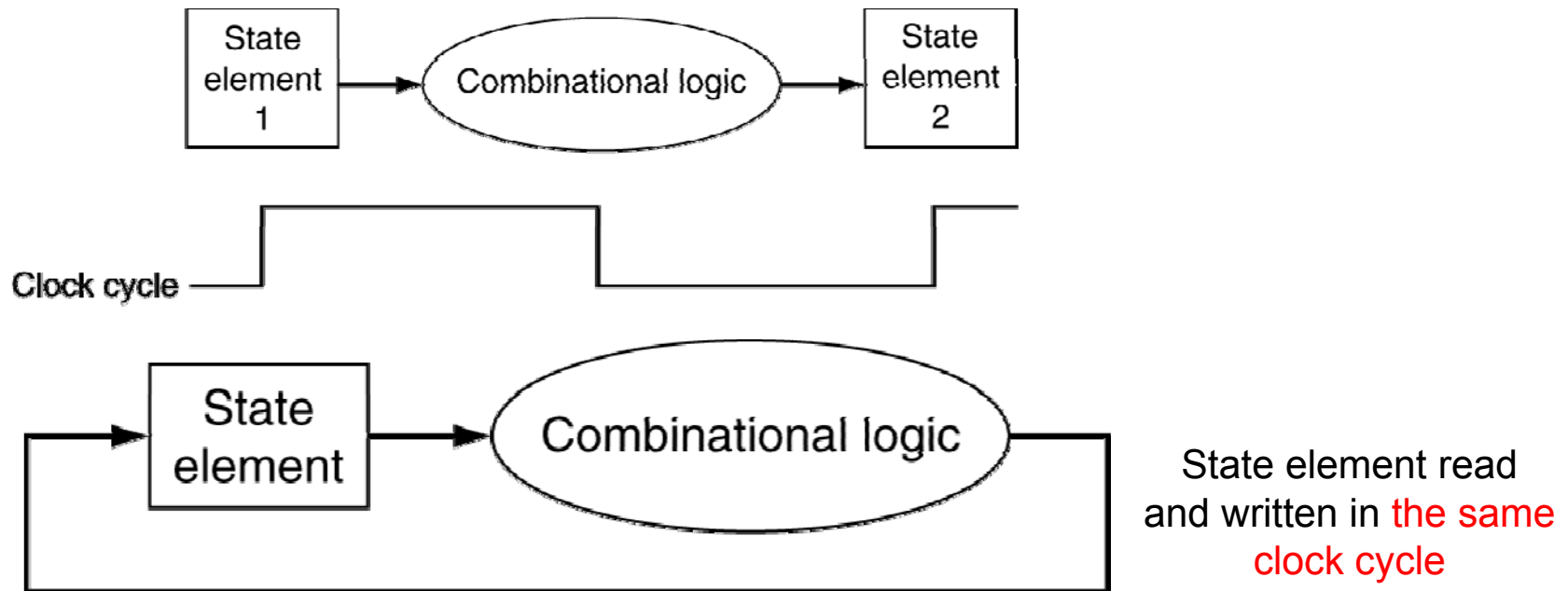
# Clocking Methodology

- **Combinational** logic transforms **data** from **state elements** to **state elements** during clock cycles
  - Between clock edges
  - Longest delay determines clock period



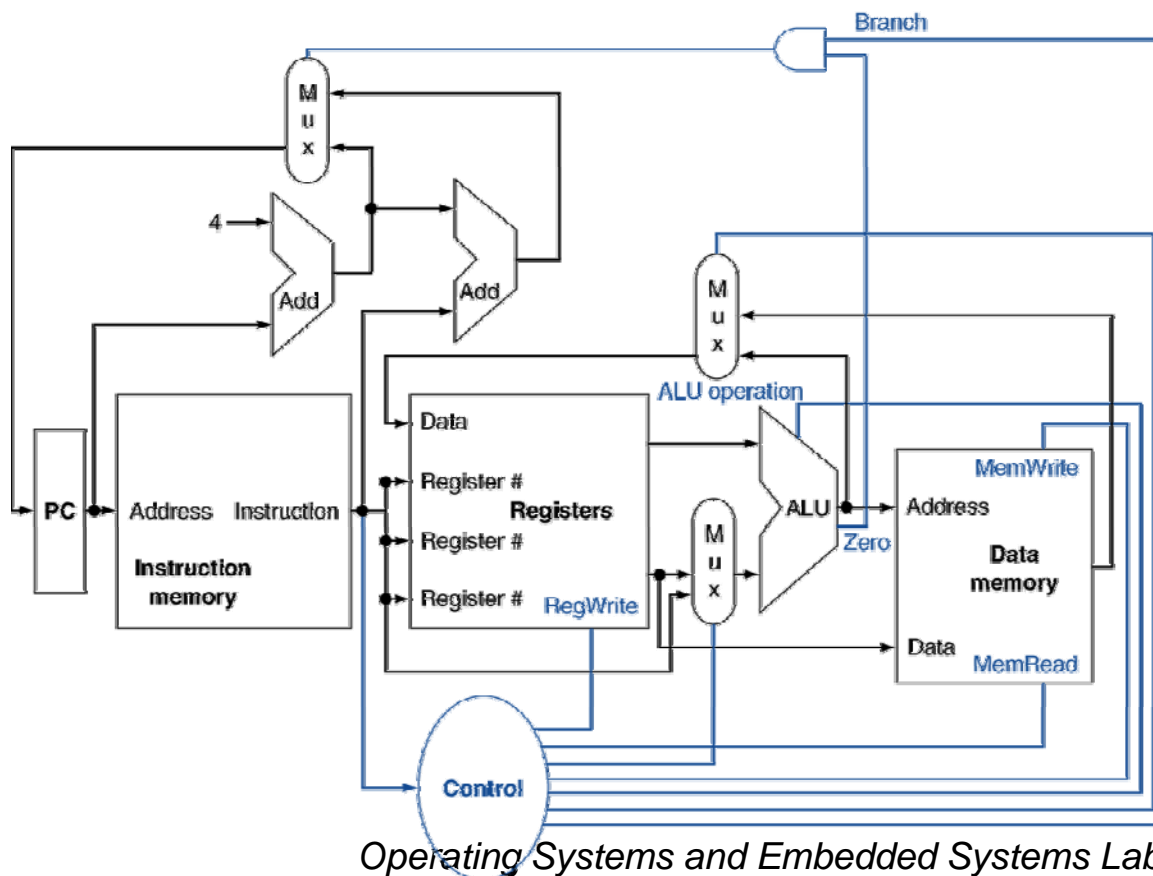
# Building a Datapath

- Datapath : elements that process **data and addresses** in the CPU
  - Registers, ALUs, mux's, memories, ...



*We will show how to build the MIPS datapath*


# Instruction Fetch

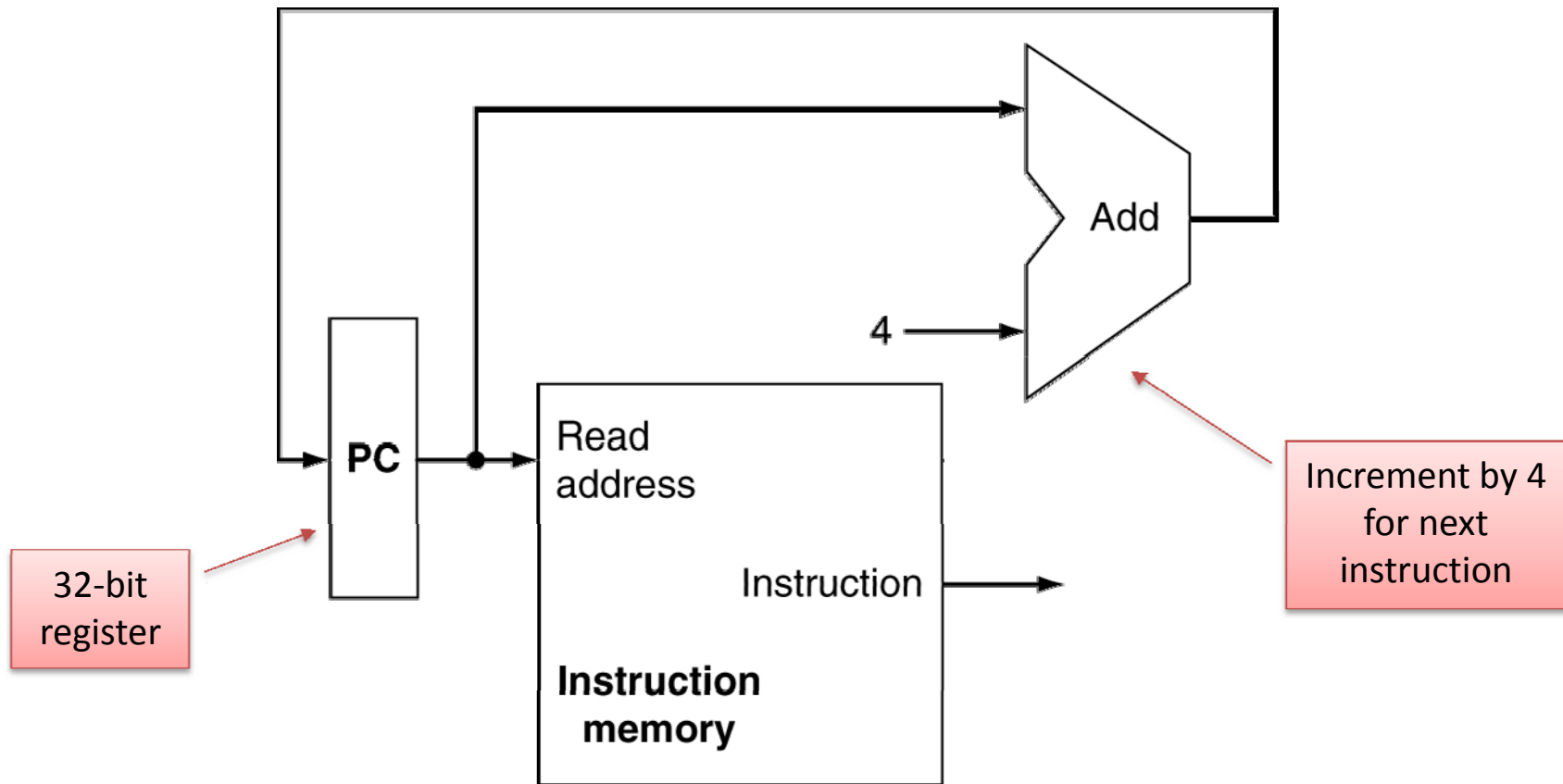

# R-Format Instructions


- **Read** two register operands
- **Perform** arithmetic/logical operation
- Write results into **destination registers**

`add $t0, $s1, $s2`

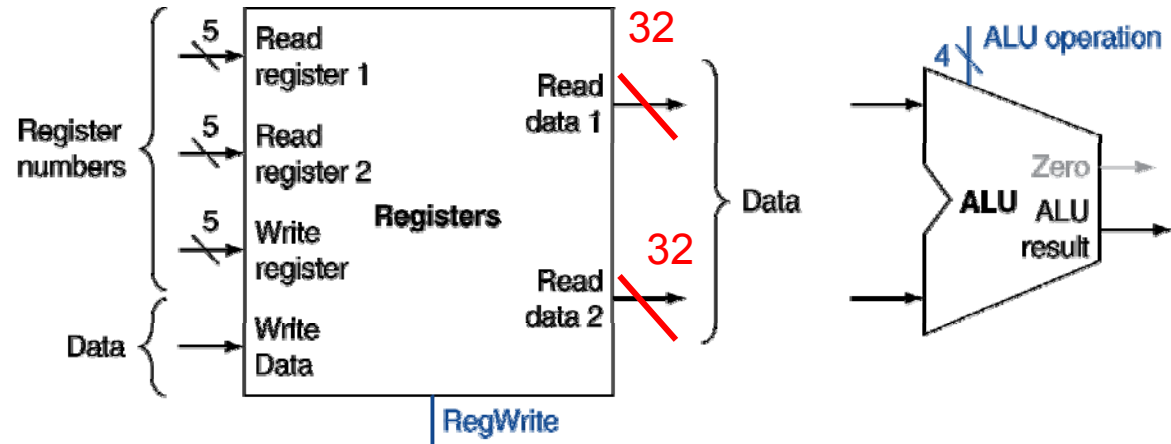

a. Registers

b. ALU

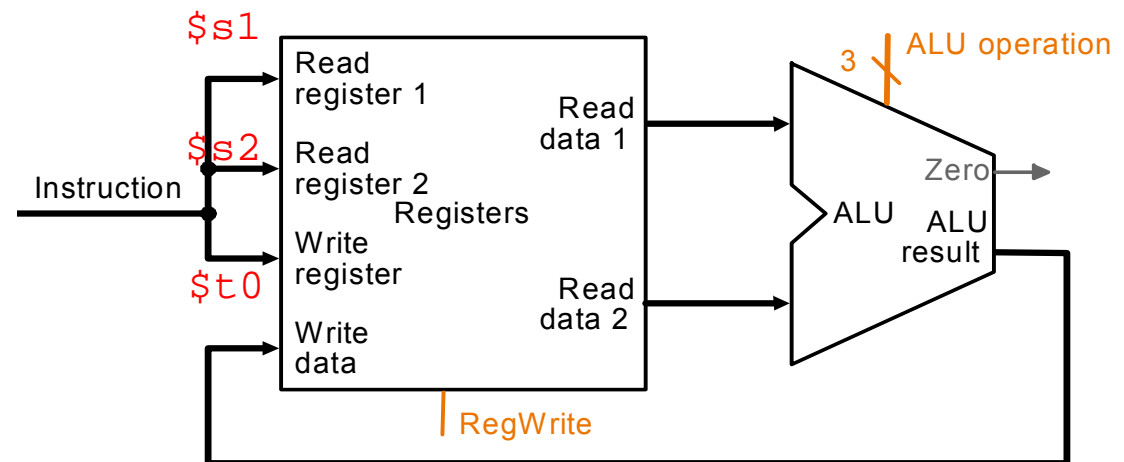



## Review: Load/Store Instructions (I-format)

- MIPS has two basic **data transfer** instructions for accessing memory

lw      \$t0, 4(\$s3) #load word from memory


sw      \$t0, 8(\$s3) #store word to memory

- The data is loaded into (**lw**) or stored from (**sw**) a register in the register file – a 5-bit address
- The memory address – a 32-bit address – is formed by adding the contents of the **base address register** to the **offset** value
  - A 16-bit field meaning access is limited to memory locations within a region of  $\pm 2^{13}$  or 8,192 **words** ( $\pm 2^{15}$  or 32,768 **bytes**) of the address in the base register
  - Note that the offset can be positive or negative

|     |    |      |      |               |
|-----|----|------|------|---------------|
| Ex. | op | rs   | rt   | 16 bit offset |
|     | lw | \$s3 | \$t0 | 4             |

 
## Review - Load Instruction (I format)

- Load/Store Instruction Format (I format):



$$24_{10} + \$s2 =$$



 
$$\begin{array}{r}
 \dots 0001\ 1000 \\
 + \dots 1001\ 0100 \\
 \hline
 \dots 1010\ 1100 = \\
 0x120040ac
 \end{array}$$


  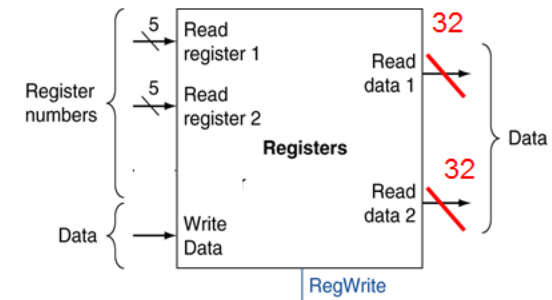
# Load/Store Instructions (need 4 components)


- Read register operands => register files
- Calculate address using 16-bit offset
  - Use **ALU**, but **sign-extend offset**
- Load/store: **read** memory and update register, and **write** register value to memory
  - Need data memory

**lw** \$t0, 4(\$s3) #load word from memory  
**sw** \$t0, 8(\$s3) #store word to memory



# Datapath: Load/Store Instruction

- Load/store

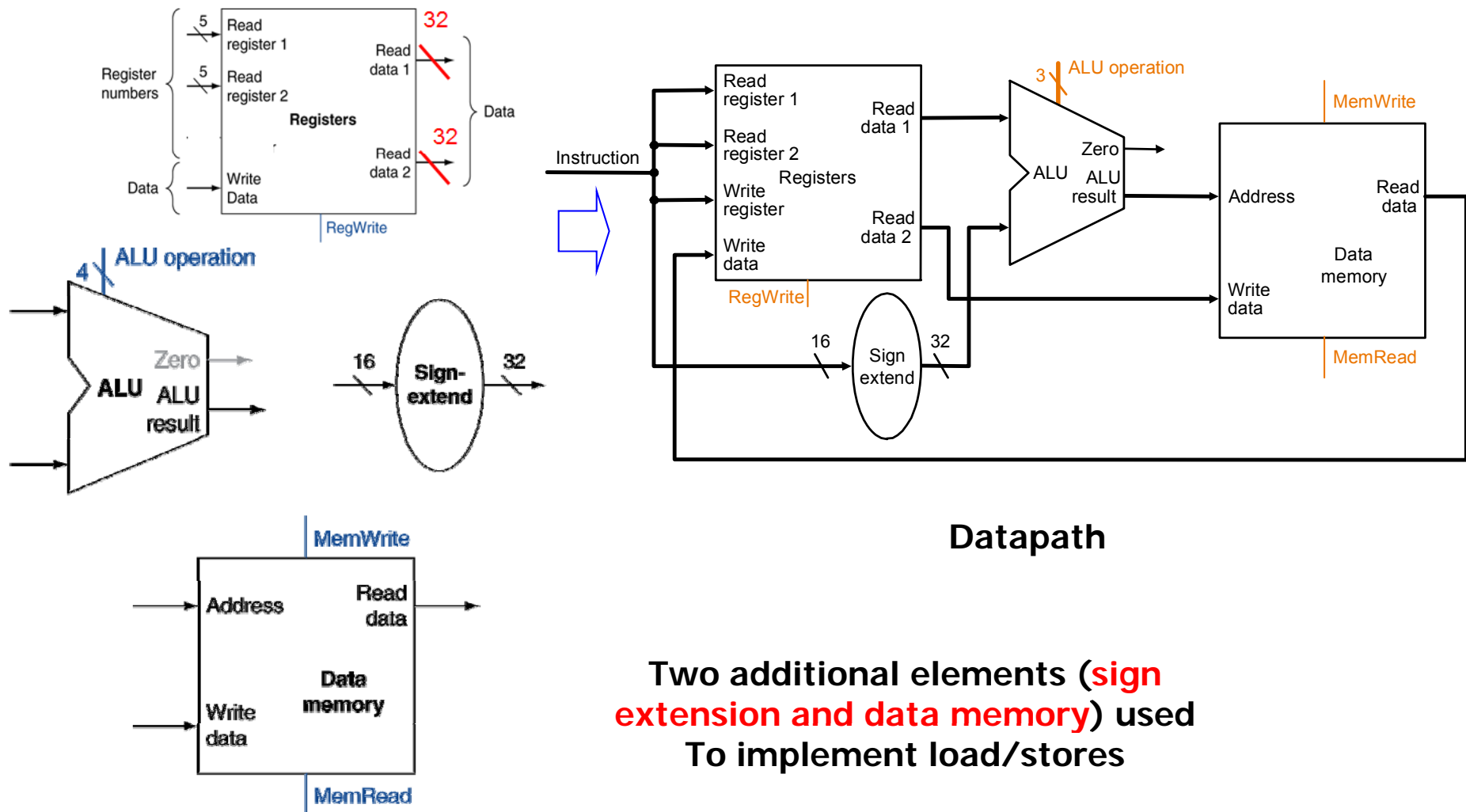

Datapath

Two additional elements (**sign extension** and **data memory**) used  
To implement load/stores


# Animating the Datapath- load

- Load

e.g. `lw $t0, 4($s3)`

- RN1: register number 1
- RN2: register number 2
- WN: register number that will be written
- WD: write data


`lw rt, offset(rs)`

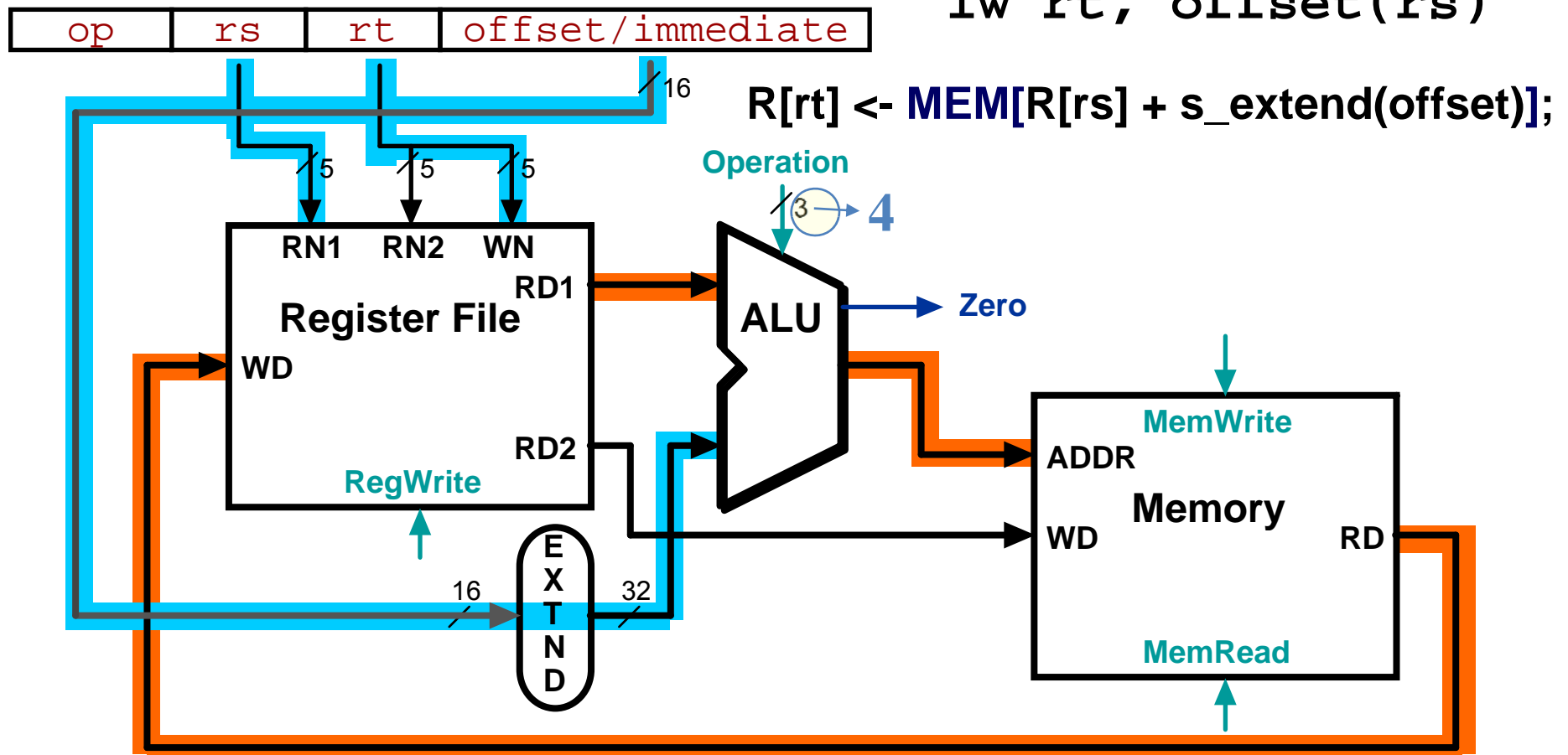

# Animating the Datapath- store

- store

sw \$t0, 8(\$s3)

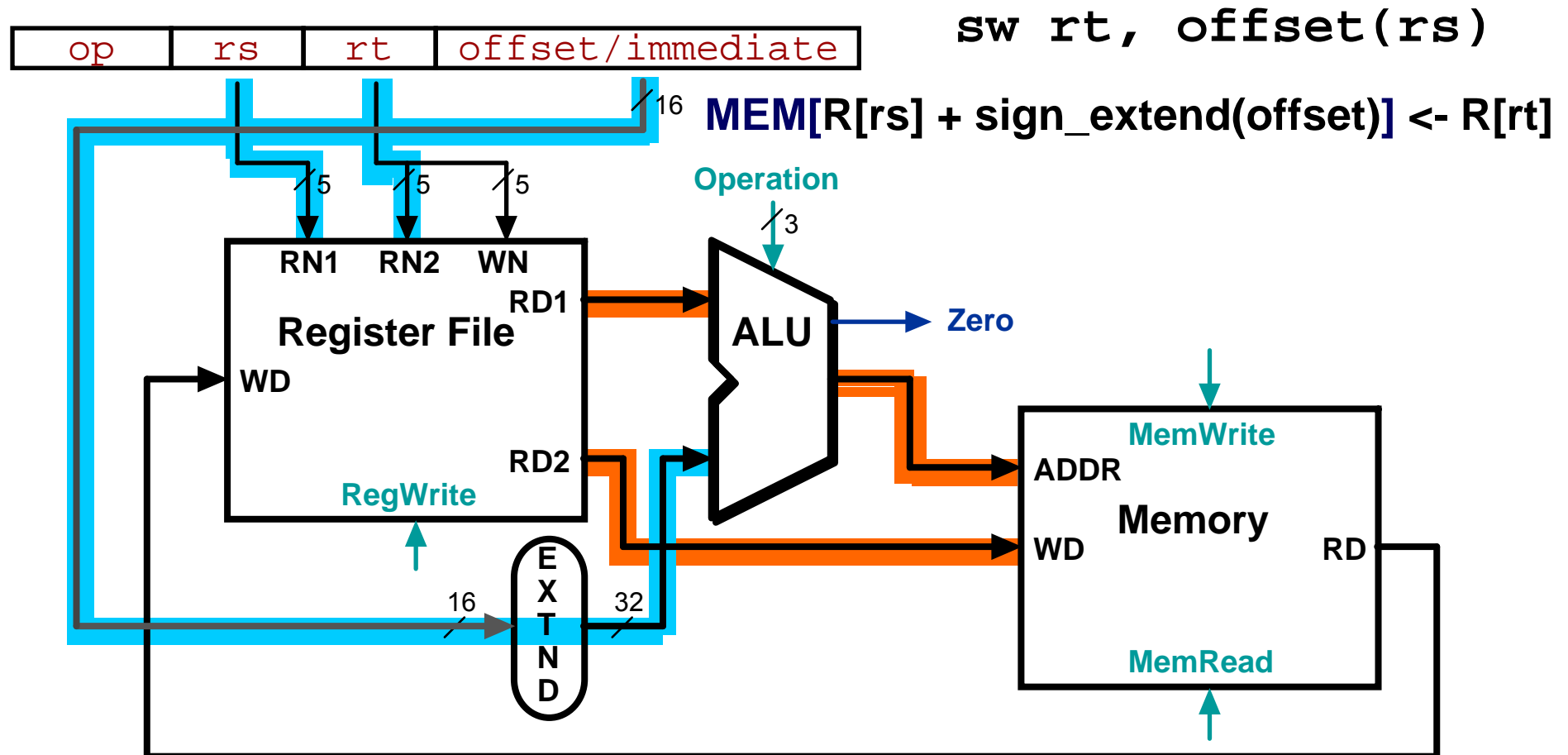

# Specifying Branch Destinations


- MIPS conditional branch instructions:

| op     | rs     | rt     | offset  |
|--------|--------|--------|---------|
| 6 bits | 5 bits | 5 bits | 16 bits |

- PC-relative addressing

- Target address =  $PC + \text{offset} \times 4$
- PC already incremented by 4 by this time

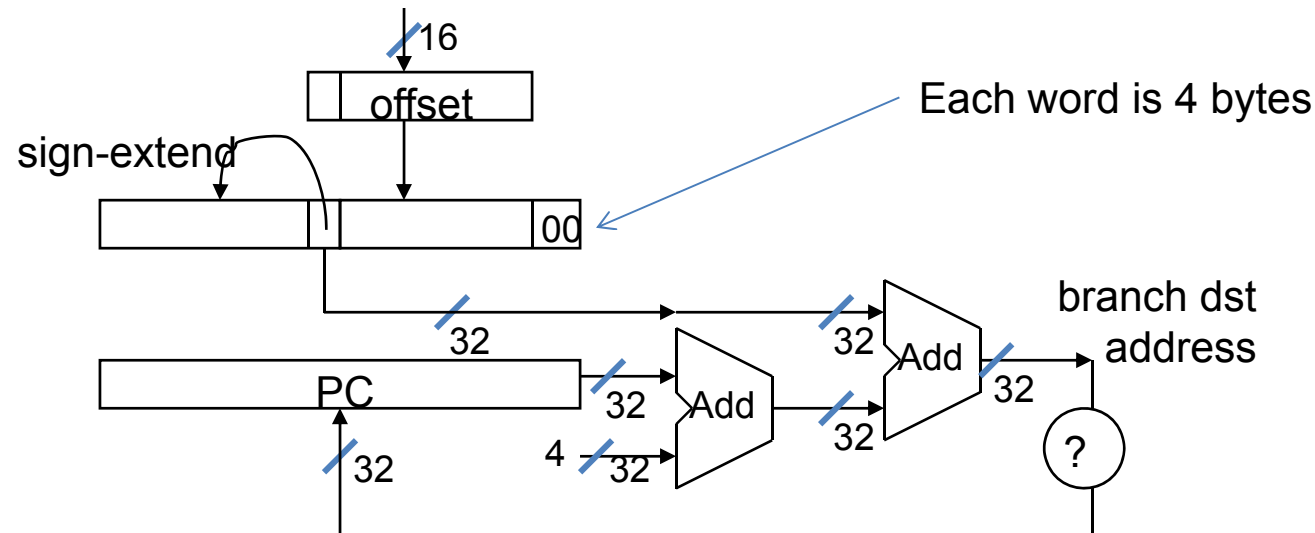from the low order 16 bits of the branch instruction




2000 beq \$s0 \$t1 2  
 2004 ....  
 2008 ...  
 200C

Target Address (address of next instruction) =?  
 200C
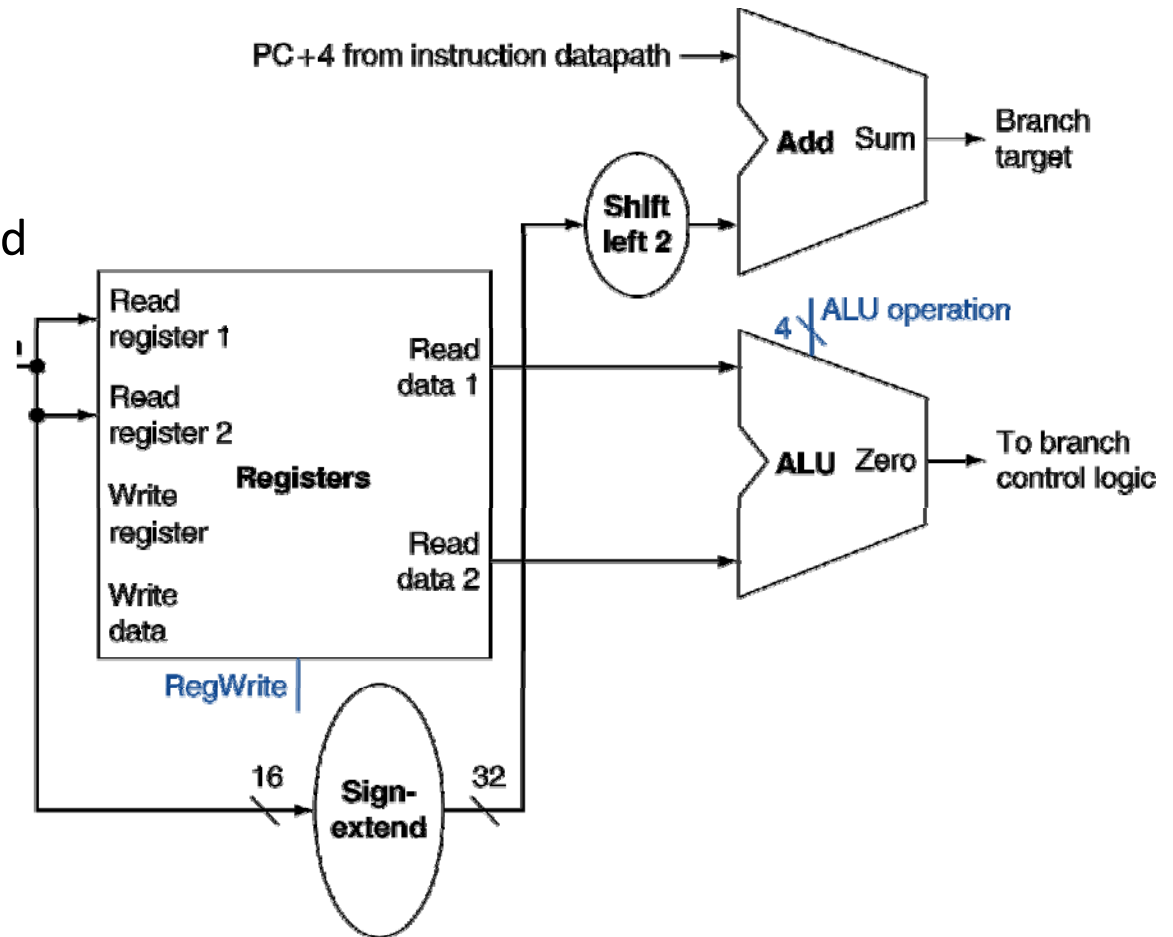
# Branch Instructions

- Read register operands
- Compare operands
  - Use **ALU**, subtract/xor and check Zero output
- Calculate target address
  - **Sign-extend** offset
  - Shift left **2 bits** (word displacement)
  - Add to **PC + 4** (already calculated by instruction fetch)




See animation in the next slide



# Animating the Datapath (beq)


- beq

e.g. beq \$s0 \$t1 2

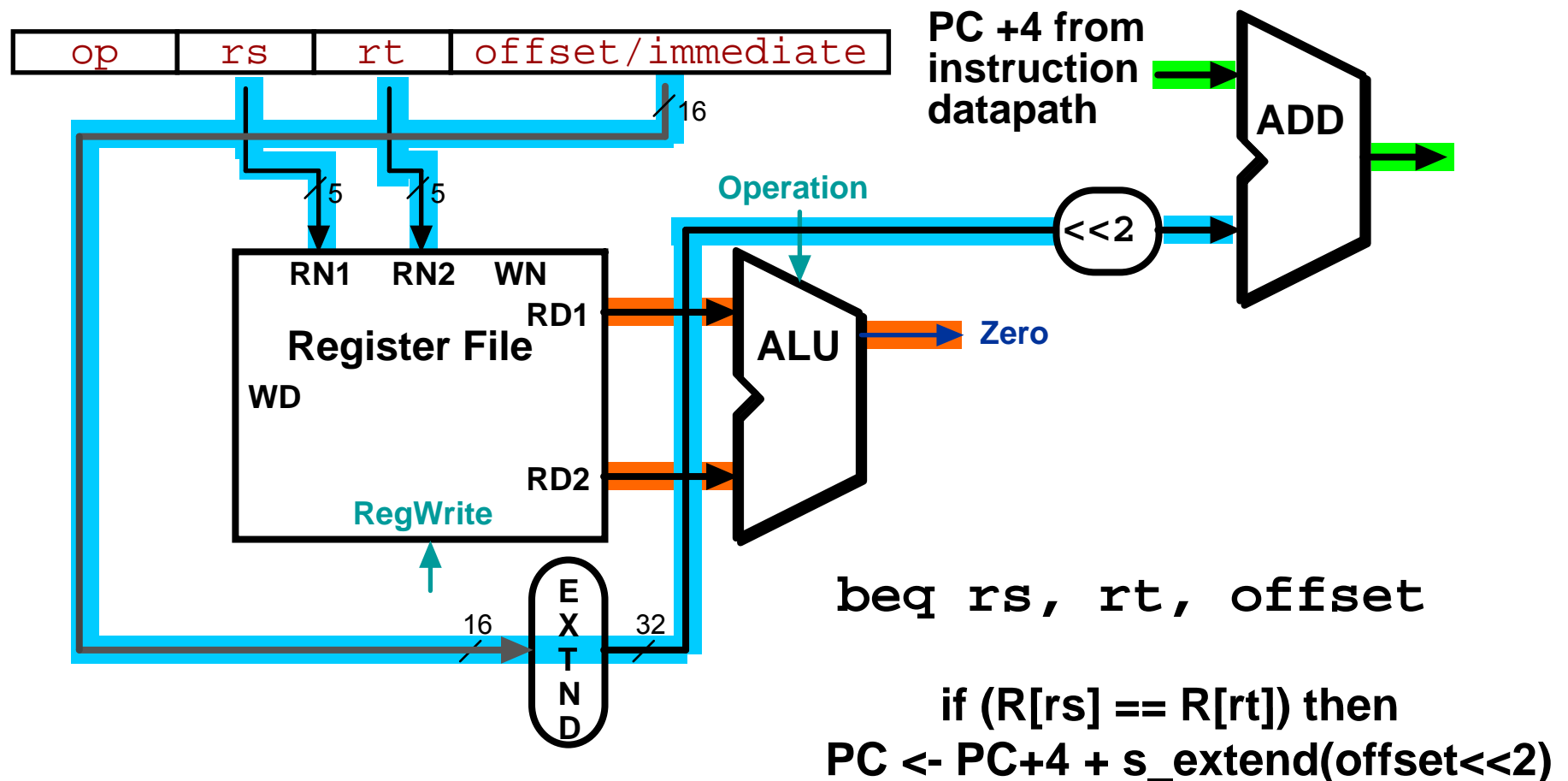
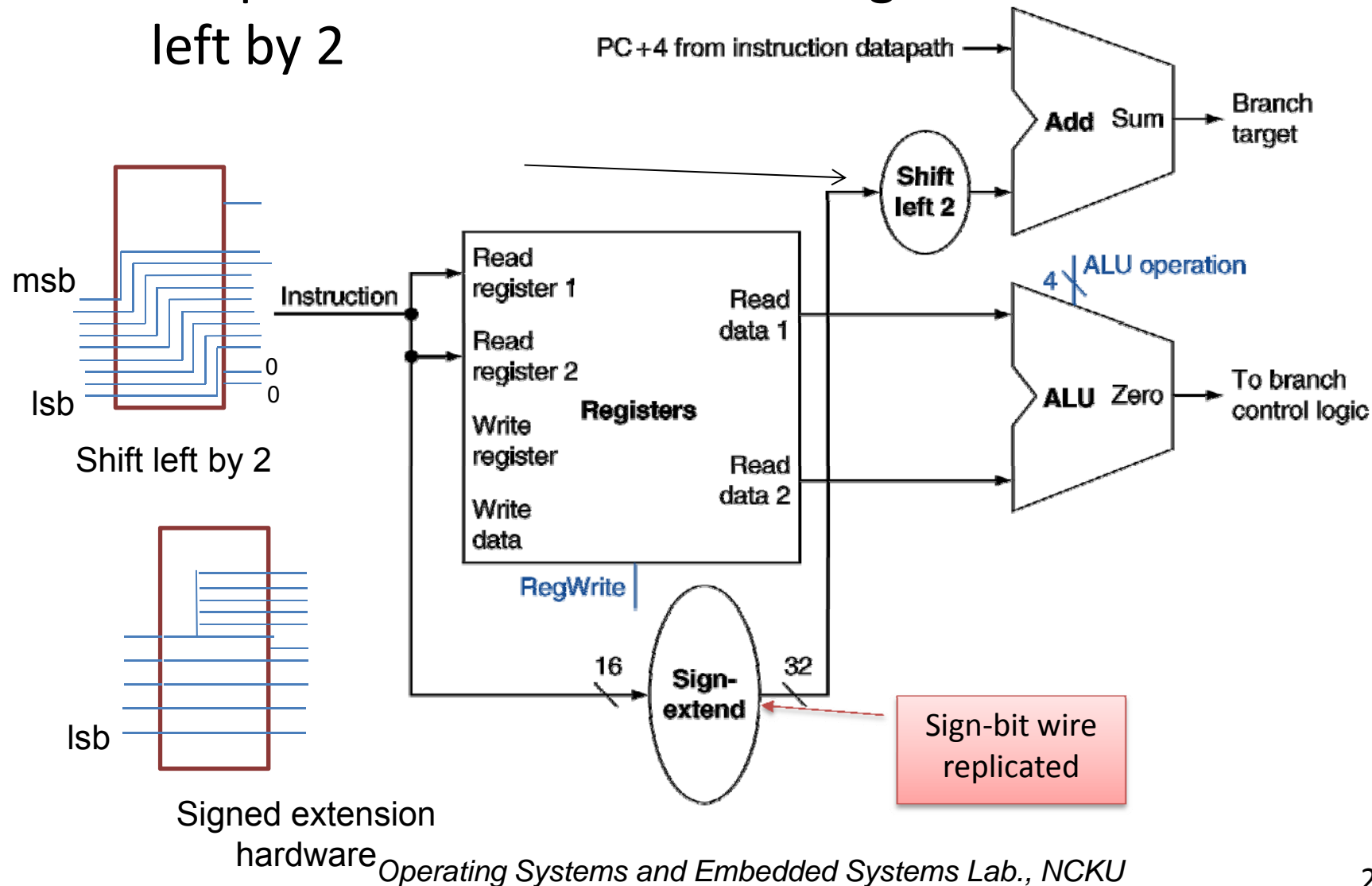
# Sign-extension and shift left by 2 hardware

- Simple hardware is used for sign extension and shift left by 2




## Composing the Elements

---

- Make Data path do an instruction in **one clock cycle**
  - Each datapath **element** can only do **one** function at a time
  - Hence, we need **separate instruction** and **data** memories
- Use **multiplexers** where alternate data sources are used for different instructions


# R-Type/Load/Store Datapath

## A Single Cycle Datapath

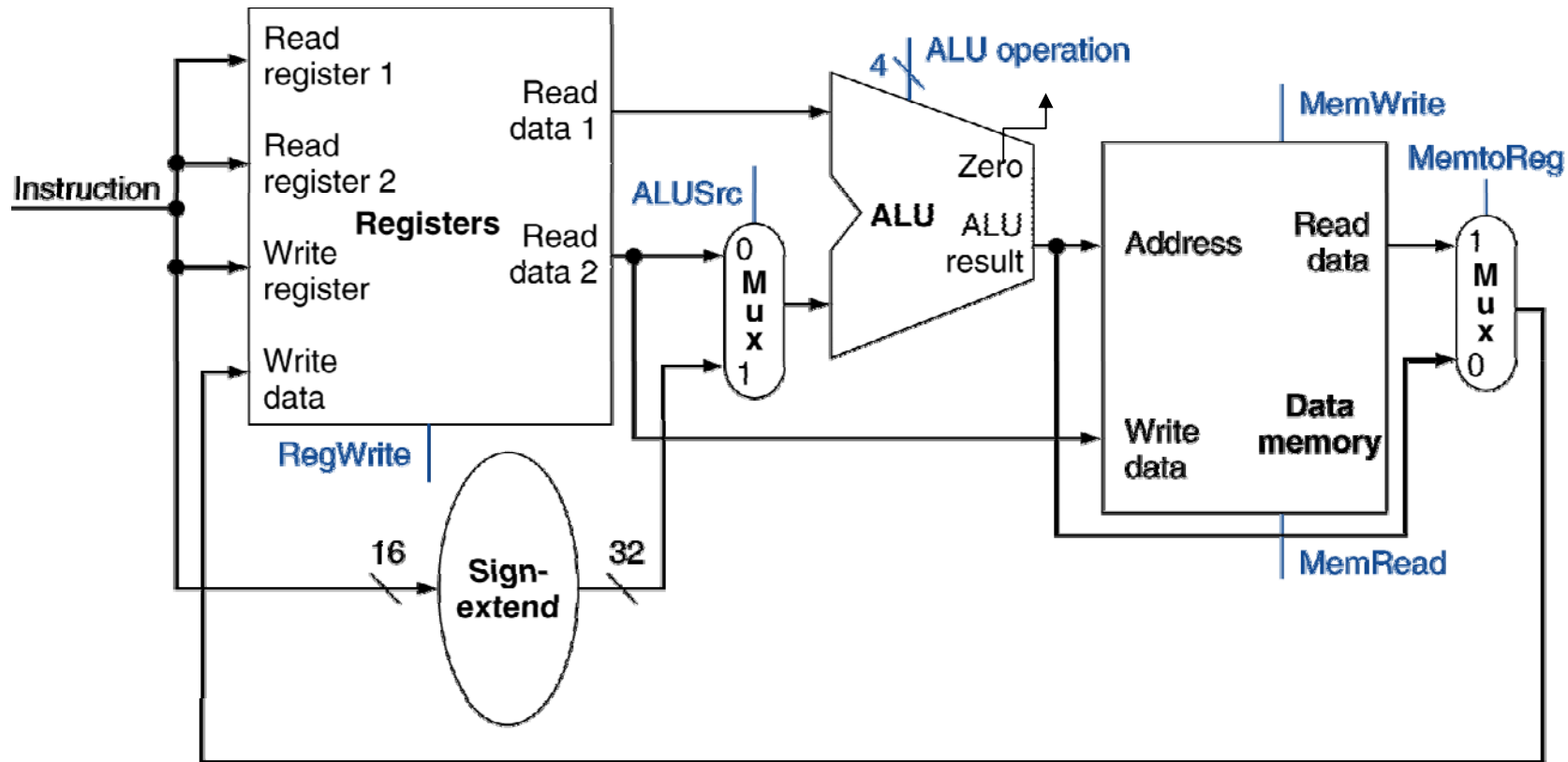


Correct Control signal (**RegWrite**, **ALUSrc**, **ALU operation**, **MemWrite**, **MemtoReg**, **MemRead**) are needed to make sure correct operation is done

# Full Datapath (Single Cycle Datapath)

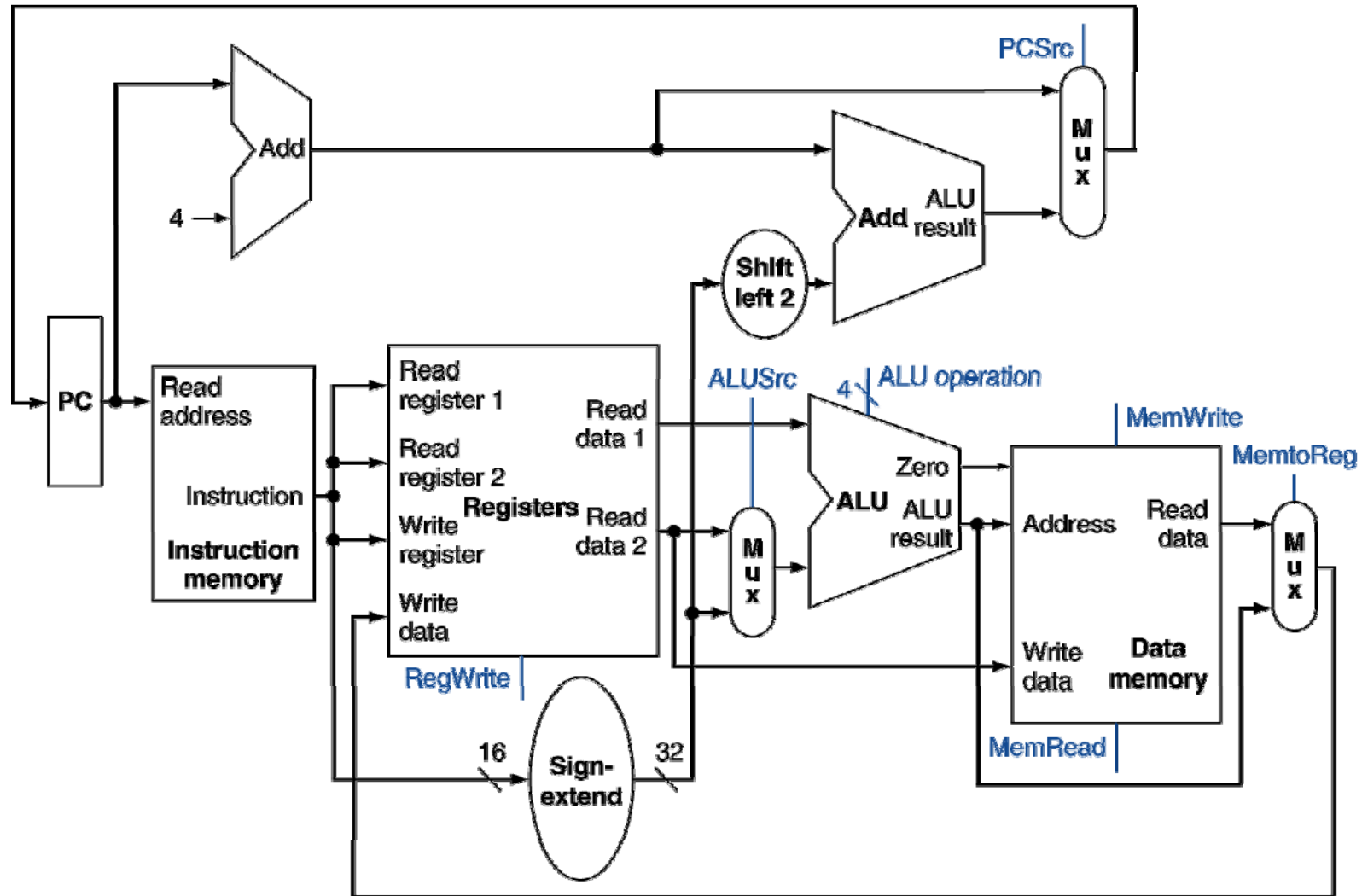


# Basic Arithmetic Logic Unit

- Basic ALU

 

One-bit ALU that performs **AND** and **OR**


| Operation(Op.) | Funct.  |
|----------------|---------|
| 0              | a AND b |
| 1              | a OR b  |

 

| Operation(Op.) | Funct.  |
|----------------|---------|
| 0              | a AND b |
| 1              | a OR b  |
| 2              | a + b   |

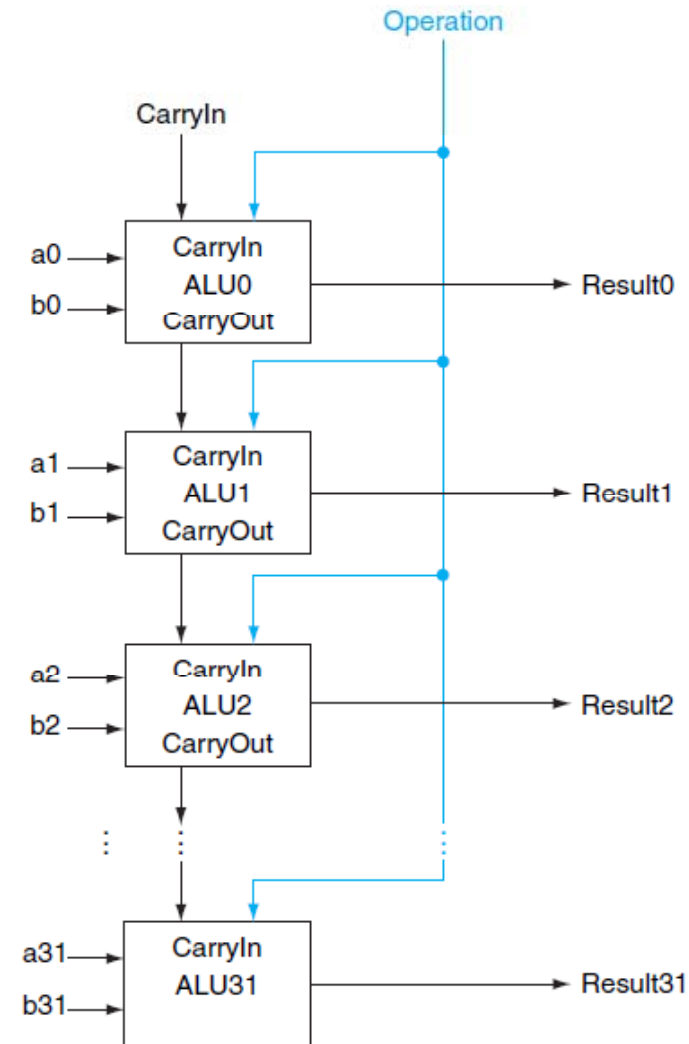
# 32-bit ALU

- Cascading 1-bit ALU to 32-bit ALU
- **carry-out** is the **carry-in** of the next bit


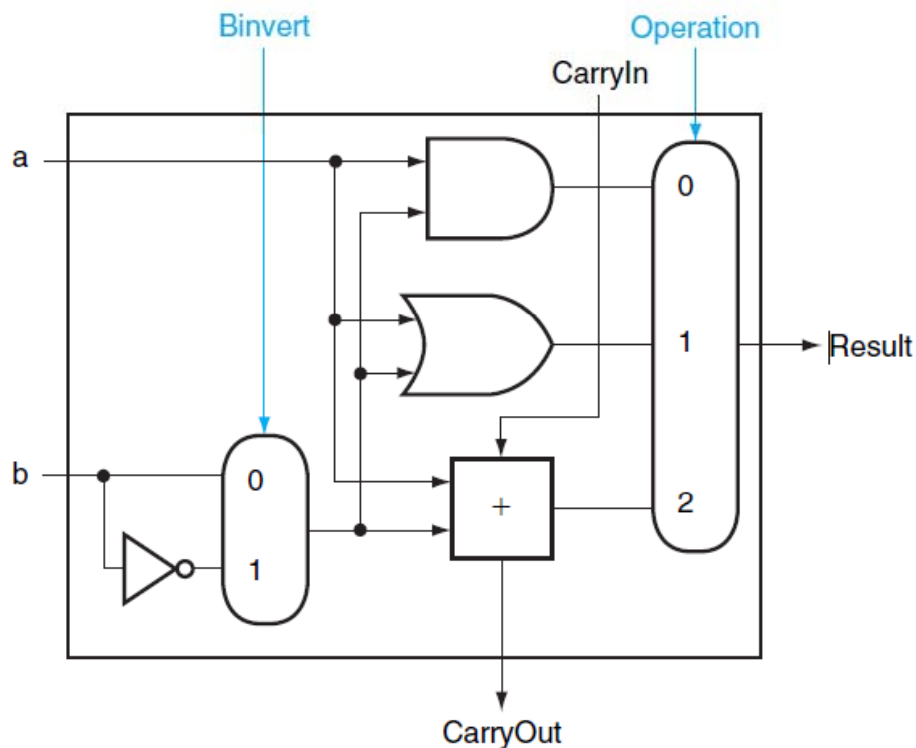
# Enhanced Arithmetic Logic Unit

- ALU that performs (a **AND** b), (a **OR** b) and (a + b ) and (a- b=a +  $\bar{b}$ +1 )
- =>Binvert=**1** and carryIn=**1**




$$a-b = a + \bar{b} + 1$$

| Binvert | CarryIn | Op. | Function |
|---------|---------|-----|----------|
| 0       | X       | 0   | a and b  |
| 0       | X       | 1   | a or b   |
| 0       | 0       | 2   | a + b    |
| 1       | 1       | 2   | a-b      |



# Enhanced Arithmetic Logic Unit

- Enhanced with **NOR** and **NAND**

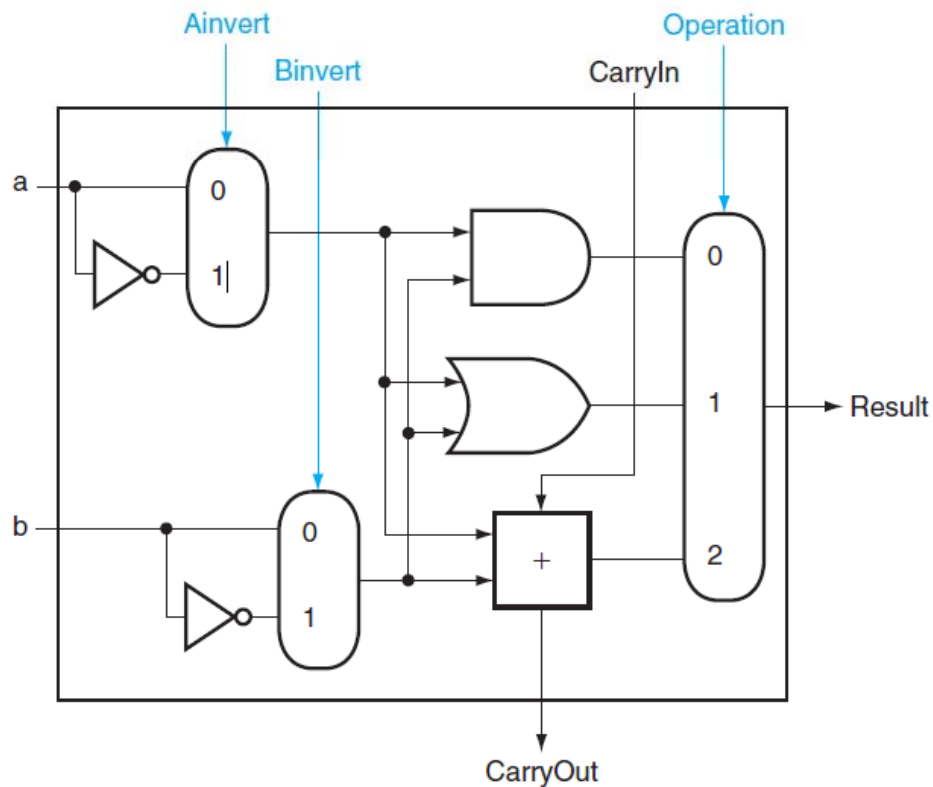

$$\bar{a} \vee \bar{b} = \overline{ab}$$

$$\overline{ab} = \bar{a} \vee \bar{b}$$


| Ainvert | Binvert | CarryIn | Op. | Func.              |
|---------|---------|---------|-----|--------------------|
| 0       | 0       | X       | 0   | a and b            |
| 0       | 0       | X       | 1   | a or b             |
| 0       | 0       | 0       | 2   | a + b              |
| 0       | 1       | 1       | 2   | a-b                |
| 1       | 1       | X       | 0   | $\overline{a + b}$ |
| 1       | 1       | X       | 1   | $\overline{ab}$    |

# ALUs with Set Less Than

Review: Set less than

`slt $t0 $t1 $t2` => When  $\$t1 < \$t2$ ,  $\$t0 = 1$ , otherwise  $\$t0 = 0$

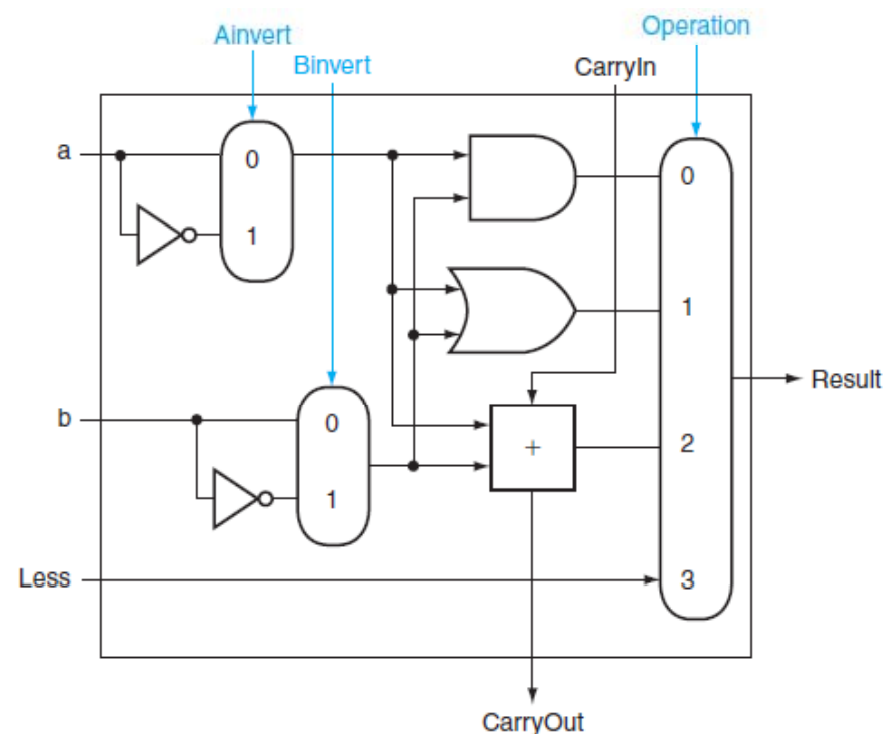- We use  $a-b$  to implement slt
  - When  $a-b < 0$ , signed bit = 1
  - When  $a-b \geq 0$ , signed bit = 0
- Less signal=>
  - Connect LSB to the signed bit of MSB (See next slide)
  - Other signals are assigned to 0




## 32-bit ALU with Set Less than

- Less signal=>
  - Connect LSB to the signed bit of MSB
  - Other signals are assigned to 0


When  $a_{31} \dots a_0 < b_{31} \dots b_0$ ,  
result is  $0 \dots 0$ , otherwise  
 $0 \dots 1$

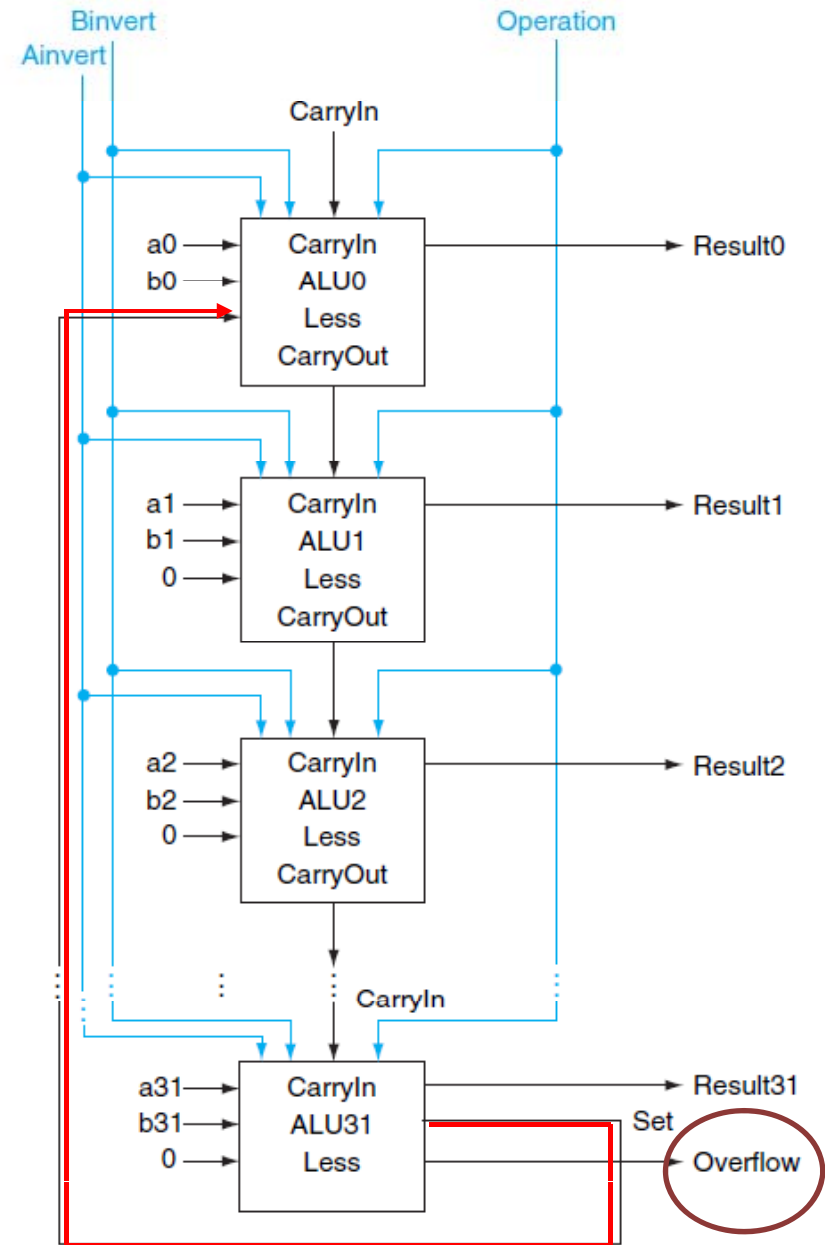Note that **MSB** is different than other bits=> it has one additional signal (Overflow) which will be discussed later



# Integer Addition and Subtraction

- Addition Example:  $7 + 6$

 

- Subtraction Example:  $7 - 6 = 7 + (-6)$

$$\begin{array}{r}
 00000111 \\
 - 00000110 \\
 \hline
 00000001
 \end{array}$$

$$\begin{array}{r}
 +7: 0000\ 0000\ \dots\ 0000\ 0111 \\
 +(-6): 1111\ 1111\ \dots\ 1111\ 1010 \\
 \hline
 +1: 0000\ 0000\ \dots\ 0000\ 0001
 \end{array}$$

## Situations when overflow occurs

- Situation that overflow occurs for signed integers

| Operation | A          | B          | Result when Overflow |
|-----------|------------|------------|----------------------|
| A+B       | $A \geq 0$ | $B \geq 0$ | $< 0$                |
| A+B       | $< 0$      | $< 0$      | $\geq 0$             |
| A-B       | $A \geq 0$ | $B < 0$    | $< 0$                |
| A-B       | $A < 0$    | $B \geq 0$ | $\geq 0$             |


$$\begin{array}{r} 0111 \\ +0001 \\ \hline 1000 \end{array} \quad 7+1 \neq -8$$

$$\begin{array}{r} 1111 \\ +1000 \\ \hline 0111 \end{array} \quad -1+(-8) \neq 7$$
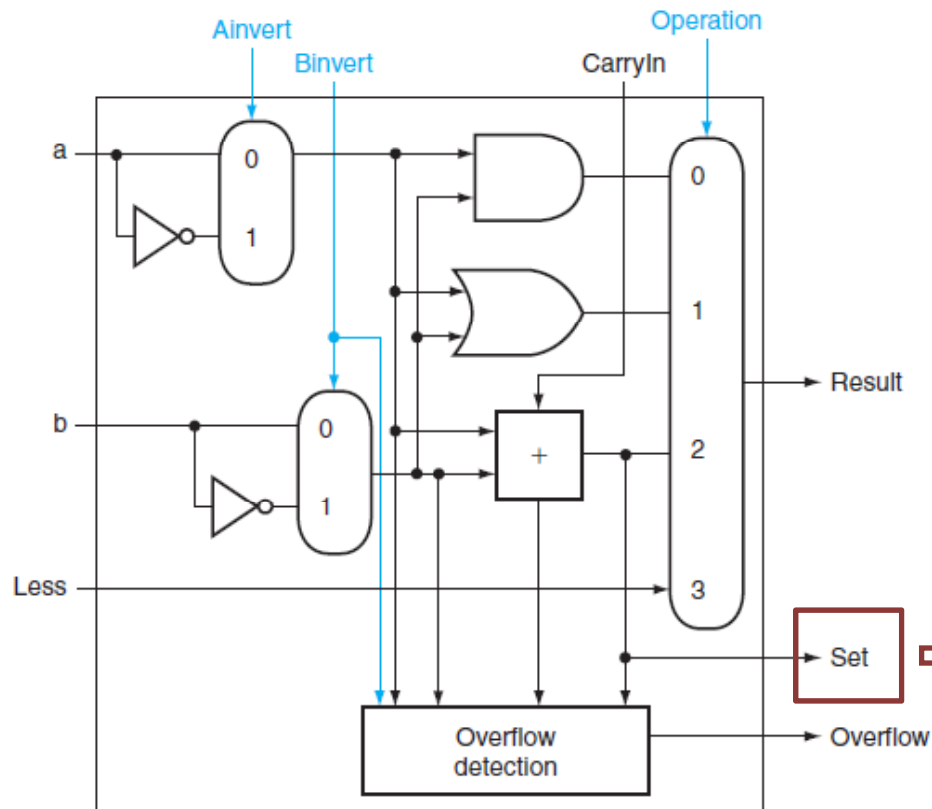
# Detecting Overflow

- Overflow detection circuit requires

- **Binvert** (to know  $a+b$  or  $a-b$  is executed)
- **Sign** bits of  $a, b$ 
  - to know if  $a$  or  $b$  is  $\geq 0$  or  $< 0$
- **MSB** of  $(a+b)$
- **Carryout** bit of  $(a+b)$



for **slt** (used to set the LSB bit when  $a < b$  is true)

$$\begin{array}{r} 1111 \\ + 1000 \\ \hline 10111 \end{array}$$

## Dealing with Overflow

---


- Some languages (e.g., C) **ignore** overflow
- Other languages (e.g., Ada, Fortran) require **raising** an **exception**
- MIPS
  - addu, addui, subu instructions ignore overflow
  - add, addi, sub instructions may cause exceptions on overflow
  - So, C compiler on MIPS generates addu, addui, subu instructions
- MIPS exception handling on overflow
  - Save PC in exception program counter (EPC) register
  - Jump to predefined **handler**
  - **mfc0** (move from coprocessor reg) instruction can retrieve EPC value, to **return after corrective action**

# Final 32-bit ALU

- Binvert is compatible to CarryIn according to the following table => Connect **Binvert** to CarryIn => is renamed to Bnegate
- Add **Zero detection circuit** => If all bit is 0 => Zero=1

| Ainvert | Binvert | CarryIn | Op. | Func.   |
|---------|---------|---------|-----|---------|
| 0       | 0       | X       | 0   | a and b |
| 0       | 0       | X       | 1   | a or b  |
| 0       | 0       | 0       | 2   | a + b   |
| 0       | 1       | 1       | 2   | a - b   |
| 0       | 1       | 1       | 3   | slt     |

| Bnegate | Op[1:0] | Func.   |
|---------|---------|---------|
| 0       | 00      | a and b |
| 0       | 01      | a or b  |
| 0       | 10      | a + b   |
| 1       | 10      | a - b   |
| 1       | 11      | slt     |

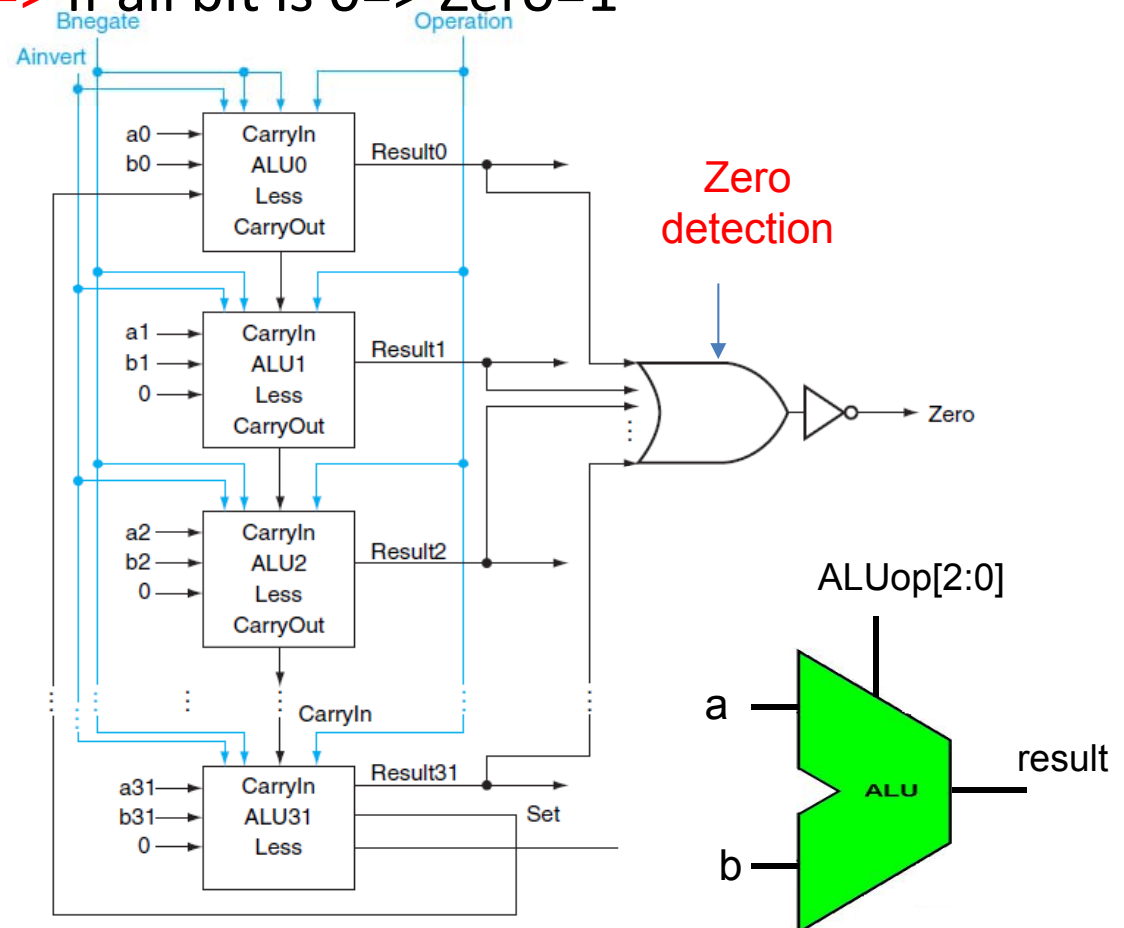




# Outline

---


- Designing a processor
- A single-cycle implementation (the datapath)
- Control for the single-cycle CPU
  - Control of CPU operations
  - ALU control
  - Main control

## Next: Building Datapath With Control

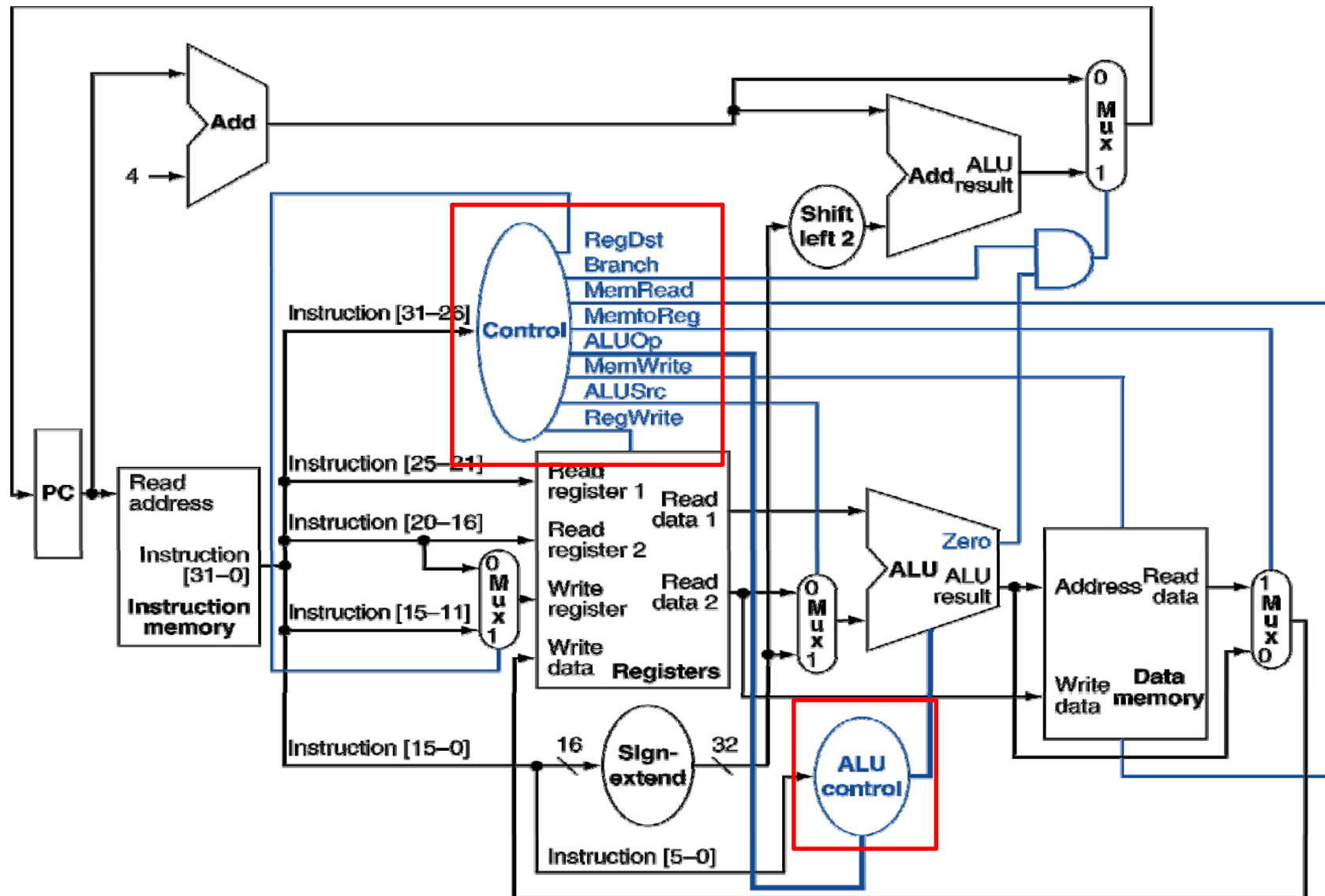
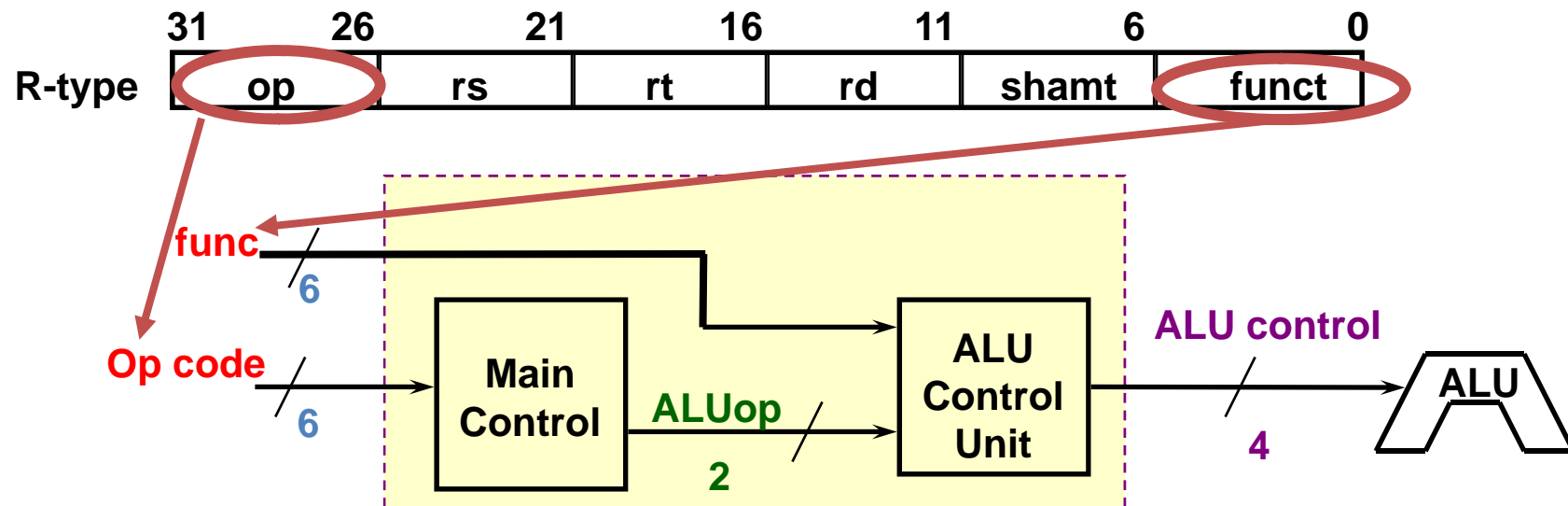
# Main Control and ALU Control

- **Main Control**: Based on opcode: generate RegDst, Branch, MemRead MemtoReg, ALUOp MemWrite, ALUSrc, RegWrite
- **ALU Control**: Based on **2-bit ALUOp** and the **6-bit funct field** of instruction, the ALU control unit generates the 4-bit ALU control field



## Deciding ALU Control

---


- Assume 2-bit ALUOp derived from opcode
  - Combinational logic derives ALU control

| opcode | ALUOp | Operation        | funct  | ALU function     | ALU control |
|--------|-------|------------------|--------|------------------|-------------|
| lw     | 00    | load word        | XXXXXX | add              | ?           |
| sw     | 00    | store word       | XXXXXX | add              | ?           |
| beq    | 01    | branch equal     | XXXXXX | subtract         | ?           |
| R-type | 10    | add              | 100000 | add              | ?           |
|        |       | subtract         | 100010 | subtract         | ?           |
|        |       | AND              | 100100 | AND              | ?           |
|        |       | OR               | 100101 | OR               | ?           |
|        |       | set-on-less-than | 101010 | set-on-less-than | ?           |

# ALU Control

- ALU Control has 4 four bits: **Ainvert**, **Binvert**, and **Operation (2 bits)**

| Function         | ALU control |
|------------------|-------------|
| AND              | 0000        |
| OR               | 0001        |
| add              | 0010        |
| subtract         | 0110        |
| set-on-less-than | 0111        |
| NOR              | 1100        |

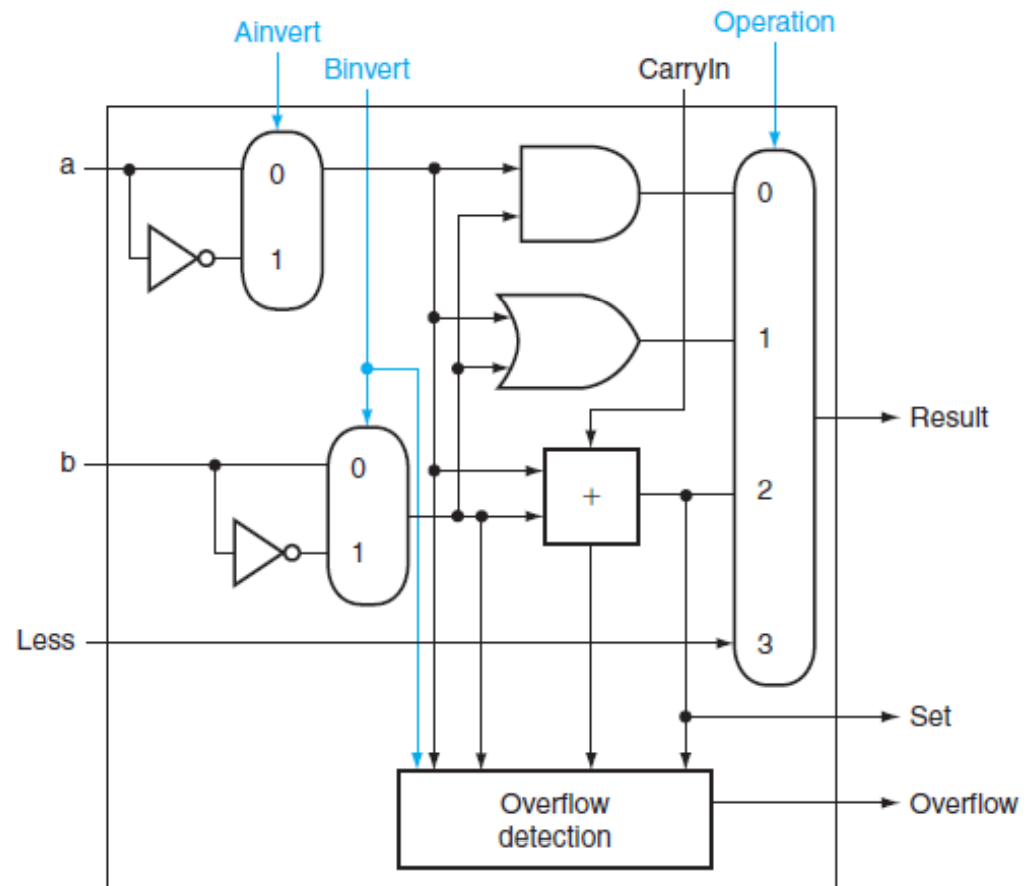


# ALU Control

- ALU used for
  - Load/Store: function = add
  - Branch: function = subtract
  - R-type: function depends on **funct** field
- Assume 2-bit ALUOp derived from opcode
  - Combinational logic derives ALU control

| opcode | ALUOp | Operation        | funct  | ALU function     | ALU control |
|--------|-------|------------------|--------|------------------|-------------|
| lw     | 00    | load word        | XXXXXX | add              | 0010        |
| sw     | 00    | store word       | XXXXXX | add              | 0010        |
| beq    | 01    | branch equal     | XXXXXX | subtract         | 0110        |
| R-type | 10    | add              | 100000 | add              | 0010        |
|        |       | subtract         | 100010 | subtract         | 0110        |
|        |       | AND              | 100100 | AND              | 0000        |
|        |       | OR               | 100101 | OR               | 0001        |
|        |       | set-on-less-than | 101010 | set-on-less-than | 0111        |


# Deciding Main Control Signals

- Control I signal

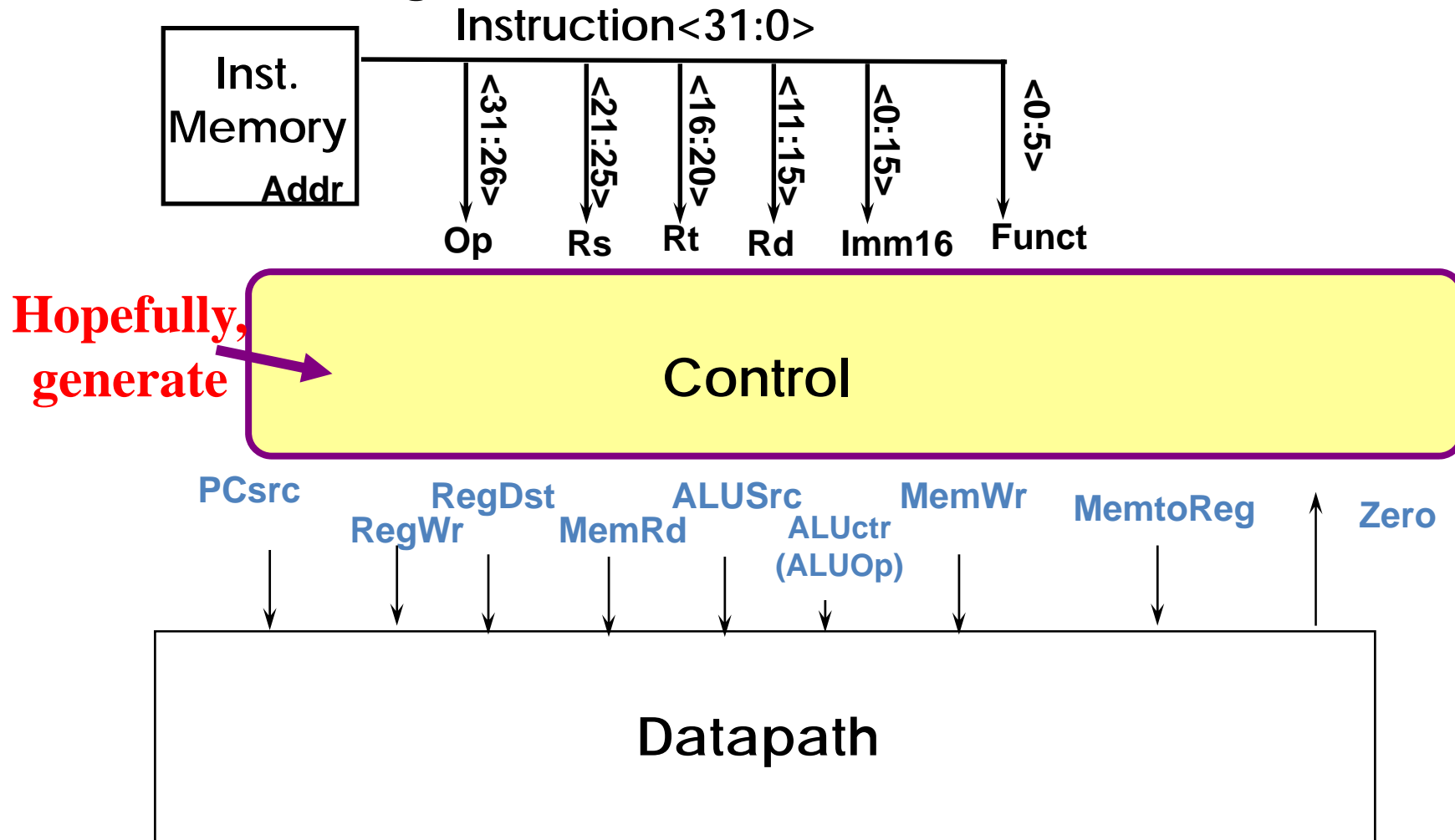

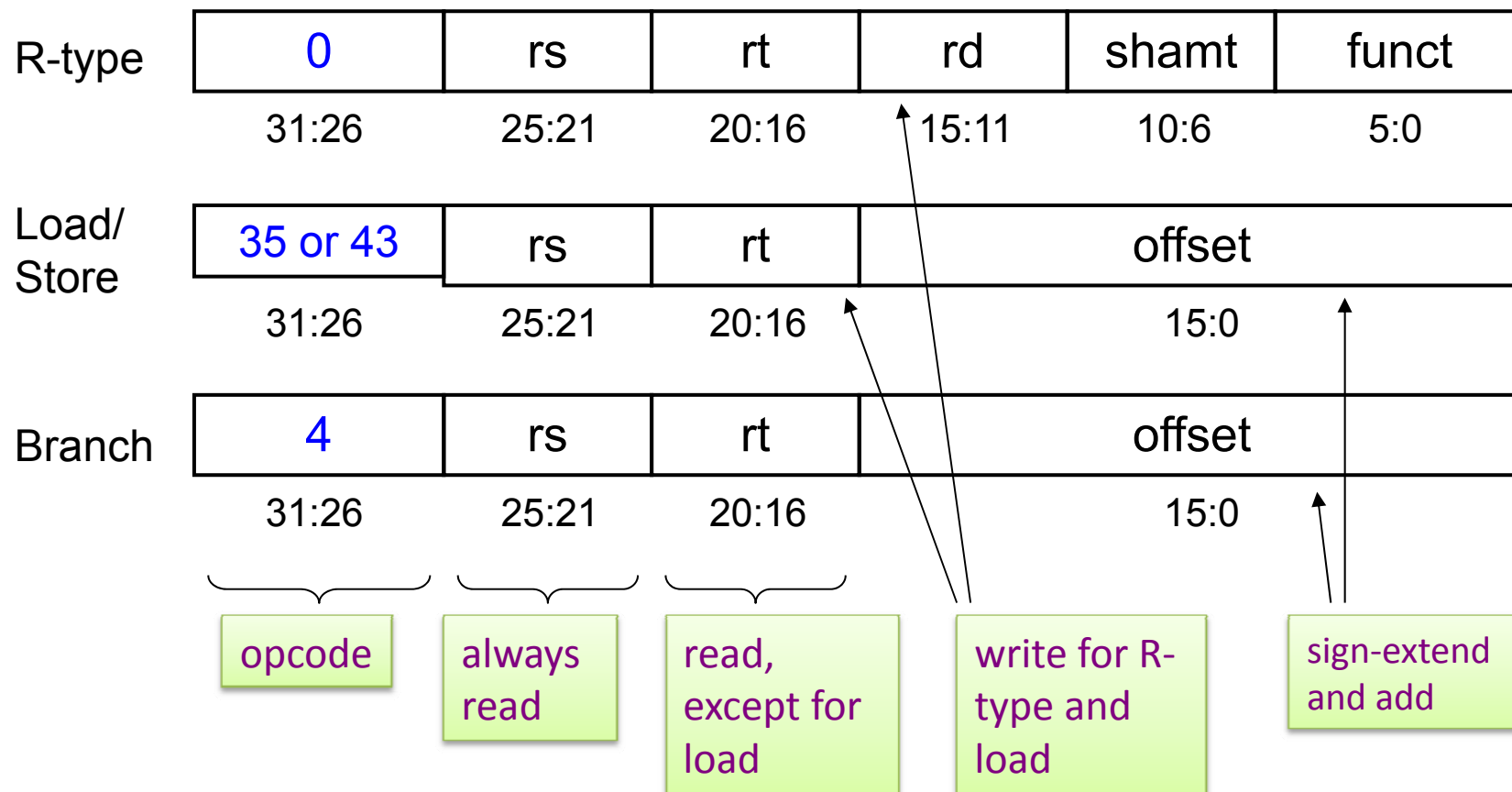
# Review: The Main Control Unit

- Control signals derived from instruction







# Control Signals for R-Type Instruction

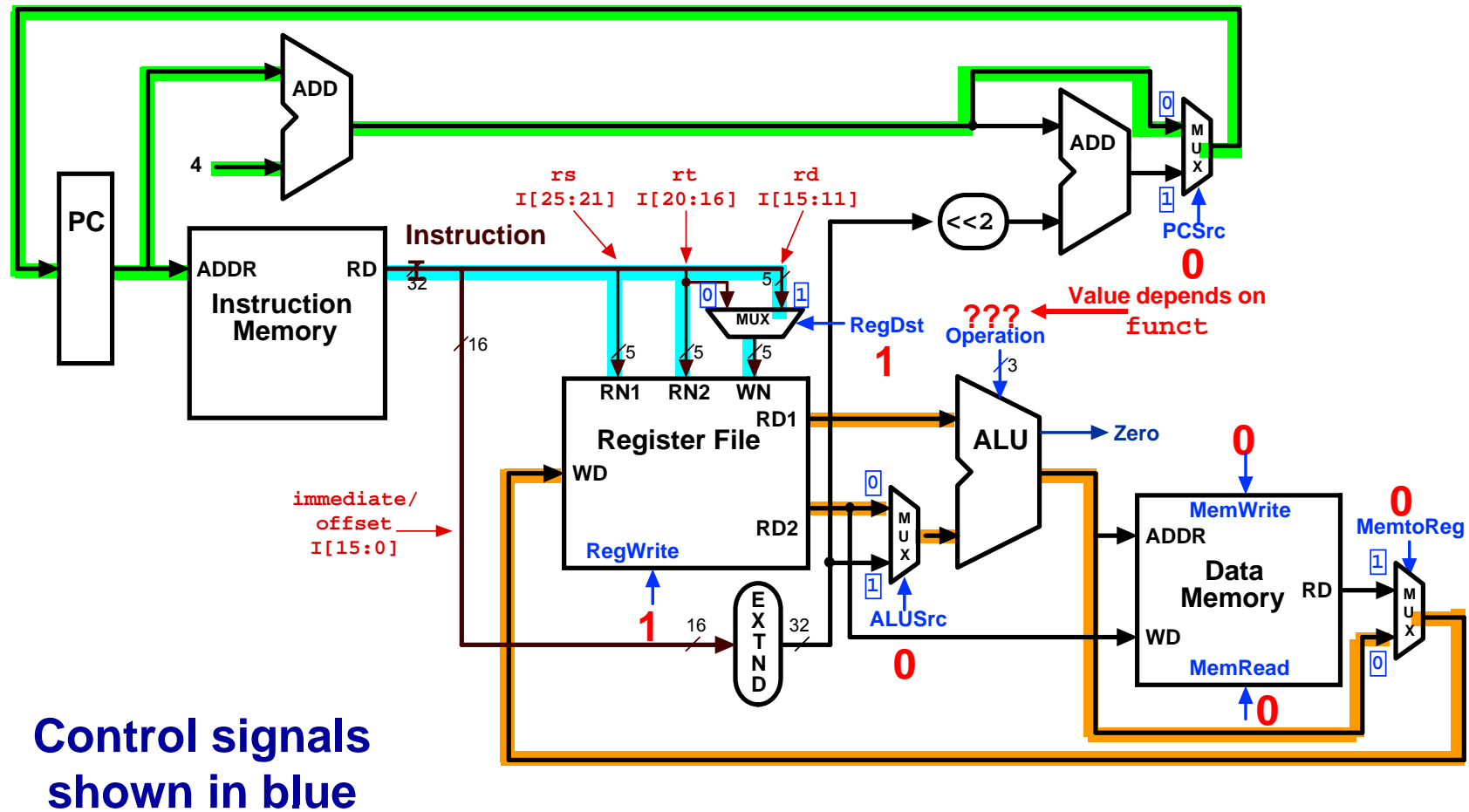


# Control Signals: `lw` Instruction

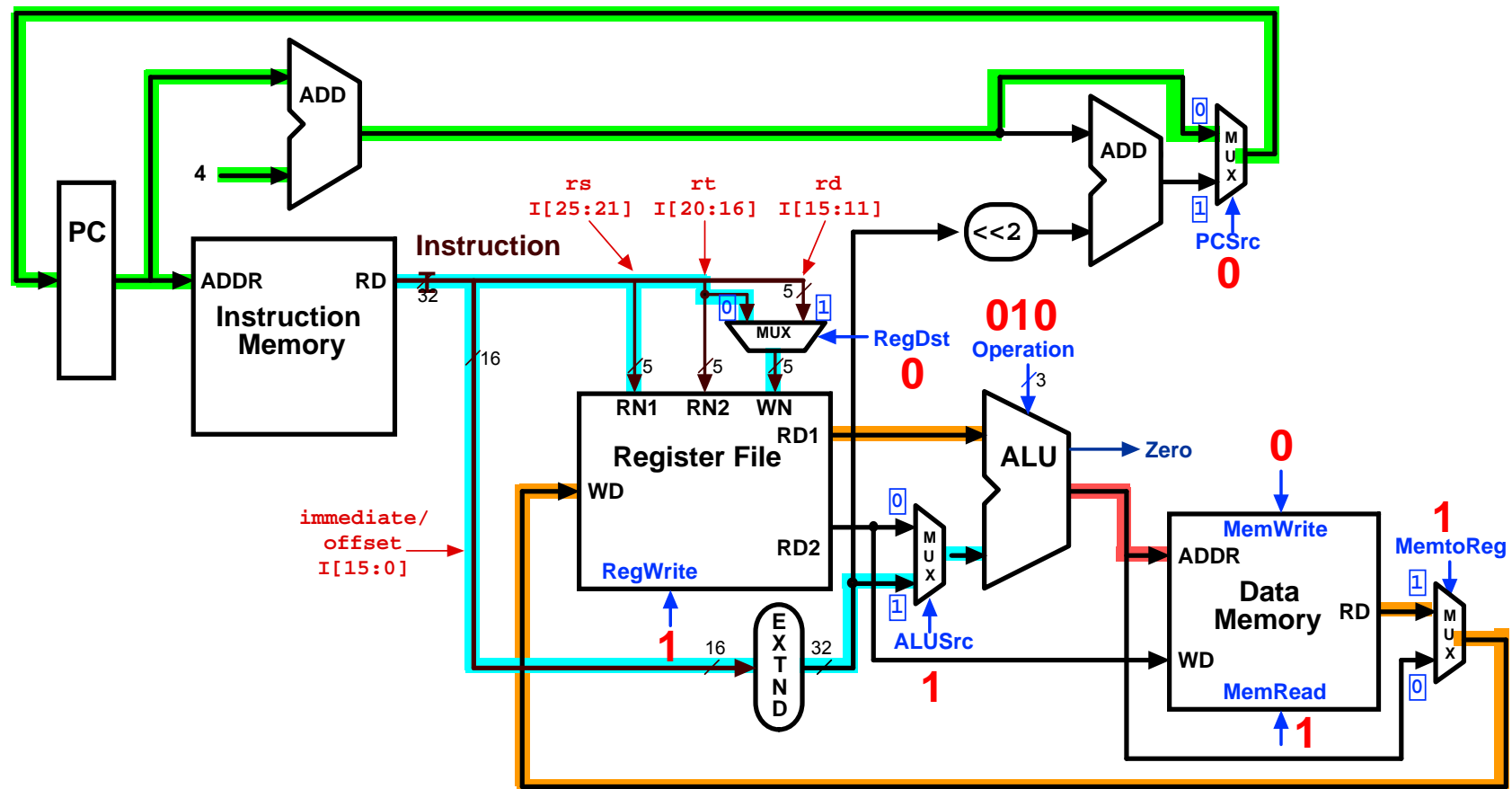


# Control Signals: sw Instruction

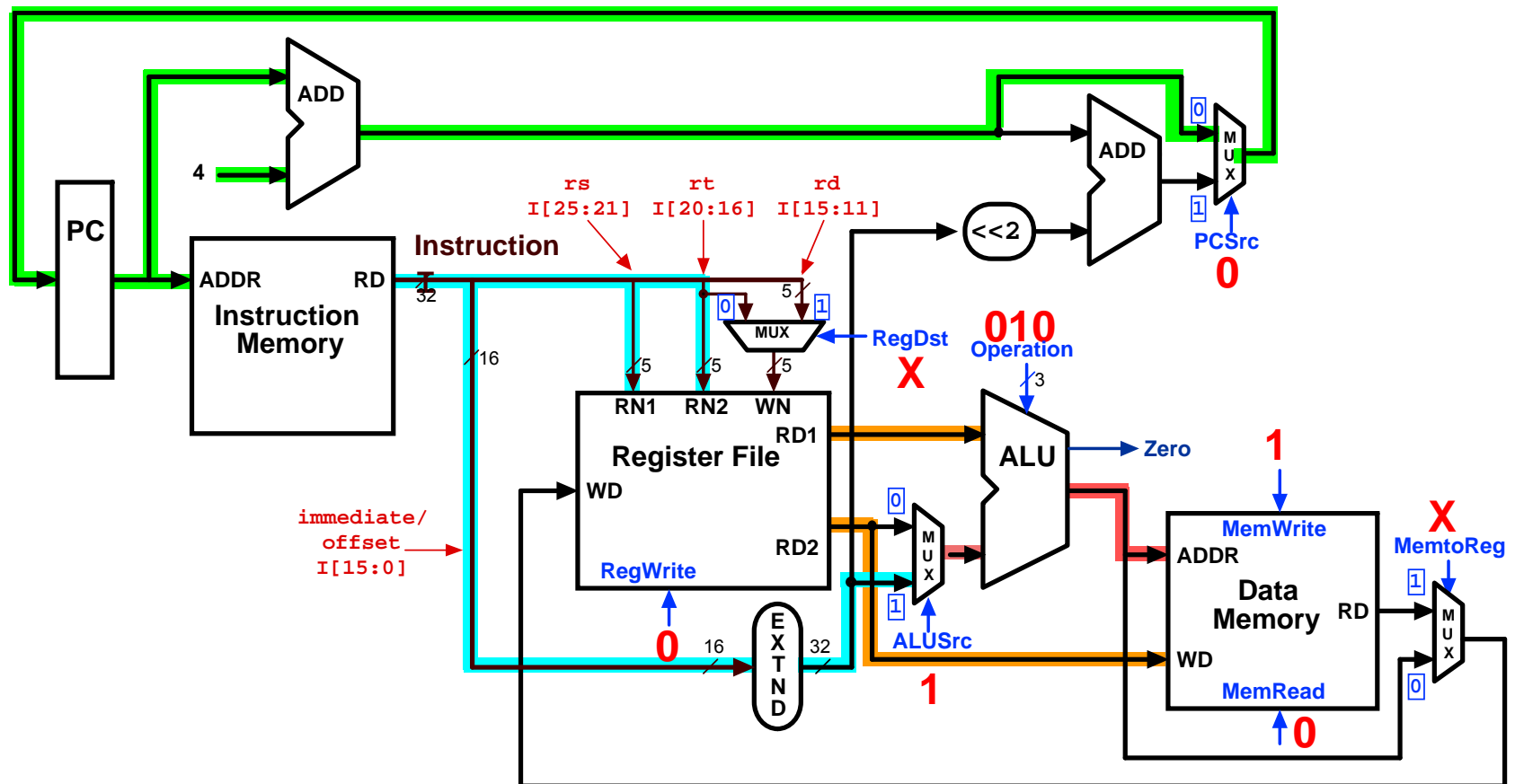

# Control Signals: beq Instruction

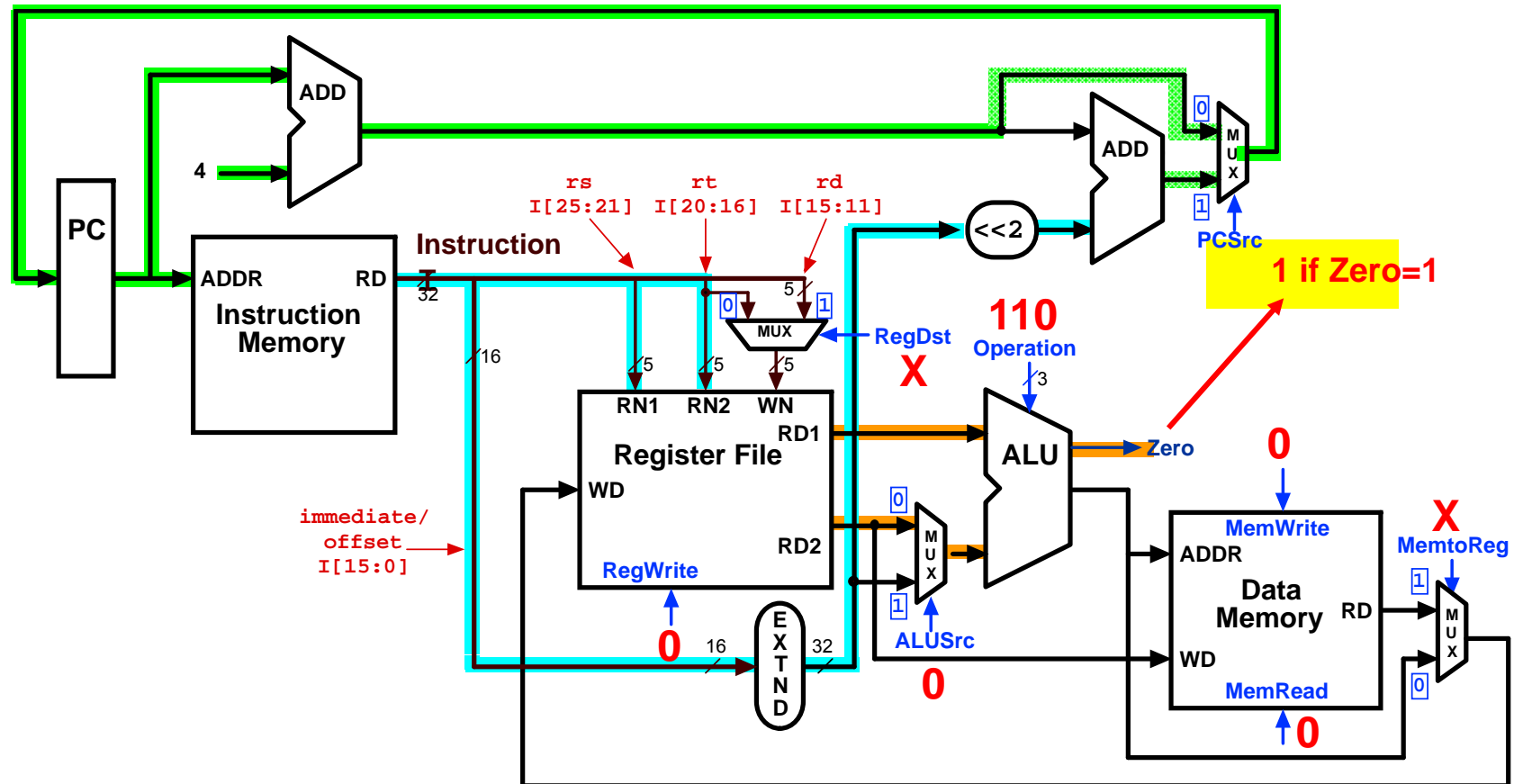


# Branch-on-Equal Instruction

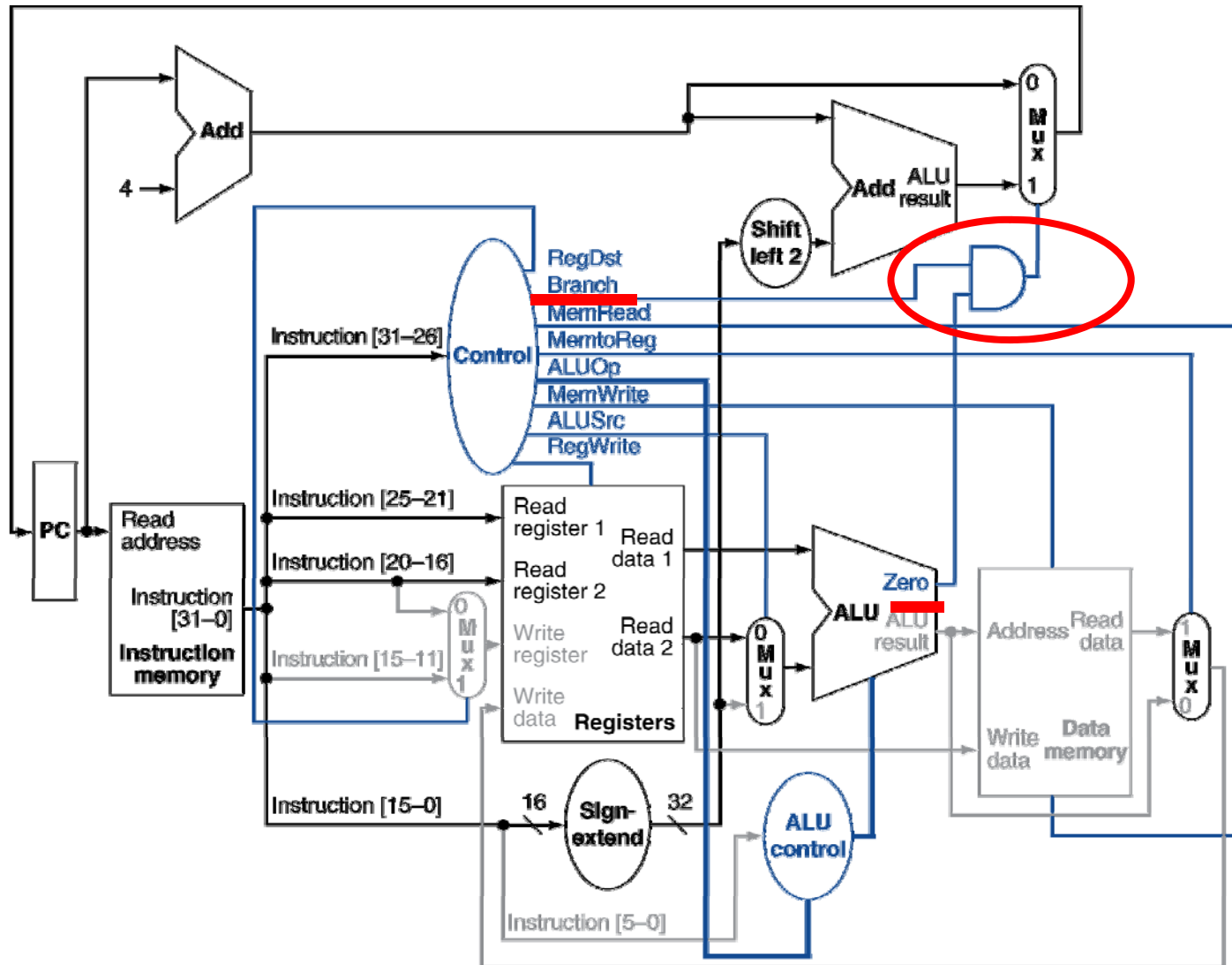
 
## Review: Target address of Jump

---


- Assume  $PC=40000000_{16}$ , what is the target address of the jump instruction?




Address in the instruction=  $0x0000201$

Target Address=  $PC[31:28]+0021_{16}*4= 0x40000804$

## Review: Implementing Jumps

 


 - Jump uses **word** address
- Update **PC** with concatenation of
  - Top 4 bits of **old PC+4**
  - **26**-bit jump address
  - **00**
- Need an extra control signal decoded from opcode




# Datapath Executing j

- j

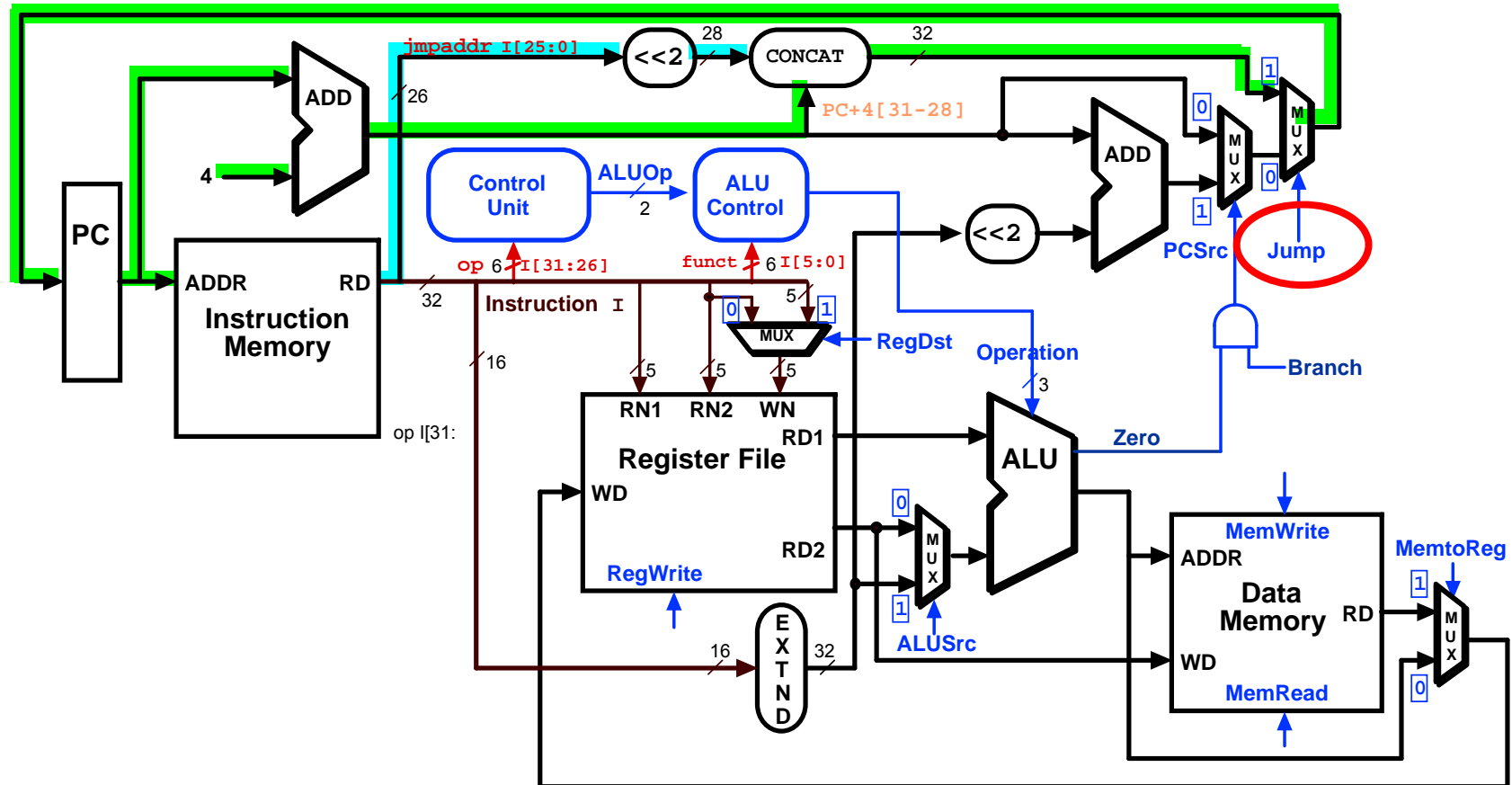



## Datapath With Jumps Added

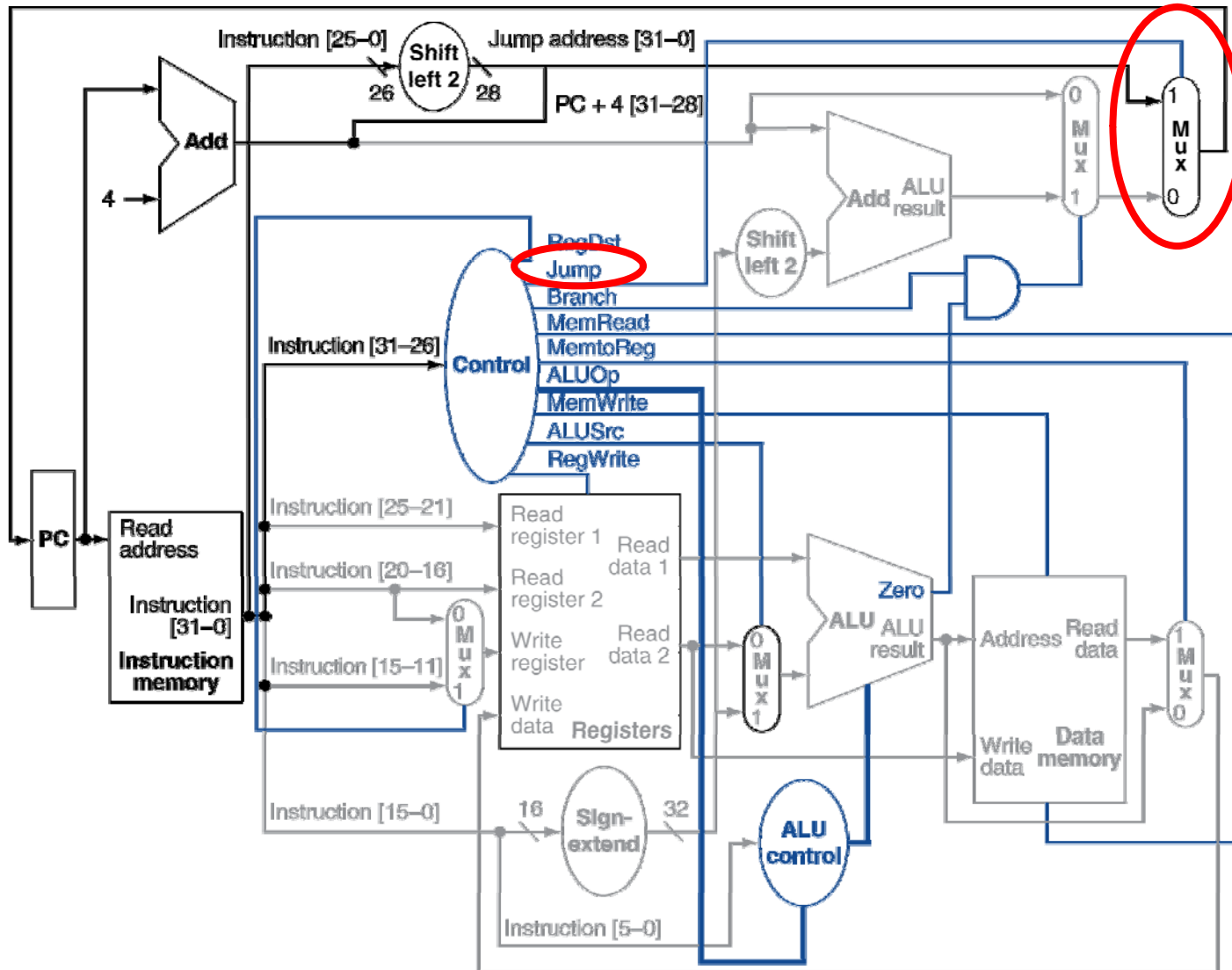

# Truth Table for Main Control Signals

- Current design of control is for
  - lw, sw, beq, and, or, add, sub, slt, nor
- I-format: lw, sw, beq
- R-format: and, or, add, sub, slt, nor
- Given 4 OP codes (each 6 bits) as “inputs”, the “outputs” are as follows  
=> a main control logic (the next slide)

See **appendix A**  
for details


| inputs             |        | outputs |           |           |          |           |        |        |        |
|--------------------|--------|---------|-----------|-----------|----------|-----------|--------|--------|--------|
| Instruction        | RegDst | ALUSrc  | Memto-Reg | Reg Write | Mem Read | Mem Write | Branch | ALUOp1 | ALUOp0 |
| R-format<br>000000 | 1      | 0       | 0         | 1         | 0        | 0         | 0      | 1      | 0      |
| lw<br>100011       | 0      | 1       | 1         | 1         | 1        | 0         | 0      | 0      | 0      |
| sw<br>101011       | X      | 1       | X         | 0         | 0        | 1         | 0      | 0      | 0      |
| beq<br>000100      | X      | 0       | X         | 0         | 0        | 0         | 1      | 0      | 1      |

# Implementation of Main Control Block (Use PLA)

- Use PLA

|         | Signal   | R-name | lw | sw | beq |
|---------|----------|--------|----|----|-----|
| Inputs  | Op5      | 0      | 1  | 1  | 0   |
|         | Op4      | 0      | 0  | 0  | 0   |
|         | Op3      | 0      | 0  | 1  | 0   |
|         | Op2      | 0      | 0  | 0  | 1   |
|         | Op1      | 0      | 1  | 1  | 0   |
|         | Op0      | 0      | 1  | 1  | 0   |
| Outputs | RegDst   | 1      | 0  | x  | x   |
|         | ALUSrc   | 0      | 1  | 1  | 0   |
|         | MemtoReg | 0      | 1  | x  | x   |
|         | RegWrite | 1      | 1  | 0  | 0   |
|         | MemRead  | 0      | 1  | 0  | 0   |
|         | MemWrite | 0      | 0  | 1  | 0   |
|         | Branch   | 0      | 0  | 0  | 1   |
|         | ALUOp1   | 1      | 0  | 0  | 0   |
|         | ALUOp0   | 0      | 0  | 0  | 1   |

Truth table for main control signals

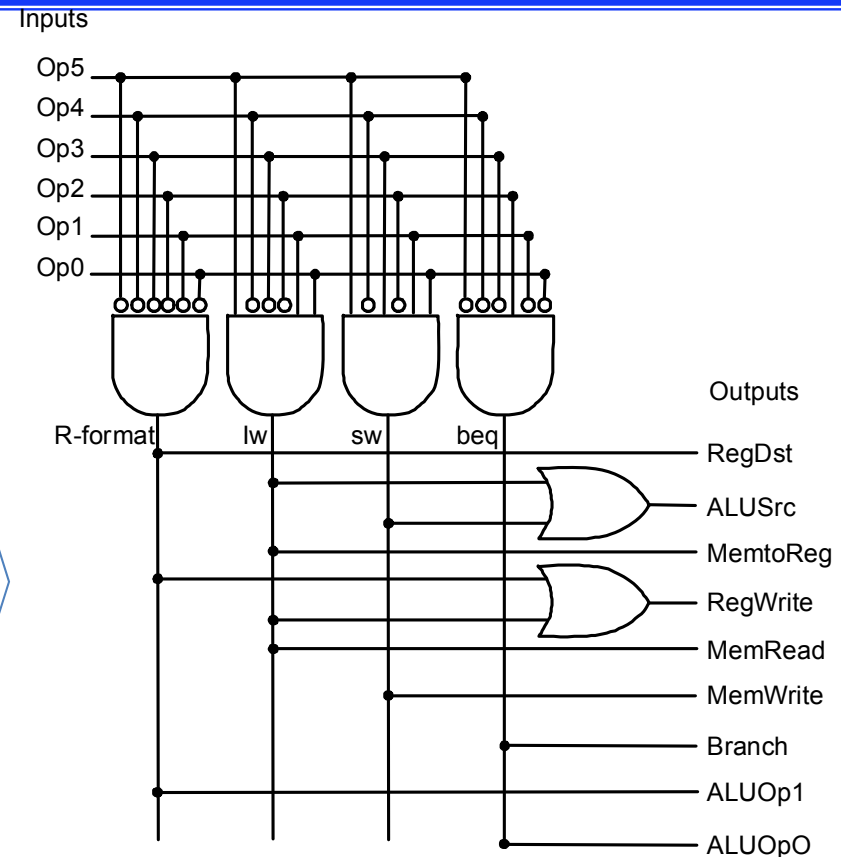

**Main control PLA (programmable logic array)**  
 principle underlying PLAs is that any logical expression can be written as a sum-of-products

| Instruction opcode | ALUOp | Instruction operation | Funct field | Desired ALU action | ALU control input |
|--------------------|-------|-----------------------|-------------|--------------------|-------------------|
| LW                 | 00    | load word             | XXXXXX      | add                | 0010              |
| SW                 | 00    | store word            | XXXXXX      | add                | 0010              |
| Branch equal       | 01    | branch equal          | XXXXXX      | subtract           | 0110              |
| R-type             | 10    | add                   | 100000      | add                | 0010              |
| R-type             | 10    | subtract              | 100010      | subtract           | 0110              |
| R-type             | 10    | AND                   | 100100      | AND                | 0000              |
| R-type             | 10    | OR                    | 100101      | OR                 | 0001              |
| R-type             | 10    | set on less than      | 101010      | set on less than   | 0111              |

## Truth Table for ALU control signals

|               |        |        |             |    |    |    |    |         |                                                        |
|---------------|--------|--------|-------------|----|----|----|----|---------|--------------------------------------------------------|
|               |        | inputs |             |    |    |    |    | outputs |                                                        |
| Merge LW & SW | ALUOp  |        | Funct field |    |    |    |    |         | Operation                                              |
|               | ALUOp1 | ALUOp0 | F5          | F4 | F3 | F2 | F1 | F0      | $C_3C_2C_1C_0$                                         |
|               | 0      | 0      | X           | X  | X  | X  | X  | X       | 0010                                                   |
|               | 0      | 1      | X           | X  | X  | X  | X  | X       | 0110                                                   |
|               | 1      | X      | X           | X  | 0  | 0  | 0  | 0       | 0010                                                   |
|               | 1      | X      | X           | X  | 0  | 0  | 1  | 0       | 0110                                                   |
|               | 1      | X      | X           | X  | 0  | 1  | 0  | 0       | 0000                                                   |
|               | 1      | X      | X           | X  | 0  | 1  | 0  | 1       | 0001                                                   |
|               | 1      | X      | X           | X  | 1  | 0  | 1  | 0       | 0111                                                   |
|               |        |        |             |    |    |    |    |         | add<br>subtract<br>add<br>subtract<br>and<br>or<br>slt |

# Implementation of ALU Control

- C3=0

ALUOp0=1  
is able to  
identify  
branch  
instruction

C2


| ALUOp  |        | Function code fields |    |    |    |    |    |
|--------|--------|----------------------|----|----|----|----|----|
| ALUOp1 | ALUOp0 | F5                   | F4 | F3 | F2 | F1 | F0 |
| X      | 1      | X                    | X  | X  | X  | X  | X  |
| 1      | X      | X                    | X  | X  | X  | 1  | X  |

C1


| ALUOp  |        | Function code fields |    |    |    |    |    |
|--------|--------|----------------------|----|----|----|----|----|
| ALUOp1 | ALUOp0 | F5                   | F4 | F3 | F2 | F1 | F0 |
| 0      | X      | X                    | X  | X  | X  | X  | X  |
| X      | X      | X                    | X  | X  | 0  | X  | X  |

C0

| ALUOp  |        | Function code fields |    |    |    |    |    |
|--------|--------|----------------------|----|----|----|----|----|
| ALUOp1 | ALUOp0 | F5                   | F4 | F3 | F2 | F1 | F0 |
| 1      | X      | X                    | X  | X  | X  | X  | 1  |
| 1      | X      | X                    | X  | 1  | X  | X  | X  |

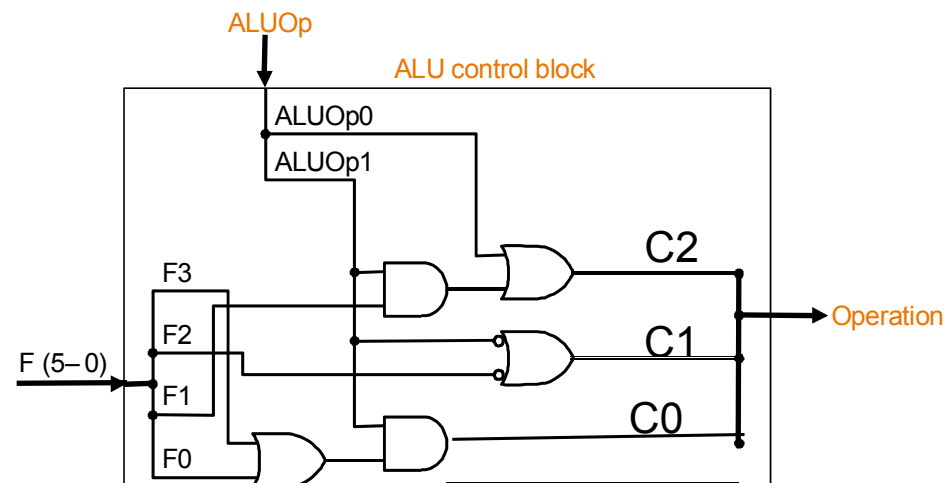

# Worst Case Timing (lw)

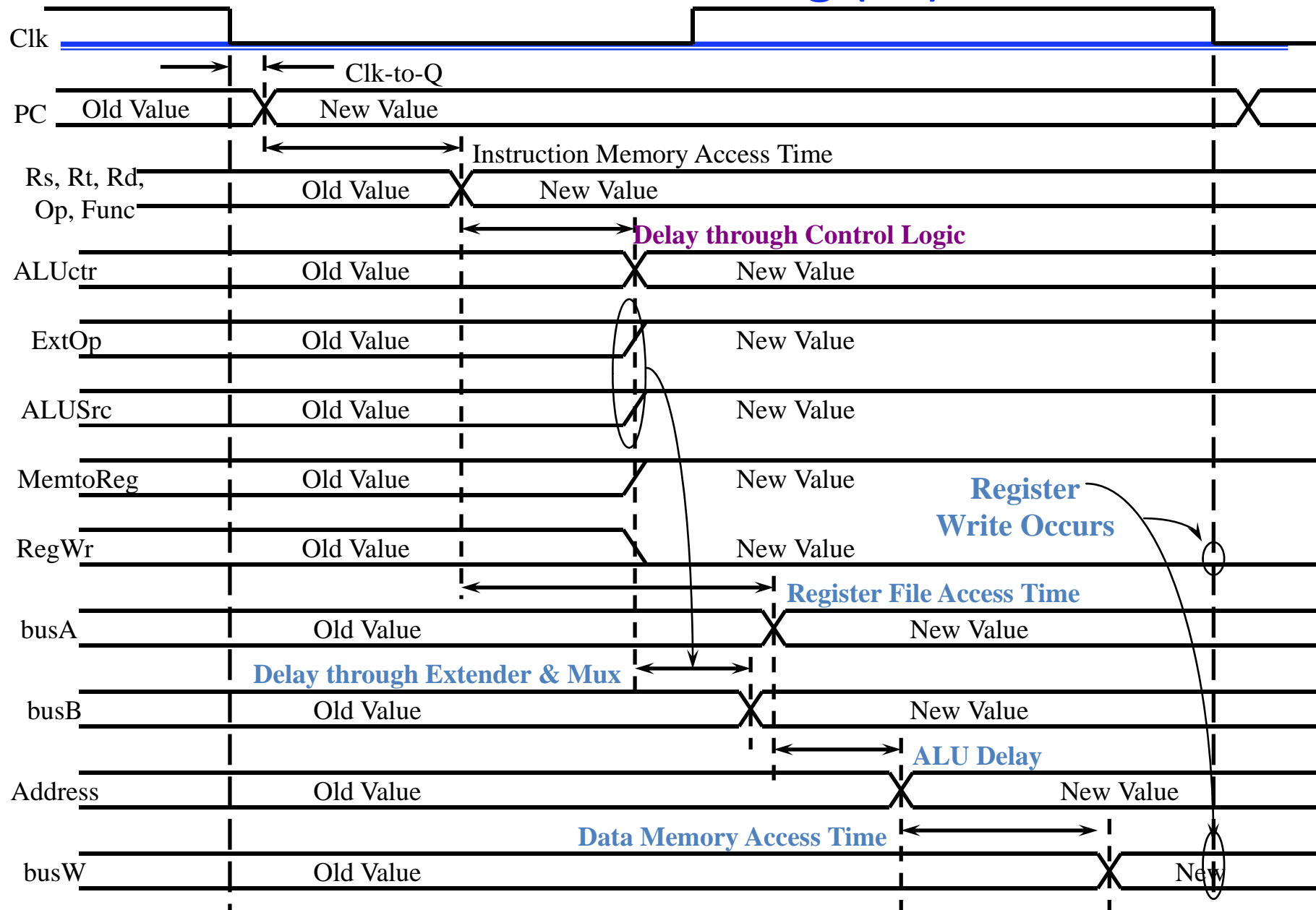

## Drawback of Single-Cycle Design

---

- Long cycle time:
  - Cycle time must be long enough for the load instruction:  
PC's Clock -to-Q +  
Instruction Memory Access Time +  
Register File Read Time +  
ALU Delay (address calculation) +  
Data Memory Access Time +  
Register File Write Time
- Cycle time for **load (lw)** is much longer than needed for all other instructions

# Summary

---

- Single cycle processor
  - CPI=1
  - Clock cycle time long
- 5 steps to design a processor:
  1. **Analyze** ISA => datapath requirements
  2. **Select** set of datapath **components**
  3. **Assemble datapath** meeting the requirements
  4. **Analyze** implementation of each instruction to determine setting of **control** points
  5. **Assemble** the **control** logic



# Summary

---

- Longest delay determines clock period
  - Critical path: load instruction
    - Instruction memory → register file → ALU → data memory → register file
- Not feasible to vary period for different instructions
- We will improve performance by pipelining