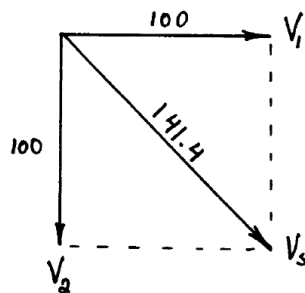


$$\text{P5.12*} \quad I_{rms} = \sqrt{\frac{1}{T} \int_0^T i^2(t) dt} = \sqrt{\frac{1}{4} \left(\int_0^2 25 dt + \int_2^4 4 dt \right)} = 3.808 \text{ A}$$

$$\begin{aligned} \text{P5.22*} \quad v_1(t) &= 100 \cos(\omega t) \\ v_2(t) &= 100 \sin(\omega t) = 100 \cos(\omega t - 90^\circ) \\ V_1 &= 100 \angle 0^\circ = 100 \\ V_2 &= 100 \angle -90^\circ = -j100 \\ V_s &= V_1 + V_2 = 100 - j100 = 141.4 \angle -45^\circ \\ v_s(t) &= 141.4 \cos(\omega t - 45^\circ) \end{aligned}$$



V_2 lags V_1 by 90°
 V_s lags V_1 by 45°
 V_s leads V_2 by 45°

$$\begin{aligned} \text{P5.25} \quad V_m &= 15 \text{ V} \quad T = 20 \text{ ms} \\ f &= \frac{1}{T} = 50 \text{ Hz} \quad \omega = 2\pi f = 100\pi \text{ rad/s} \\ \theta &= -360^\circ \frac{t_{max}}{T} = 72^\circ \\ v(t) &= 15 \cos(100\pi t + 72^\circ) \text{ V} \\ V &= 15 \angle 72^\circ \text{ V} \\ V_{rms} &= \frac{15}{\sqrt{2}} = 10.61 \text{ V} \end{aligned}$$

$$\begin{aligned} \text{P5.34} \quad (a) \quad &\text{Notice that the current is a sine rather than a cosine.} \\ V &= 100 \angle 30^\circ \quad I = 2.5 \angle -60^\circ \quad Z = \frac{V}{I} = 40 \angle 90^\circ = j40 \\ &\text{Because } Z \text{ is pure imaginary and positive, the element is an inductance.} \\ \omega &= 200 \quad L = \frac{|Z|}{\omega} = 200 \text{ mH} \end{aligned}$$

$$\begin{aligned} (b) \quad &\text{Notice that the voltage is a sine rather than a cosine.} \\ V &= 100 \angle -60^\circ \quad I = 4 \angle 30^\circ \quad Z = \frac{V}{I} = 25 \angle -90^\circ = -j25 \\ &\text{Because } Z \text{ is pure imaginary and negative, the element is a capacitance.} \\ \omega &= 200 \quad C = \frac{1}{|Z|\omega} = 200 \text{ } \mu\text{F} \end{aligned}$$

$$\begin{aligned} (c) \quad V &= 100 \angle 30^\circ \quad I = 5 \angle 30^\circ \quad Z = \frac{V}{I} = 20 \angle 0^\circ = 20 + j0 \\ &\text{Because } Z \text{ is pure real, the element is a resistance of } 20 \Omega. \end{aligned}$$

- 5.35 (a) From the plot, we see that $T = 4 \text{ ms}$, so we have $f = 1/T = 250 \text{ Hz}$ and $\omega = 500\pi$. Also, we see that the current lags the voltage by 1 ms or

90° , so we have an inductance. Finally, $\omega L = V_m / I_m = 5000 \Omega$, from which we find that $L = 3.183 \text{ H}$.

(b) From the plot, we see that $T = 16 \text{ ms}$, so we have $f = 1/T = 62.5 \text{ Hz}$ and $\omega = 125\pi$. Also, we see that the current leads the voltage by 4 ms or 90° , so we have a capacitance. Finally, $1/\omega C = V_m / I_m = 2500 \Omega$, from which we find that $C = 1.019 \mu\text{F}$.

P5.36 (a) $Z = \frac{V}{I} = 20 \angle -90^\circ = -j20$

Because Z is pure imaginary and negative, the element is a capacitance.

$$\omega = 1000 \quad C = \frac{1}{|Z|\omega} = 50 \mu\text{F}$$

(b) $Z = \frac{V}{I} = 10 \angle 90^\circ = j10$

Because Z is pure imaginary and positive, the element is an inductance.


$$\omega = 1000 \quad L = \frac{|Z|}{\omega} = 10 \text{ mH}$$

(c) $Z = \frac{V}{I} = 20 \angle 0^\circ = 20$

Because Z is pure real, the element is a resistance of 20Ω .

P5.38*
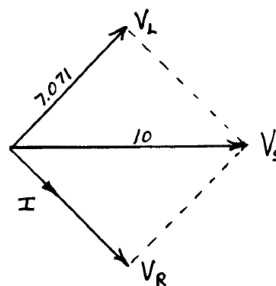
$$\begin{aligned} \mathbf{I} &= \frac{\mathbf{V}_s}{R + j\omega L} \\ &= \frac{10 \angle 0^\circ}{100 + j100} \\ &= 70.71 \angle -45^\circ \text{ mA} \\ \mathbf{V}_R &= R\mathbf{I} = 7.071 \angle -45^\circ \text{ V} \\ \mathbf{V}_L &= j\omega L\mathbf{I} = 7.071 \angle 45^\circ \text{ V} \\ \mathbf{I} &\text{ lags } \mathbf{V}_s \text{ by } 45^\circ \end{aligned}$$



P5.45*


$$\mathbf{I}_s = 10 \angle 0^\circ \text{ mA}$$

$$\begin{aligned} \mathbf{V} &= \mathbf{I}_s \frac{1}{1/R + 1/j\omega L + j\omega C} \\ &= 10^{-2} \frac{1}{1/1000 - j0.005 + j0.005} \\ &= 10 \angle 0^\circ \text{ V} \end{aligned}$$

$$\mathbf{I}_R = \mathbf{V}/R = 10 \angle 0^\circ \text{ mA}$$

$$\mathbf{I}_L = \mathbf{V}/j\omega L = 50 \angle -90^\circ \text{ mA}$$
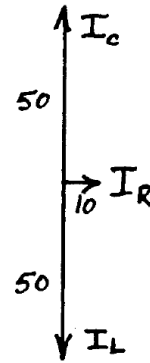
$$\mathbf{I}_C = \mathbf{V}(j\omega C) = 50 \angle 90^\circ \text{ mA}$$



The peak value of $i_L(t)$ is five times larger than the source current! This is possible because current in the capacitance balances the current in the inductance (i.e., $\mathbf{I}_L + \mathbf{I}_C = 0$).

5.46


$$\mathbf{I}_s = 0.5 \angle -90^\circ$$

$$\begin{aligned} \mathbf{V} &= \mathbf{I}_s \frac{1}{1/200 + 1/j100} \\ &= 44.72 \angle -26.56^\circ \end{aligned}$$

$$\mathbf{I}_R = \mathbf{V}/R = 0.2236 \angle -26.56^\circ$$

$$\mathbf{I}_L = \mathbf{V}/j\omega L = 0.4472 \angle -116.56^\circ$$

\mathbf{V} leads \mathbf{I}_s by 63.44°

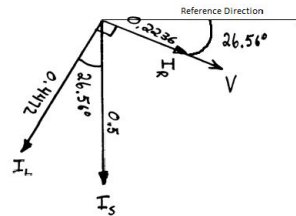

P5.51

$$\begin{aligned} \mathbf{Z}_{total} &= j\omega L + \frac{1}{1/R + j\omega C} \\ &= j100 + \frac{1}{0.01 + j0.01} \\ &= j100 + 50 - j50 \\ &= 50 + j50 \\ &= 70.71 \angle 45^\circ \end{aligned}$$

$$\mathbf{I} = \frac{100 \angle 0^\circ}{\mathbf{Z}_{total}} = 1.414 \angle -45^\circ$$

$$\begin{aligned} \mathbf{I}_R &= \mathbf{I} \frac{\mathbf{Z}_C}{R + \mathbf{Z}_C} = (1.414 \angle -45^\circ) \times \frac{-j100}{100 - j100} \\ &= 1 \angle -90^\circ \end{aligned}$$

$$\begin{aligned} \mathbf{I}_C &= \mathbf{I} \frac{R}{R + \mathbf{Z}_C} = (1.414 \angle -45^\circ) \times \frac{100}{100 - j100} \\ &= 1 \angle 0^\circ \end{aligned}$$

