

Chapter 9

Asynchronous Sequential Logic


**Most topics mentioned in Text Book
are skipped here.**

Hazards


- **Unwanted switching transients at the output**
 - **different paths exhibit different propagation delays**
 - **temporary false-output value in combinational circuits**
 - **may result in a transition to a wrong stable state in asynchronous sequential circuits**

Hazards

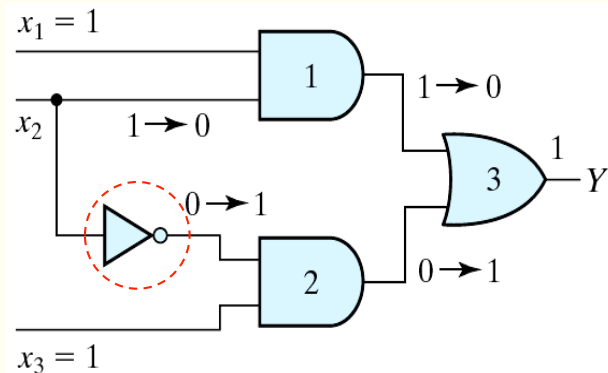- Hazards in combinational circuits
 - examples



(a) AND-OR circuit

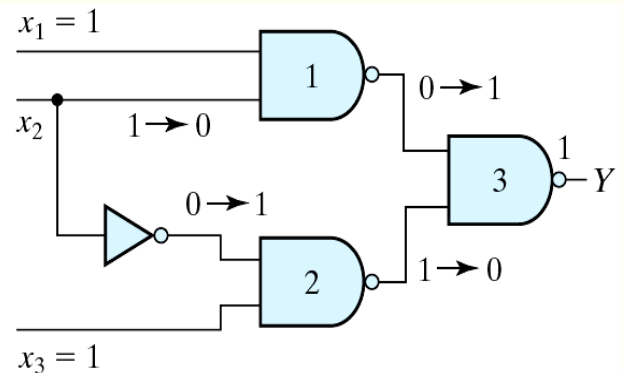

(b) NAND circuit

input	Y
1 1 1	1
1 0 1	1

1 0 1 1 (the output may momentarily go to 0, then go to 1)

Static Hazard


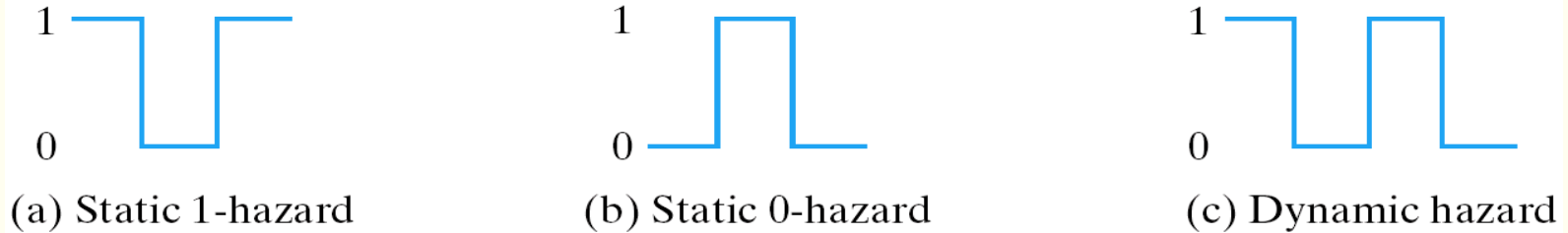


Fig. 9.34
Types of hazards


- ▣ **static 1-hazard (sum of products)**
 - the removal of static 1-hazard guarantees that no static 0-hazards or dynamic hazards

Hazard Free

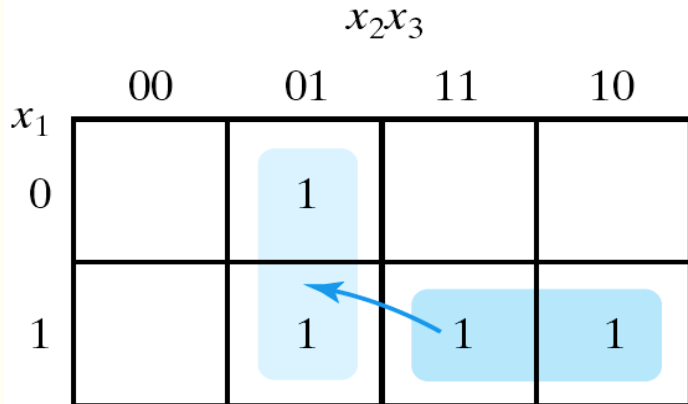- the circuit moves from one product term to another
- additional redundant gate



(a) $Y = x_1x_2 + x'_2x_3$

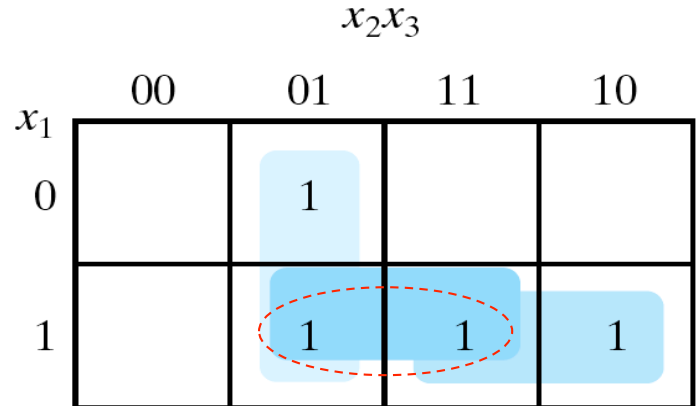

(b) $Y = x_1x_2 + x'_2x_3 + x_1x_3$

Hazard-free circuit

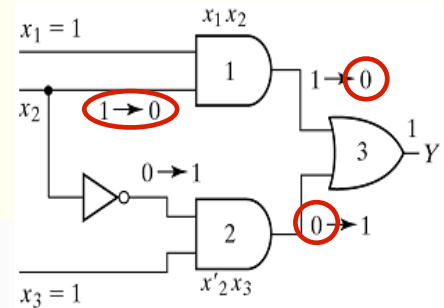
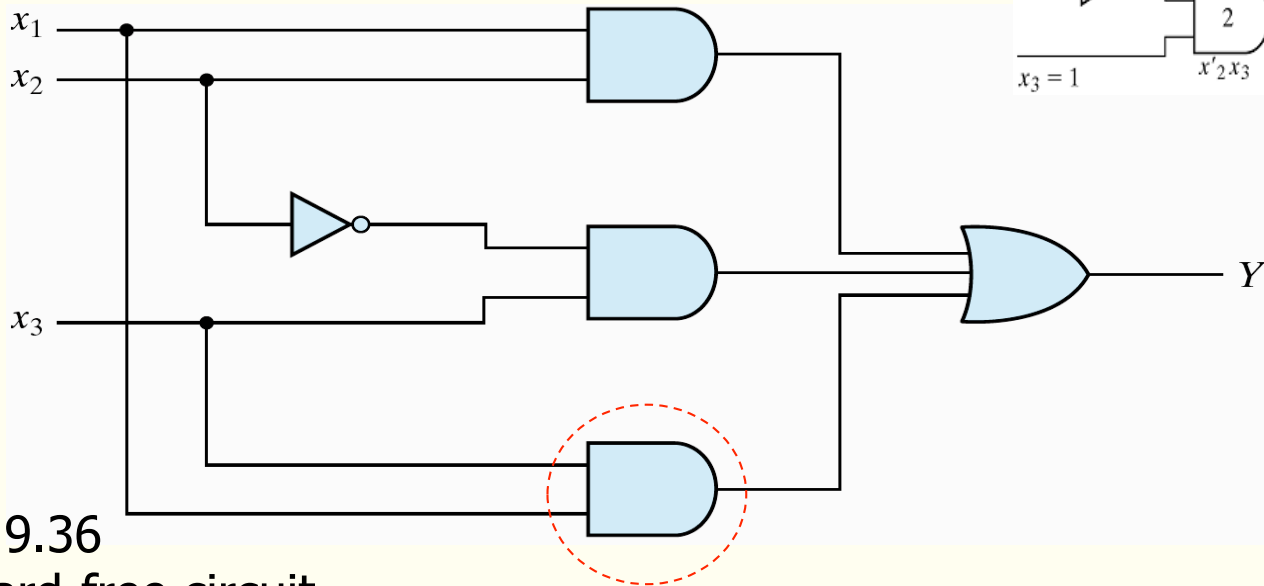


Fig. 9.36
Hazard-free circuit