

Chapter 7


Memory and Programmable Logic

Introduction


- Memory
 - information storage
 - a collection of cells storing binary information
- RAM – Random Access Memory
 - read operation
 - write operation
- ROM – Read Only Memory
 - read operation only
 - a programmable logic device

Programmable Logic Device (PLD)

 - ROM
- PLA – programmable logic array
- PAL – programmable array logic
- FPGA – field-programmable gate array
 - programmable logic blocks
 - programmable interconnects




(a) Conventional symbol

 

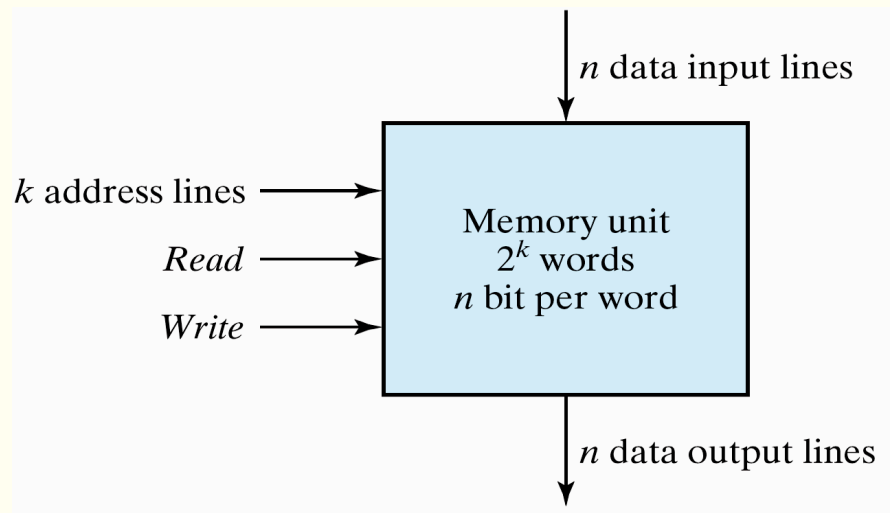(b) Array logic symbol

Random-Access Memory

- A memory unit
 - stores binary information in groups of bits (words)
 - 8 bits (a byte), 2 bytes, 4 bytes
- Block diagram



1024 × 16 Memory

Memory address		Memory content
Binary	Decimal	
0000000000	0	1011010101011101
0000000001	1	1010101110001001
0000000010	2	0000110101000110
	⋮	⋮
1111111101	1021	1001110100010100
1111111110	1022	0000110100011110
1111111111	1023	1101111000100101

Fig. 7.3
Contents of a
1024 × 16
memory

Write and Read Operations

- Write operation
 - Apply the binary address to the address lines
 - Apply the data bits to the data input lines
 - Activate the *write* input
- Read operation
 - Apply the binary address to the address lines
 - Activate the *read* input

Table 7.1
Control Inputs to Memory Chip


Memory Enable	Read/Write	Memory Operation
0	X	None
1	0	Write to selected word
1	1	Read from selected word

Timing Waveforms

- The operation of the memory unit is controlled by an external device
- The access time
 - the time required to select a word and read it
- The cycle time
 - the time required to complete a write operation
- Read and write operations must be synchronized with an external clock


A Write Cycle

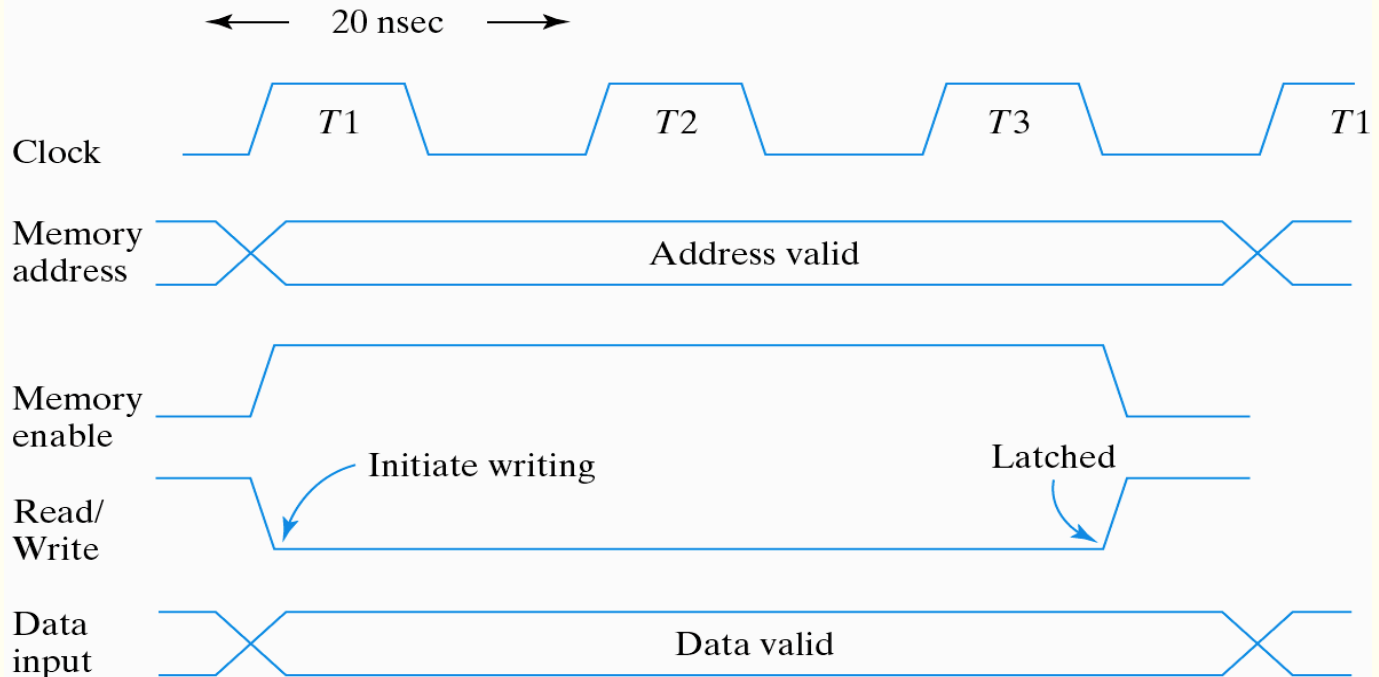- CPU clock – 50 MHz, access/cycle time < 50 ns



(a) Write cycle

A read cycle

 

(b) Read cycle

Types of RAM


- Static RAM (cache memory)
 - Information are stored in latches
 - remains valid as long as power is applied
 - short read/write cycle
- Dynamic RAM
 - Information are stored in the form of charges on capacitors
 - the stored charge tends to discharge with time
 - need to be refreshed (read and write back)
 - reduced power consumption
 - Larger memory capacity

Memory


- Volatile
 - lose stored information when power is turned off
 - SRAM, DRAM
- Non-volatile
 - Retains its stored information after the removal of power
 - ROM
 - EPROM, EEPROM
 - Flash memory

Memory Decoding

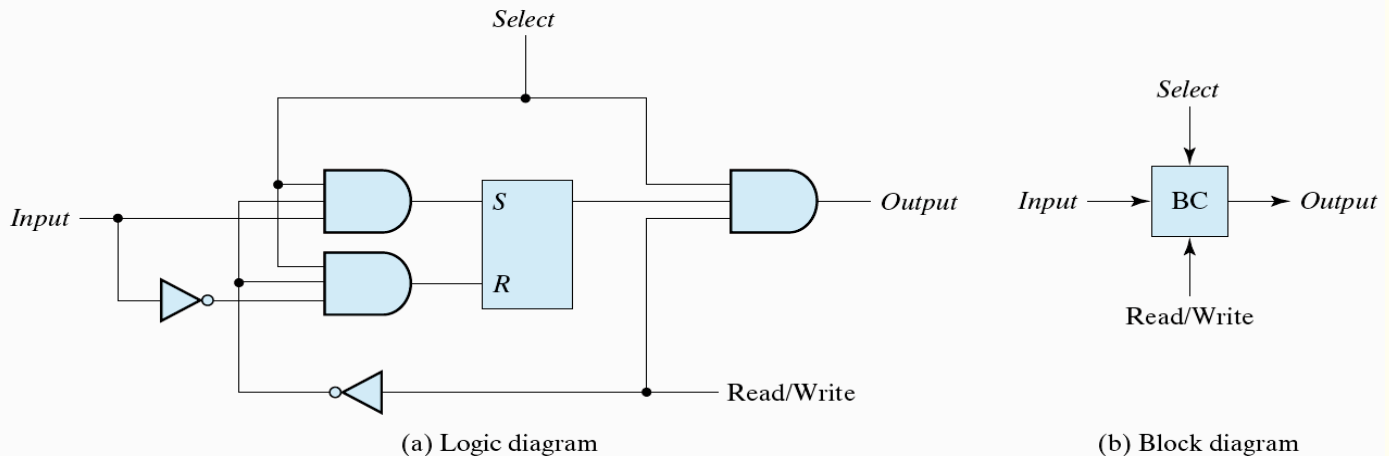- A memory unit
 - the storage components
 - the decoding circuits to select the memory word
- A memory cell



A 4x4 RAM

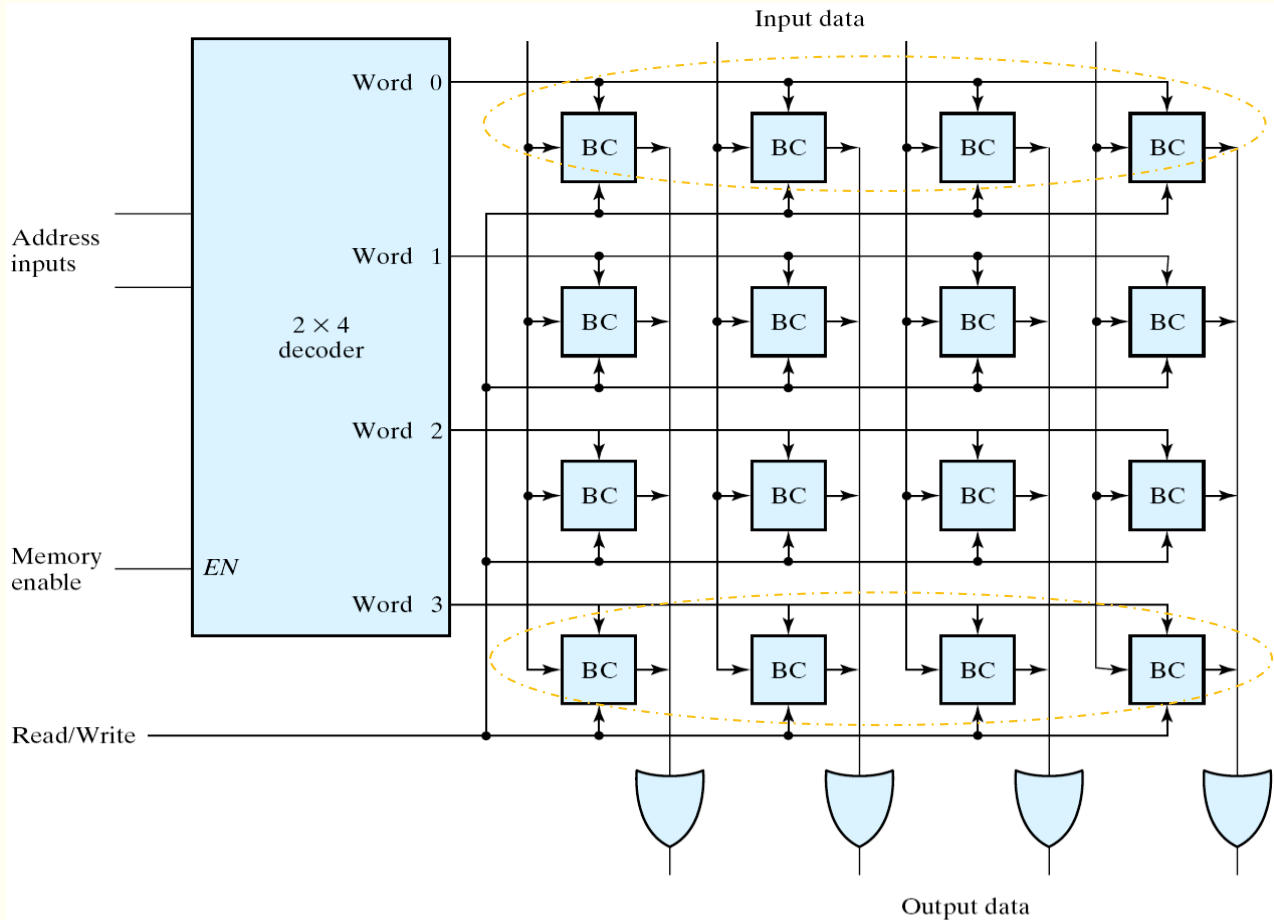

Coincident Decoding

- A two-dimensional selection scheme
 - reduce the complexity of the decoding circuits

 


Fig. 7.7
Two-dimensional
decoding structure
for a 1K-word
memory

Error Detection And Correction

- Improve the reliability of a memory unit
- A simple error detection scheme
 - **a parity bit (Sec. 3-9)**
 - **a single bit error can be detected, but cannot be corrected**
- An error-correction code
 - **generates multiple parity check bits**
 - **the check bits generate a unique pattern, called a syndrome**
 - **the specific bit in error can be identified**

Hamming Code

- k parity bits are added to an n -bit data word
 - $(2^k - 1 \geq n + k)$
 - The bit positions are numbered in sequence from 1 to $n + k$
 - Those positions numbered as a power of 2 are reserved for the parity bits
 - The remaining bits are the data bits

Hamming Code

- 8-bit data word 110000100

- Include 4 parity bits and the 8-bit word \Rightarrow 12 bits

$$2^k - 1 \geq n + k, n = 8 \Rightarrow k = 4$$

Bit position: 1 2 3 4 5 6 7 8 9 10 11 12

P_1 P_2 1 P_4 1 0 0 P_8 0 1 0 0

- Calculate the parity bits: even parity — assumption

$$P_1 = \text{XOR of bits (3, 5, 7, 9, 11)} = 1 \oplus 1 \oplus 0 \oplus 0 \oplus 0 = 0$$

$$P_2 = \text{XOR of bits (3, 6, 7, 10, 11)} = 1 \oplus 0 \oplus 0 \oplus 1 \oplus 0 = 0$$

$$P_4 = \text{XOR of bits (5, 6, 7, 12)} = 1 \oplus 0 \oplus 0 \oplus 0 = 1$$

$$P_8 = \text{XOR of bits (9, 10, 11, 12)} = 0 \oplus 1 \oplus 0 \oplus 0 = 1$$

- Store the 12-bit composite word in memory.

Bit position: 1 2 3 4 5 6 7 8 9 10 11 12

0 0 1 1 1 0 0 1 0 1 0 0

Hamming Code

- When the 12 bits are read from the memory

- Check bits are calculated

$$C_1 = \text{XOR of bits (1, 3, 5, 7, 9, 11)}$$

$$C_2 = \text{XOR of bits (2, 3, 6, 7, 10, 11)}$$

$$C_4 = \text{XOR of bits (4, 5, 6, 7, 12)}$$

$$C_8 = \text{XOR of bits (8, 9, 10, 11, 12)}$$

- If no error has occurred

Bit position: 1 2 3 4 5 6 7 8 9 10 11
12

0 0 1 1 1 0 0 1 0 1 0 0

$$\Rightarrow C = C_8 C_4 C_2 C_1 = 0000$$

Hamming Code

- **One-bit error**

- **error in bit 1**


- $C_1 = \text{XOR of bits (1, 3, 5, 7, 9, 11)} = 1$
 - $C_2 = \text{XOR of bits (2, 3, 6, 7, 10, 11)} = 0$
 - $C_4 = \text{XOR of bits (4, 5, 6, 7, 12)} = 0$
 - $C_8 = \text{XOR of bits (8, 9, 10, 11, 12)} = 0$
 - $C_8C_4C_2C_1 = 0001$

- **error in bit 5**

- $C_8C_4C_2C_1 = 0101$


Read-Only Memory

 - Store permanent binary information
- $2^k \times n$ ROM
 - **k address input lines**
 - **enable input(s)**
 - **three-state outputs**



32 x 8 ROM

 - 5-to-32 decoder
- 8 OR gates
 - each has 32 inputs
- 32x8 internal programmable connections




Programmable Interconnections32

- close (two lines are connected)
- or open
- A fuse that can be blown by applying a high voltage pulse

Table 7.3
ROM Truth Table (Partial)

Inputs					Outputs							
I_4	I_3	I_2	I_1	I_0	A_7	A_6	A_5	A_4	A_3	A_2	A_1	A_0
0	0	0	0	0	1	0	1	1	0	1	1	0
0	0	0	0	1	0	0	0	1	1	1	0	1
0	0	0	1	0	1	1	0	0	0	1	0	1
0	0	0	1	1	1	0	1	1	0	0	1	0
		\vdots							\vdots			
1	1	1	0	0	0	0	0	0	1	0	0	1
1	1	1	0	1	1	1	1	0	0	0	1	0
1	1	1	1	0	0	1	0	0	1	0	1	0
1	1	1	1	1	0	0	1	1	0	0	1	1

 

Types of ROM

- **Types of ROM**
 - **mask programming ROM**
 - IC manufacturers
 - is economical only if large quantities
 - **PROM: Programmable ROM**
 - fuses
 - universal programmer
 - **EPROM: erasable PROM**
 - floating gate
 - ultraviolet light erasable
 - **EEPROM: electrically erasable PROM (E²PROM)**
 - longer time is needed to write
 - limited times of write operations
 - **Flash (like EEPROM)**

Combinational PLDs

- **Programmable two-level logic**
 - **an AND array and an OR array**

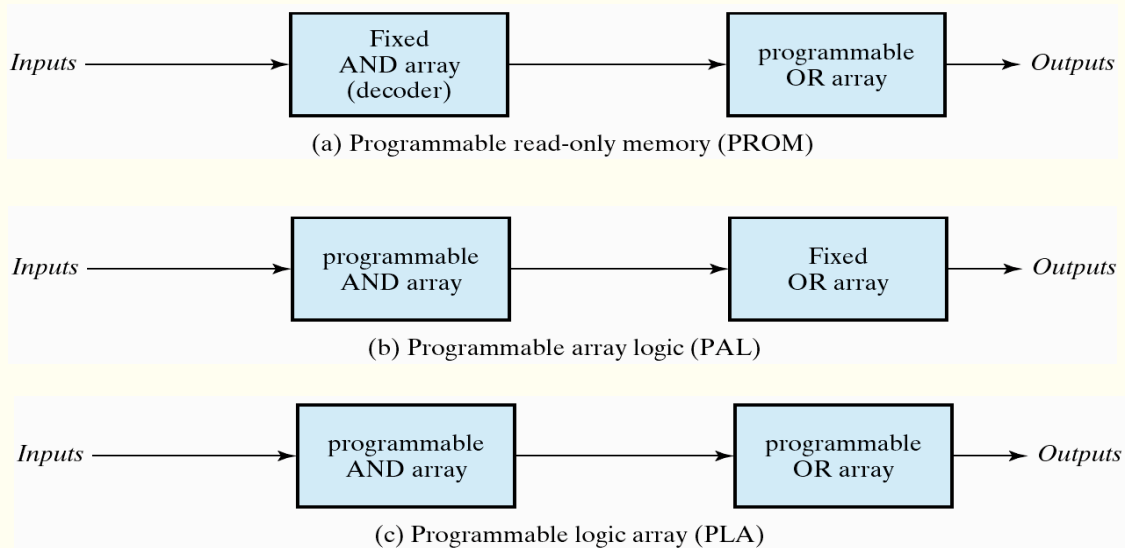


Fig. 7.13
Basic configuration of three PLDs


Sequential PLDs

Three types of sequential PLDs

- Simple programmable logic device (SPLD)
- Complex programmable logic device
(CPLD)
- Field programmable gate array (FPGA)

SPLD

A typical SPLD contains 8-10 macrocells

 

Field-Programmable Gate Arrays

- Logic blocks
 - To implement combinational and sequential logic
- Interconnect
 - Wires to connect inputs and outputs to logic blocks
- I/O blocks
 - Special logic blocks at periphery of device for external connections
- Key questions:
 - How to make logic blocks programmable?
 - How to connect the wires?
 - *After the chip has been fabbed*

