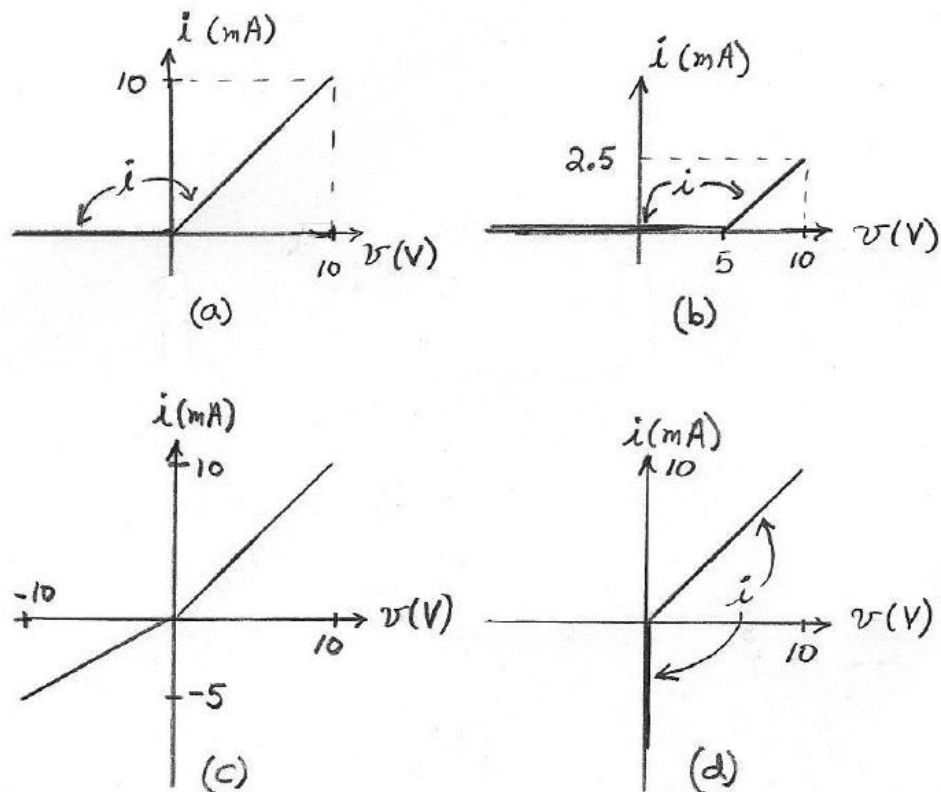


- P10.36*** (a) D_1 is on and D_2 is off. $V = 10$ volts and $I = 0$.
 (b) D_1 is on and D_2 is off. $V = 6$ volts and $I = 6$ mA.
 (c) Both D_1 and D_2 are on. $V = 30$ volts and $I = 33.6$ mA.

- P10.37** (a) The diode is on, $V = 0$ and $I = \frac{10}{5000} = 2$ mA.
 (b) The diode is off, $I = 0$ and $V = 5$ V.
 (c) The diode is on, $V = 0$ and $I = \frac{6}{3000} = 2$ mA.
 (d) The diode is on, $I = 3$ mA and $V = 6$ V.

P10.40



- P10.48** (a) Assuming that the diode is an open circuit, we can compute the node voltages using the voltage-division principle.

$$v_1 = 16 \frac{300}{100 + 300} = 12 \text{ V} \quad v_2 = 16 \frac{200}{200 + 200} = 8 \text{ V}$$

Then, the voltage across the diode is $v_D = v_1 - v_2 = 4$ V. Because v_D is greater than $V_f = 0.7$ V, the diode is in fact operating as an closed circuit.

(b) Assuming that the diode operates as a voltage source, we can use KVL to write:

$$v_1 - v_2 = 0.7$$

Placing a closed surface around the diode to form a super node and writing a KCL equation gives


$$\frac{v_1 - 16}{100} + \frac{v_1}{300} + \frac{v_2 - 16}{100} + \frac{v_2}{200} = 0$$

Solving these equations, we find $v_1 = 11.665$ V and $v_2 = 9.965$ V. Then, writing a KCL equation at node 1 gives the diode current.

$$i_D = \frac{16 - v_1}{100} - \frac{v_1}{300} = 4.47 \text{ mA}$$

Because the diode current is positive, the diode operation is consistent with the model.

P10.63

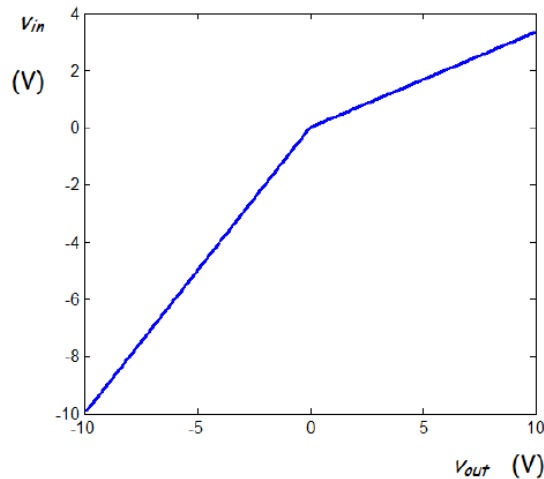

P10.64 Refer to Figure P10.64 in the book. When the source voltage is positive, diode D_3 is on and the output $v_o(t)$ is zero. For source voltages between 0 and 5 V, none of the diodes conducts and $v_o(t) = v_s(t)$. Finally, when the source voltage falls below -5 V, D_1 is on and D_2 is in the breakdown region so the output voltage is 5 V. The waveforms are:

