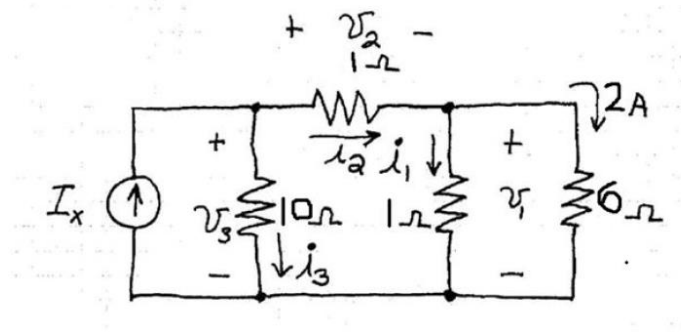


P1.42* Summing voltages for the lower left-hand loop, we have $-5 + v_a + 10 = 0$, which yields $v_a = -5$ V. Then for the top-most loop, we have $v_c - 15 - v_a = 0$, which yields $v_c = 10$ V. Finally, writing KCL around the outside loop, we have $-5 + v_c + v_b = 0$, which yields $v_b = -5$ V.

P1.69



Ohm's law for the $6\text{-}\Omega$ resistor yields: $v_1 = 12$ V. Then, we have $i_1 = v_1 / 1 = 12$ A. Next, KCL yields $i_2 = i_1 + 2 = 14$ A. Then for the top $2\text{-}\Omega$ resistor, we have $v_2 = 14 \times 1 = 14$ V. Using KVL, we have $v_3 = v_2 + v_1 = 26$ V. Next, applying Ohm's law, we obtain $i_3 = v_3 / 10 = 2.6$ A. Finally applying KCL, we have $I_x = i_2 + i_3 = 16.6$ A.


- P1.78**
- (a) $4 = i_1 + i_2$
 - (b) $i_1 = v / 15$
 $i_2 = v / 10$
 - (c) $4 = v / 15 + v / 10$
 $v = 24$ V
 - (d) $P_{\text{current source}} = -I_s v = -96$ W (Power is supplied by the source.)
 $P_1 = v^2 / R_1 = 38.4$ W (Power is absorbed by R_1 .)
 $P_2 = v^2 / R_2 = 57.6$ W (Power is absorbed by R_2 .)

However i_3 and i_y are the same current: $i_y = i_3$. Simplifying and solving, we find that $i_3 = i_y = 2.31$ A.

P2.4* The $12\text{-}\Omega$ and $6\text{-}\Omega$ resistances are in parallel having an equivalent resistance of $4\text{ }\Omega$. Similarly, the $18\text{-}\Omega$ and $9\text{-}\Omega$ resistances are in parallel and have an equivalent resistance of $6\text{ }\Omega$. Finally, the two parallel combinations are in series, and we have

$$R_{ab} = 4 + 6 = 10\text{ }\Omega$$

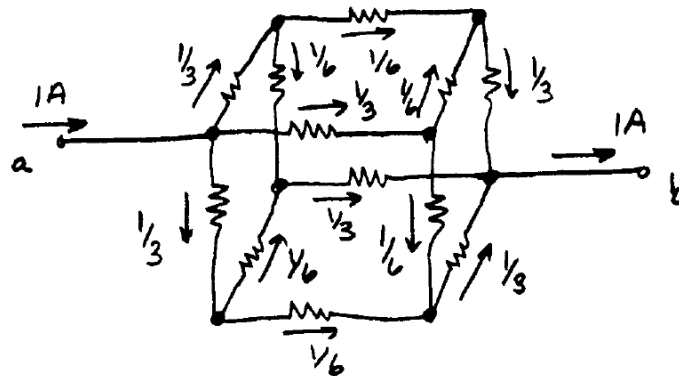P2.17 By symmetry, we find the currents in the resistors as shown below:




Then, the voltage between terminals a and b is

$$V_{ab} = R_{eq} = 1/3 + 1/6 + 1/3 = 5/6$$

P2.25* Combining resistors in series and parallel, we find that the equivalent resistance seen by the current source is $R_{eq} = 17.5\text{ }\Omega$.

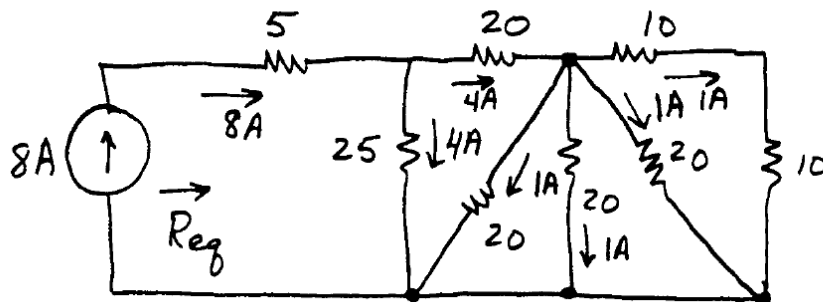Thus, $v = 8 \times 17.5 = 140\text{ V}$. Also, $i = 1\text{ A}$.



P2.34 $i = \frac{P}{v} = \frac{4.5\text{ W}}{15\text{ V}} = 0.3\text{ A}$ $R_{eq} = R + \frac{1}{1/R + 1/R} + R = 2.5R$

$$i = 0.3 = \frac{15}{R_{eq}} = \frac{15}{2.5R}$$

$$R = 20\text{ }\Omega$$

P2.51 Writing KCL equations at nodes 1, 2, and 3, we have

$$\frac{v_1}{R_4} + \frac{v_1 - v_2}{R_2} + \frac{v_1 - v_3}{R_1} = 0$$

$$\frac{v_2 - v_1}{R_2} + \frac{v_2 - v_3}{R_3} = I_s$$

$$\frac{v_3}{R_5} + \frac{v_3 - v_2}{R_3} + \frac{v_3 - v_1}{R_1} = 0$$

In standard form, we have:

$$0.6167v_1 - 0.20v_2 - 0.25v_3 = 0$$

$$-0.20v_1 + 0.325v_2 - 0.125v_3 = 4$$

$$-0.25v_1 - 0.125v_2 + 0.50v_3 = 0$$

Using Matlab, we have

$$G = [0.6167 \ -0.20 \ -0.25; \ -0.20 \ 0.325 \ -0.125; \ -0.25 \ -0.125 \ 0.500];$$

$$I = [0; \ 4; \ 0];$$

$$V = G \backslash I$$

$$V =$$

$$13.9016$$

$$26.0398$$

$$13.4608$$

P2.53* Writing a KVL equation, we have $v_1 - v_2 = 10$.

At the reference node, we write a KCL equation: $\frac{v_1}{5} + \frac{v_2}{10} = 1$.

Solving, we find $v_1 = 6.667$ and $v_2 = -3.333$.

Then, writing KCL at node 1, we have $i_s = \frac{v_2 - v_1}{5} - \frac{v_1}{5} = -3.333 \text{ A}$.

P2.58* $v_x = v_2 - v_1$

Writing KCL at nodes 1 and 2:

$$\frac{v_1}{5} + \frac{v_1 - 2v_x}{15} + \frac{v_1 - v_2}{10} = 1$$

$$\frac{v_2}{5} + \frac{v_2 - 2v_x}{10} + \frac{v_2 - v_1}{10} = 2$$

Substituting and simplifying, we have

$$15v_1 - 7v_2 = 30 \quad \text{and} \quad v_1 + 2v_2 = 20.$$

Solving, we find $v_1 = 5.405$ and $v_2 = 7.297$.