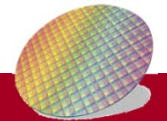




成功大學


National Cheng Kung University

Control Signal for Pipeline Processor




Outline

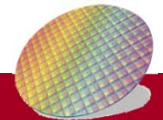- A pipelined datapath
- **Pipelined control**
- Data hazards and forwarding
- Data hazards and stalls
- Branch hazards



Pipeline Control


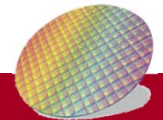
- Three steps are needed
 - Step 1: Begin with the same control signal with **single-cycle** datapath control
 - Group control lines into **five** groups according to pipeline stage
 - Since **control signals** are associated with **components** active during a single pipeline stage
 - **Set** control signals during **each** pipeline stage





Pipelined Datapath with Control – Step 1

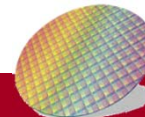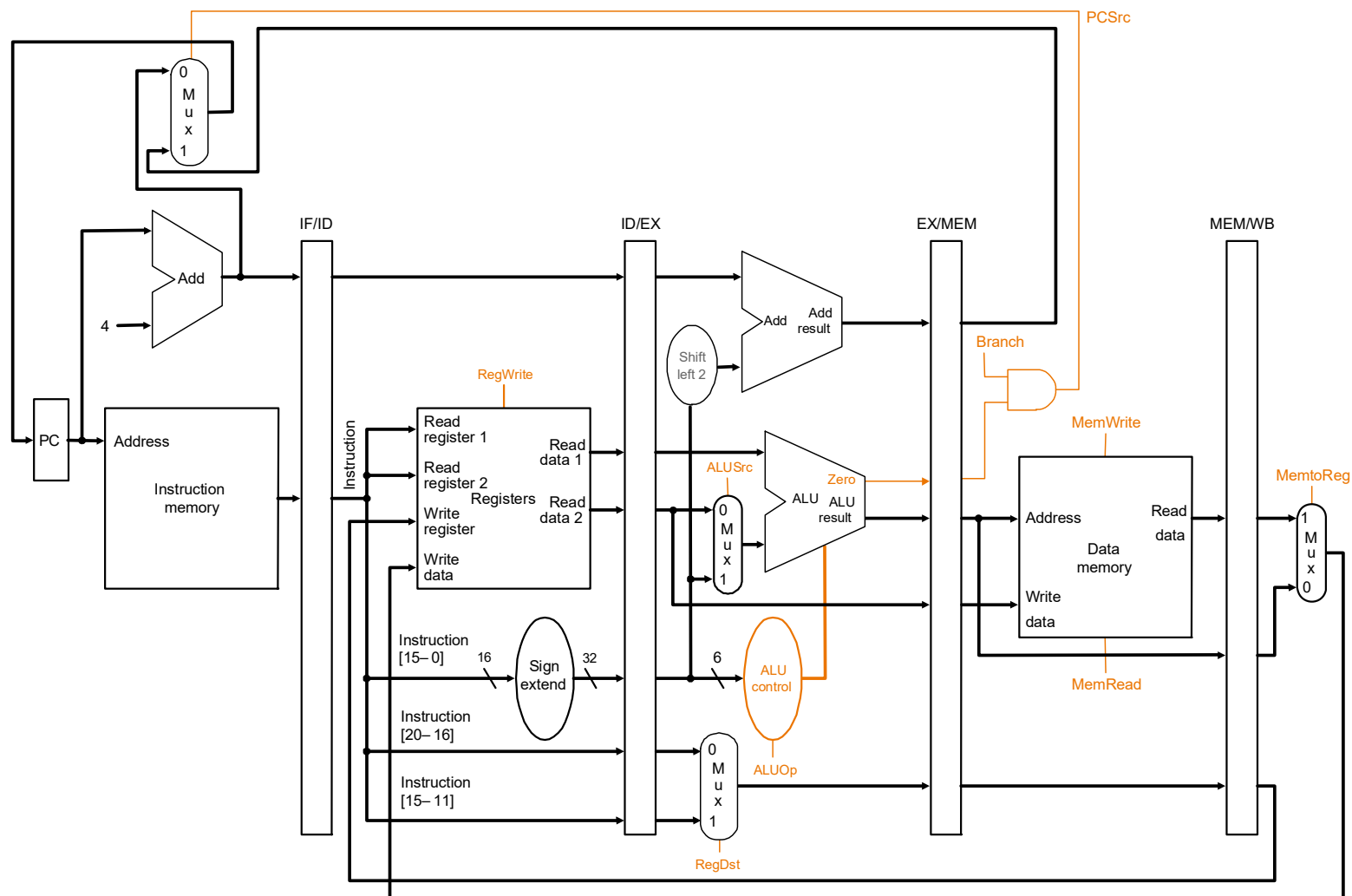Start with Same control signals as the single-cycle datapath



Pipeline Control Signals- Step 2


- Group control lines into **five** groups according to pipeline stage
 - instruction fetch / PC increment (IF)
 - instruction decode / register fetch (ID)
 - execution / address calculation (**EX**)
 - memory access (**M**)
 - write back (**WB**)
- } **Nothing to control as instruction memory read and PC write are always enabled**
 } (the following table)

Instruction	Execution/Address Calculation stage control lines				Memory access stage control lines			Write-back stage control lines	
	Reg Dst	ALU Op1	ALU Op0	ALU Src	Branch	Mem Read	Mem Write	Reg write	Mem to Reg
R-format	1	1	0	0	0	0	0	1	0
lw	0	0	0	1	0	1	0	1	1
sw	X	0	0	1	0	0	1	0	X
beq	X	0	1	0	1	0	0	0	X




Pipeline Control Implementation

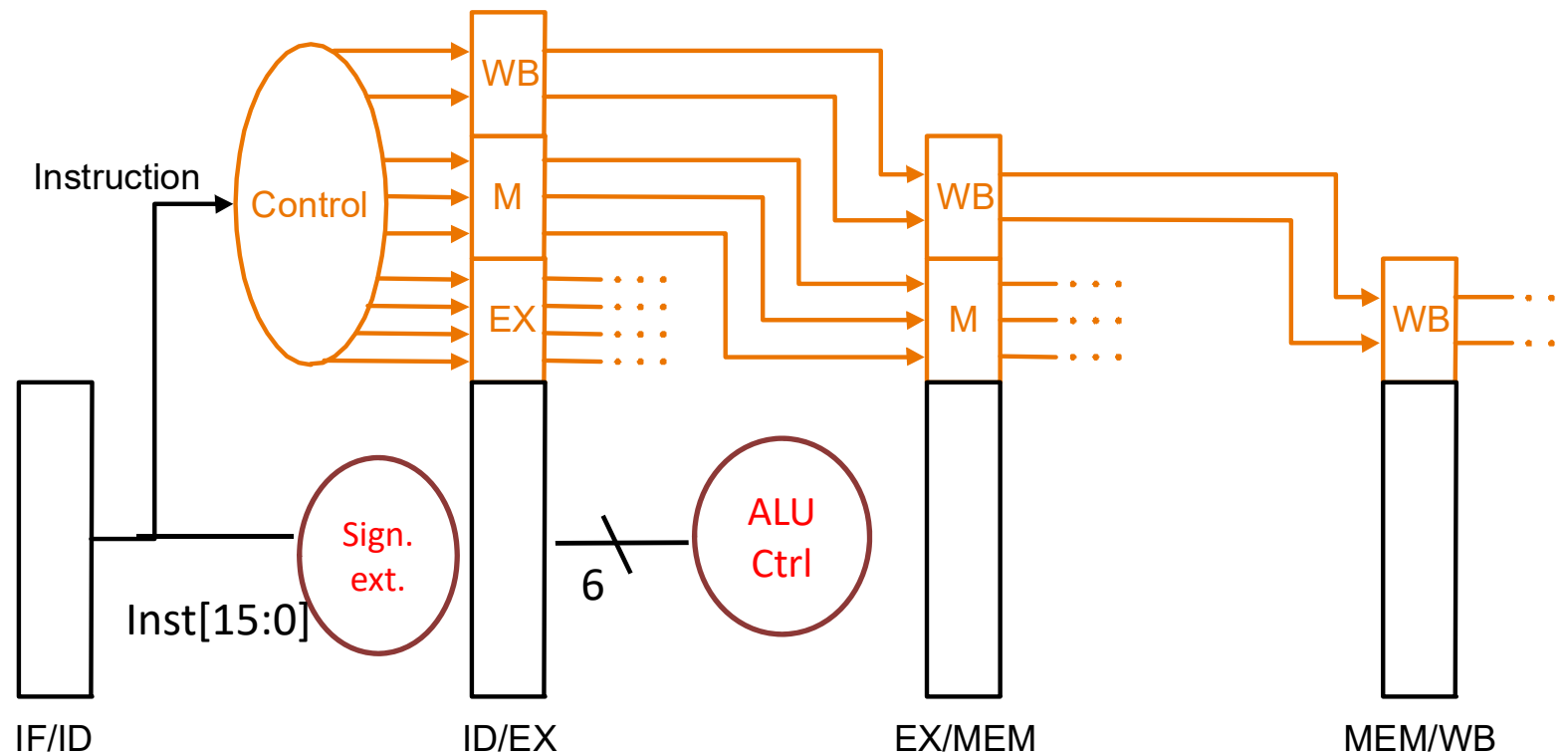- *Pass control signals along just like the data* – extend each pipeline register to hold needed control bits for succeeding stages





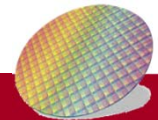- *Note:* The 6-bit *funct* field of the instruction required in the EX stage to generate ALU control can be retrieved as the 6 least significant bits of the immediate field which is sign-extended and passed from the IF/ID register to the ID/EX register





Pipelined Datapath with Control – Step 3

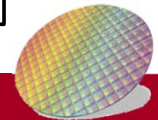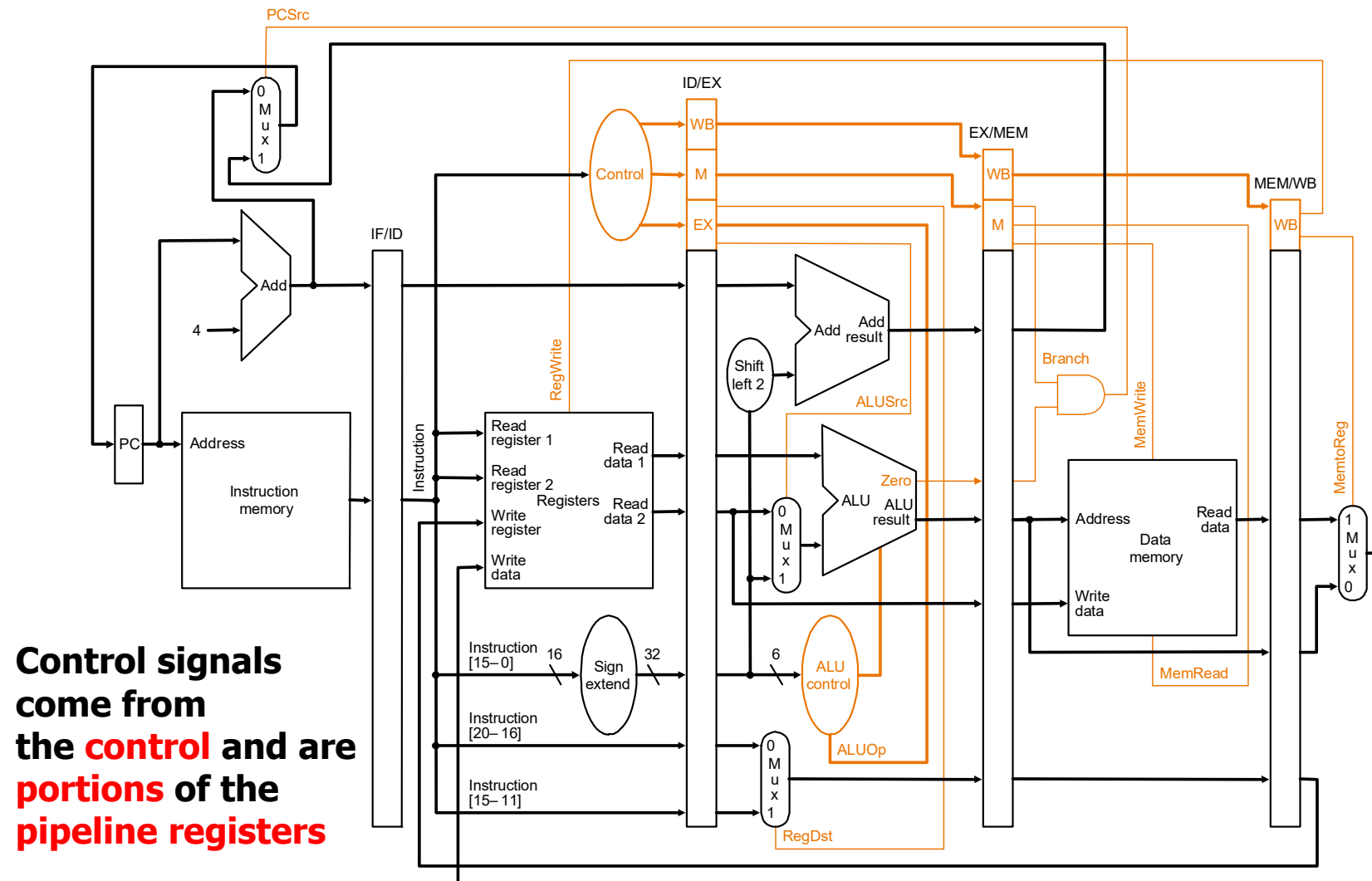

An Example


lw \$10, 20(\$1)

sub \$11, \$2, \$3


and \$12, \$4, \$5

or \$13, \$6, \$7

add \$14, \$8, \$9


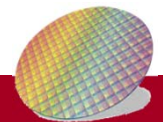



```
lw $10, 20($1)
sub $11, $2, $3
and $12, $4, $5
or $13, $6, $7
add $14, $8, $9
```

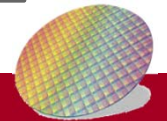



Cycle 2

```
lw $t0, 20($t1)
sub $t1, $t2, $t3
and $t2, $t4, $t5
or $t3, $t6, $t7
add $t4, $t8, $t9
```

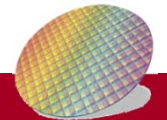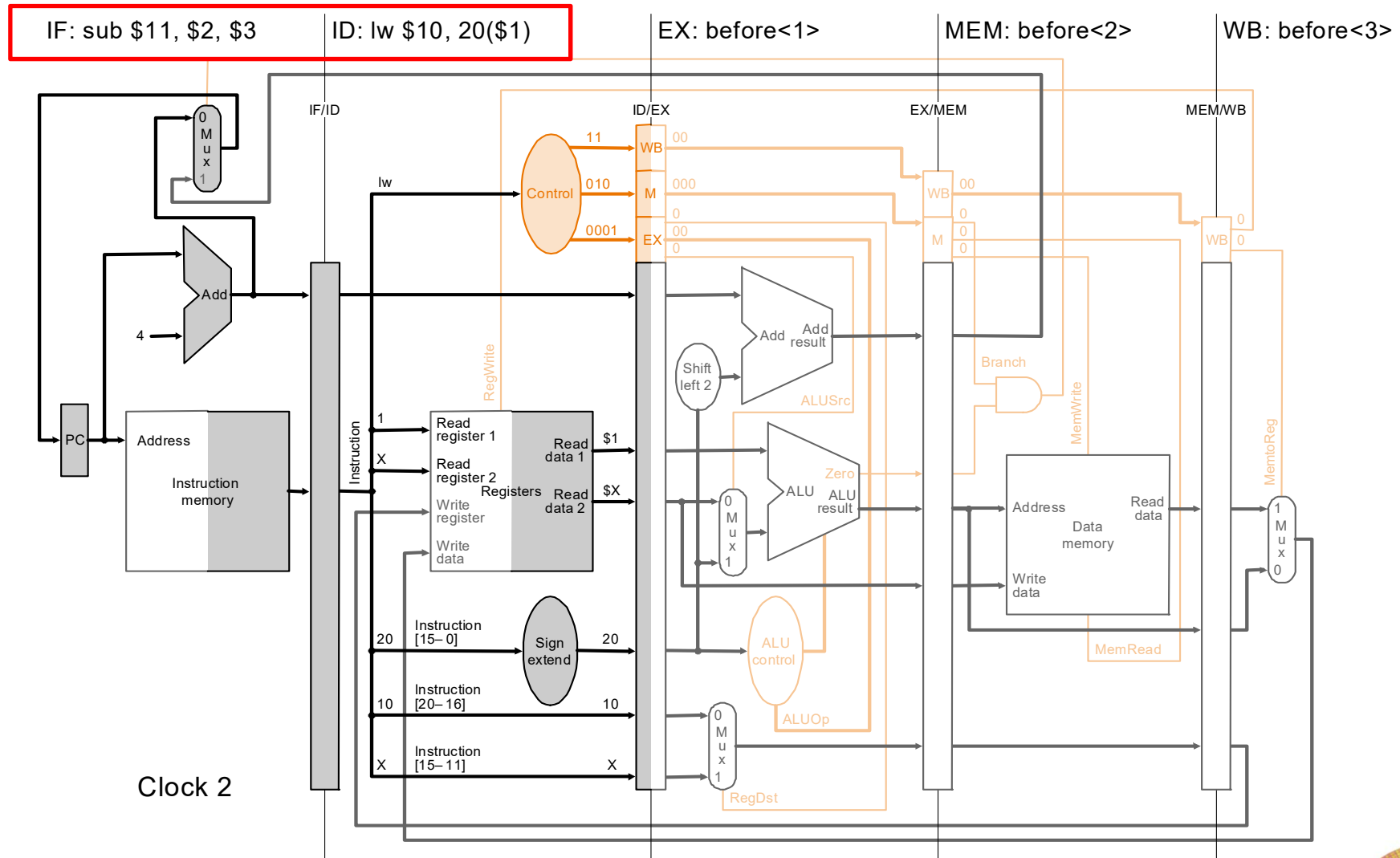



Cycle 3

```
lw $10, 20($1)
sub $11, $2, $3
and $12, $4, $5
or $13, $6, $7
add $14, $8, $9
```

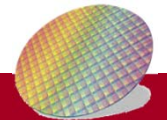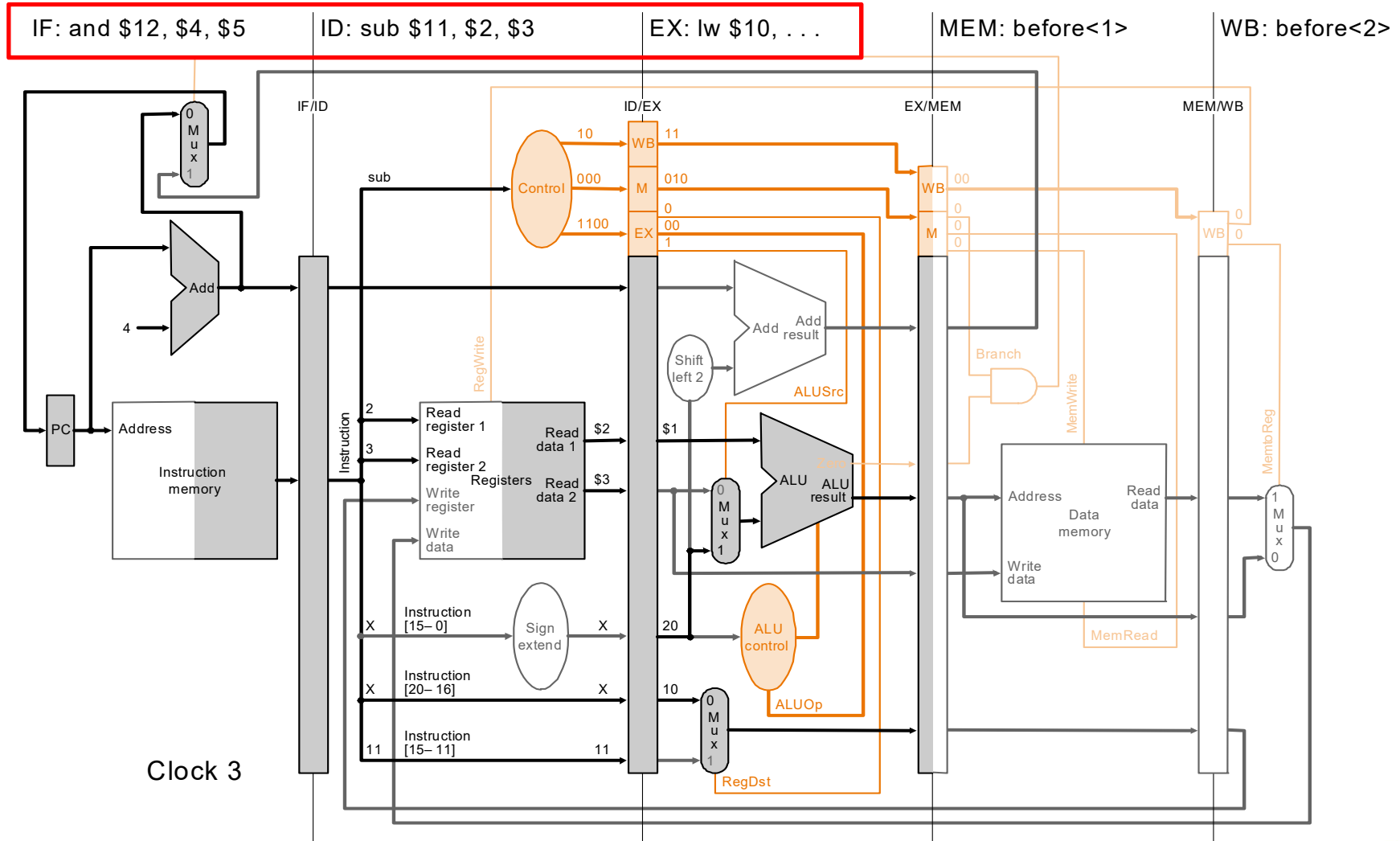



Cycle 4

```
lw $10, 20($1)
sub $11, $2, $3
and $12, $4, $5
or $13, $6, $7
add $14, $8, $9
```

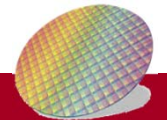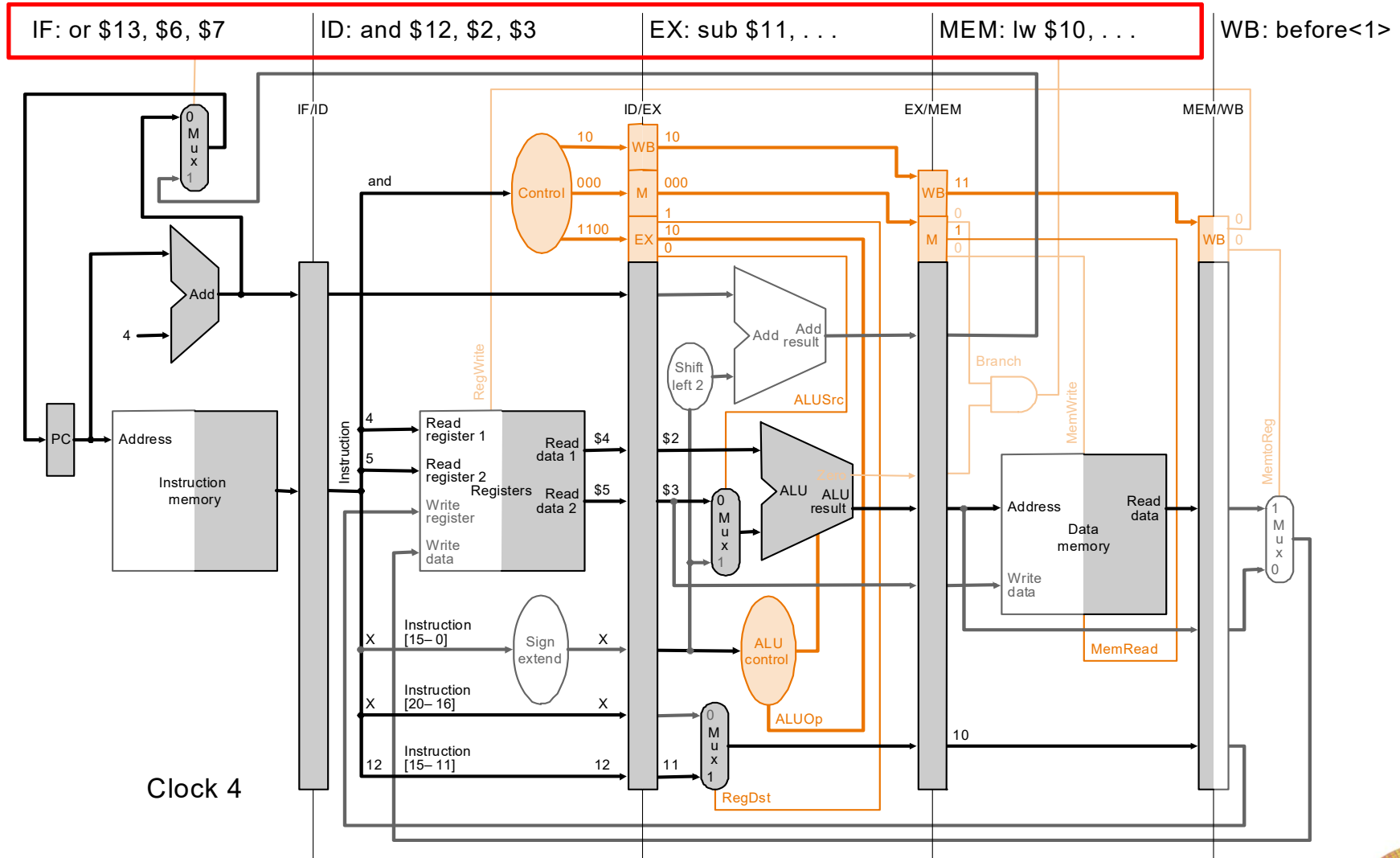

Cycle 5

```
lw $10, 20($1)
sub $11, $2, $3
and $12, $4, $5
or $13, $6, $7
add $14, $8, $9
```

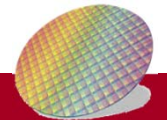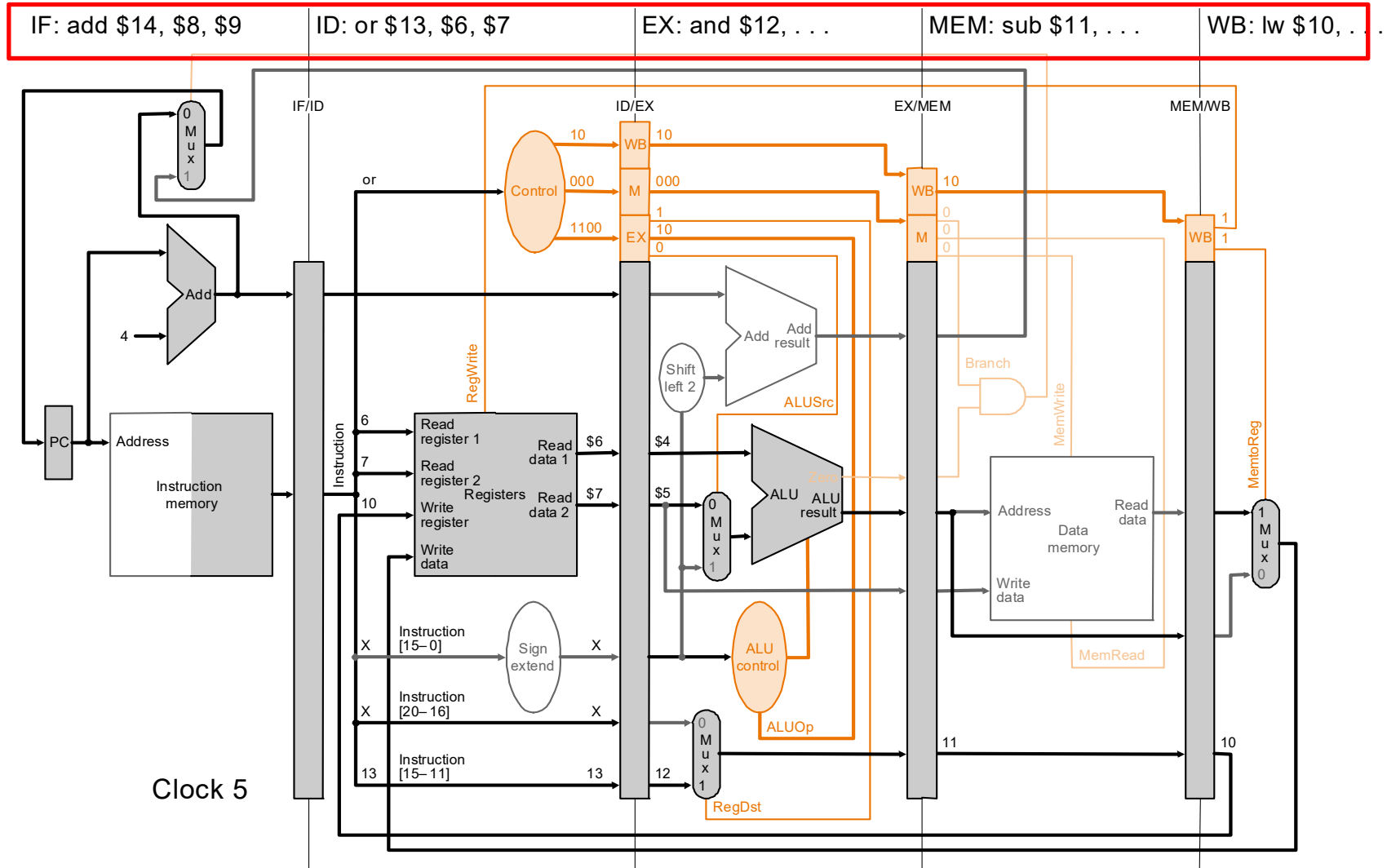

Cycle 6

```
lw $10, 20($1)
sub $11, $2, $3
and $12, $4, $5
or $13, $6, $7
add $14, $8, $9
```



IF: after<1>

ID: add \$14, \$8, \$9

EX: or \$13, ...



MEM: and \$12, ...

WB: sub \$11, ...

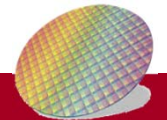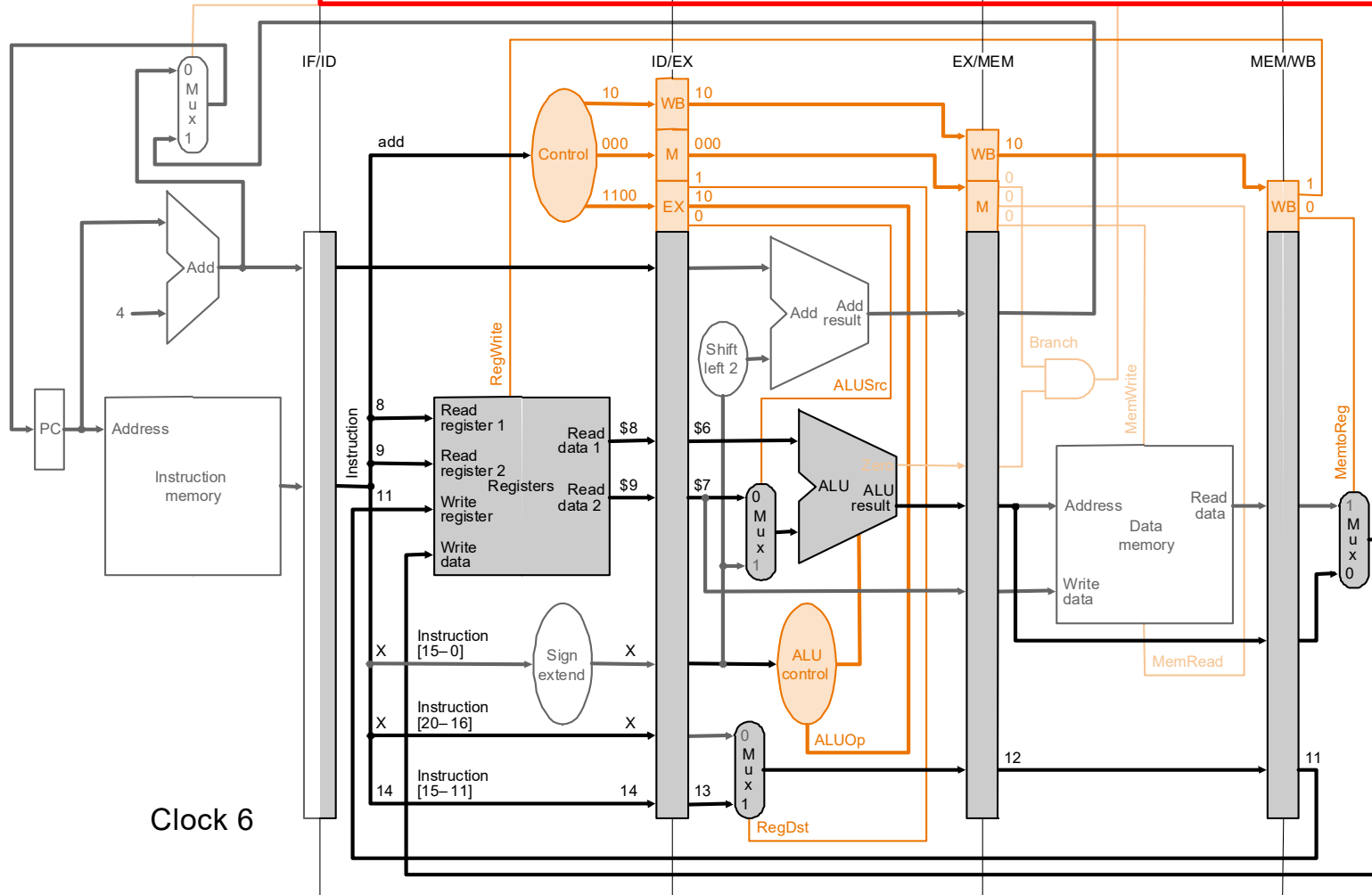



Cycle 7

```
lw $t0, 20($t1)
sub $t1, $t2, $t3
and $t2, $t4, $t5
or $t3, $t6, $t7
add $t4, $t8, $t9
```

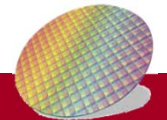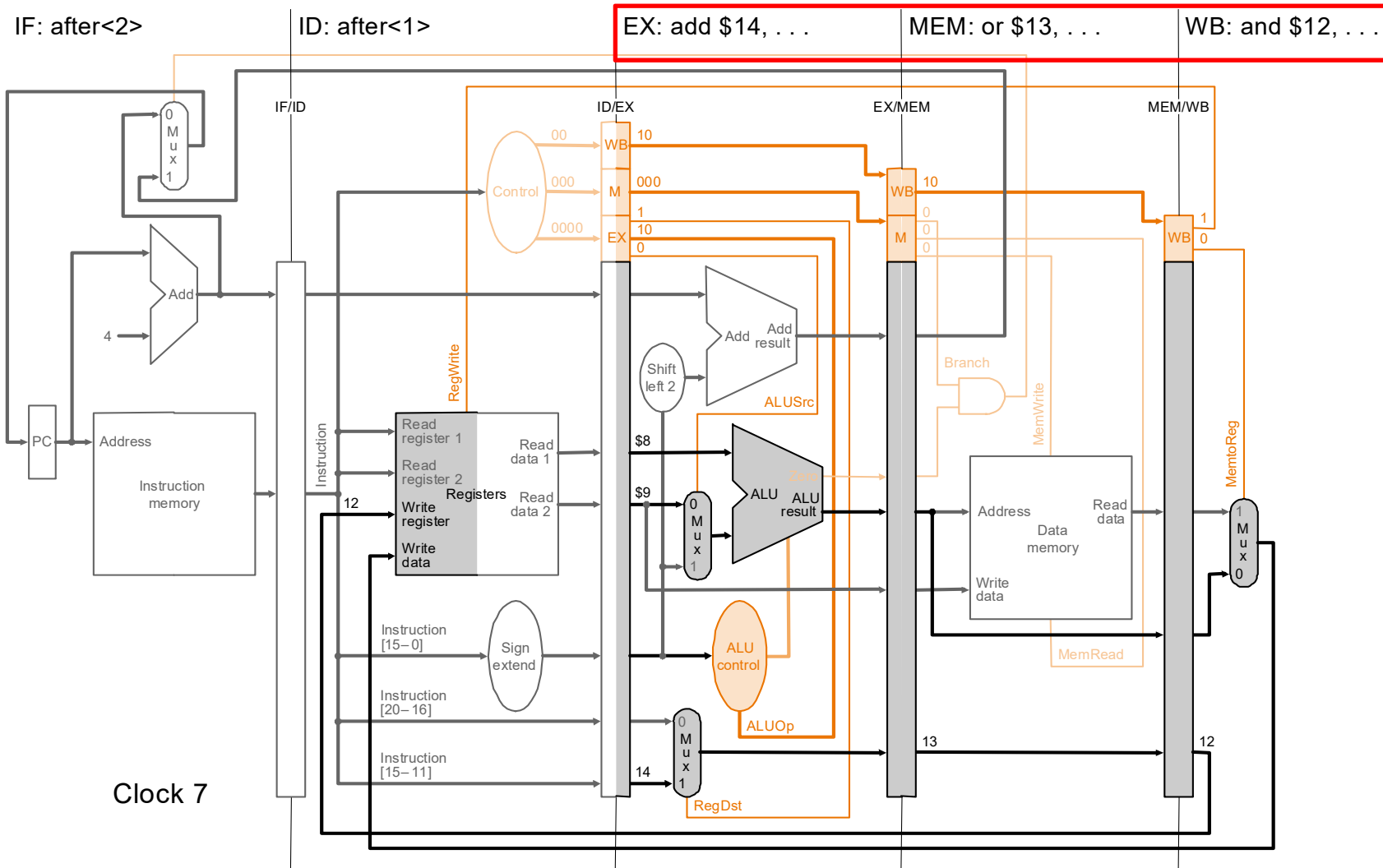



Cycle 8

```
lw $10, 20($1)
sub $11, $2, $3
and $12, $4, $5
or $13, $6, $7
add $14, $8, $9
```

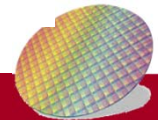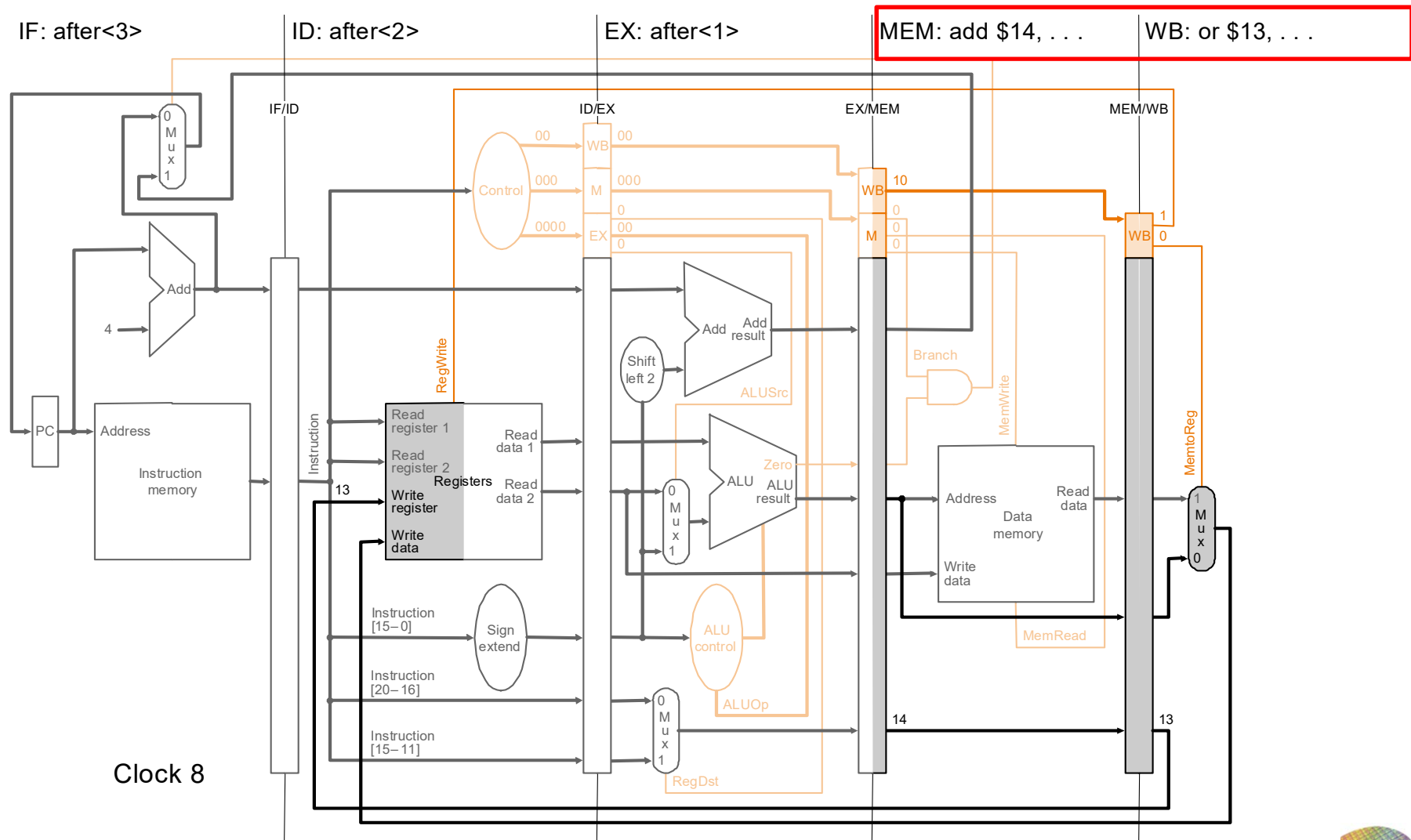


Cycle 9
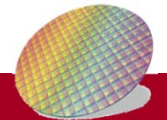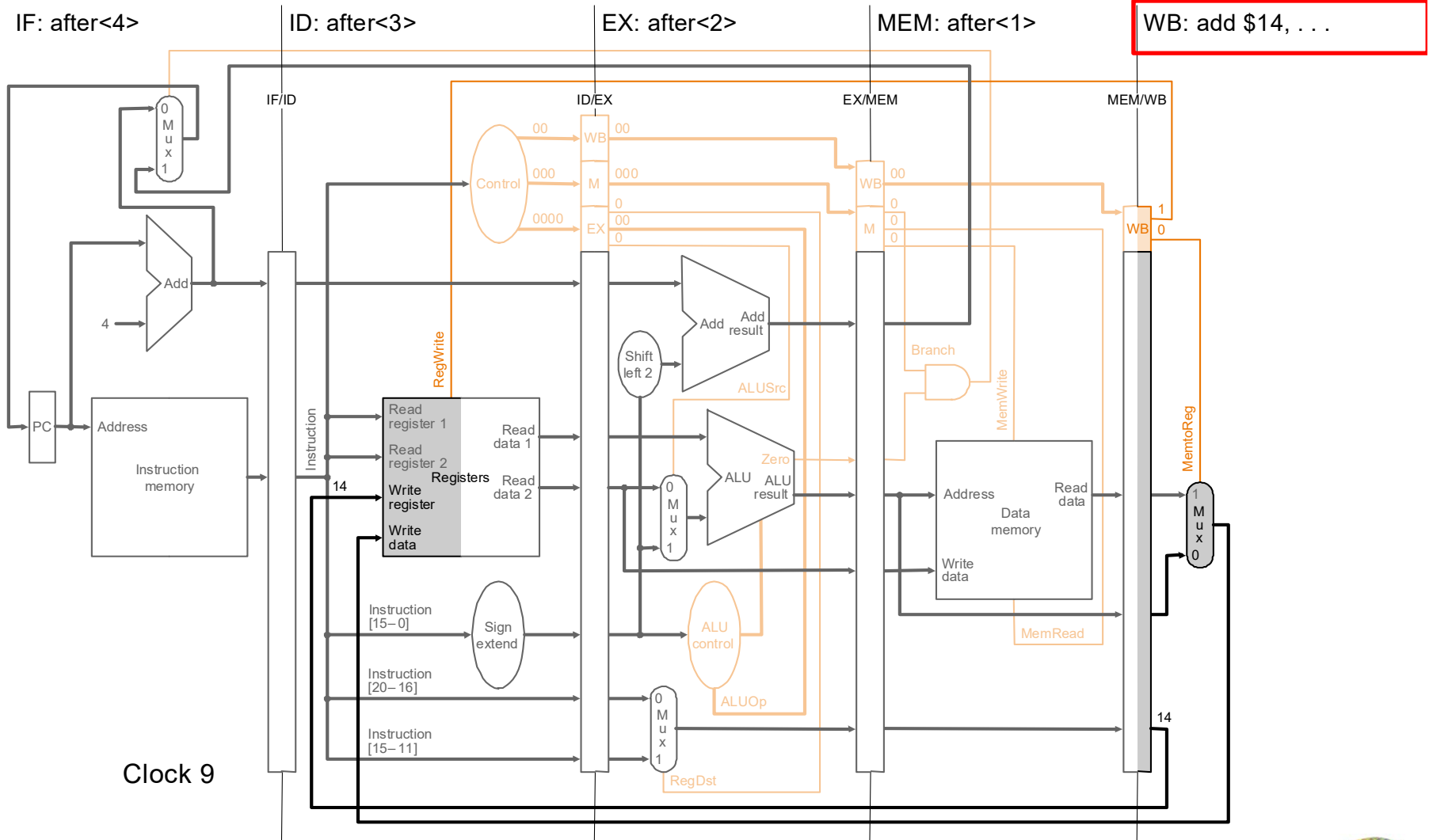
```
lw $t0, 20($t1)
sub $t1, $t2, $t3
and $t2, $t4, $t5
or $t3, $t6, $t7
add $t4, $t8, $t9
```





Outline

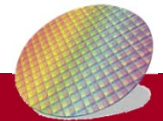- A pipelined datapath
- Pipelined control
- Data hazards and forwarding
- Data hazards and stalls
- Branch hazards



Pipeline Hazards

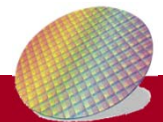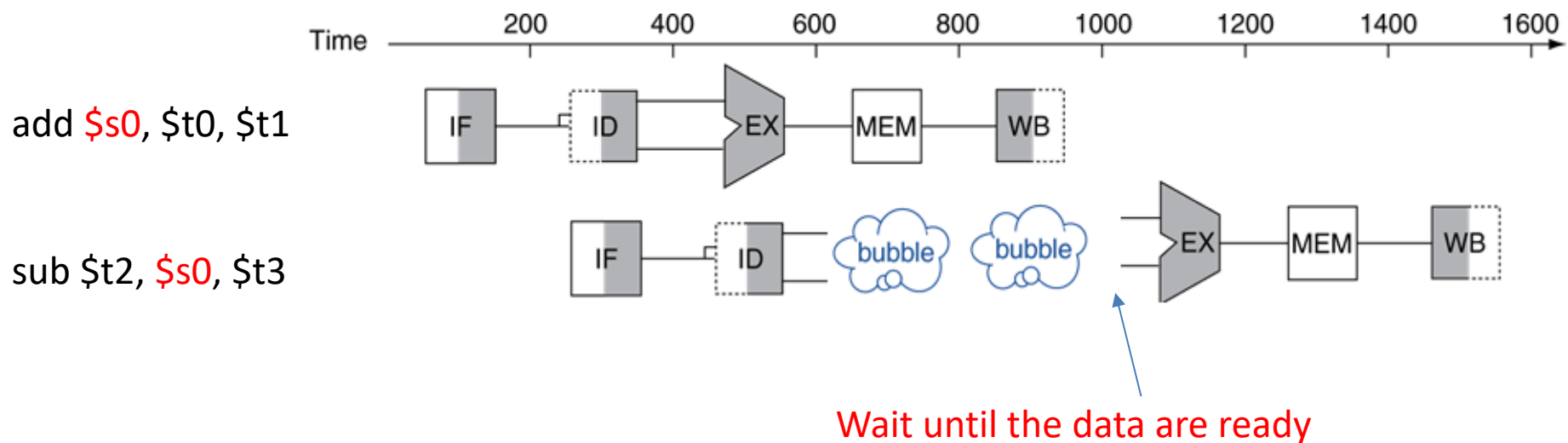- Pipeline Hazards:
 - Structural hazards, Data hazards, Control hazards
- Hazards can be resolved by **waiting (add stalls/bubble)**
 - pipeline control must detect the hazard
 - take action (or delay action) to resolve hazards




Data Hazards in ALU Instructions

- Consider this sequence:



```
sub $2, $1, $3  
and $12, $2, $5  
or  $13, $6, $2  
add $14, $2, $2  
sw  $15, 100($2)
```

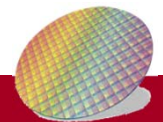- We can resolve hazards with forwarding
 - How do we detect when to forward?





Data Hazards

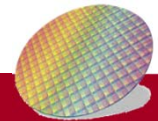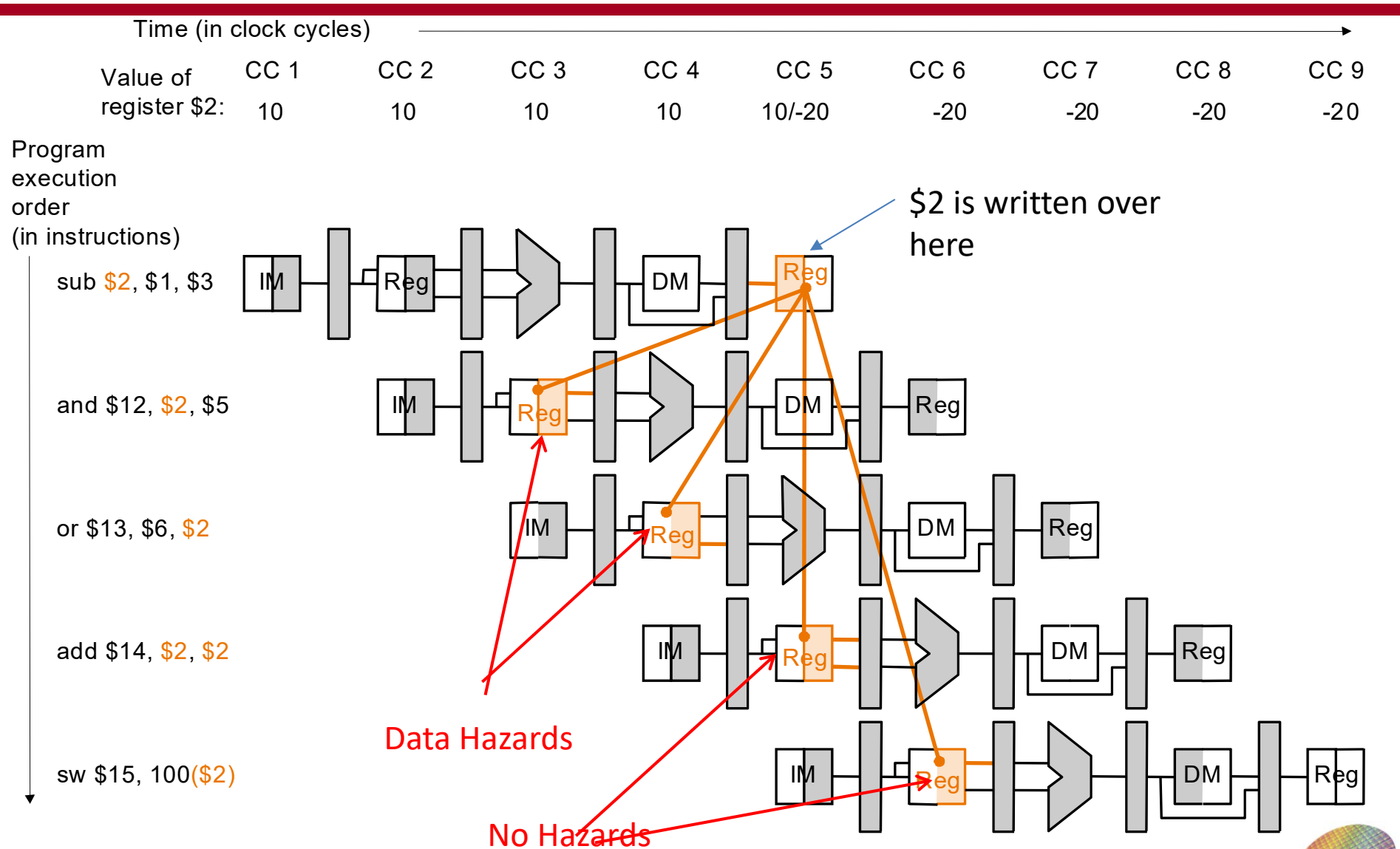



Three Types of Data Dependency (RAW, WAR, WAW)

- RAW (read after write):

i2 tries to read operand before i1 writes it



*RAW is Data
Dependence
also cause data
hazard*


W R R
sub \$2 \$1 \$3
add \$4 \$3 \$2
W R R

- WAR (write after read):


i2 tries to write operand before i1 reads it

add \$4 \$2 \$3
sub \$2 \$1 \$3

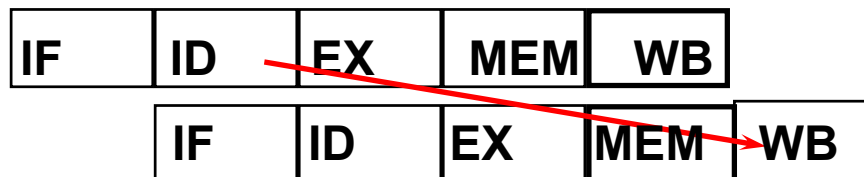- WAR is **not** a issue in MIPS 5-stage pipeline because all instructions take 5 stages, and reads are always in stage 2, and writes are always in stage 5, the following instruction never corrupt the previous instruction



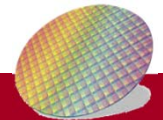*Do not cause stall !!!
WAR is not data hazard*






Types of Data Dependency (RAW, WAR, WAW)

Three types: (inst. **i1** followed by inst. **i2**)

- **WAW (write after write):**

i2 tries to write operand before **i1** writes it

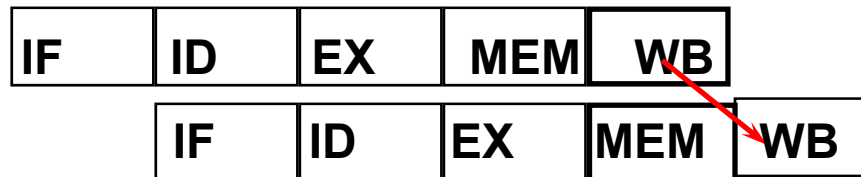- WAW is not an issue in MIPS 5-stage pipeline because all instructions take 5 stages, and writes are always in stage 5




Do not cause stall !!!
WAW is not data hazard

Quick summary:

Three data dependency: **RAW**, **WAR**, **WAW**

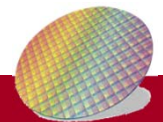only **RAW** may cause data hazard in MIPS



Exercise

- Identify the data dependency (RAW, WAW, WAR) in the following instruction

Ans:


lw \$1,40(\$6)
add \$6, \$2, \$2
sw \$6, 50(\$1)

lw \$1,40(\$6)
W R
add \$6, \$2, \$2
W R R
sw \$6, 50(\$1)
R R

I1 to I2: WAR on \$6


I1 to I3: RAW on \$1

I2 to I3: RAW on \$6

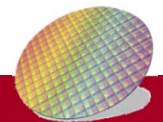

Hardware Solution: Forwarding

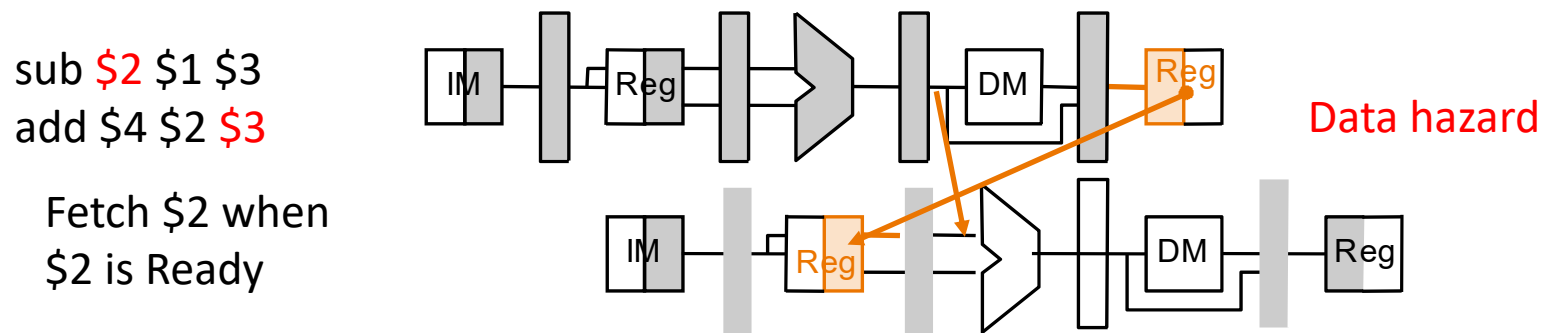- Idea: fetch “fresh” data as early as possible




- Two steps:

Step 1: **Detect** data hazard:

Is the datum just produced required by the following inst.?



Step 2: **Forward** intermediate data to resolve hazard

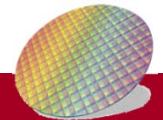If yes, then forward the requested datum to the requesting inst. immediately.







Data Hazards

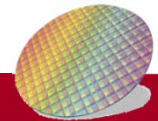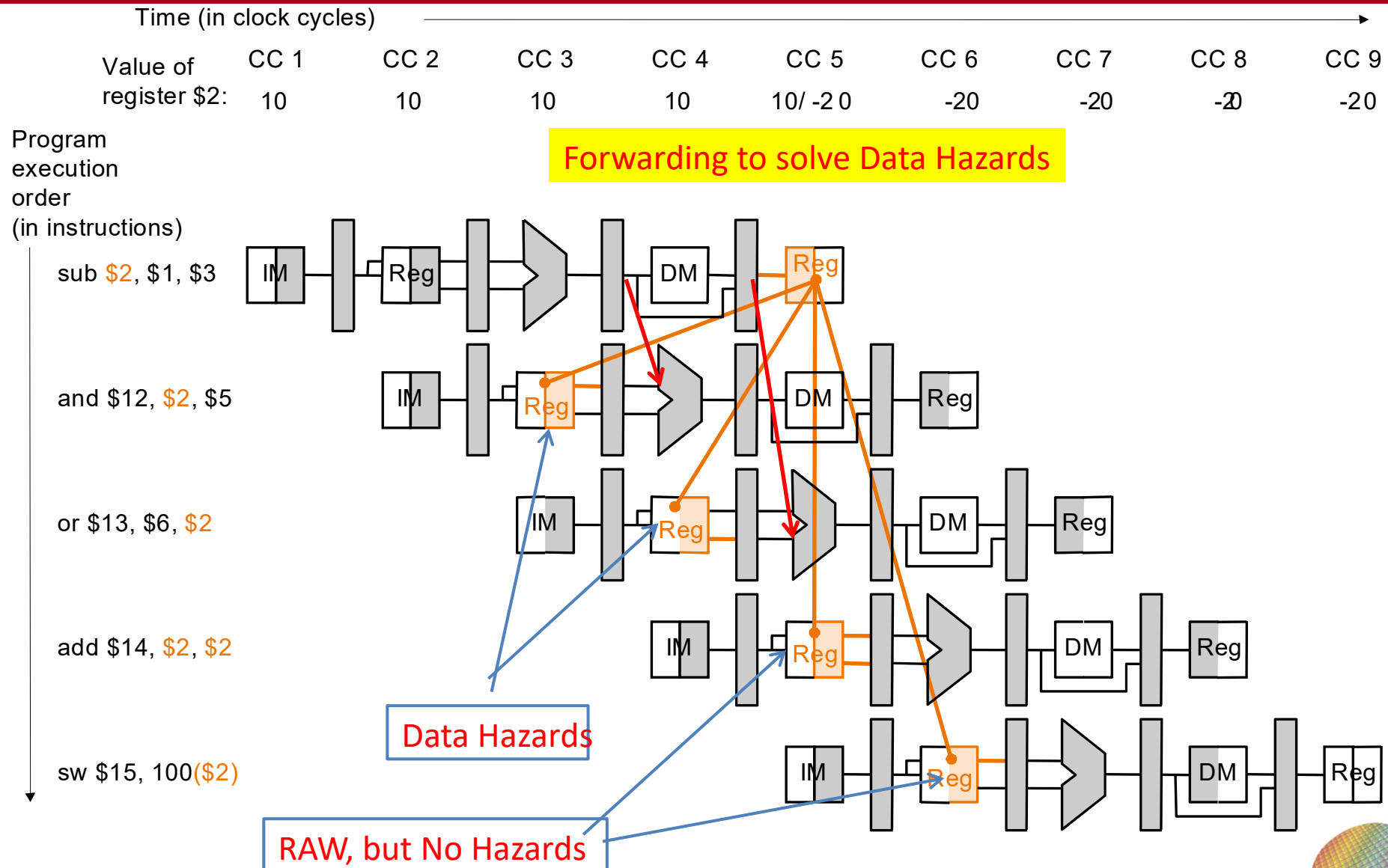



Forwarding Hardware: Multiplexor Control

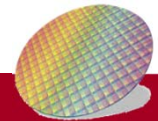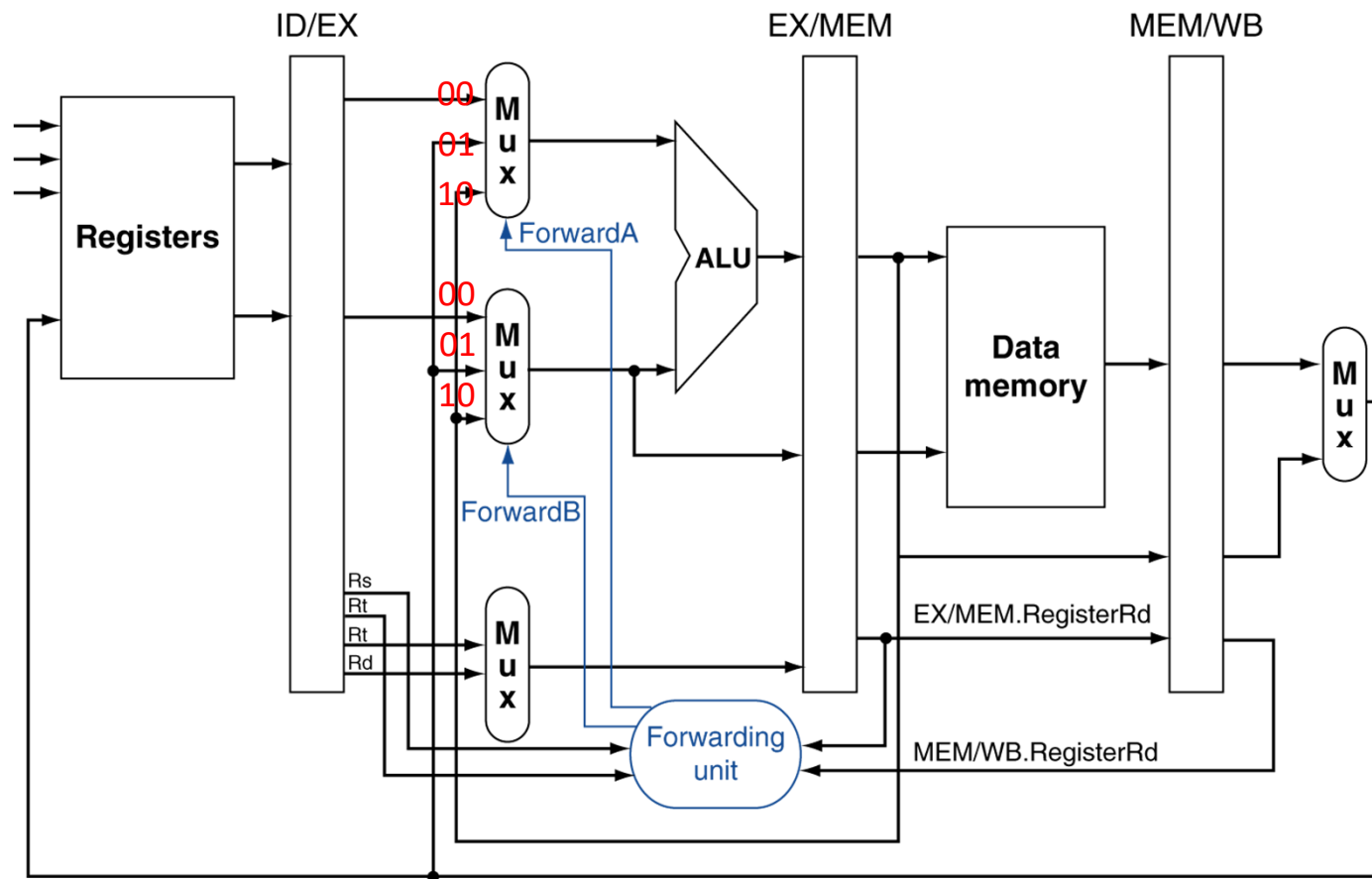- Add **Forwarding unit** and **ForwardA** and **ForwardB** control signal to control mux (See next slides)






Forwarding Hardware: Multiplexor Control

Mux control Source Explanation

ForwardA = 00	ID/EX	The first ALU operand (Rs) comes from the register file
ForwardA = 10	EX/MEM	The first ALU operand is forwarded from prior ALU result
ForwardA = 01	MEM/WB	* The first ALU operand is forwarded from data memory or an earlier ALU result



ForwardB = 00	ID/EX	The second ALU operand (Rt) comes from the register file
ForwardB = 10	EX/MEM	The second ALU operand is forwarded from prior ALU result
ForwardB = 01	MEM/WB	* The second ALU operand is forwarded from data memory or an earlier ALU result

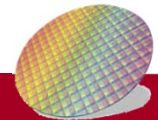* Depending on the selection in the rightmost multiplexor (see datapath with control diagram)



Detecting the Need to Forward

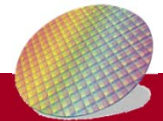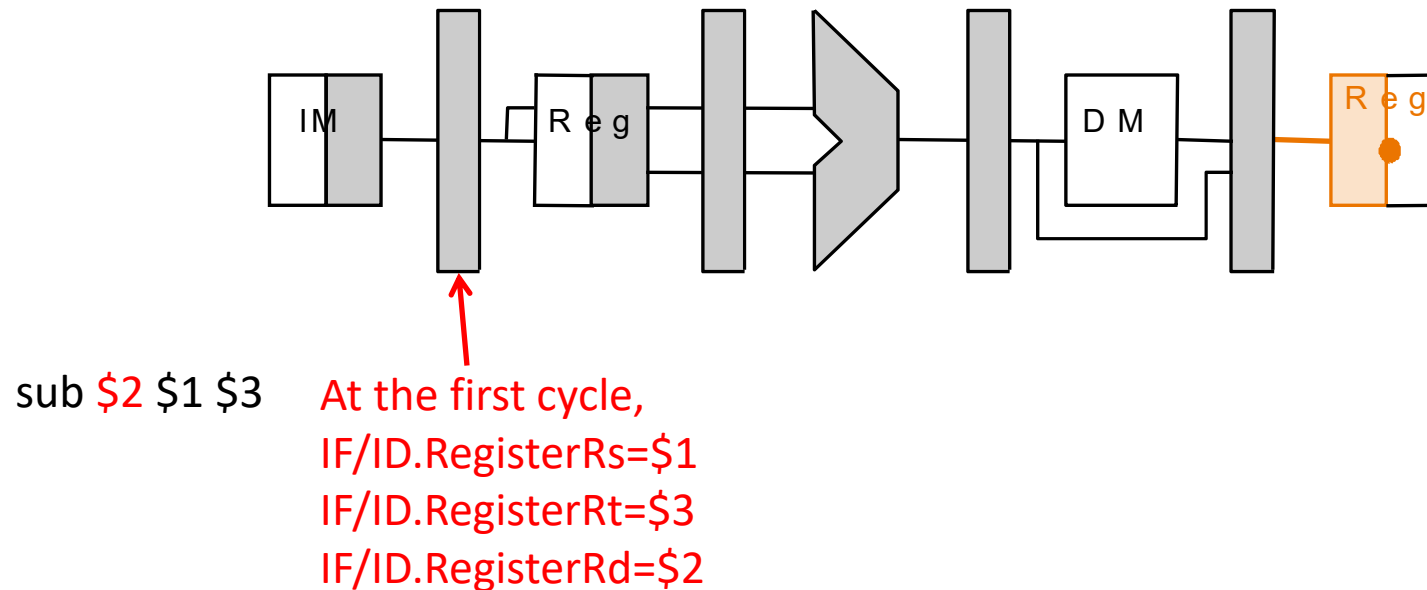- **Register numbers** are passed along pipeline
 - e.g., **ID/EX.RegisterRs** = register number for **Rs** sitting in **ID/EX** pipeline register
- E.g.: ALU operand **register numbers** in EX stage are given by
 - ID/EX.Register**Rs**, ID/EX.Register**Rt**





Detecting hazard- EX and MEM hazard

- Data hazards when

1a. EX/MEM.RegisterR_d = ID/EX.RegisterR_s


1b. EX/MEM.RegisterR_d = ID/EX.RegisterR_t

2a. MEM/WB.RegisterR_d = ID/EX.RegisterR_s

2b. MEM/WB.RegisterR_d = ID/EX.RegisterR_t

Fwd from
EX/MEM
pipeline reg


Fwd from
MEM/WB
pipeline reg

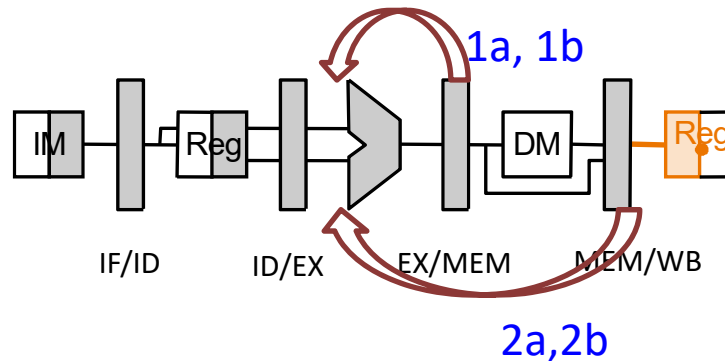

```
sub $2, $1, $3  
and $12, $2, $5
```

Hazard is detected when the **and** is in EX stage and the **sub** is in MEM stage because

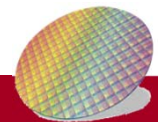EX/MEM.RegisterR_d = ID/EX.RegisterR_s = \$2 (1a)





Detecting EX hazard and forward

- Forwarding is needed if **earlier** instruction **write** to a register!
 - Check if EX/MEM.RegWrite, MEM/WB.RegWrite is 1

```
Inst1 sub $2, $1, $3
Inst2 and $12, $2, $5
```

Forwarding is needed if **Rd** is not **\$zero**

If **Rd=\$zero**, result is always 0

Check if EX/MEM.RegisterRd \neq 0, MEM/WB.RegisterRd \neq 0


```
Inst1 sub $2, $1, $3
Inst2 and $0, $2, $5
```

**Inst 1 does not
need to forward to
inst2 because inst2
always produce 0
(\$zero)**

Summary for EX hazard

If(**EX/MEM.RegWrite** and (EX/MEM.RegisterRd !=0)
and (EX/MEM.RegisterRd=ID/EX.Register**Rs**)) **ForwardA=10**

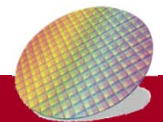If(**EX/MEM.RegWrite** and (EX/MEM.RegisterRd !=0)
and (EX/MEM.RegisterRd=ID/EX.Register**Rt**)) **ForwardB=10**




Detecting hazard – MEM hazard (1)



- MEM hazards when

2a. MEM/WB.RegisterR_d = ID/EX.RegisterR_s

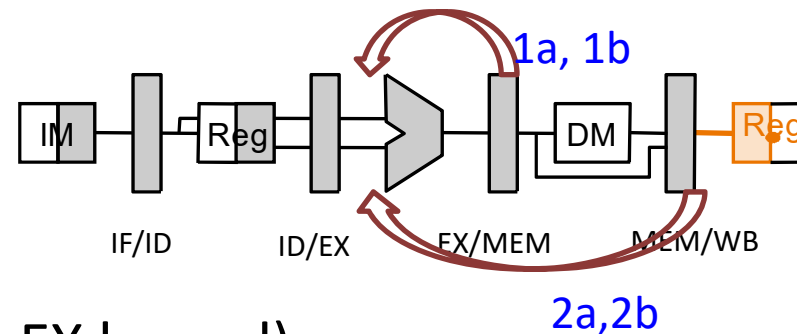2b. MEM/WB.RegisterR_d = ID/EX.RegisterR_t




Fwd from
EX/MEM
pipeline reg

Fwd from
MEM/WB
pipeline reg

Version 1 (similar to EX hazard)

If(MEM/WB.RegWrite
and (MEM/WB.RegisterR_d != 0)
and (MEM/WB.RegisterR_d = ID/EX.RegisterR_s)) ForwardA = 01

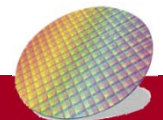If(MEM/WB.RegWrite
and (MEM/WB.RegisterR_d != 0)
and (MEM/WB.RegisterR_d = ID/EX.RegisterR_t)) ForwardB = 01






Additional rule for MEM hazard

- Forwarding is not needed if the later instruction is going to write the same register, even if there is register number match as in conditions above


Inst1 **add \$7, \$7, \$9**
Inst2 **add \$7, \$7, \$10**
Inst3 **add \$7, \$7, \$11**

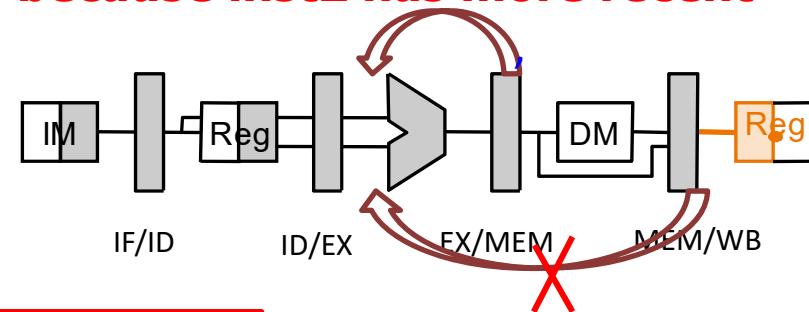Inst 1 does not need to forward to inst 3 because inst2 has more recent data




If(MEM/WB.RegWrite
and (MEM/WB.RegisterRd !=0)
and **not (EX/MEM.RegWrite and (EX/MEM.RegisterRd != 0))**
and **(EX/MEM.RegisterRd != ID/EX.RegisterRs)**
and (MEM/WB.RegisterRd=ID/EX.RegisterRs)) **ForwardA =01**

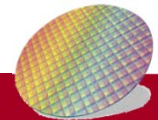If(MEM/WB.RegWrite
and (MEM/WB.RegisterRd !=0)
and **not (EX/MEM.RegWrite and (EX/MEM.RegisterRd != 0))**
and **(EX/MEM.RegisterRd != ID/EX.RegisterRt)**
and (MEM/WB.RegisterRd=ID/EX.RegisterRt) **ForwardB=01**



Outline

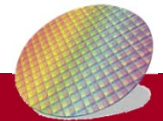- A pipelined datapath
- Pipelined control
- Data hazards and forwarding
- Data hazards and stalls
- Branch hazards




Load-Use Data Hazard

- One **stall** is needed for load-use data hazard
=> similar to add a nop (no operation) instruction


```
lw  $2, 20($1)
and $4, $2, $5
```


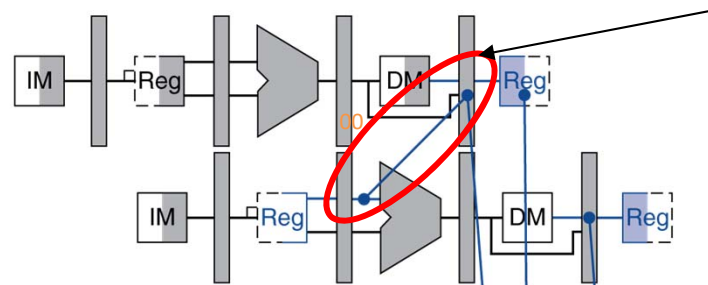
```
lw  $2, 20($1)
nop
and $4, $2, $5
```




Need to stall
one cycle

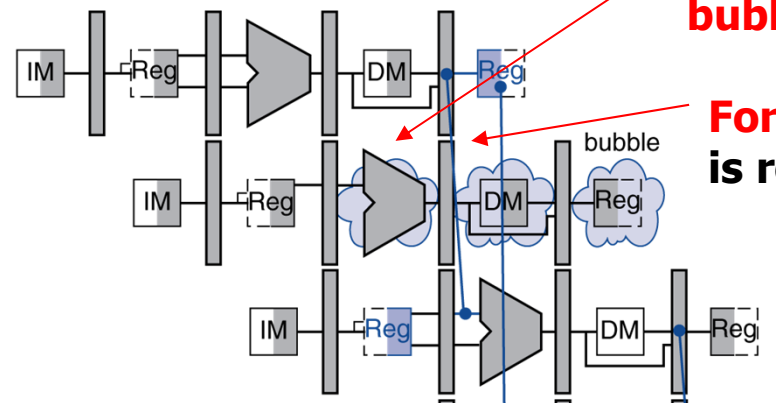

Hazard detection unit
**inserts a 1-cycle
bubble** in the pipeline

Forward data when it
is ready

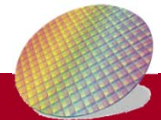



Hazard Detection Logic to Stall

- Recall: lw instruction format: `lw Rt, offset(Rs)`
- Hardware to check if **stall** is needed

Destination Register in lw instruction.



```

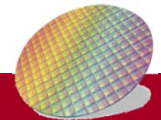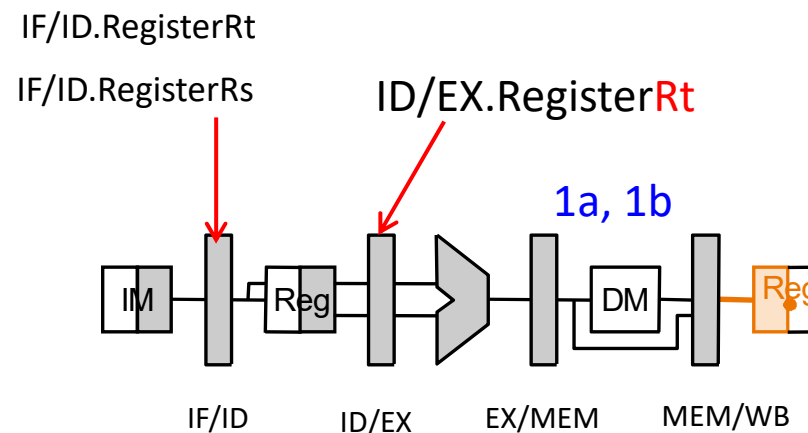if ( ID/EX.MemRead // if the instruction in the EX stage is a load...
    and ( ( ID/EX.RegisterRt = IF/ID.RegisterRs ) // and the destination register
        or ( ID/EX.RegisterRt = IF/ID.RegisterRt ) ) // matches either source register
    stall the pipeline // of the instruction in the ID stage
  
```




How to stall the Pipeline

- Only **Stall 1 clock** cycle after the load
 - the forwarding unit can resolve the dependency
- How hardware stalls the pipeline 1 cycle:
 - **Disable write on PC** => this will cause the instruction in the **IF stage** to repeat, i.e., *stall*
 - **Disable write on IF/ID register** => this will cause the instruction in the **ID** stage to repeat, i.e., *stall*
 - **Changes all the EX, MEM and WB control fields in the ID/EX pipeline register to 0** => , so the instruction just behind the **load** becomes a **nop** – a **bubble** is said to have been inserted into the pipeline

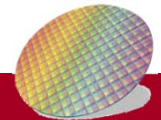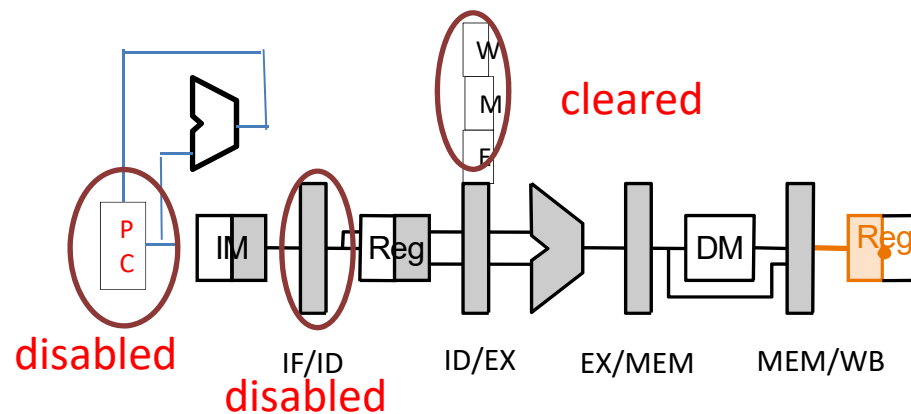




Adding Hazard Detection Unit


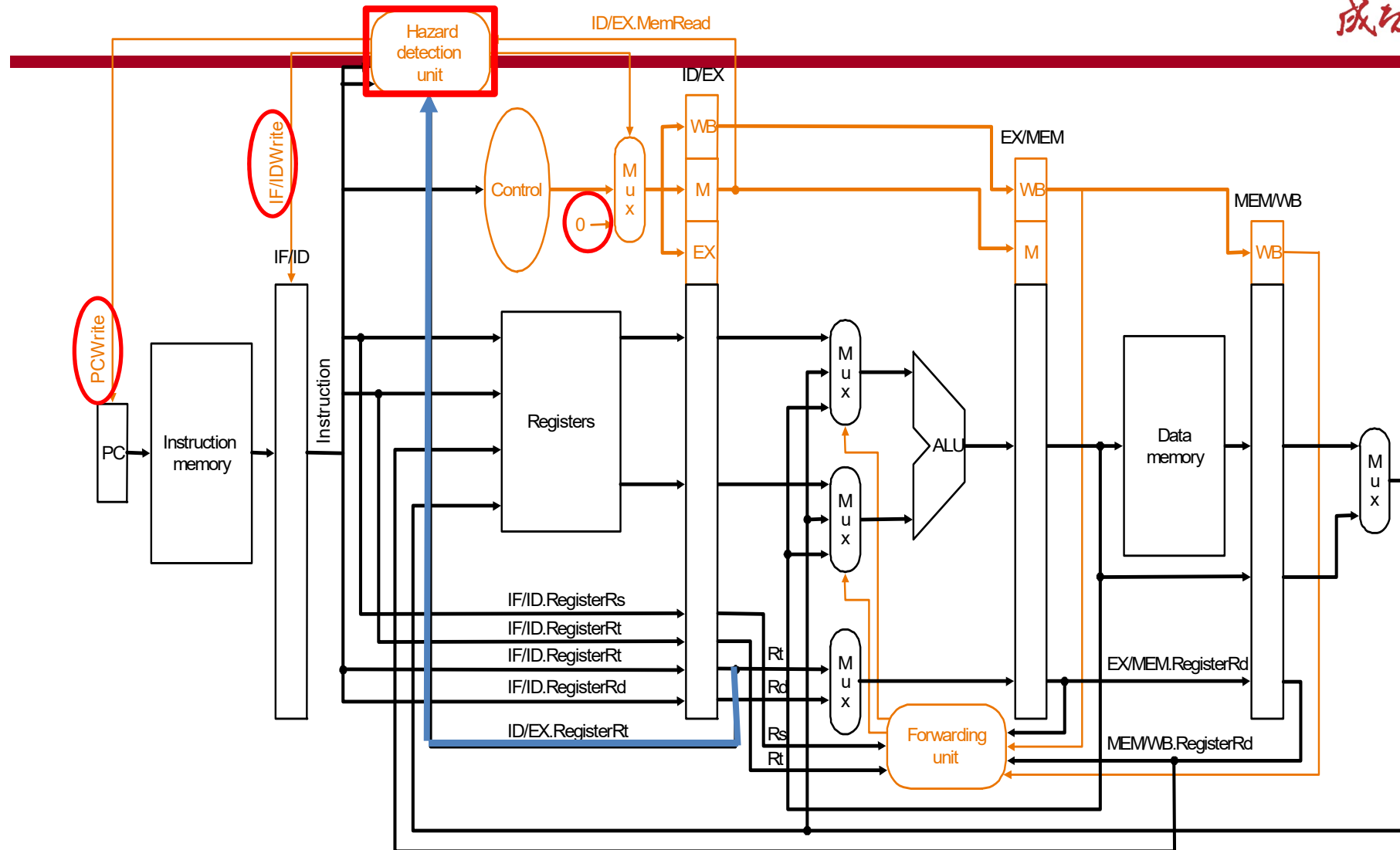


Datapath with forwarding hardware, the hazard detection unit and controls wires – certain details, e.g., branching hardware are omitted to simplify the drawing

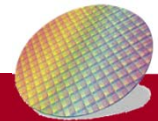

Cycle 2

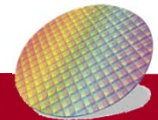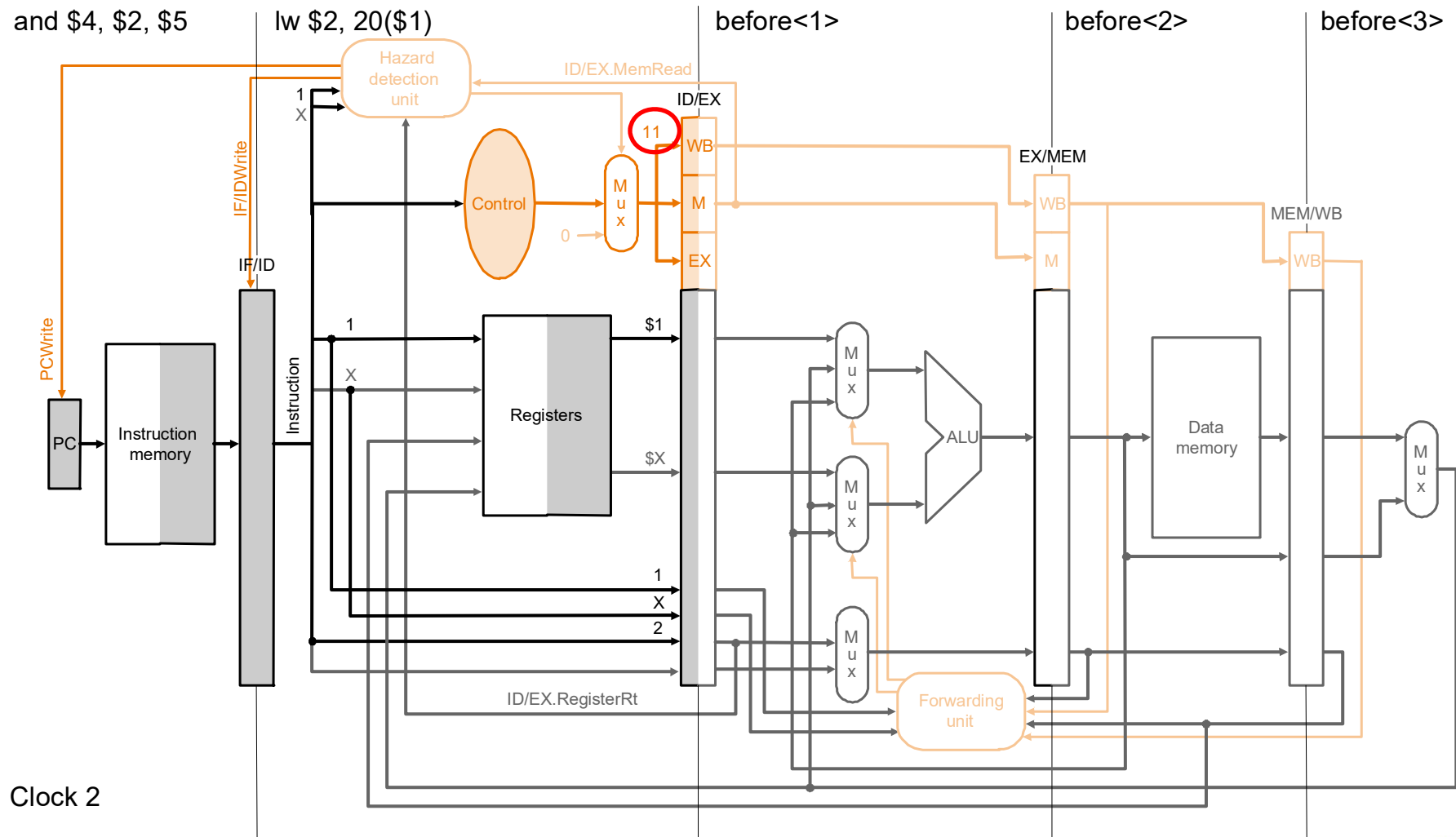
```
lw    $2, 20($1)
and   $4, $2, $5
or    $4, $4, $2
add   $9, $4, $2
```




Detect a hazard and insert a stall

Cycle 3

```
lw    $2, 20($1)
and    $4, $2, $5
or     $4, $4, $2
add    $9, $4, $2
```

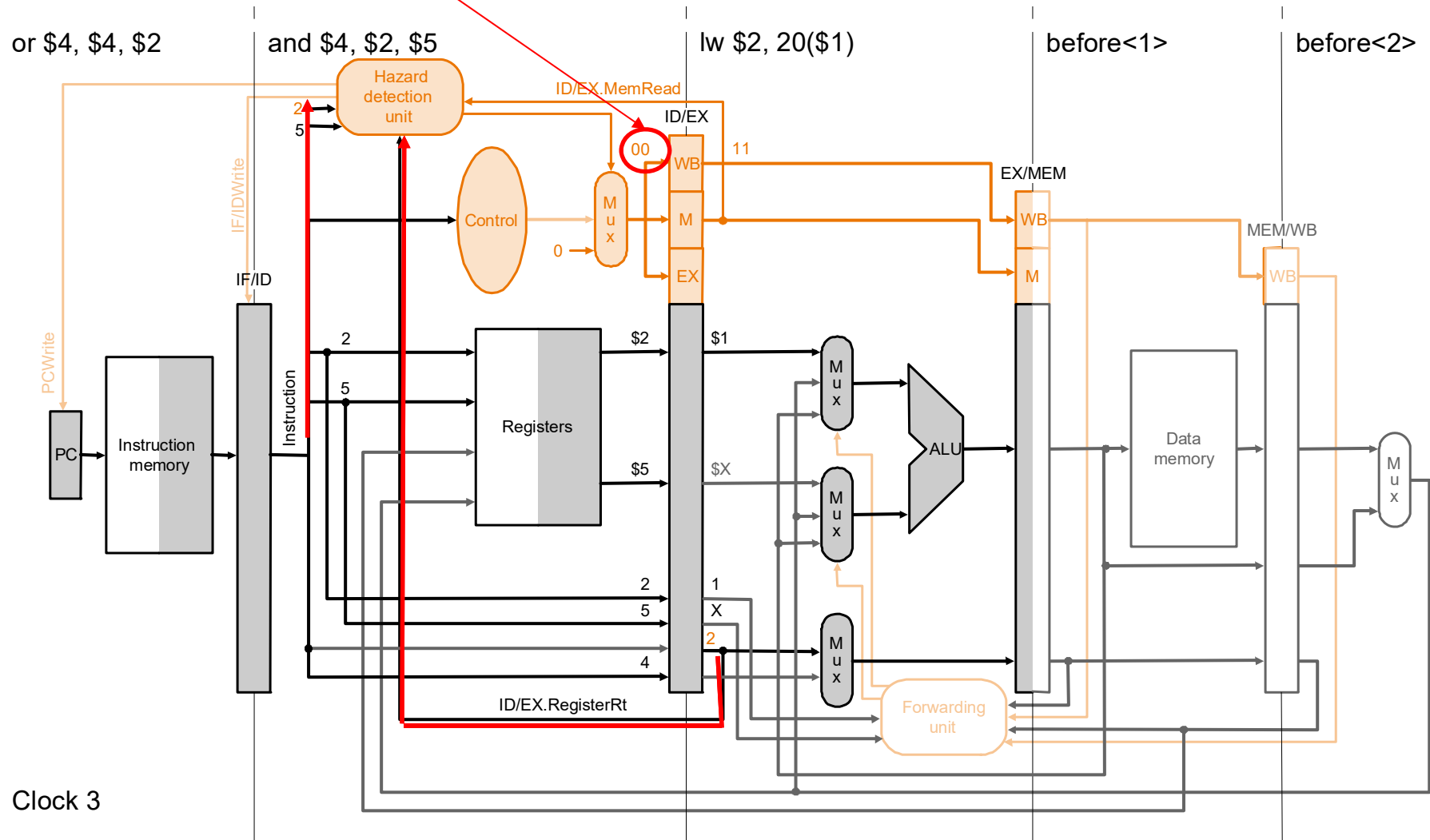


Clock 3

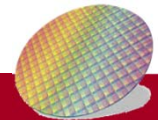


Cycle 4

```
lw  $2, 20($1)
and $4, $2, $5
or  $4, $4, $2
add $9, $4, $2
```

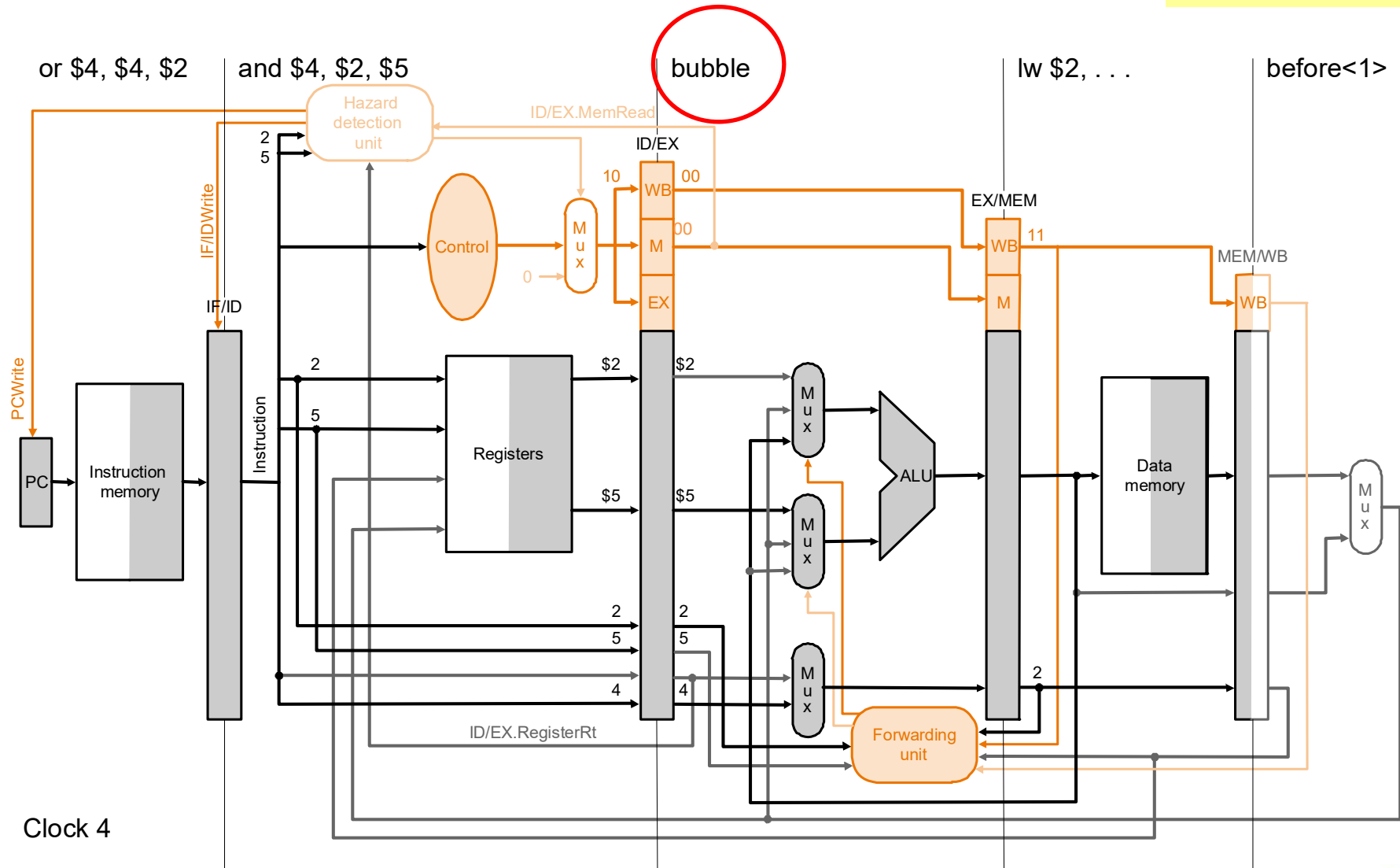


Clock 4

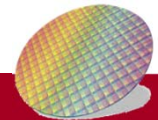


Cycle 5

```
lw    $2, 20($1)
and    $4, $2, $5
or     $4, $4, $2
add    $9, $4, $2
```


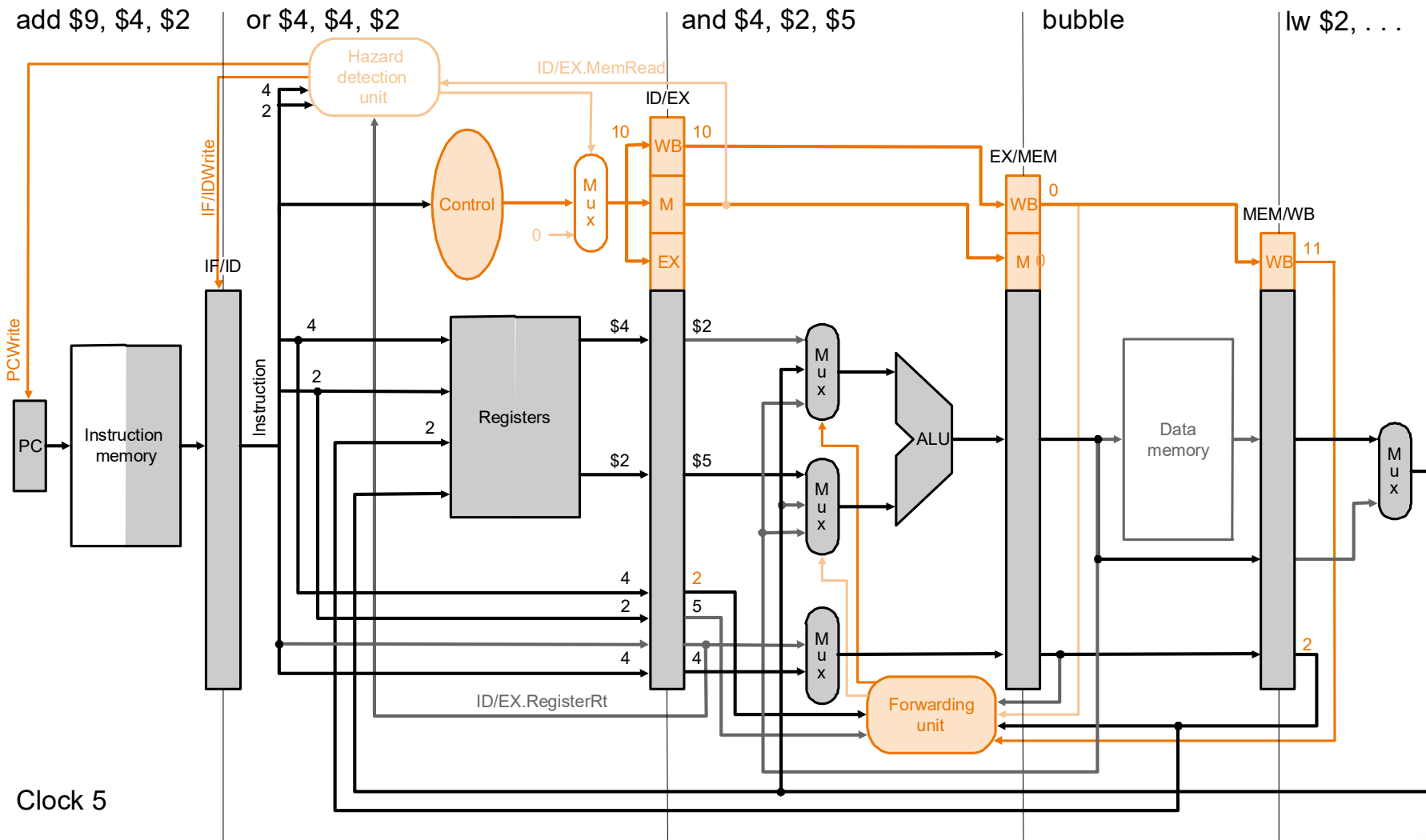


Clock 5

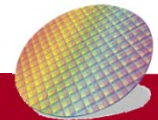

Cycle 7
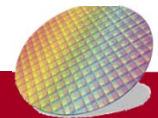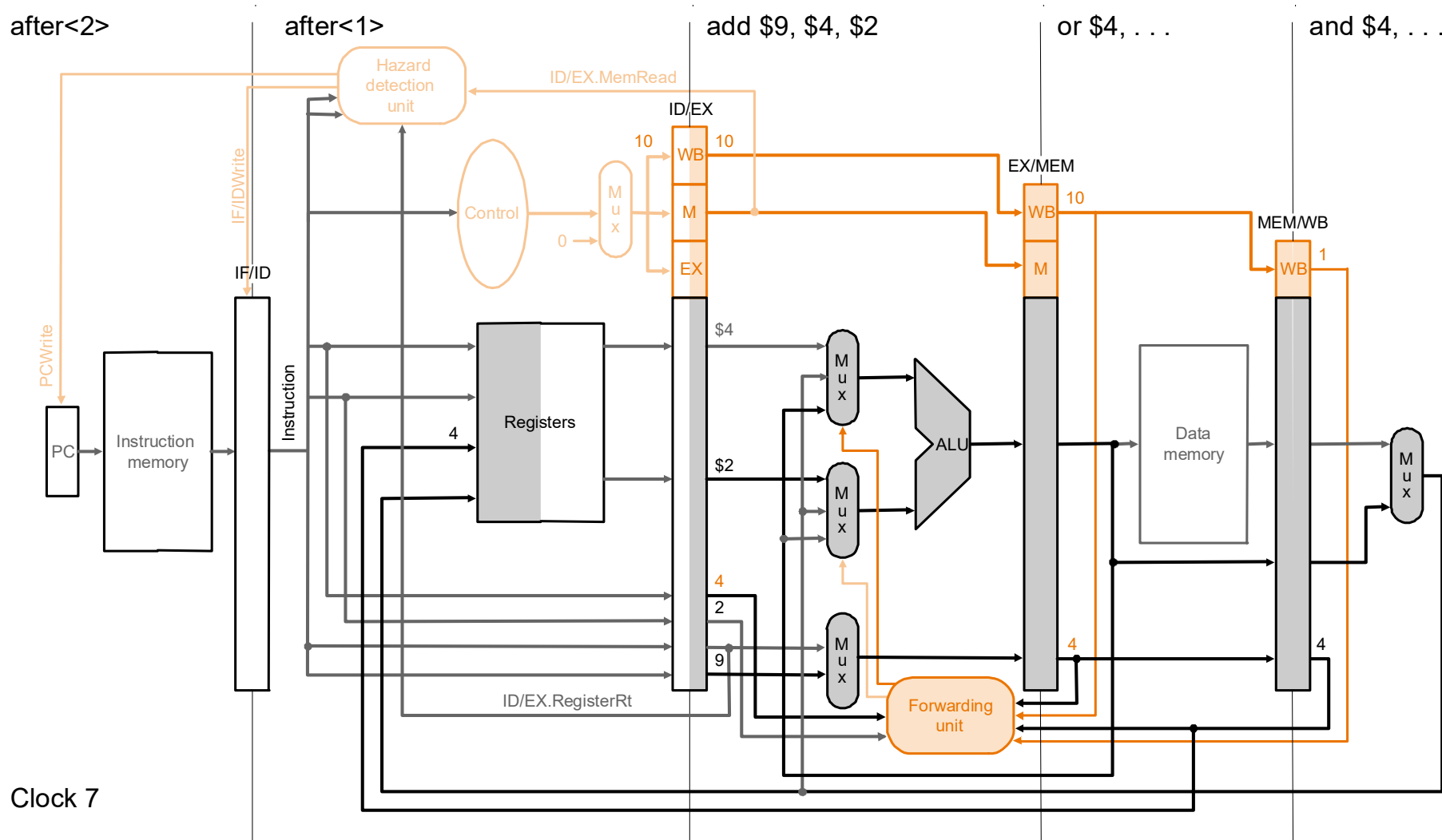
```
lw    $2, 20($1)
and    $4, $2, $5
or     $4, $4, $2
add    $9, $4, $2
```



Special case: load store pair

- Are there any stalls in the following instructions if forwarding is used? If yes, how many?


lw **\$2**, 20(\$1)

and \$4, **\$2**, \$5

- Are there any stalls in the following instructions if forwarding is used? If yes, how many?

lw **\$2**, 20(\$1)

sw **\$2**, 4(\$3)

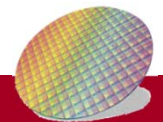



成功大學

National Cheng Kung University

Backup Slides

